

$$3. \quad i = \frac{|\mathcal{E}|}{R}, \quad |\mathcal{E}| = \frac{\Phi_{B,f} - \Phi_{B,i}}{\Delta t} \cdot N$$

$$\text{and } \Phi_{B,\text{final}} = 0 \quad (\text{since } i_f = 0)$$

$$\Phi_{B,\text{initial}} = B_{\text{initial}} \cdot \text{Area}$$

$$= (\mu_0 i n) (\pi r^2)$$

$$= \mu_0 (1.5)(2200)(\pi)(0.016)^2$$

$$\rightarrow i = 30 \text{ mA}$$

$$7. \quad \Phi_B = 4t^2 + 7t$$

$$|\mathcal{E}| = \frac{d\Phi_B}{dt} = 12t + 7$$

$$|\mathcal{E}| \text{ @ } t=2 \rightarrow \underline{31 \times 10^{-3} \text{ V}}$$

$$9. \quad B = \mu_0 i n = \mu_0 (85400) \sin(\omega t) \cdot (1.28)$$

$$\Phi_B = B \cdot \pi r^2$$

$$|\mathcal{E}| = \frac{d\Phi_B}{dt} = \mu_0 (85400) \omega \cdot 1.28 \cos(\omega t) \cdot \text{Area}$$

$$11. \quad |\mathcal{E}| = N \frac{d\Phi_B}{dt} \quad \text{and} \quad \Phi_B = B \cdot A$$

$$\text{Area} = a \cdot b \cdot \cos \omega t$$

net flux since then $\Phi_B = 0$ at $t=0$

$$\text{so } |\mathcal{E}| = \frac{N B a b \cos \omega t}{dt} = \underline{N B a b \omega \sin(\omega t)}, \quad \omega = 2\pi f$$

13. $B = 0.042 - 0.87t$, $Area = \frac{2 \cdot 2}{2} = 2m^2$

$$\mathcal{E}^{ind} = -\frac{d\Phi_B}{dt} = -\frac{2(0.042 - 0.87t)}{dt} = 2(0.87)$$

\vec{B} is \odot and decreasing w time, so induced \vec{B} must increase with time and is \odot , too.

$\hookrightarrow \therefore$ current is c.c.w.

$$\text{and } \mathcal{E}^{net} = \mathcal{E}_{bat} + \mathcal{E}^{ind} = 21.7V$$

27. $\Phi_B = B \cdot Area$

$$= \int_0^{0.02} (4t^2 y)(0.02) dy$$

\leftarrow the x value of area


a)

$$= (0.04t^2)(0.02)^2$$

$$|\mathcal{E}| = \frac{d\Phi_B}{dt} = 2(0.04t)(0.02)^2 = 80 \mu V$$

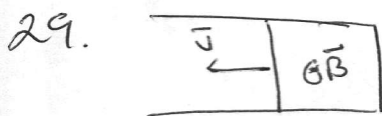b) \vec{B} is \odot and increasing (\uparrow)

so B^{ind} is \otimes and $\uparrow \Rightarrow i$ is clockwise



a) $|\mathcal{E}| = \frac{d\Phi_B}{dt} = BLV = 0.048V$

b) $i = \frac{|\mathcal{E}|}{R} = 2.7mA$


c) $P = i^2 R = 1.3 \times 10^{-4} W$

33. $\Phi = \int_S \vec{B} \cdot d\vec{S}$
 $= \int_a^{a+L} \frac{\mu_0 I}{2\pi R} dR$

$= \frac{\mu_0 I}{2\pi} \ln\left(\frac{a+L}{a}\right)$

c) $|\mathcal{E}| = \frac{d\Phi_B}{dt} = \frac{\mu_0 I}{2\pi} \ln\left(\frac{a+L}{a}\right) \cdot v = 240 \mu\text{V}$

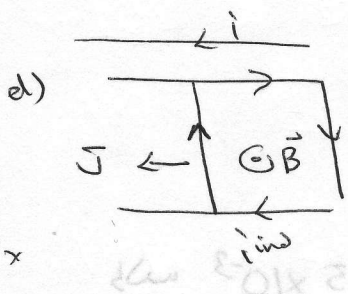b) $i = \frac{\mathcal{E}}{R} = 0.6 \text{ mA}$ e) $P = i^2 R = 0.14 \mu\text{W}$



flux \uparrow as rod moves (\because Area \uparrow)

so induced \vec{B} should be into page

$\hookrightarrow i$ is c.w.

$\vec{F} = i d\vec{l} \times \vec{B}$
 \uparrow
induced i

$\therefore \vec{F} = i \int_a^{a+L} d\vec{l} \left(\frac{\mu_0 I}{2\pi L} \right) \hat{x}$

$= \frac{i \mu_0 I}{2\pi} \ln\left(\frac{a+L}{a}\right) \hat{x}$

$= 2.87 \times 10^{-8} \text{ N}$ (apply in $-ve \hat{x}$)

e) $P = \vec{F} \cdot \vec{v} = 0.14 \mu\text{W}$

35. a) $\mathcal{E} = B \cdot L \cdot v = 0.6 \text{ V}$

b) flux \uparrow so B_{ind} is \otimes and i_{ind} is c.w

c) $i = \frac{\mathcal{E}}{R} = 1.5 \text{ A}$

d) c.w

f) $F = I d\vec{l} \times \vec{B}$
 $= \frac{\mathcal{E}L}{R} \cdot \vec{B} = 0.18 \text{ N}$

e) $P = (i^2)R = 0.9 \text{ W}$

g) $P = F \cdot v = 0.9 \text{ W}$

40. $L = \frac{N\Phi_B}{i}$

$5 \text{ mA} = \frac{(400)\Phi_B}{5 \text{ mA}}$

$\Phi_B = 0.1 \mu\text{Wb}$

41. a) Area = $\pi r^2 = 0.03 \text{ m}^2$

flux through N turns is $NB \cdot A = 2.45 \times 10^{-3} \text{ Wb}$

b) $L = \frac{N\Phi_B}{i}$ and $|N\Phi_B| = 2.45 \times 10^{-3}$ (to cancel original flux)
 $= 0.65 \text{ mH}$


45. $\mathcal{E} = -L \frac{di}{dt}$

a) $\frac{di}{dt}$ is -ve, so \mathcal{E} is +ve
(i.e. i is \downarrow so \mathcal{E} opposes that decrease)

b) $|\mathcal{E}| = L (25 \text{ kA/s})$

$L = 0.68 \text{ mH}$

47.

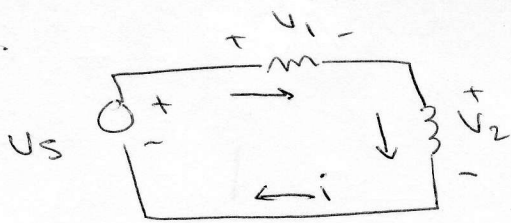KVL

$$-U_S + U_1 + U_2 = 0$$


$$U_S = L_1 \frac{di}{dt} + L_2 \frac{di}{dt}$$

i.e. $L_{eq} = L_1 + L_2 + \dots + L_n$

$$= (L_1 + L_2) \frac{di}{dt}$$

$$= L_{eq} \frac{di}{dt}$$

49.

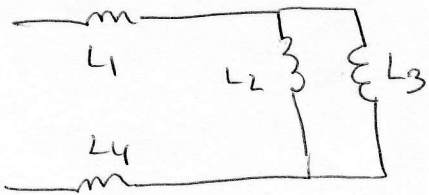

$$L_{eq} = L_1 + L_2 // L_3 + L_4$$

$$= L_1 + \left(\frac{1}{L_2} + \frac{1}{L_3} \right)^{-1} + L_4$$


Chap 1

3. $i = \frac{dq}{dt} \rightarrow 30,000 = \frac{q}{50 \times 10^{-6}} \rightarrow q = 1.5 \text{ C} = 1.5 \text{ C} = 1.5 \text{ C}$

8. in time T , $i = \frac{q}{T}$ and energy $W = P \cdot T$


$\therefore P = iV$
 $\frac{W}{T} = \frac{q}{T} V$
 $V = -24 \text{ V}$

-ve since have

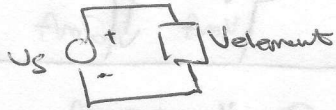


and $V_S + V_{\text{Resistor}} = 0$

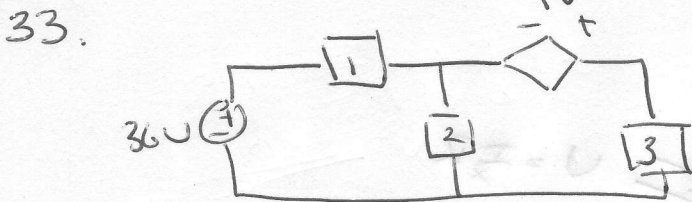26. $P = iV$
 $i = \frac{72}{18}$
 $= 4 \text{ A}$



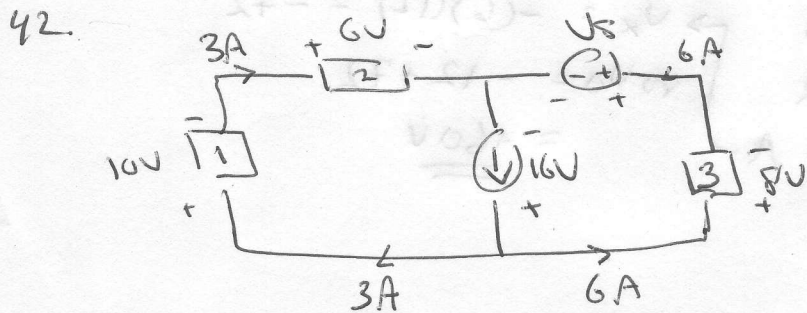- Absorbed Supplied
- ① $P = iV = (4)(12) \quad P_{Ix} = -(Ix)(2A)$
 - ② $P = (2)(24) \quad P_{36V} = -(36)(4)$
 - ③ $P = (2)(28)$



- $P_1 = 30 \text{ W}$
- $P_2 = 18 \text{ W}$
- $P_3 = 48 \text{ W}$
- $P_{9A} = (9)(-16) = -144$

and sum of power = 0

$P_1 + P_2 + P_3 + P_{9A} + P_{V_S} = 0 \rightarrow P_{V_S} = 48 \text{ W}$ (Supplied)
 so $V = 48/6 = 8 \text{ V}$


Chap 3

3. $V = IR = 24 V$

$P = I^2 R = 48 W$

7. $P = \frac{V^2}{R} = \frac{(2 \times 1.5)^2}{1} = 9 W$

12

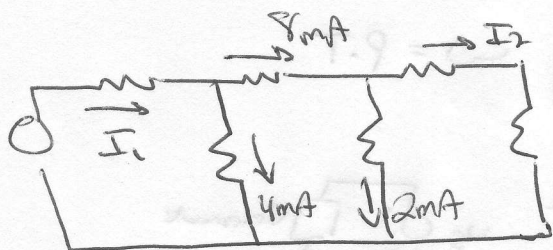

$I_1 = 8 + 4 = 12 mA$

$8 mA = I_2 + 2$

$I_2 = 6 mA$

24. $V_{ad} = -3 - 2 + 12 = +7 V$

25. $V_{fb} = 2 + 2 - 12 = -8 V$



$V_{ec} = 1 + 2 + 2 - 12 + 1 = -6 V$

32. $V_o = -12 - V_x$ and $V_x = \frac{I_x}{12} \quad U = I_x R$

Sum of voltages in loop must be 0:

$$\begin{aligned}
 -2I_x + 4I_x - 12 - V_x + V_x &= 0 \\
 2I_x &= 12 \\
 I_x &= 6 A
 \end{aligned}
 \quad \left. \begin{aligned}
 &\rightarrow V_x = -(6)(12) = -72 \\
 &\text{so } V_o = -12 + 72 \\
 &= \underline{\underline{+60V}}
 \end{aligned} \right\}$$

6.

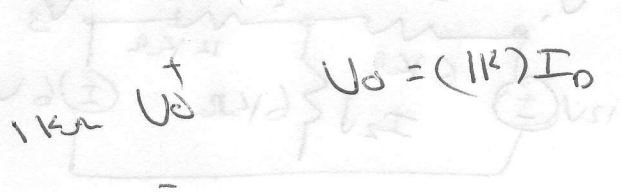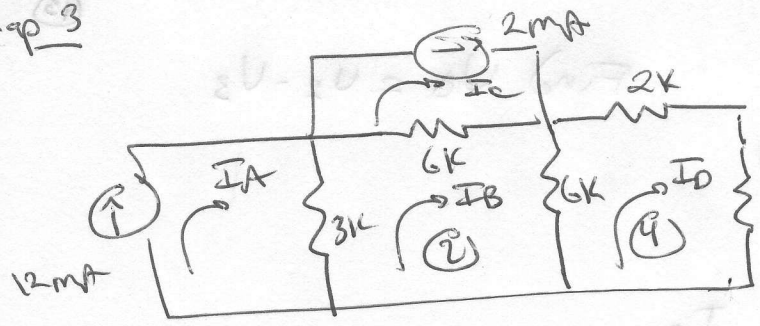

$V_0 = (1k) I_D$

② KVL $3k(I_B - I_A) + 6k(I_B - I_C) + 6k(I_B - I_D) = 0$

and $I_A = 12mA$, $I_C = 2mA$

$15k I_B - 6k I_D - 36 - 12 = 0$

④ KVL $6k(I_D - I_B) + 2k I_D + 1k I_D = 0$

$\rightarrow I_B = \frac{3}{2} I_D$ sub in above

and $15k (\frac{3}{2} I_D) - 6k I_D = 48$


$I_D = 2.9mA \rightarrow I_B = 4.4mA$

$\rightarrow V_0 = (1k) I_D = \underline{2.9V}$

from $V_1 = 3k(I_A - I_B) = (3k)(12mA - 4.4mA) = \underline{22.8V}$

$$\begin{array}{l} I_2 + I_1 = Ams \\ \frac{50 - V_1}{2k} + \frac{50 - AV}{2k} = Ams \\ \frac{50 - V_1}{2k} + \frac{50 - AV}{2k} = Ams \\ \frac{50 - V_1}{2k} + \frac{50 - AV}{2k} = Ams \\ \frac{50 - V_1}{2k} + \frac{50 - AV}{2k} = Ams \end{array}$$

12

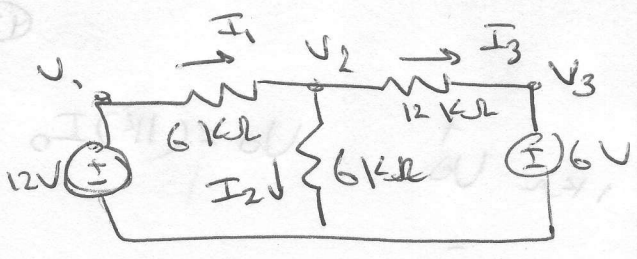

Find $V_0 = U_2 - U_3$

at node V_2 : $I_1 = I_2 + I_3$

$$\frac{U_1 - U_2}{6k\Omega} = I_2 + \frac{U_2 - U_3}{12k\Omega}$$

and $U_1 = 12V$
 $U_3 = 6V$
 $U_2 = 6k\Omega I_2$


$$\frac{12}{6k} - \frac{U_2}{6k} = I_2 - \frac{6}{12k} + \frac{U_2}{12k}$$

$$2.5mA = 2.5I_2$$

$$I_2 = 1mA \rightarrow U_2 = 6V$$

and $V_0 = U_2 - U_3 = 0$

15.

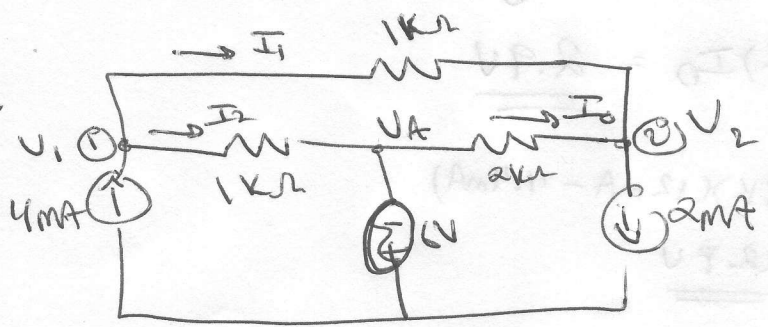

$$V_A = -6V$$

$$I_0 = \frac{U_A - U_2}{2k}$$

$$4mA = I_1 + I_2$$

$$= \frac{U_1 - U_A}{1k} + \frac{U_1 - U_2}{1k}$$

$$2mA = I_0 + I_1$$

$$2mA = \frac{U_A - U_2}{2k} + \frac{U_1 - U_2}{1k}$$

$$4 = 2U_1 + 6 - U_2$$

$$4 = U_A - U_2 + 2U_1 - 2U_2$$

$$-2 = 2U_1 - U_2 \quad (1)$$


$$10 = +2U_1 - 3U_2 \quad (2)$$

$$(1) - (2) : +12 = -2U_2$$

$$U_2 = -6V \rightarrow I_0 = \frac{U_A - U_2}{2k}$$

$$= 0$$

19.

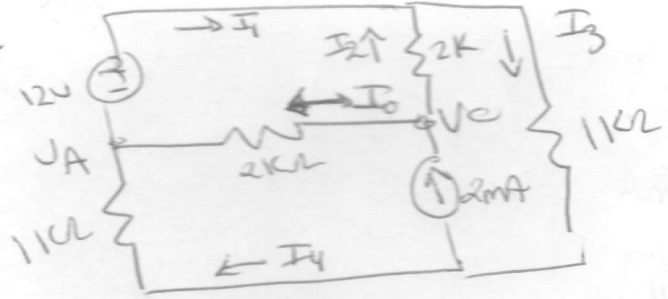

$$\textcircled{1} \quad 2\text{mA} = I_0 + I_2$$

$$= \frac{V_c - V_A}{2\text{k}} + \frac{V_c - (V_A + 12)}{2\text{k}}$$

$$16 = 2V_c - 2V_A$$

$$\textcircled{2} \quad \left. \begin{aligned} I_1 &= I_0 + I_4 \\ I_1 + I_2 &= I_3 \end{aligned} \right\} I_3 - I_2 - I_0 - I_4 = 0$$

$$I_4 = -\frac{V_A}{1\text{k}}$$

$$\frac{V_A + 12}{1\text{k}} - \frac{V_c - (V_A + 12)}{2\text{k}} - \frac{(V_c - V_A)}{2\text{k}} + \frac{V_A}{1\text{k}} = 0$$


$$-36 = 6V_A - 2V_c$$

$$\textcircled{1} + \textcircled{2} \quad -20 = 4V_A$$

$$V_A = -5 \rightarrow V_c = +3$$

$$\hookrightarrow I_0 = \frac{V_c - V_A}{2\text{k}} = 4\text{mA} \quad (\text{to left})$$

25.

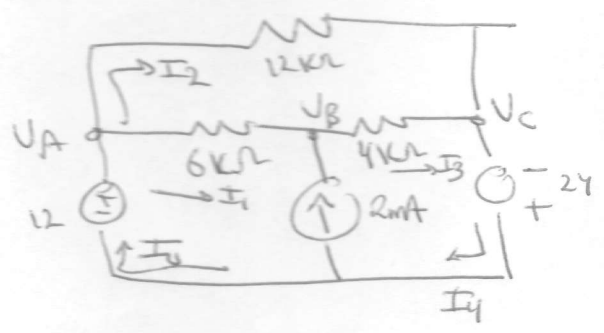

$$\left. \begin{aligned} V_A &= 12\text{V} \\ V_c &= -24\text{V} \end{aligned} \right\} I_2 = \frac{V_A - V_c}{12\text{k}} = -3\text{mA}$$

$$\textcircled{1} \quad I_0 = I_1 + I_2 \quad \textcircled{2} \quad I_3 + I_2 = I_4 \quad \textcircled{3} \quad I_4 = 2\text{mA} + I_0$$

$$\textcircled{2} = \textcircled{3} \quad 2\text{mA} + I_0 = I_3 - 3\text{mA}$$

$$I_3 - I_0 = 5\text{mA}$$


$$\textcircled{1} \quad I_1 - I_0 = +3\text{mA}$$

$$\text{Subtract} \quad I_3 - I_1 = 2\text{mA}$$

$$I_3 = \frac{V_B - V_C}{4k}$$

$$I_1 = \frac{V_A - V_B}{6k}$$

(45)

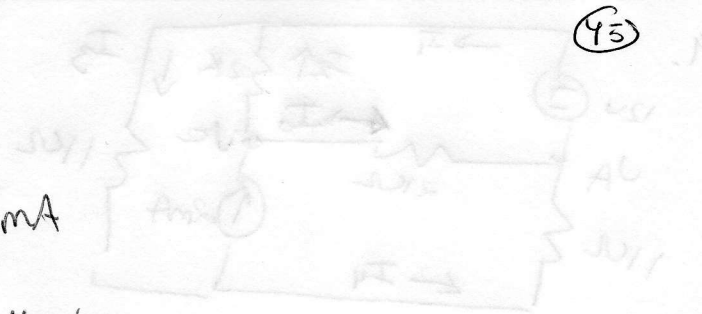

So, get $\frac{V_B + 24}{4k} - \frac{(12 - V_B)}{6k} = 2mA$

$$V_B = -\frac{24}{5} V$$

$$\frac{(5I + 4V) - 2V}{2k} + \frac{4V - 2V}{2k} = 2mA$$

$$4V - 2V = 2I$$

$\frac{4V}{2k} = 2I \rightarrow I = 1mA$

$$0 = \frac{4V}{2k} + \frac{(4V - 2V)}{2k} - \frac{(5I + 4V) - 2V}{2k} - \frac{5I + 4V}{2k}$$


$$2V - 4V = 2I - 2I$$

$$-2V = 2I \rightarrow I = -1mA$$

$$V_A - 2V = 2I \rightarrow V_A = 2V + 2I$$

$$I_1 = \frac{V_A - V_B}{6k} = \frac{2V + 2I - (-24/5)}{6k}$$
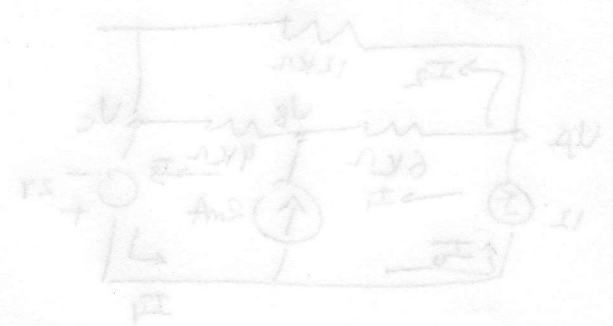
$$I_3 = \frac{V_B - V_C}{4k} = \frac{-24/5 - 12}{4k} = -3mA$$



$$I_1 + I_2 = I_3 \quad I_3 = I_4 + I_5 \quad I_4 + I_5 = I_6$$

$$2mA - I_3 = I_4 + I_5 \quad I_4 = 2mA - I_3$$

$$I_5 = I_6 - I_4$$

$$I_5 = I_6 - (2mA - I_3)$$

$$I_5 = I_6 - 2mA + I_3$$

Substit