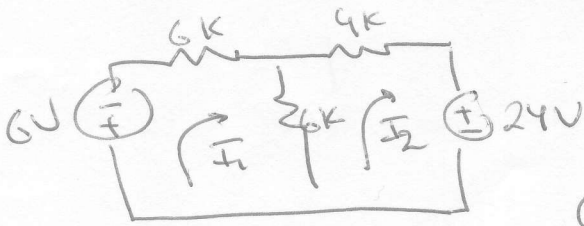


53.



$$\textcircled{1} \quad +6 + 6k(I_1) + 6k(I_1 - I_2) = 0$$

$$12kI_1 - 6kI_2 = -6$$

$$\textcircled{2} \quad 6k(I_2 - I_1) + 4kI_2 + 24 = 0$$

$$-6kI_1 + 10kI_2 = -24$$


$$\textcircled{1} + 2 \times \textcircled{2} : 14kI_2 = -54$$

$$I_2 = \frac{-54}{14} \text{ mA}$$

$$= -\frac{27}{7} \text{ mA} = I_0$$



56.

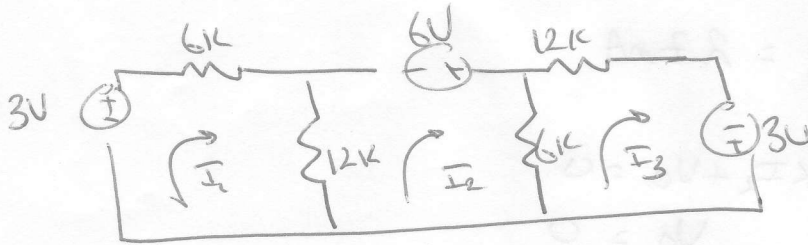

$$I_0 = I_2 - I_3$$

$$\textcircled{1} \quad -3 + 6kI_1 + 12k(I_1 - I_2) = 0$$

$$18kI_1 - 12kI_2 = 3$$

$$\textcircled{2} \quad 12k(I_2 - I_1) + 6 + 6k(I_2 - I_3) = 0$$

$$18kI_2 - 12kI_1 - 6kI_3 = +6$$

$$\textcircled{3} \quad 6k(I_3 - I_2) + 12kI_3 + 3 = 0$$

$$18kI_3 - 6kI_2 = 3$$

$$\textcircled{1} \rightarrow I_1 = \frac{3 + 12kI_2}{18k}$$

$$\textcircled{3} \quad I_3 = \frac{3 + 6kI_2}{18k}$$


in  $\textcircled{2}$

$$18kI_2 - 12k\left(\frac{3 + 12kI_2}{18k}\right) - 6k\left(\frac{3 + 6kI_2}{18k}\right) = 6$$

$$18kI_2 - 2 - 8kI_2 - 1 - 2kI_2 = 6$$

$$8kI_2 = 9$$


$$I_2 = \frac{9}{8} \text{ mA}$$

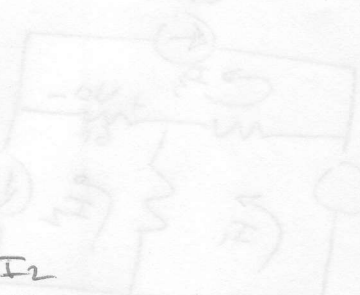


in ③  $18kI_3 - 6kI_2 = 3$   
 $18kI_3 - 6k\left(\frac{9}{8}mA\right) = 3$   
 $18kI_3 = 3 + \frac{27}{4}$

$I_3 = 0.54mA$

$I_0 = I_2 - I_3$   
 $= 0.58mA$

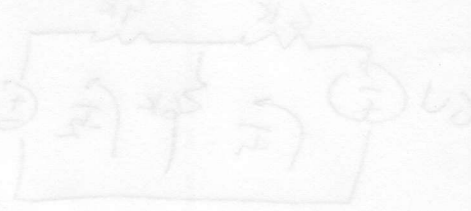

60.

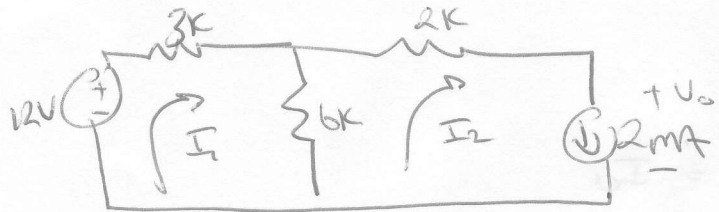


$I_2 = 2mA$

①  $-12 + 3kI_1 + 6k(I_1 - I_2) = 0$   
 $I_1 = 2.7mA$

outer loop  $-12 + 3kI_1 + 2kI_2 + V_0 = 0$   
 $V_0 = 0$

or ②  $6k(2mA - I_1) + 2k(2mA) + V_0 = 0$   
 $V_0 = 0$



69.

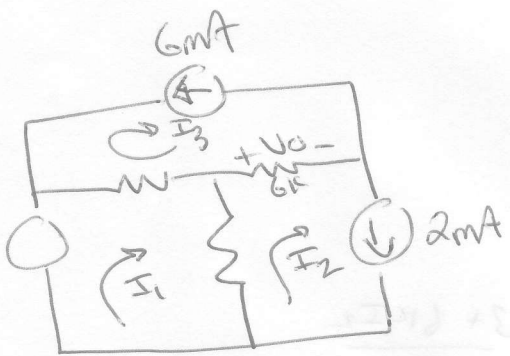

$V_0 = 6k(I_2 - I_3)$   
 $= 6k(2mA - (-6mA))$   
 $= \underline{\underline{48V}}$

$\Delta = \frac{(10 \times 10^{-3}) \times 100}{100} - \frac{(10 \times 10^{-3}) \times 100}{100}$   
 $\Delta = 10^{-3} - 10^{-3} = 0$   
 $P = \dots$   
 $A_{avg} = \dots$

30.

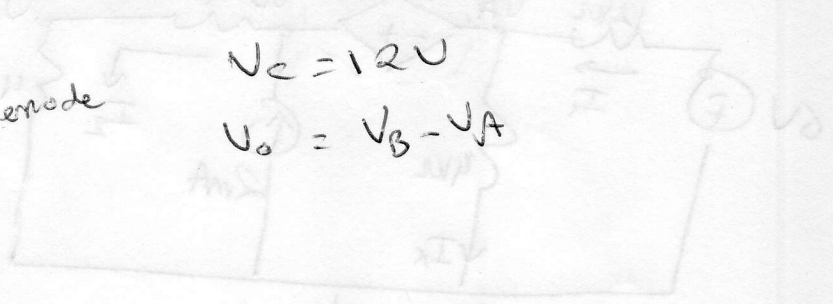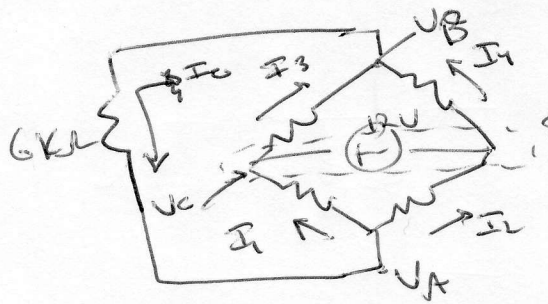

Supernode KCL:

$$I_1 + I_2 = I_3 + I_4$$

$$\frac{V_A - V_C}{6k} + \frac{V_A}{6k} = \frac{V_C - V_B}{6k} = \frac{V_B}{6k}$$

$$2V_A + 2V_B - 2V_C = 0 \quad (1)$$

@ VA

$$I_0 = I_1 + I_2$$

$$\frac{V_B - V_A}{6k} = \frac{V_A - V_C}{6k} + \frac{V_A}{6k}$$

$$0 = 3V_A - V_B - V_C \quad (2)$$

$$\therefore (1) \quad 2V_A + 2V_B = 24$$


$$(2) \quad 3V_A - V_B = 12$$

---


$$V_A = 6V \rightarrow V_B = 6V$$

$$\therefore \underline{\underline{V_0 = 0}}$$

47.

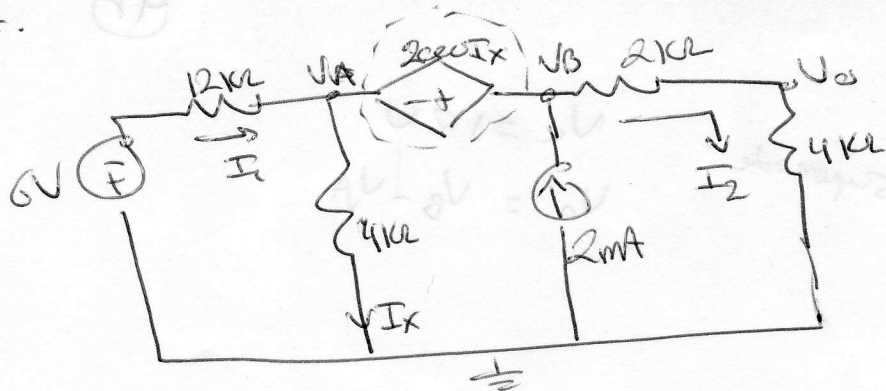

KCL Super node

$$2\text{mA} + I_1 = I_x + I_2$$

$$2\text{mA} + \left(\frac{-6 - V_A}{12\text{k}}\right) = \frac{V_A}{4\text{k}} + \frac{V_o}{4\text{k}}$$

$$1.5 = \frac{7V_A}{12}$$

$$V_A = 2.57\text{V}$$

$$\hookrightarrow V_o = V_A$$

$$V_B = 3.58\text{V}$$

$$\text{and } I_2 = 0.6\text{mA}$$

$$I_2 = \frac{V_o}{4\text{k}} = \frac{V_B - V_o}{2\text{k}} \quad \frac{4V}{4\text{k}} = \frac{5V - 4V}{2\text{k}}$$

$$I_x = \frac{V_A}{4\text{k}}$$

$$V_B = V_A + 2000I_x$$


$$= \frac{3V_A}{2}$$

$$\hookrightarrow \text{from } I_2: \frac{V_o}{4\text{k}} = \frac{V_B - V_o}{2\text{k}}$$

$$3V_o = 2V_B$$

$$\hookrightarrow V_o = V_A$$



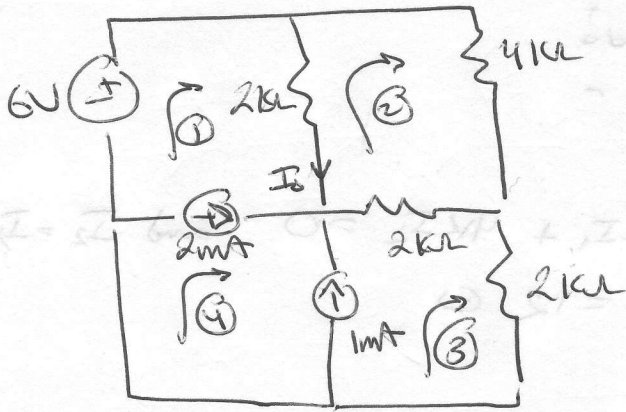

$$I_0 = I_1 - I_2$$

KVL ~~for~~ outer loop:

$$-6 + 4kI_2 + 2kI_3 + 6kI_4 = 0 \quad (1)$$

KVL (2):

$$2k(I_2 - I_1) + 4kI_2 + 2k(I_2 - I_3) = 0$$

$$8kI_2 - 2kI_1 - 2kI_3 = 0 \quad (2)$$

$$\left. \begin{aligned} I_4 - I_1 &= 2mA \\ I_3 - I_4 &= 1mA \end{aligned} \right\} \begin{aligned} I_3 &= 3mA + I_1 \end{aligned} \text{ sub in above}$$

$$(1) \quad -6 + 4kI_2 + 2k(3mA + I_1) + 6k(2mA + I_1) = 0$$

$$8kI_1 + 4kI_2 = -12$$


$$(2) \quad 8kI_2 - 2kI_1 - 2k(3mA + I_1) = 0$$

$$8kI_2 - 4kI_1 = 6$$

$$\text{do } (1) + 2 \times (2) \rightarrow I_2 = 0 \rightarrow I_1 = -\frac{3}{2} mA \rightarrow I_0 = I_1 - I_2$$

$$I_0 = -\frac{3}{2} mA$$

$$V_{0.8} = 0V$$

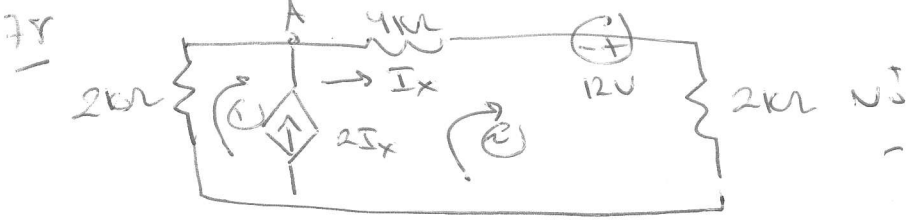

KVL outer loop:  $-12 + 2kI_2 + 2kI_1 + 4kI_2 = 0$  and  $I_2 = I_1$


$$2kI_1 + 6kI_x = 12 \quad (1)$$

at A:  $I_1 + 2I_x = I_x$

$$I_x = -I_1$$

∴  $-2kI_x + 6kI_x = 12$
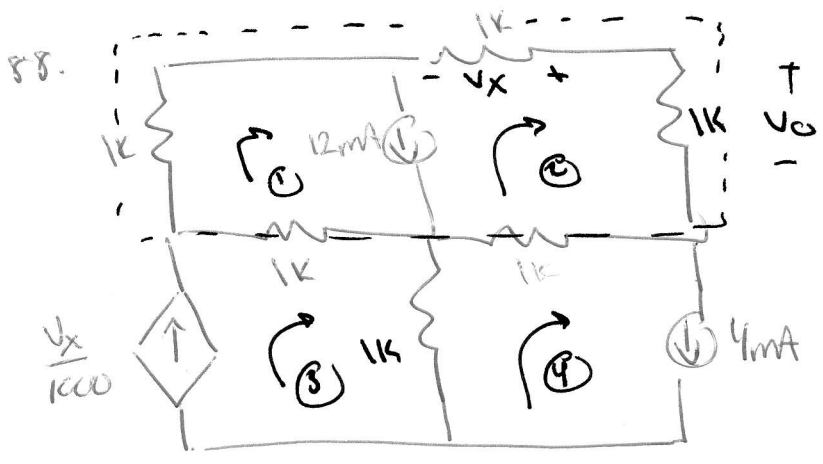
$$I_x = 3 \text{ mA} \rightarrow V_0 = 2kI_x = \underline{\underline{6 \text{ V}}}$$



$$V_0 = (1k)I_2$$

$$V_x = -(1k)I_2$$

$$I_1 - I_2 = 12 \text{ mA}$$

$$I_4 = 4 \text{ mA}$$

$$I_3 = \frac{V_x}{1k} = \frac{-1k I_2}{1k} = -I_2$$

$$\therefore I_1 + I_3 = 12 \text{ mA}$$

KVL in top loop:

$$1k I_1 - V_x + 1k I_2 + 1k(I_2 - I_4) + 1k(I_1 - I_3) = 0$$

$$1k(12 \text{ mA} + I_2) - V_x + 1k I_2 + 1k(I_2 - 4 \text{ mA}) + 1k(12 \text{ mA} + I_2 + I_2) = 0$$

$$\hookrightarrow 5k I_2 = V_x - 20$$

$$I_2 = \frac{V_x - 20}{5k} \text{ and } I_3 = -I_2 \rightarrow \frac{V_x}{1k} = \frac{20 - V_x}{5k}$$

$$6V_x = 20$$


$$V_x = \frac{10}{3}$$

$$\therefore I_3 = \frac{(10/3)}{1k} = 3.3 \text{ mA} \rightarrow I_2 = -3.3 \text{ mA}$$

$$\hookrightarrow V_0 = \underline{\underline{-3.3 \text{ V}}}$$

Lec 24 - Chap 5

(52)

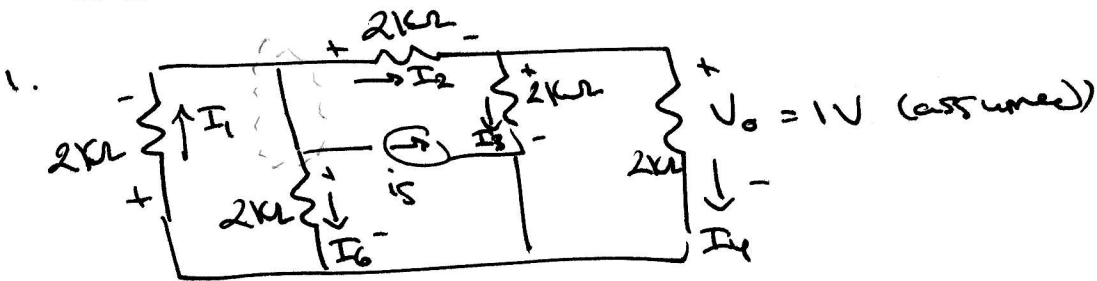

$$i_4 = \frac{1}{2} \text{ mA}$$

Right loop:  $-V_3 + V_0 = 0 \rightarrow V_3 = V_0 = 1\text{V}$

$$\hookrightarrow i_3 = \frac{1}{2} \text{ mA}$$

$$i_2 = i_3 + i_4 = 1 \text{ mA}$$

$$V_2 = 2\text{V}$$

Middle loop

$$-V_6 + V_2 + V_3 = 0$$

$$V_6 = 3\text{V}$$

$$\hookrightarrow i_6 = \frac{3}{2} \text{ mA}$$

outside loop:

$$V_1 + V_2 + V_0 = 0$$

$$V_1 = -3\text{V}$$

$$i_1 = -\frac{3}{2} \text{ mA}$$


$$\therefore i_1 = i_2 + i_6 + i_s \text{ (supernode)}$$

$$i_s = -4 \text{ mA}$$

but  $i_{s, \text{actual}} = 2 \text{ mA}$

$$\text{so } V_{0, \text{actual}} = \underline{\underline{-3\text{V}}}$$

5.

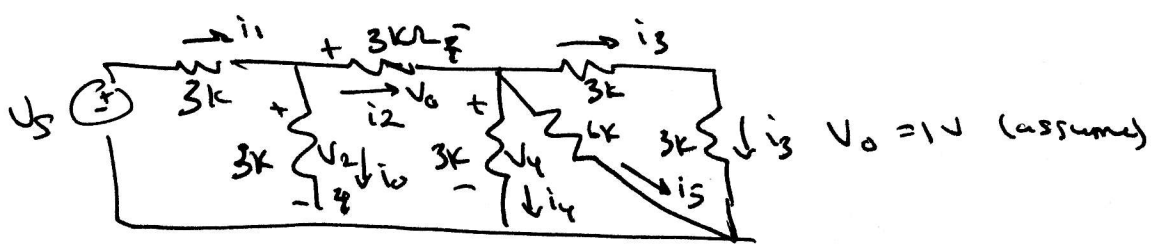

$$i_3 = \frac{1}{3k} \rightarrow V_4 = (6k)i_3 = 2V$$

$$\therefore i_4 = \frac{V_4}{3k} = 2i_3 \text{ and } i_5 = \frac{V_4}{6k} = i_3$$

$$i_2 = i_3 + i_4 + i_5 = 4i_3$$

$$\text{so } V_0 = (3k)i_2 = 12ki_3 = 4V$$

$$\text{KVL in middle: } -V_2 + V_0 + V_4 = 0$$

$$V_2 = 6V \rightarrow i_0 = \frac{V_2}{3k} = 2mA$$

$$i_1 = i_0 + i_2 = \frac{2}{mA} + \frac{4}{3k} = \frac{10}{3k} A$$

$$\rightarrow V_1 = (3k)i_1 = 10V$$



$$\text{KVL on left: } -U_s + V_1 + V_2 = 0$$

$$U_s = 16V$$

$$U_{s, \text{actual}} = 8V \text{ so } V_{0, \text{actual}} = \underline{\underline{0.5V}}$$



7.


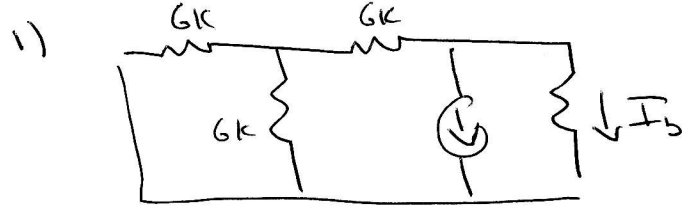
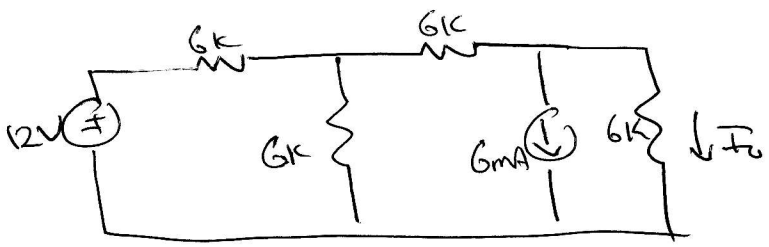


current division:


$$I_3 = \frac{9k}{(6+9)k} \cdot 6mA$$

$$= -1.8 mA$$

↑  
5  
note sign of current

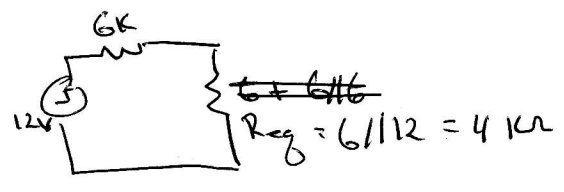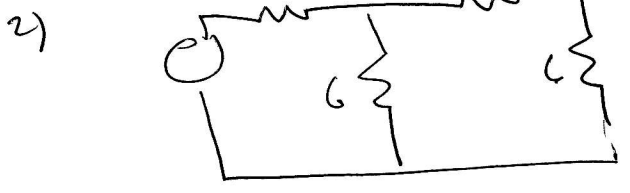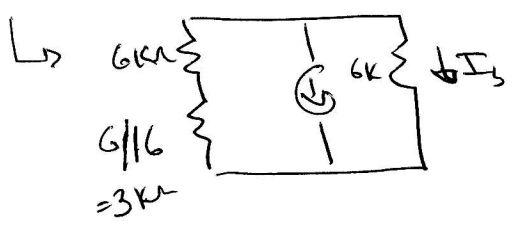

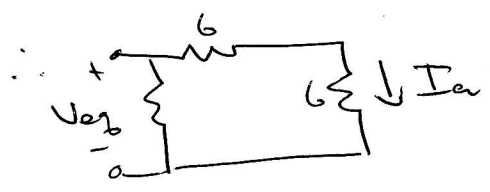
Voltage divider:  $V_{eg} = \left(\frac{4}{10}\right) V_s = 4.8V$



$$I_a = \frac{V_{eg}}{12k} = 0.4 mA$$

∴  $I_0 = I_a + I_3 = -3.2 mA$

11. 1)

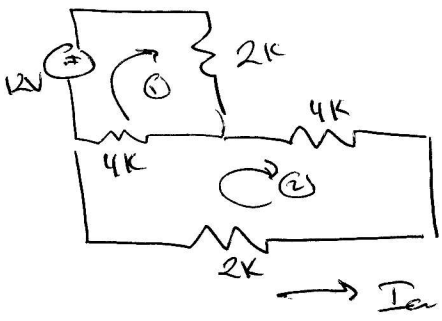

$$i_2 = -i_a$$


KVL ①  $-12 + 2k i_1 + 4k(i_1 - i_2) = 0$

②  $4k(i_2 - i_1) + 6k i_2 = 0$


...  $i_2 = \frac{12}{11} \text{ mA}$

$i_a = -\frac{12}{11} \text{ mA}$

2)

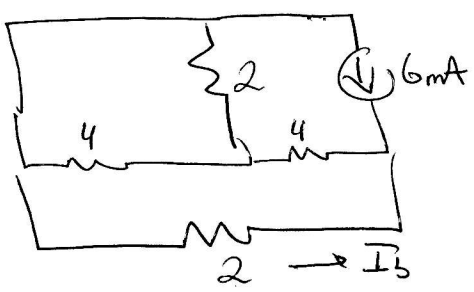

Redraw:

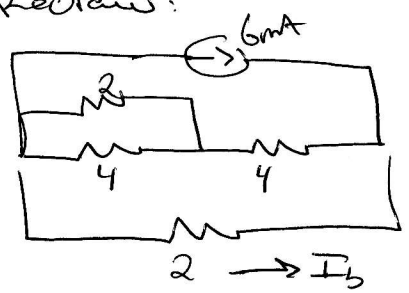


current division

$$\Rightarrow I_b = \left[ \frac{(2 \parallel 4 + 4)}{(2 \parallel 4 + 4) + 2} \right] \cdot 6 \text{ mA}$$

$= -\frac{48}{11} \text{ mA}$  ← note current direction


∴  $I_0 = I_a + I_b$

13. 1)

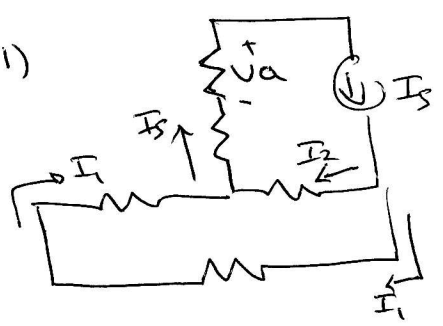

$V_a = - (4 \text{ mA})(2 \text{ k}\Omega) = -8 \text{ V}$

2)

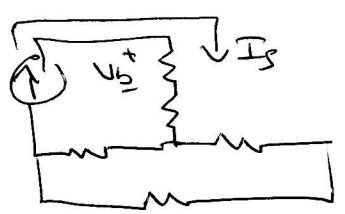

$V_b = (6 \text{ mA})(2 \text{ k}\Omega) = 12 \text{ V}$

∴  $V_0 = V_a + V_b = \underline{4 \text{ V}}$