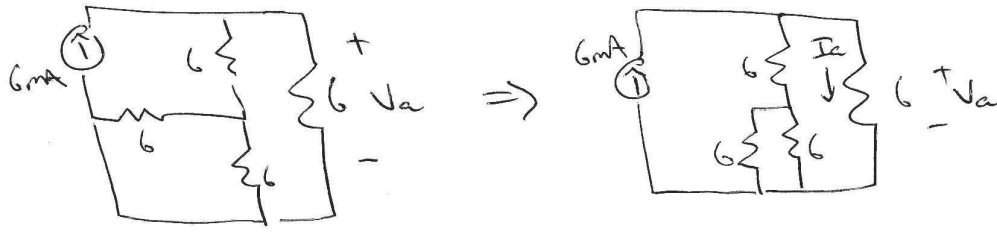


chp 5.

#15
1)



$$I_a = \left[\frac{3+6}{(4/6+6)+6} \right] \cdot 6mA = \frac{18}{5} mA \rightarrow V_a = \left(\frac{18}{5} \right) (6k) = 21.6V$$

2)




KVL ① $12 + 6i_1 + 6(i_1 - i_2) = 0$
 ② $6(i_2 - i_1) + 6i_2 + 6i_2 = 0$
 $\rightarrow i_1 = 3i_2$

$$\rightarrow i_2 = -\frac{2}{5} mA \text{ so } V_b = \left(-\frac{2}{5} \right) (6) = -2.4V$$

$$V_o = V_a + V_b = \underline{\underline{19.2V}}$$


17

1)

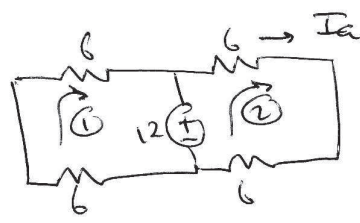


KVL ① $6i_1 + 12 + 6i_1 = 0 \rightarrow i_1 = -1mA$
 ② $-12 + 12i_2 = 0 \rightarrow i_2 = 1mA = I_a$

2)

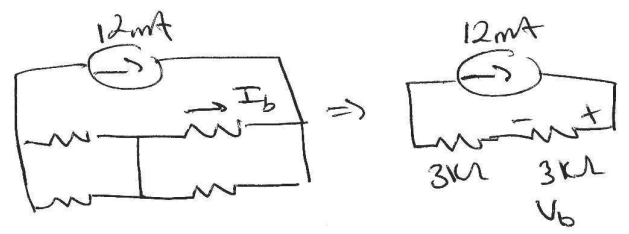


$V_b = 36V$ so hence

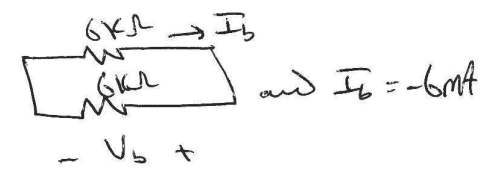

3)


similarity

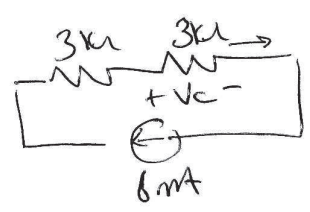

$V_c = 18V \rightarrow I_c = +3mA$

$$I_o = I_a + I_b + I_c = -2mA$$

21. 1)

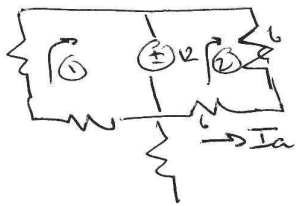


$\sum V = 0 \Rightarrow -12 + 12i_2 = 0$

$i_2 = -i_1 = 1 \text{ mA}$


$\therefore i_1 = -1 \text{ mA}$

(57)

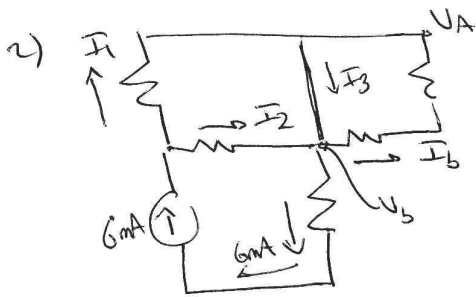

$i_1 = i_3$ since right loop is shorted

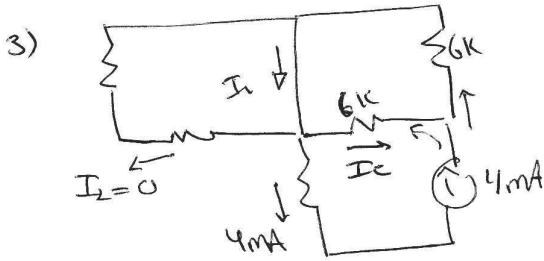$(V_a = V_b = 0 \rightarrow \underline{i_3 = 0})$




resistance in 2 paths is equal, so $i_3 = 4 \text{ mA}$ splits evenly:

$i_C = -2 \text{ mA}$



Lec 26

Chap 5 # 23.

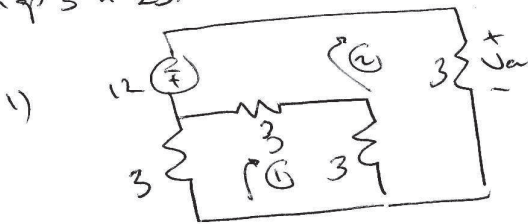

$\textcircled{1} 3k i_1 + 3k(i_1 - i_2) + 3k(i_1 - i_2) = 0$
 $\rightarrow 3i_1 = 2i_2$

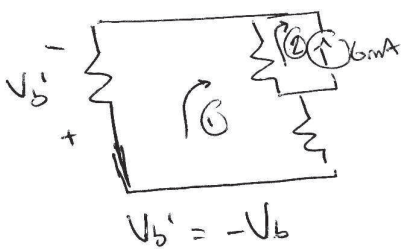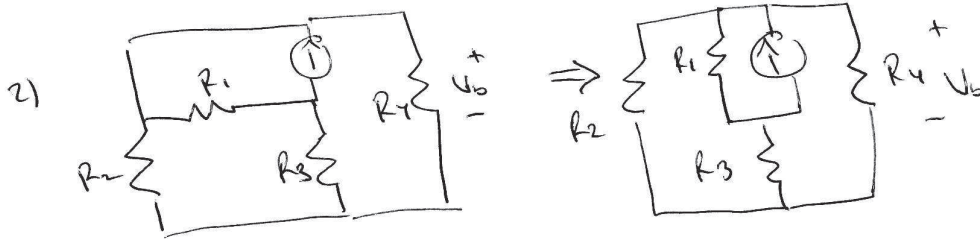$\textcircled{2} 6k(i_2 - i_1) + 12 + 3k i_2 = 0$
 $i_2 = \frac{-12}{5} \text{ mA} \rightarrow V_a = \frac{-36}{5} \text{ V}$




$i_2 = -6 \text{ mA}$
 $\textcircled{1} (R_2 \parallel R_4) i_1 + R_1(i_1 - i_2) + R_3 i_1 = 0$

$i_1 = -2.4 \text{ mA}$

$V_b' = -3.6 \text{ V}$

$V_b = \underline{\underline{+3.6 \text{ V}}}$

33.

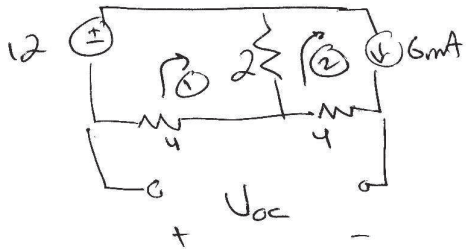


$$i_2 = 6 \text{ mA}$$

$$\textcircled{1} -12 + 2k(i_1 - 6 \text{ mA}) + 4ki_1 = 0$$

$$i_1 = 4 \text{ mA}$$
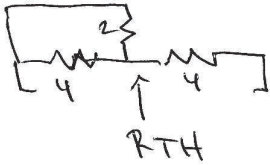
$$\# V_{oc} = -(4ki_1 + 4ki_2) = -40 \text{ V}$$





$$R_{TH} = 4 + 4 \parallel 4 = 5.3 \text{ k}\Omega$$



$$I_0 = \frac{-40}{(R_{TH} + 2k)}$$

Lec 27.

52

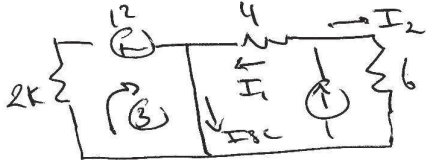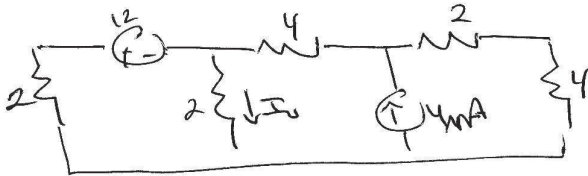


$$I_2 = \left(\frac{4}{10}\right) 4 \text{ mA} \quad I_1 = \left(\frac{6}{10}\right) 4 \text{ mA}$$


$$I_{sc} = I_1 + I_3 = -3.6 \text{ mA}$$

$$\textcircled{3} 2ki_3 + 4 = 0$$


$$i_3 = -6 \text{ mA}$$

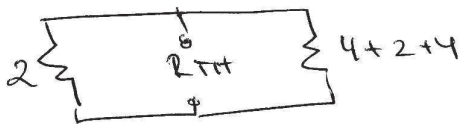
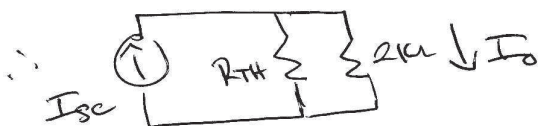
$$R_{TH} = 2 \parallel 10 = 1.67 \text{ k}\Omega$$


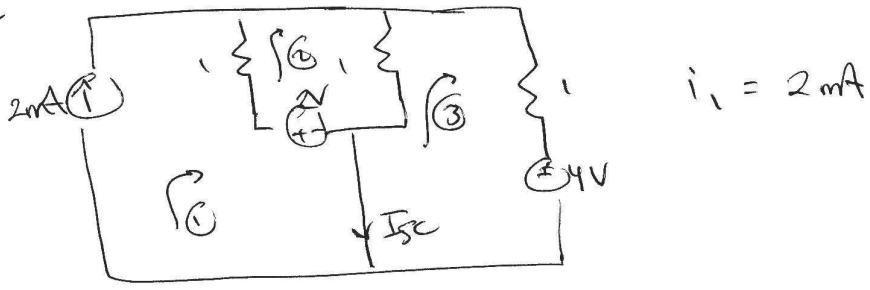
$$I_0 = \left(\frac{R_{TH}}{2k + R_{TH}}\right) I_{sc} = -1.6 \text{ mA}$$




① ~~$i_1 - i_2 + 2 = 0$~~

② $-2 + 1k(i_2 - i_1) + 1k(i_2 - i_3) = 0$


③ $1k(i_3 - i_2) + 1ki_3 + 4 = 0$

$\Rightarrow i_3 = \frac{-4}{3} \text{ mA}$

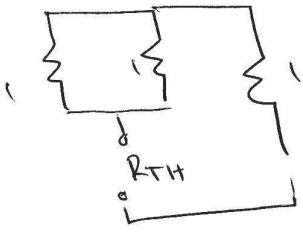$I_{sc} = I_1 - I_3 = \frac{10}{3} \text{ mA}$










$R_{TH} = (1k || 1k) + 1k = 1.5k\Omega$

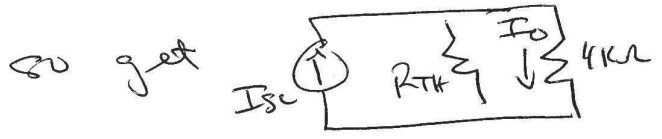

$I_o = \left(\frac{R_{TH}}{R_{TH} + 4k} \right) I_{sc} = 0.91 \text{ mA}$

85.

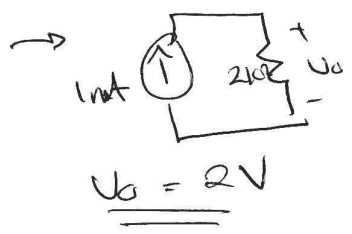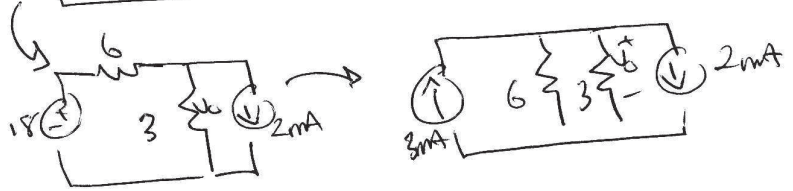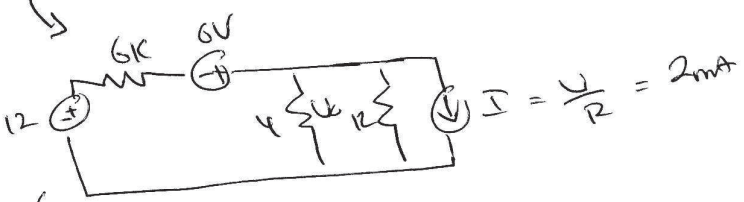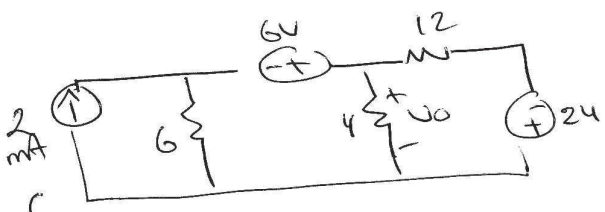

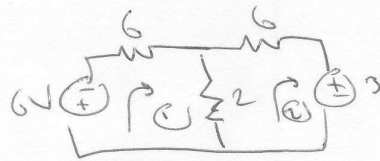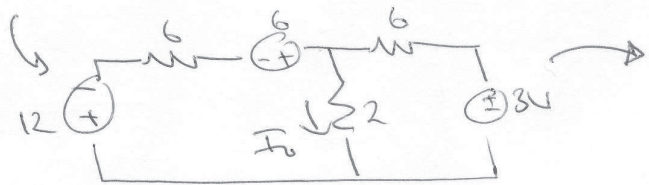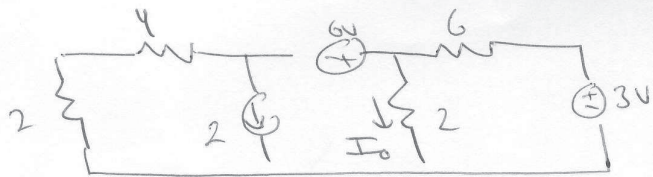

$$\textcircled{1} \quad 6 + 6i_1 + 2(i_1 - i_2) = 0 \quad \textcircled{2} \quad 2(i_2 - i_1) + 6i_2 + 3 = 0$$

$$\dots \quad i_1 = -0.9 \text{ mA}, \quad i_2 = -0.6 \text{ mA}$$

$$I_0 = i_1 - i_2$$

$$= \underline{\underline{-0.3 \text{ mA}}}$$