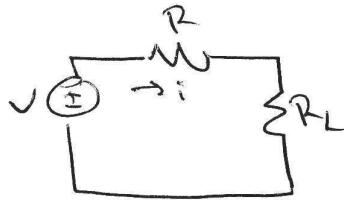


Lec 28

(1)


For circuit



Max Power delivered to load if $R = R_L$


R like Thevenin equiv circuit.

#106. For R_{TH} :



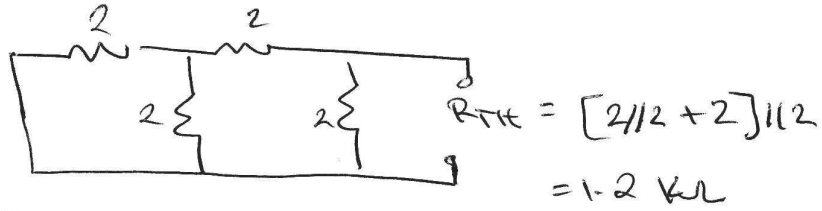


and $R_L = R_{TH}$


108. For R_{TH}

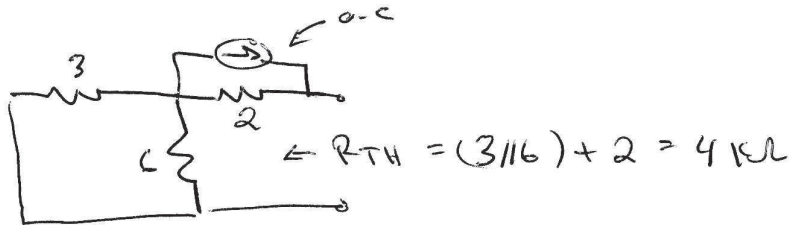

To find power, need V_{oc} :

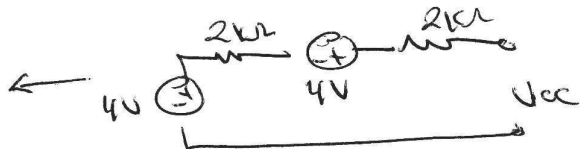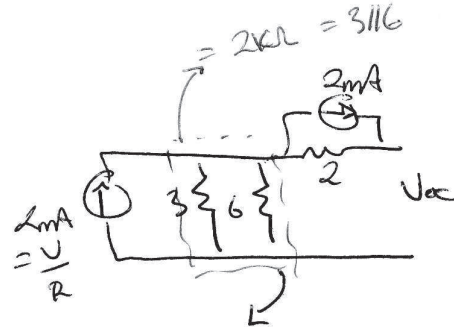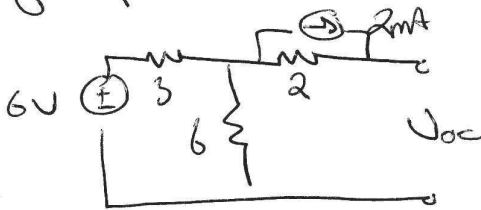


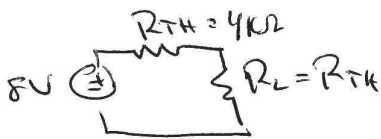
$\therefore V_{oc} = 8V$ and power is $P = I^2 R$



$$= \left(\frac{8}{8k\Omega}\right)^2 (4k\Omega) = \underline{\underline{4mW}}$$

111.

52

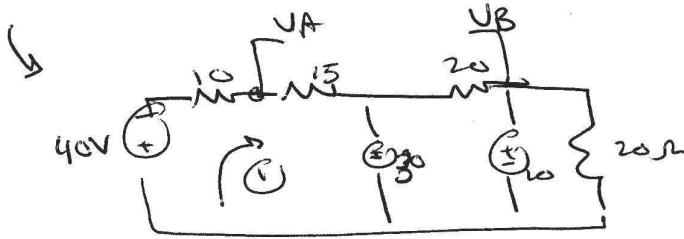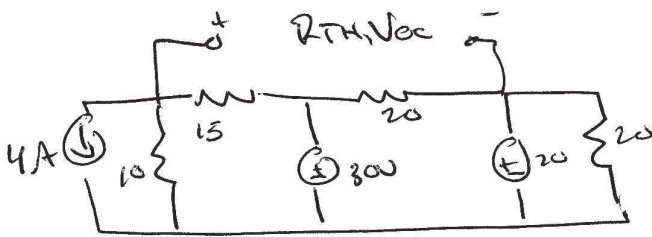

KVL @

$$+40 + 25i_1 + 30 = 0$$

$$i_1 = -2.8 \text{ A}$$

$$V_{10\Omega} = -28 \text{ V}$$


$$\therefore V_A = -40 - (-28) = -12 \text{ V}$$

i.e



and $V_B = +20 \text{ V}$ (by inspection)
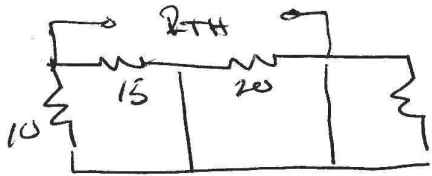
$$\therefore V_{oc} = V_A - V_B = \underline{\underline{-32 \text{ V}}}$$




$$R_{TH} = 10 \parallel 15 = 6 \Omega$$




∴ get



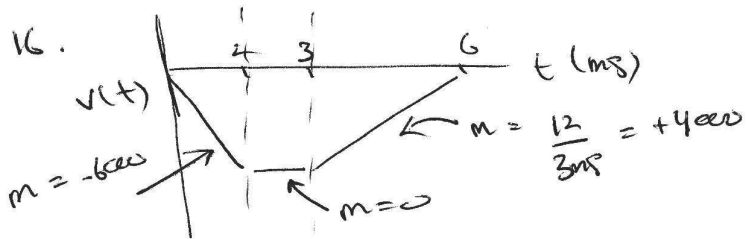
$$P_L = I^2 R = \left(\frac{-32}{12}\right)^2 \cdot 6 = \underline{\underline{42.7 \text{ W}}}$$


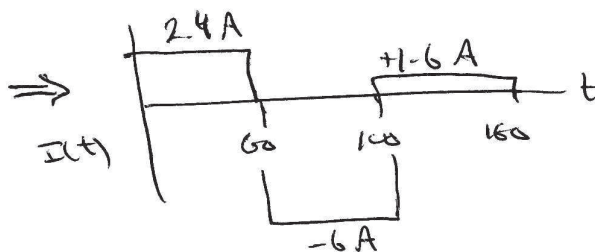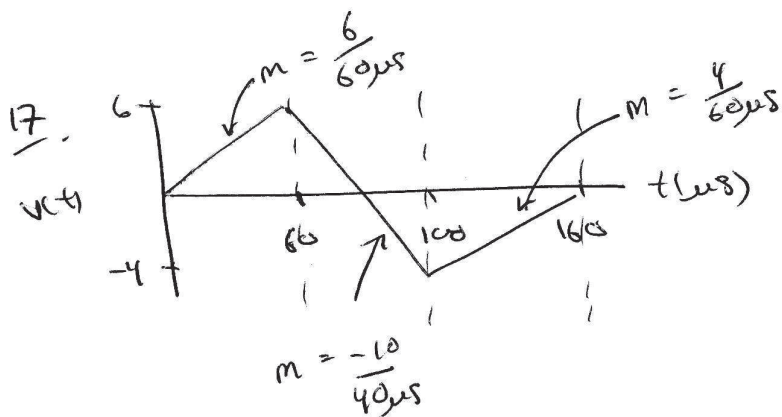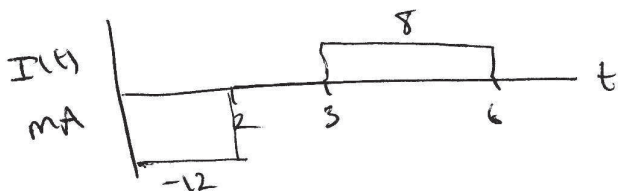
$$I_c = C \cdot \frac{\partial V}{\partial t}, \quad C = 2 \mu F$$




$$C = 24 \mu F$$

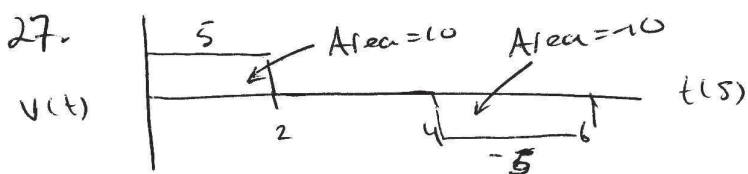

$$V_L = L \frac{di}{dt}$$

$$I = \frac{1}{L} \int V(t) dt$$

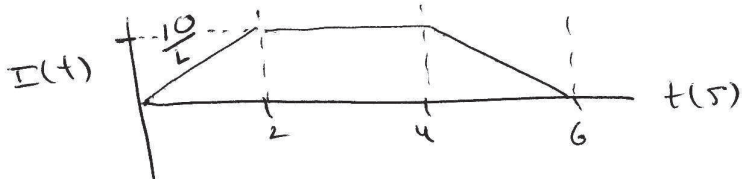


check:

$m = \frac{10}{2-0}$ $m = 0$ $m = \frac{-10}{2L}$

$\therefore V = 5$ $V = 0$ $V = -5$

65.

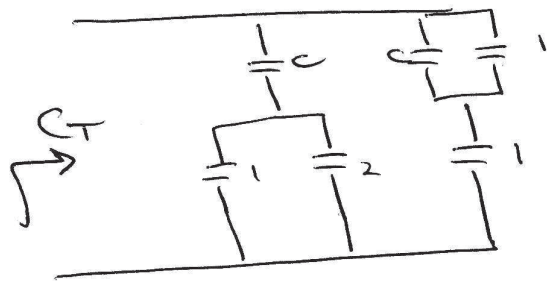


$$C_T = \left(\frac{1}{c+1} + \frac{1}{1} \right)^{-1} + \left(\frac{1}{c} + \frac{1}{3} \right)^{-1}$$


$$1 = \frac{c+1}{c+2} + \frac{3c}{c+3}$$

$$= \frac{4c^2 + 10c + 3}{c^2 + 5c + 6}$$


$$\dots \quad c = 0.468 \mu\text{F}$$

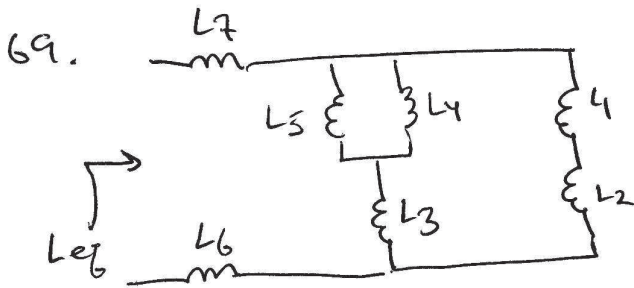
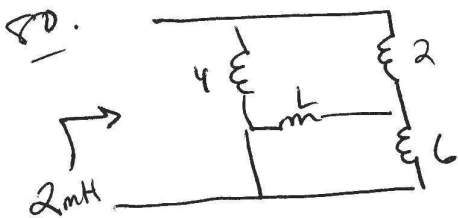
$$L_{eq} = L_7 + \left[\left(\frac{1}{L_5 + L_4} \right) + \frac{1}{L_3 + \left(\frac{1}{L_4} + \frac{1}{L_2} \right)^{-1}} \right]^{-1} + L_6$$



$L_{eq} \Leftrightarrow$

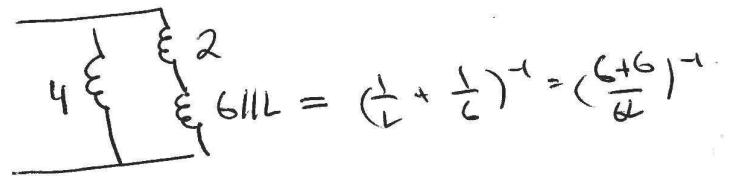

$$L_{eq} = 2mH = \left(\frac{1}{4} + \frac{1}{2 + \frac{6}{6+L}} \right)^{-1} = \frac{48 + 32L}{36 + 12L}$$




$$\underline{\underline{L = 3mH}}$$

(64)

Lec 30

Chap 7.

#16 1) $i(t) = K_1 + K_2 e^{-t/\tau}$

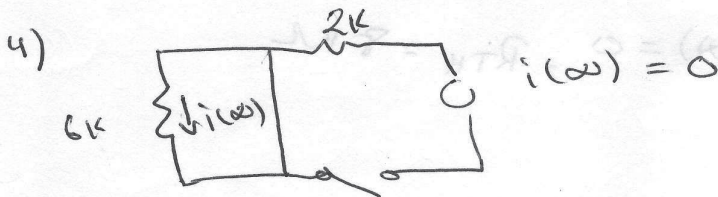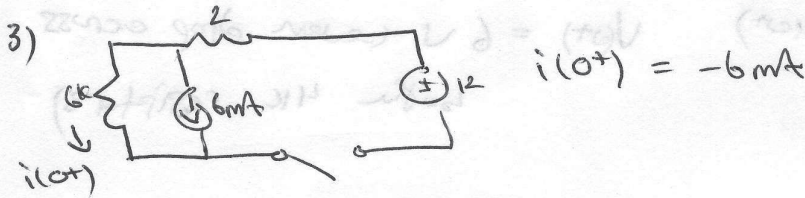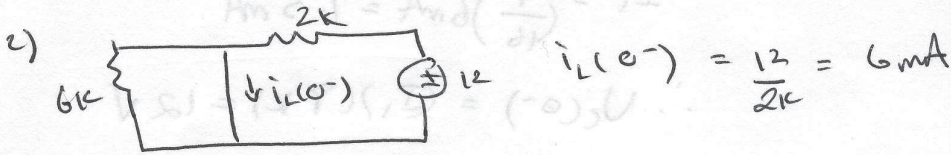

5) $R_{TH} = 6k\Omega$ and $\tau = \frac{L}{R_{TH}} = \frac{2H}{6k\Omega}$


$i(0^+) = K_1 + K_2$

$i(\infty) = K_1 = 0 \rightarrow K_2 = -6 \text{ mA}$


$\therefore i(t) = (-6 \text{ mA}) e^{-t/\tau}$

17.

2)

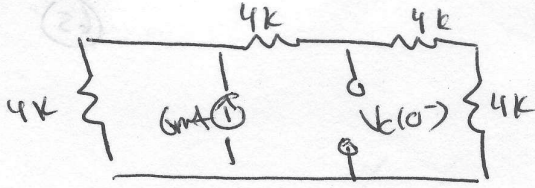


⇒

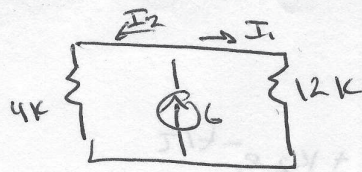

$$I_1 = \left(\frac{4}{16}\right) 6 \text{ mA} = 1.5 \text{ mA}$$


$$\therefore V_c(0^-) = (I_1)(12 \text{ k}) = 12 \text{ V}$$

3)

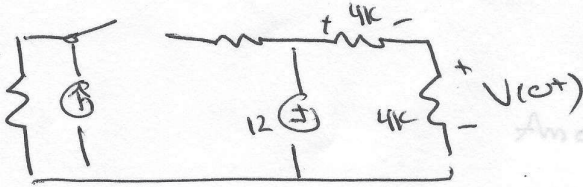

$$V_c(t+) = 6 \text{ V (even drop across both 4k resistors)}$$

4)

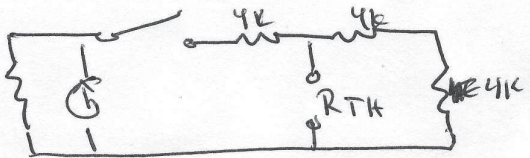

$$V_c(t) = 0, R_{TH} = 8 \text{ k}\Omega$$

$$V_c(t+) = V_1 + V_2$$

$$V_c(\infty) = V_1 = 0 \rightarrow V_2 = 6 \text{ V}$$

$$\tau = RC = (8 \text{ k})(100 \mu)$$

$$\text{and } V_c(t) = 6e^{-t/\tau}$$