


Lec 35

chp 8.

5. $I_c = e \frac{dV}{dt}$

c) $= e \frac{d(10 \cos(377t - 30^\circ))}{dt}$
 $= (e)(10)(-377) \sin(377t - 30^\circ)$
 $= 3770e \sin(377t + 150^\circ)$

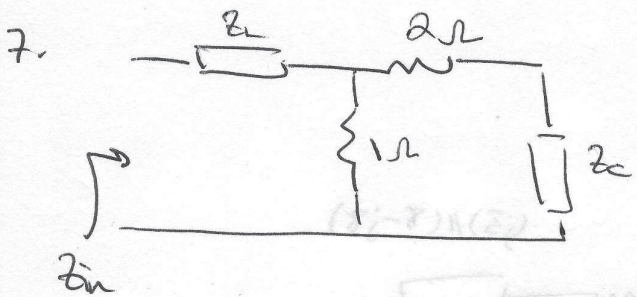
b) $I_c = (e)(12)(377) \cos(377t + 60^\circ)$



$Z_c = \frac{1}{j\omega C} = \frac{1}{j(2\pi)(60)(10 \times 10^{-6})}$
 $= -j265.3 \Omega$
 $Z_L = j\omega L = j(2\pi)(60)(10 \times 10^{-3})$
 $= j3.7 \Omega$


$Z_{in} = Z_L + [1 \parallel (2 + Z_c)]$
 $= Z_L + \left(\frac{1}{1} + \frac{1}{2 - j265} \right)^{-1}$
 $= Z_L + \frac{2 - j265}{3 - j265} \approx 1$

$\approx 1 + Z_L$

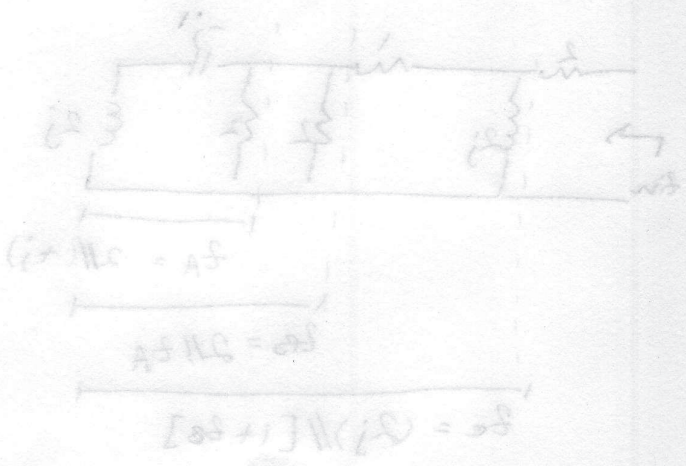

$\frac{1}{Z_{in}} = \frac{1}{Z_L + [1 \parallel (2 + Z_c)]}$
 $\frac{1}{Z_{in}} = \frac{1}{j\omega L + \left(\frac{1}{1} + \frac{1}{2 - j265} \right)^{-1}}$
 $\frac{1}{Z_{in}} = \frac{1}{j3.7 + \frac{2 - j265}{3 - j265}}$

8.

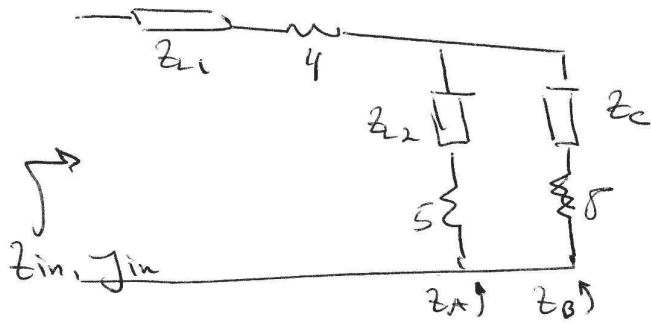

$$Z_{L1} = j\omega L$$

$$= j(10)(0.01) = 1j \Omega$$

$$Z_{L2} = 2j \Omega$$

$$Z_c = \frac{1}{j\omega C} = \frac{1}{j(10)(0.01)} = -j10 \Omega$$



$$Z_{in} = Z_{L1} + 4 + Z_A \parallel Z_B$$

$$\text{and } Z_A = Z_{L2} + 5 = 5 + j2$$

$$Z_B = Z_c + 8 = 8 - j10$$


$$\text{and } j_{in} = \frac{1}{Z_{in}}$$

9.

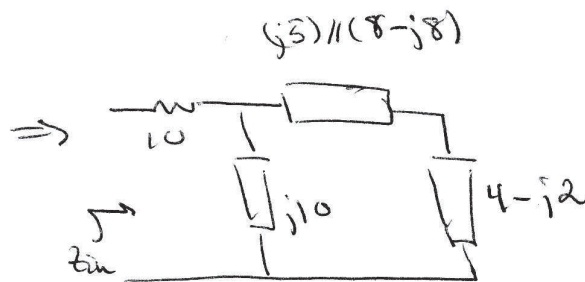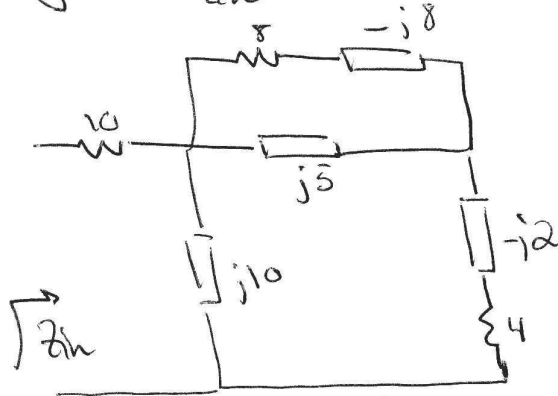

$$Z_{in} = 10 + (j10) \parallel [(j5 \parallel (8 - j8)) + 4 - j2]$$

11.

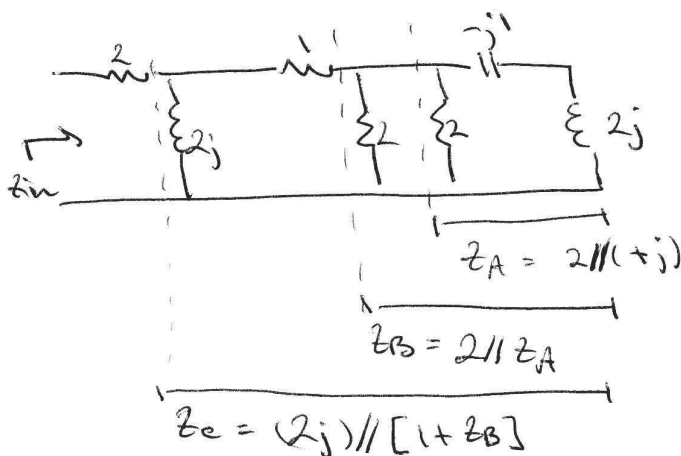


$$Z_A = 2 \parallel (1 + j)$$

$$Z_B = 2 \parallel Z_A$$

$$Z_c = (2j) \parallel [1 + Z_B]$$

$$Z_{in} = 2 + Z_c$$

16.

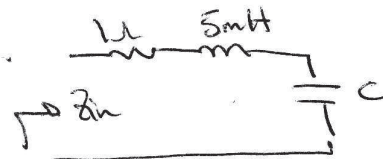

Need $Z_L = -Z_c$ and then

$$Z_{in} = 1 + Z_L + Z_c = 1$$

$$Z_L = j\omega L = j(2\pi)(60)(5 \times 10^{-3})$$

$$= j1.9$$

$$Z_c = \frac{1}{j\omega C} = \frac{-j}{\omega C}$$


$$\therefore \frac{1}{\omega C} = 1.9 \rightarrow C = \underline{\underline{1.4 \times 10^{-3} \text{ F}}}$$

Lec 36

chap 8

$v(t) = 50 \cos(100t) \rightarrow \omega = 100$

29.

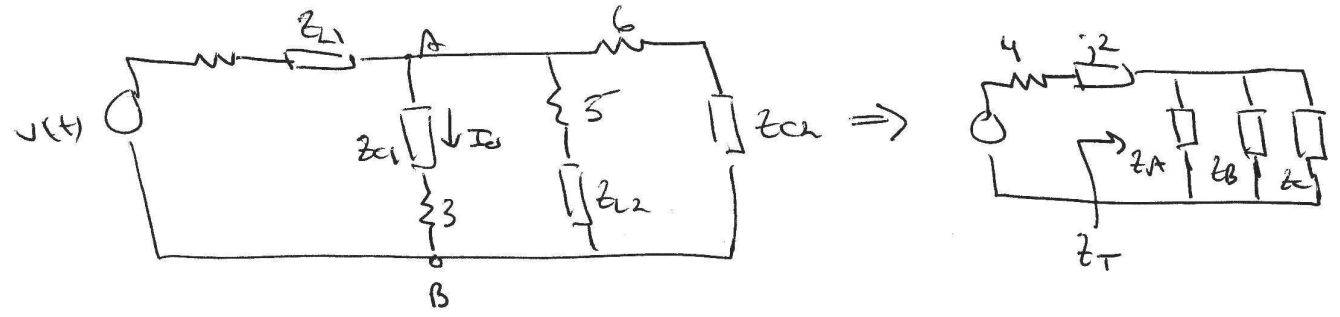


Find voltage V_{AB} and then find I_0 through branch $Z = 3 + z_{c1} = 3 - j5 \Omega$

$z_B = 5 + j5 \quad z_c = 6 - j10$

$z_T = \left(\frac{1}{z_A} + \frac{1}{z_B} + \frac{1}{z_C} \right)^{-1}$

$= \dots = 3.4 - j1.8$

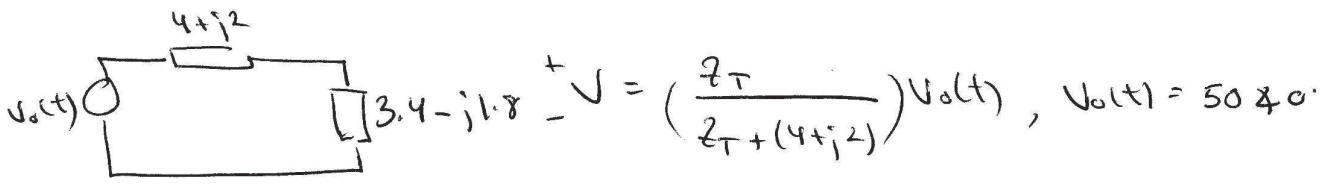


$V = \left(\frac{z_T}{z_T + (4 + j2)} \right) v(t), \quad v(t) = 50 \angle 0^\circ$

$\approx 26.4 - 29^\circ$

and $I_0 = \frac{V}{3 - j5}$

$\approx \underline{\underline{4.44 \angle 30^\circ \text{ A}}}$


30.

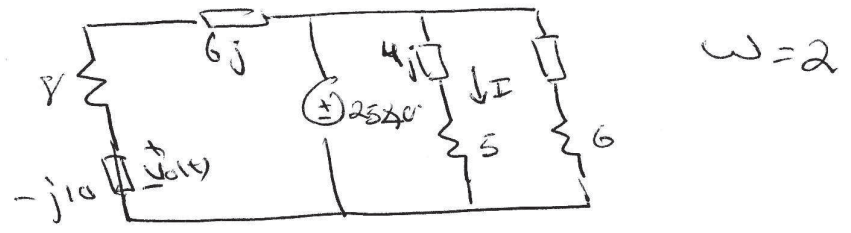

$$I(t) = \frac{25\angle 0^\circ}{5+j4} = 4.4-39^\circ \text{ A}$$

$$V_o(t) = \left(\frac{-j10}{8-j10+j6} \right) (25\angle 0^\circ) = \underline{\underline{28.4-63^\circ \text{ V}}}$$

34.

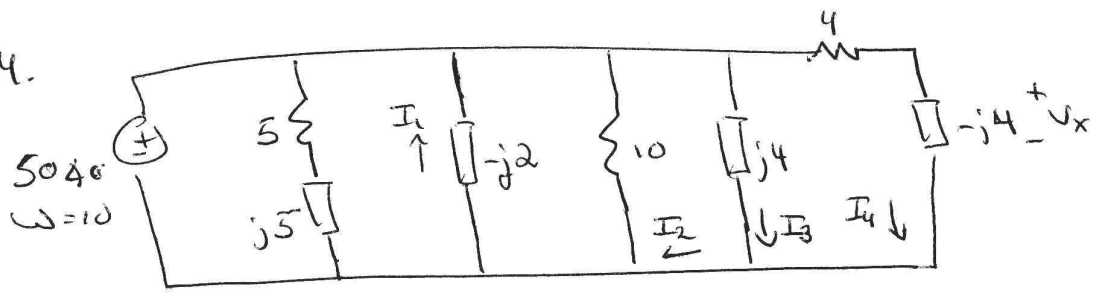


$$V_x = \left(\frac{-j4}{4-j4} \right) (50\angle 0^\circ) = 35.4-45^\circ$$

$$I_1 = \frac{-50}{-j2} = 25\angle -90^\circ$$

note direction of current

$$I_2 = I_3 + I_4 = \frac{50}{j4} + \frac{50}{4-j4} = \underline{\underline{9.4-45^\circ \text{ A}}}$$

41.

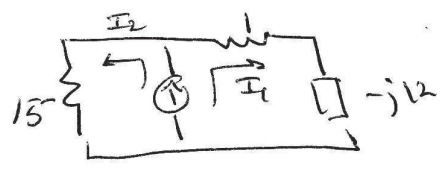

$$I_1 = \left(\frac{15}{1-j12+13} \right) (15\angle 30^\circ) = 3.7\angle 67^\circ$$

$$\therefore V_o = (I_1)(-j12) = \underline{\underline{45\angle -23^\circ \text{ V}}}$$