

# **ECE1371 Advanced Analog Circuits**

## **Lecture 11**

# **SWITCHING REGULATORS**

**Richard Schreier**

`richard.schreier@analog.com`

**Trevor Caldwell**

`trevor.caldwell@utoronto.ca`


**Many thanks to Jonathan Audy for the material from his 2008 ISSCC Tutorial on Power Management and to Prof. Aleks Prodic for his many helpful comments.**

## **Course Goals**

- **Deepen understanding of CMOS analog circuit design through a top-down study of a modern analog system**  
The lectures will focus on Delta-Sigma ADCs, but you may do your project on another analog system.
- **Develop circuit insight through brief peeks at some nifty little circuits**  
The circuit world is filled with many little gems that every competent designer ought to know.


Date	Lecture		Ref	Homework
2008-01-07	RS	1	Introduction: MOD1 & MOD2	S&T 2-3, A Matlab MOD2
2008-01-14	RS	2	Example Design: Part 1	S&T 9.1, J&M 10 Switch-level sim
2008-01-21	RS	3	Example Design: Part 2	J&M 14 Q-level sim
2008-01-28	TC	4	Pipeline and SAR ADCs	J&M 11, 13 Pipeline DNL
2008-02-04	ISSCC– No Lecture			
2008-02-11	RS	5	Advanced $\Delta\Sigma$	S&T 4, 6.6, 9.4, B $\Delta\Sigma$ Toolbox; Proj.
2008-02-18	Reading Week– No Lecture			
2008-02-25	RS	6	Comparator & Flash ADC	J&M 7
2008-03-03	TC	7	SC Circuits	J&M 10
2008-03-10	TC	8	Amplifier Design	
2008-03-17	TC	9	Amplifier Design	
2008-03-24	TC	10	Noise in SC Circuits	S&T C
2008-03-31	RS	11	Switching Regulator	
2008-04-07	Project Presentation			
2008-04-14	TC	12	Matching & MM-Shaping	Project Report

## NLCOTD: High-Side Current Sensing

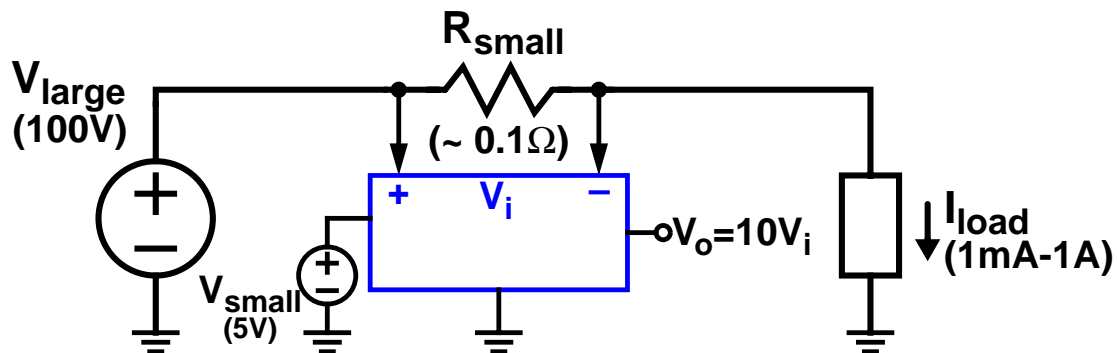

- **Want to amplify a small differential voltage which has a large common-mode component**  
The common-mode component is large because we don't want (or can't have) a resistor in the low-side (ground) path.

# NLCOTD: H-Bridge Application

 


- The sense resistor is switched between the supply and ground, so it is not possible to sense the load current without also sensing a large common-mode component

ECE1371

11-5

# NLCOTD: Differential Amplifier?

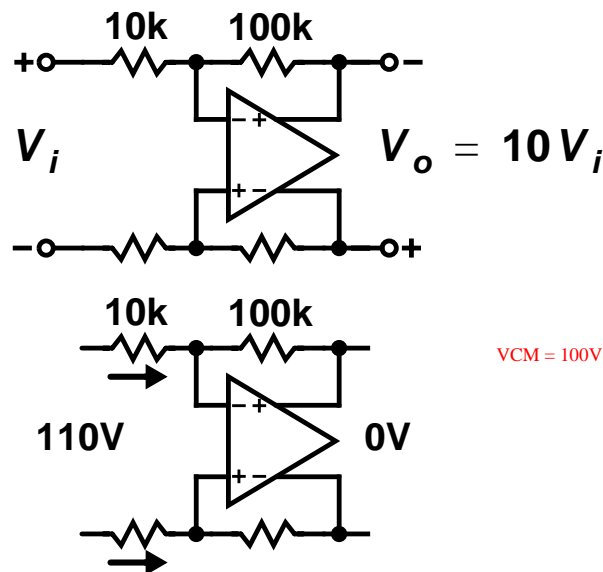

- Amplifier sees high CM voltage
- CM current + resistor mismatch  $\Rightarrow$  offset

ECE1371

11-6

# Highlights

(i.e. What you will learn today)

- 1 Basic Buck and Boost Topologies
- 2 Design Considerations
- 3 Inverting Buck-Boost, SEPIC and Çuk Topologies
- 4 Basic Control Strategies


ECE1371

11-7

## Review: A Switched Inductor

- When a constant voltage is applied across an inductor, the current ramps up with a constant slope


At least until the core starts to saturate.

 

ECE1371

11-8


# Review: Opening the Switch

 

ECE1371

11-9

# The Power Converter Problem

 

- **Battery voltage usually does not equal the desired load voltage**  
Often there are many loads and many voltage requirements.  
Even the voltage requirements of a single load can vary with time, e.g. a CPU or DSP with power-saving.
- **Battery voltage changes as the battery is charged/discharged**

ECE1371

11-10


# Features & Specifications

- 1 Input/Output Voltages and Currents
  - 2 Efficiency
  - 3 Voltage ripple
  - 4 Line/load regulation; source/sink capability
  - 5 Dynamics: response to line/load step; overshoot
  - 6 Over-current and over-voltage protection
  - 7 Under-voltage lockout; thermal shutdown
  - 8 Soft startup; adjustability
  - 9 Frequency synchronization
- **Plus absolute reliability**– if a power converter behaves badly for even  $1\mu\text{s}$ , the entire system may be destroyed  
When it comes to power, mistakes can be forever.

ECE1371

11-11

## Linear Regulator

 


- **Just a high-power voltage follower**
- $V_o < V_i$   
The “dropout voltage” is the minimum  $V_i - V_o$  required for proper regulator operation.  
PMOS FET used to make a low-dropout (LDO) reg.
- **Inefficient**  
E.g. if  $V_i = 4\text{ V}$  and  $V_o = 1\text{ V}$ , then  $\eta_{\text{max}} = 25\%$ .

ECE1371

11-12
 
# Switching Regulator— Buck Configuration





- Energy is transferred from the battery to the inductor, capacitor and load when the switch is up
- Energy stored in the inductor is transferred to the capacitor and load when the switch is down
- + Ideally, energy is not dissipated in the regulator  
Typically,  $\eta > 90\%$ .

ECE1371


11-13

## Buck Waveforms— Ideal

  

$$\Delta I = t_1 \left( \frac{V_i - V_o}{L} \right)$$

$$= t_2 \left( \frac{V_o}{L} \right)$$

 

$$\Delta V = Q/C$$

$$= \frac{V_o(1-D)}{8LCf^2}$$

ECE1371

11-14

# Buck Formulae

- $V_o = DV_i$ , where  
 $D \equiv t_1 / (t_1 + t_2)$  is the *duty cycle*
- Ripple current is  $\Delta I / 2 = (t_2 V_{out}) / (2L)$   
 Up to 40% of peak  $I_o$
- Example:  $V_i = 4 \text{ V}$ ,  $V_o = 1 \text{ V}$ ,  $T = 1 \mu\text{s}$   
 $D = V_o / V_i = 0.25 \Rightarrow t_1 = 0.25 \mu\text{s}$ ,  $t_2 = 0.75 \mu\text{s}$




Want  $I_o = 1 \text{ A}$ , and say  $\Delta I = 0.75 \text{ A}$

$$\Rightarrow L = \frac{t_2 V_{out}}{\Delta I} = \frac{0.75 \mu\text{s} \cdot 1 \text{ V}}{0.75 \text{ A}} = 1 \mu\text{H}$$

Want  $\Delta V = 20 \text{ mV} \Rightarrow$

$$C = \frac{V_o(1-D)}{8Lf^2\Delta V} = \frac{1 \text{ V} \cdot 0.75}{8 \cdot 1 \mu\text{H} \cdot (1 \text{ MHz})^2 \cdot 20 \text{ mV}} = 5 \mu\text{F}$$

# Boost Configuration

   

$$\begin{aligned} \Delta I &= t_1 \left( \frac{V_i}{L} \right) \\ &= t_2 \left( \frac{V_o - V_i}{L} \right) \end{aligned}$$


$$V_o = \frac{V_i}{1-D}$$

$$\Delta V = t_1 I_o / C$$

$$= \frac{I_o \left( 1 - \frac{V_i}{V_o} \right)}{fC}$$


 
# Boost Converter with Diode (Old-fashioned)




- **SPDT switch implemented by a FET and a diode**  
Diode automatically turns on when FET turns off.  
Schottky diode minimizes losses.
- **Can do the same in a Buck converter, but the efficiency hit is usually unacceptable because  $V_{fwd}$  is a significant compared to  $V_{out}$**
- **Synchronous rectification is usually preferred**

ECE1371

11-17

# Multi-Output Boost

 


- **Use a single inductor to provide multiple outputs**  
Tricky control problem—a good research topic!
- **Can do both buck and boost with more switches**

ECE1371

11-18

# Inverting Buck/Boost

 

$$\Delta I = t_1 \left( \frac{V_i}{L} \right)$$

$$= t_2 \left( \frac{V_o}{L} \right)$$

$$\frac{V_o}{V_i} = \frac{D}{1-D}$$

$$\Delta V = t_1 I_o / C$$

$$= \frac{I_o}{fC \left( 1 + \frac{V_i}{V_o} \right)}$$

ECE1371

11-19


## Loss Mechanisms

- **Switch on-resistance**  
10 mΩ to 1 Ω.
- **Switch capacitance**  
 $C_{gs}$ : 100 pF to 1 nF;  $C_d$ : 20 to 200 pF.  
Limit switching frequency to limit this loss.
- **Inductor resistance**  
5 mΩ to 0.5 Ω.
- **Capacitor resistance**  
Equivalent Series Resistance (ESR)  
“Low ESR”: 100 mΩ for  $C = 10 \mu\text{F}$   
“Ultra-low ESR”: 10 mΩ for  $C = 10 \mu\text{F}$

ECE1371

11-20


# Effect of ESR on Voltage Ripple

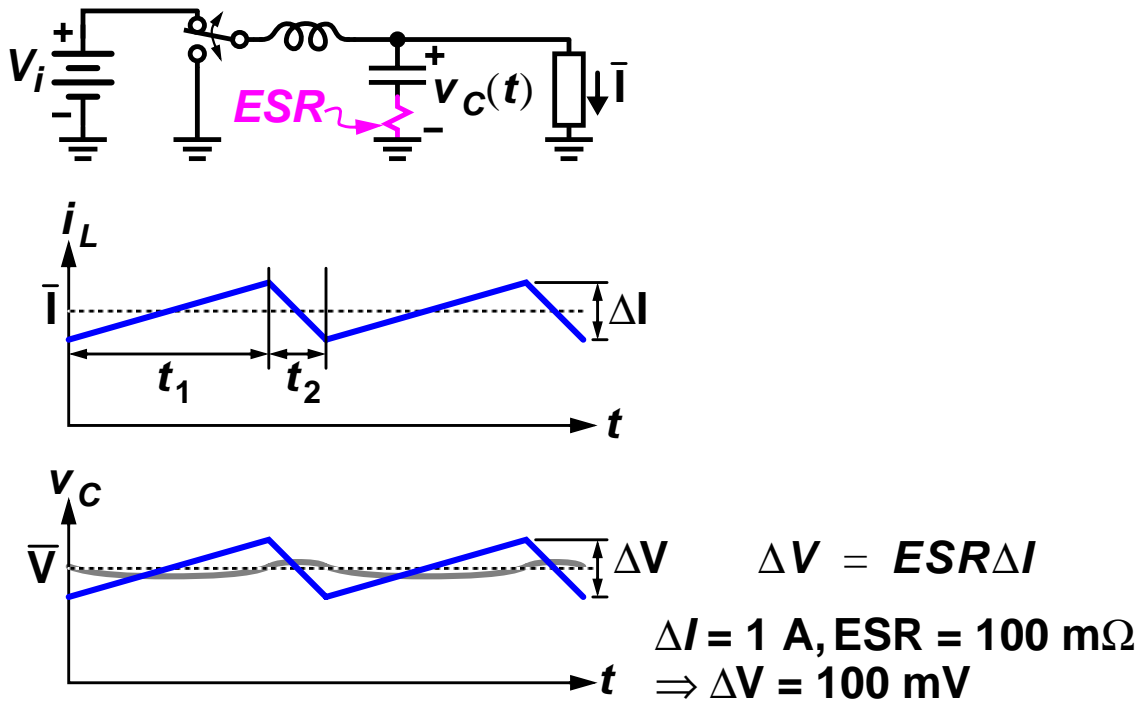

ECE1371

11-21

# Multi-Phase Buck Converter

 


- $n$  synchronized switches drive  $n$  inductors in an interleaved manner
- + Reduces ripple voltage  
Can achieve  $\Delta V \sim 10\text{mV}$  when driving 100A!

ECE1371

11-22

# Example Multi-phase Converter

## 1.5 V 60 A 3 $\phi$ for AMD Processor

 


ECE1371

11-23

 
## Improved Topologies

**SEPIC:** “Single-Ended Primary Inductor Converter”



+ Input current is continuous

**Cuk:**

 


+ Input and output currents are continuous

- Output voltage is negative


ECE1371

11-24


# SEPIC Operation

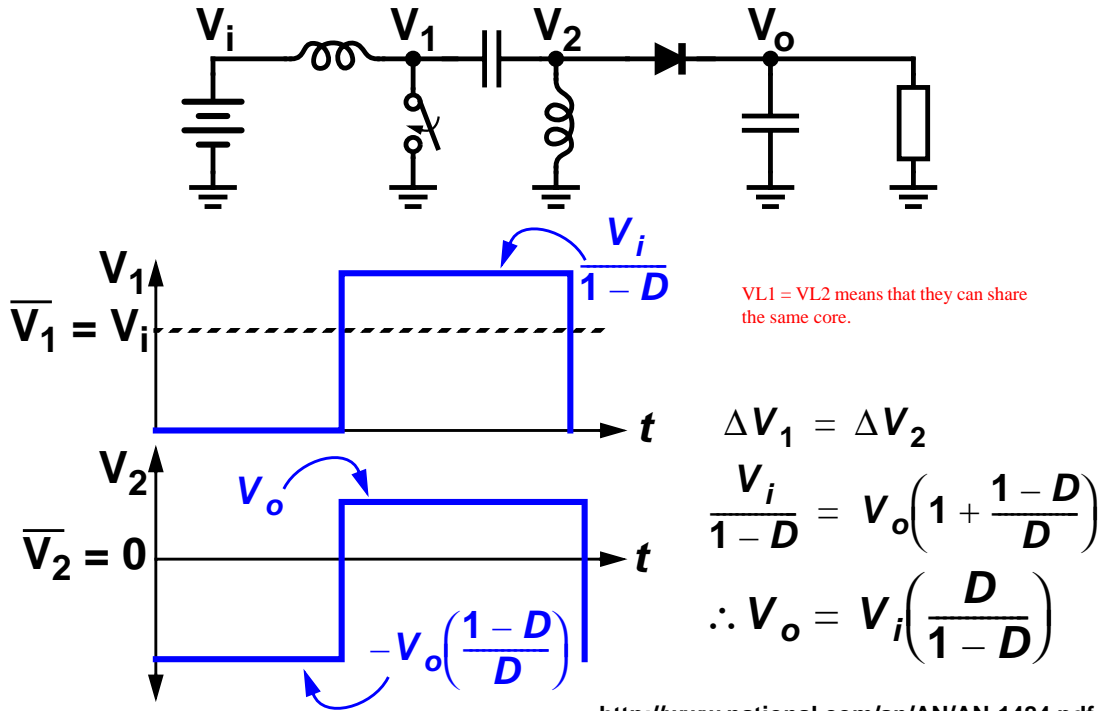

# Cuk Operation

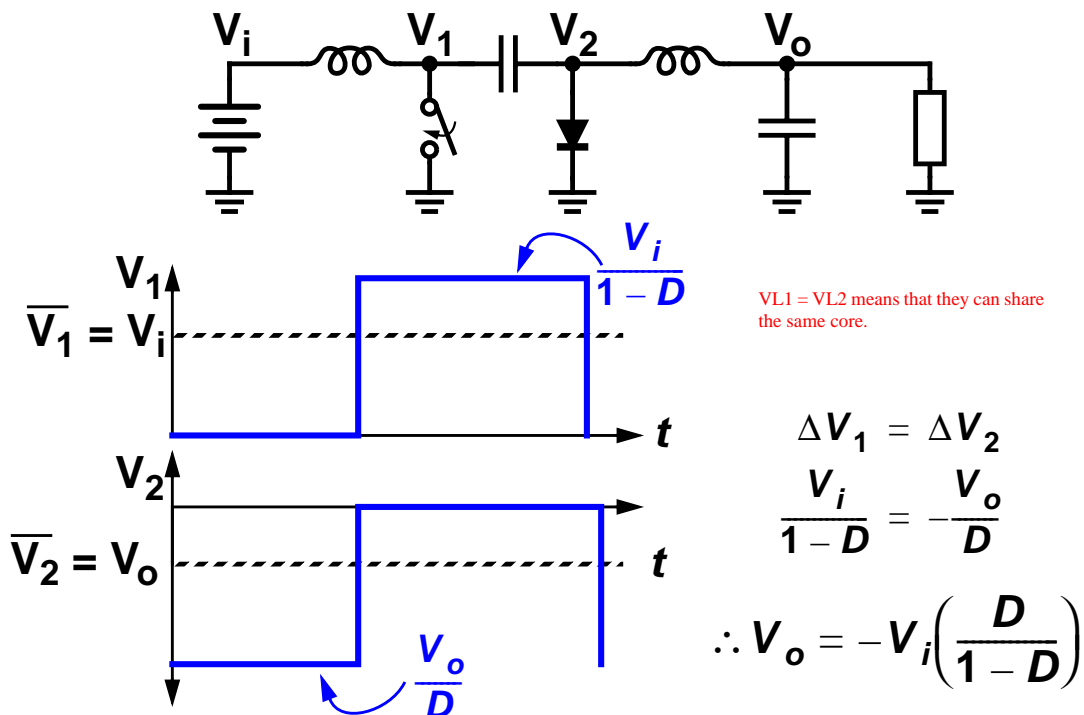

# Load Removal Buck Converter

 

- If the load current drops to zero, the inductor's energy is dumped into the capacitor and the output voltage goes up

$$\frac{1}{2}LI^2 + \frac{1}{2}CV^2 = \frac{1}{2}C(V + \Delta V)^2$$

$$\Rightarrow \frac{\Delta V}{V} = \sqrt{\frac{LI^2}{CV^2} + 1} - 1 \approx \frac{LI^2}{2CV^2} \sim 10\% \text{ for our ex.}$$

⇒ Need to increase  $C$  to make  $\Delta V$  acceptable



## Exceptional Case— Discontinuous Conduction Mode

- “Switching Regulators are about 20% basic concept, and 80% fixes to problems with the basic concept” [Audy, 2008 ISSCC]
- Discontinuous Conduction Mode (DCM) occurs in a diode-based switcher if the inductor current goes to zero

DCM does not occur if a diode is not used to make the switch, unless a zero-crossing detection circuit is added to the synchronous rectifier

- DCM improves  $\eta$  at low  $I_o$   
But since DCM dynamics differ from CCM dynamics, fancier control algorithms are needed.


# DCM in a Buck Converter

  


$i_L$  hits zero if  $\Delta I = 2I_o$

$$\frac{t_2 V_o}{L} = \frac{(1-D)V_o}{fL} = 2I_o$$
 
$$I_o = \frac{(1-D)DV_i}{2fL} = \frac{(V_o/V_i)(1-V_o/V_i)V_i}{2fL}$$





## DCM in a Buck Converter (cont'd)

 

$$D = \frac{t_1}{T} = \sqrt{\frac{2fLV_o I_o}{V_i(V_i - V_o)}} \quad \leftarrow D \text{ now depends on lots of parameters}$$

$$I_{o, \min} = (t_{1, \min})^2 \frac{fV_i(V_i - V_o)}{2LV_o}$$


# DCM in a Boost Converter

  

$i_L$  hits zero if  $\Delta I = 2\bar{I}$


$$\frac{t_1 V_i}{L} = \frac{D V_i}{fL} = 2\bar{I} = \frac{2I_o}{1-D}$$
 
$$I_o = \frac{(1-D) D V_i}{2fL} = \frac{(V_i/V_o)(1 - V_i/V_o) V_i}{2fL}$$


 
## Control Strategies [Audy 2008]


- The control problem involves deciding when to open/close the switch



- Want to achieve a specific  $V_o$   
Except if load current is too great, or if the input voltage is too low, or ...
- SMPS control is a fertile research area



# Hysteretic Ripple Voltage Regulator

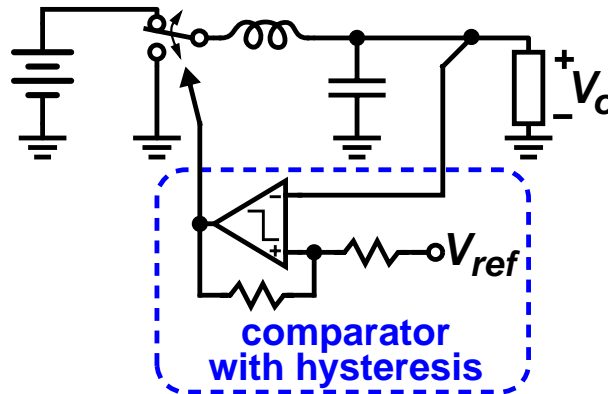


- If  $V_o < V_{ref}$ , turn on the switch and keep it on until  $V_o > V_{ref} + V_{hyst}$
- + Simple; fast; stable
- Behavior depends on ESR: ill-controlled dynamics & excess ripple; Nothing limits  $t_{on}$

ECE1371

11-33

# Constant $t_{on}$ Hysteretic Regulator

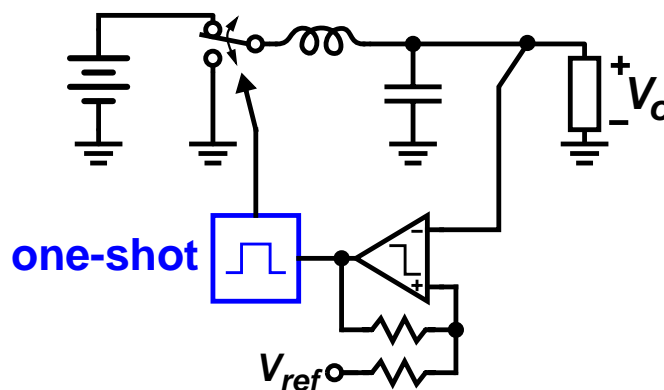


- $t_{on}$  is fixed
- Need to add circuitry to ensure minimum  $t_{off}$

ECE1371

11-34

# Constant-Frequency Voltage-Mode

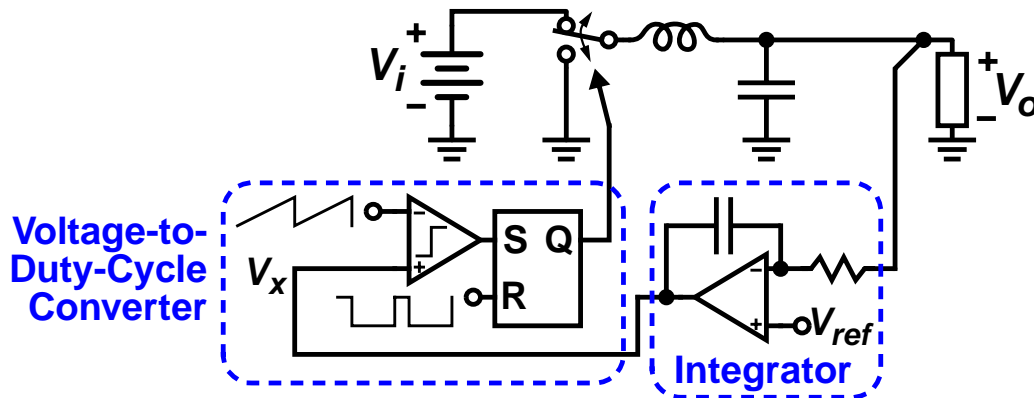



- + Frequency is well-controlled (fixed)
- Duty cycle is regulated to achieve desired  $V_o$
- Loop is slow to respond to  $V_i$  changes  
Effectively a triple integration:  $V_i \rightarrow i_L \rightarrow V_o \rightarrow V_x$

ECE1371

11-35
  
## Other Control Schemes— Ripple Current Control

- In a Buck converter, regulating inductor ripple current  $\Rightarrow$  D tracks  $V_i$  &  $V_o$  changes automatically




- + Fast!
- Still need a slow voltage loop to get desired  $V_o$

ECE1371

11-36

# Valley Current Control

## Buck converter; Constant $t_{off}$

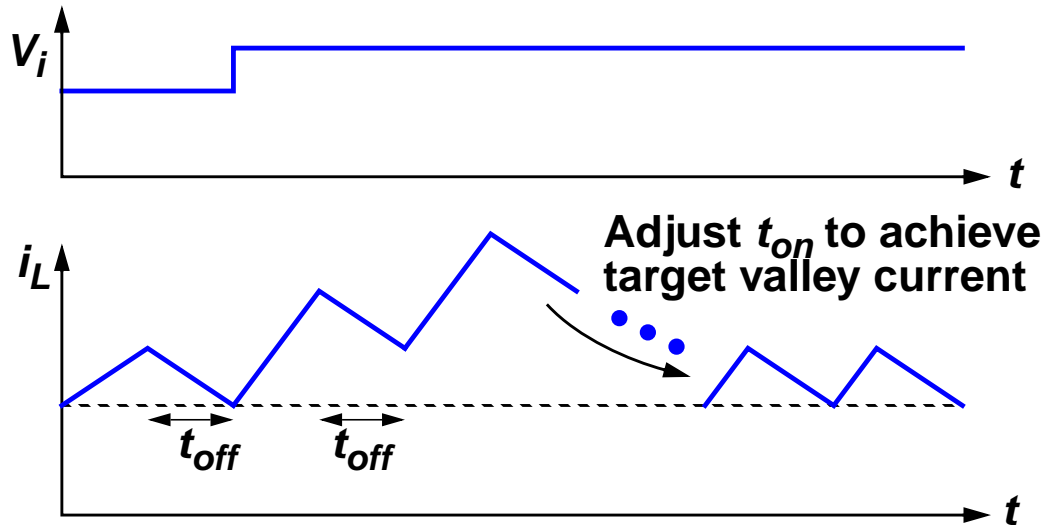


- Average current control is automatic

ECE1371

11-37
 
## Digital Control

- Controlling the switch with digital logic offers many advantages in flexibility, programmability and adaptability, not to mention ease of design!




- ADC only needs a few bits of resolution
- DSP needs a digitally-controlled delay in order to set the on/off times with fine resolution

ECE1371

11-38
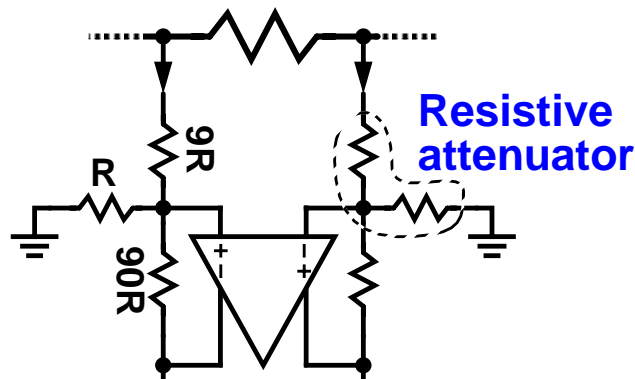
# NLCOTD: High-Voltage Differential Amplifier




- + Amplifier sees low voltages
- Resistor trimming needed for low error  
AD8206 uses resistors trimmed to 0.01% to get  
CMRR > 80 dB

ECE1371

11-39

# NLCOTD: Current-Sense Amplifier

 

- + Very low CM current  $\Rightarrow$  less sensitive to mismatch  
AD8210 achieves CMRR ~ 100 dB
- High-voltage amplifier needed

ECE1371

11-40

# What You Learned Today

- 1 Basic Buck and Boost Topologies**
- 2 Design Considerations**
- 3 Inverting Buck-Boost, SEPIC and Çuk Topologies**
- 4 Basic Control Strategies**