

ECE1371 Advanced Analog Circuits

Lecture 11

ADVANCED $\Delta\Sigma$

Richard Schreier
richard.schreier@analog.com

Trevor Caldwell
trevor.caldwell@utoronto.ca

Course Goals

- **Deepen understanding of CMOS analog circuit design through a top-down study of a modern analog system— a delta-sigma ADC**
- **Develop circuit insight through brief peeks at some nifty little circuits**

The circuit world is filled with many little gems that every competent designer ought to know.

NLCOTD: High-Q Resonator

- Want $Q \gg \sqrt{3} \frac{f_0}{BW}$ for small SQNR degradation
- In a TV tuner ADC $f_0 = 44$ MHz and $BW = 8.5$ MHz, so we needed $Q \gg 9$

In actuality the requirement was $Q > 20$.

How can Q be kept high despite finite amplifier gain and bandwidth?

ECE1371


11-3

Date	Lecture			Ref	Homework
2012-01-12	RS	1	Introduction: MOD1	ST 2, A	1: MOD1 in Matlab
2012-01-19	RS	2	MOD2 & MODN	ST 3, 4, B	2: MOD2 in Matlab
2012-01-26	RS	3	Example Design: Part 1	ST 9.1, CCJM 14	3: Sw.-level MOD2
2012-02-02	TC	4	SC Circuits	R 12, CCJM 14	4: SC Integrator
2012-02-09	TC	5	Amplifier Design		
2012-02-16	TC	6	Amplifier Design		5: SC Int w/ Amp
2012-02-23	Reading Week + ISSCC– No Lecture				
2012-03-01	RS	7	Example Design: Part 2	CCJM 18	Start Project
2012-03-08	RS	8	Comparator & Flash ADC	CCJM 10	
2012-03-15	TC	9	Noise in SC Circuits	ST C	
2012-03-22	TC	10	Matching & MM-Shaping	ST 6.3-6.5, +	
2012-03-29	RS	11	Advanced $\Delta\Sigma$	ST 6.6, 9.4	
2012-04-05	TC	12	Pipeline and SAR ADCs	CCJM 15, 17	
2012-04-12	No Lecture				
2012-04-19	Project Presentation				

ECE1371

11-4

Active-RC Resonator Structure

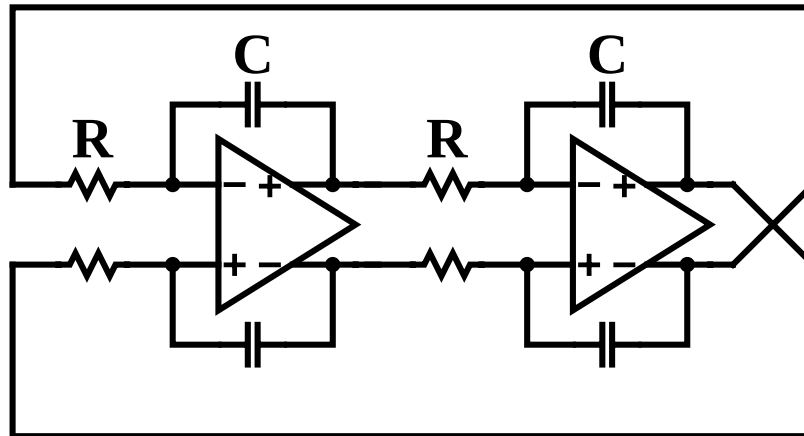

$$f_0 = \frac{1}{2\pi RC}$$

- **Frequency-tuning:** adjust C until the desired resonant frequency is achieved
 No Q-tuning.
- Amplifier drives both R and C $\Rightarrow$ Q trouble?

ECE1371

11-5


Highlights (i.e. What you will learn today)

- 1 State-space (ABCD) representation of the loop filter in the $\Delta\Sigma$ Toolbox
- 2 MASH Modulators
- 3 Continuous-Time Modulators
- 4 Bandpass and Quadrature Bandpass $\Delta\Sigma$

ECE1371

11-6

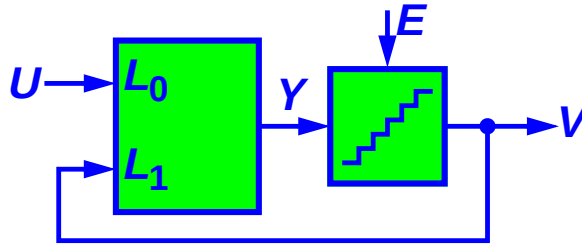Review: Generic Single-Loop $\Delta\Sigma$ ADC



$$\begin{aligned} Y &= L_0 U + L_1 V \\ V &= Y + E \end{aligned} \Rightarrow \boxed{V = STF \cdot U + NTF \cdot E}, \text{ where}$$

$$NTF = \frac{1}{1 - L_1} \quad \& \quad STF = L_0 \cdot NTF$$

Inverse Relations:


$$L_1 = 1 - 1/NTF, \quad L_0 = STF / NTF$$

ECE1371

11-7

Review: $\Delta\Sigma$ Toolbox Model

Modulator:


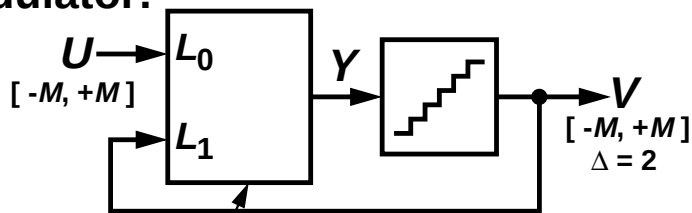


$$NTF = \frac{1}{1 - L_1}$$


$$STF = \frac{L_0}{1 - L_1}$$

Loop filter can be specified by NTF or by ABCD, a state-space representation

Quantizer:

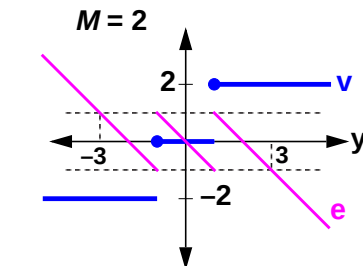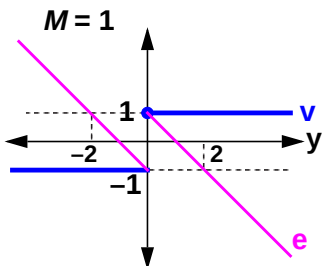

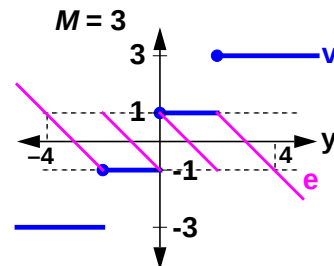Mid-tread quantizer;
v: even integers $[-M, +M]$




Mid-rise quantizer;
v: odd integers $[-M, +M]$

ECE1371

11-8

Feedback Topology

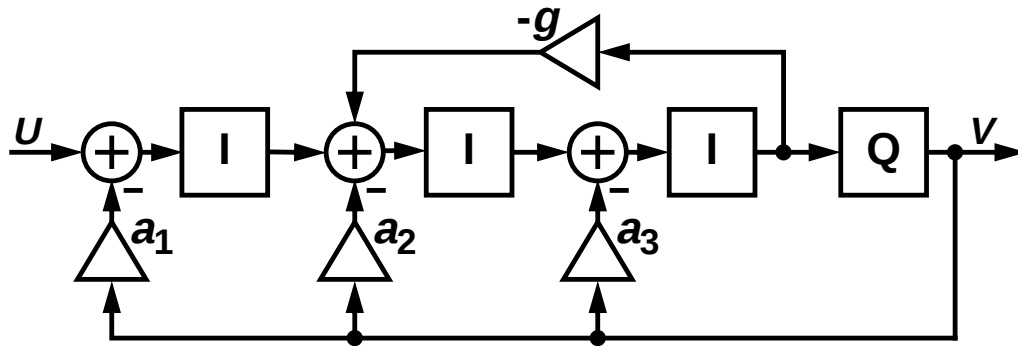


- N integrators precede the quantizer
- Feedback from the quantizer to the input of each integrator (via a DAC)
- Local feedback around pairs of integrators to set the NTF's zeros
- Multiple input feed-in branches are possible

ECE1371

11-9

Feedforward Topology

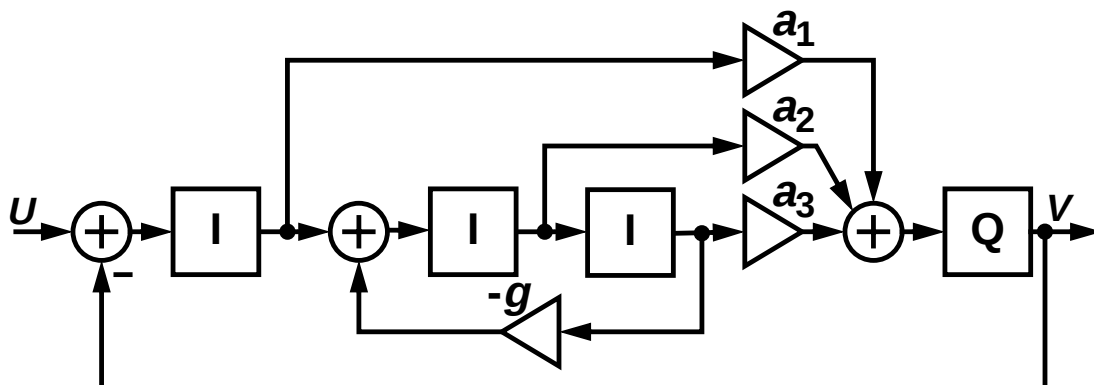


- N integrators in a row
- Each integrator output is fed forward to the quantizer
- Local feedback around pairs of integrators to control NTF zeros
- Multiple input feed-in branches also possible

ECE1371

11-10

Feedback vs. Feedforward STF

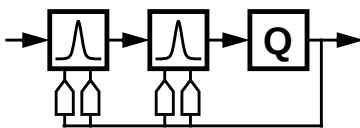


$$L_0(z) = \frac{N_0(z)}{D(z)} \quad L_1(z) = \frac{N_1(z)}{D(z)}$$

$$NTF(z) = \frac{1}{1 - L_1(z)} = \frac{D(z)}{N_1(z) - D(z)}$$

poles of LF are zeros of NTF

$$STF(z) = \frac{L_0(z)}{1 - L_1(z)} = \frac{N_0(z)}{N_1(z) - D(z)}$$

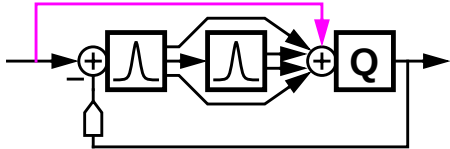
same poles as NTF
zeros = zeros of L_0
STF often has no zeros, only poles.



$$L_0(z) = -L_1(z) = L(z)$$

$$NTF(z) = \frac{1}{1 - L_1(z)} = \frac{1}{1 + L(z)}$$
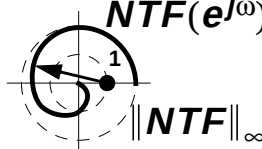
$$STF(z) = \frac{L(z)}{1 + L(z)} = 1 - H(z)$$




$\|STF\|_\infty \approx \|NTF\|_\infty + 1$

With extra feed-in to Q, $STF(z) = 1$.

ECE1371

11-11

STF Comparison 5th-Order; Single Feed-In

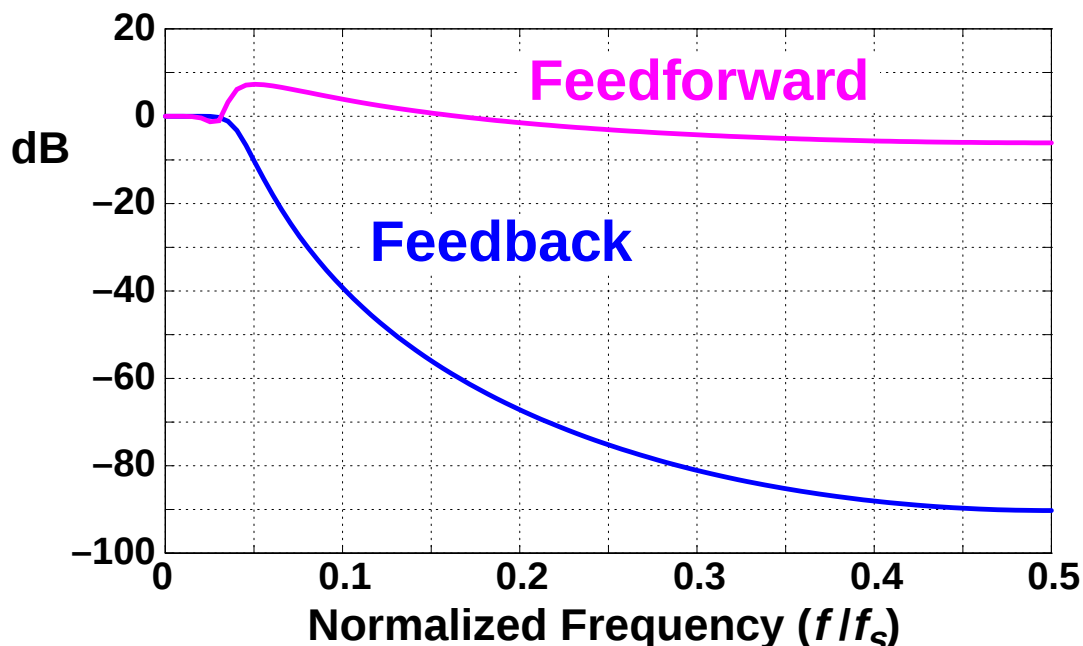

ECE1371

11-12


Feedforward vs. Feedback

- FF has relaxed dynamic range requirements
“All stages except the last have attenuated signal components.”
- FB has better STF and, for CT modulators, a better AAF
In a discrete-time modulator, the STF of FF can be made unity by adding a signal feedforward term to the input of the quantizer.
- FB needs many DACs;
FF needs a summation block
Can do partial summation before the last integrator.
- FF timing can be tricky
Need to quantize u and feed it back in zero time.

ECE1371

11-13


ABCD: A *State-Space* Representation of the Loop Filter

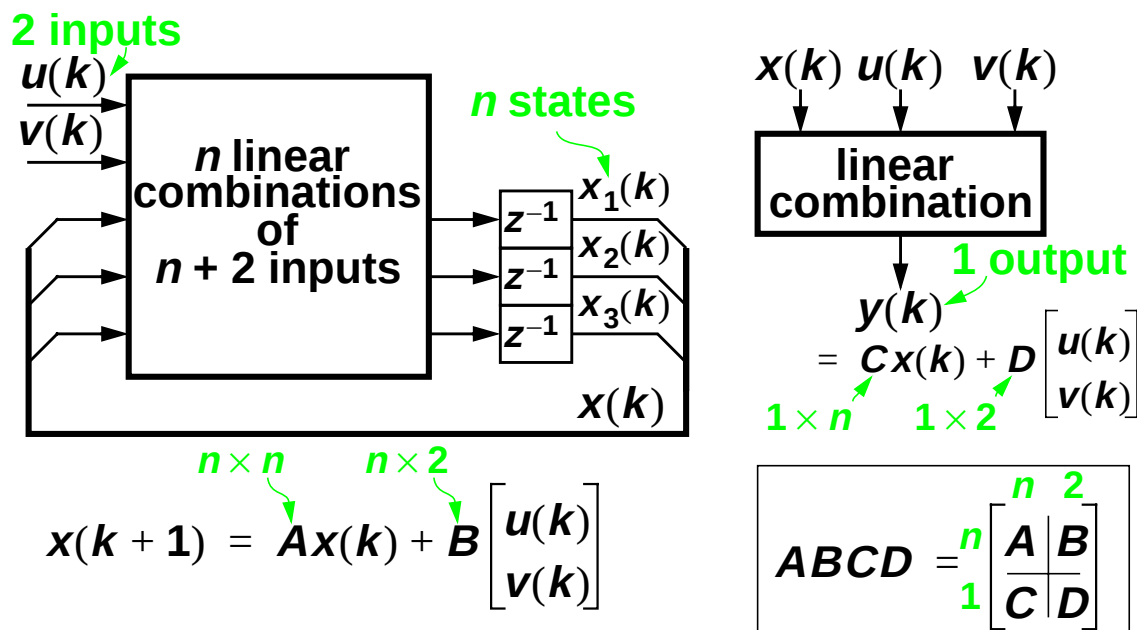

ECE1371

11-14


Ex.: Cascade of Integrators Feedback (CIFB) Topology

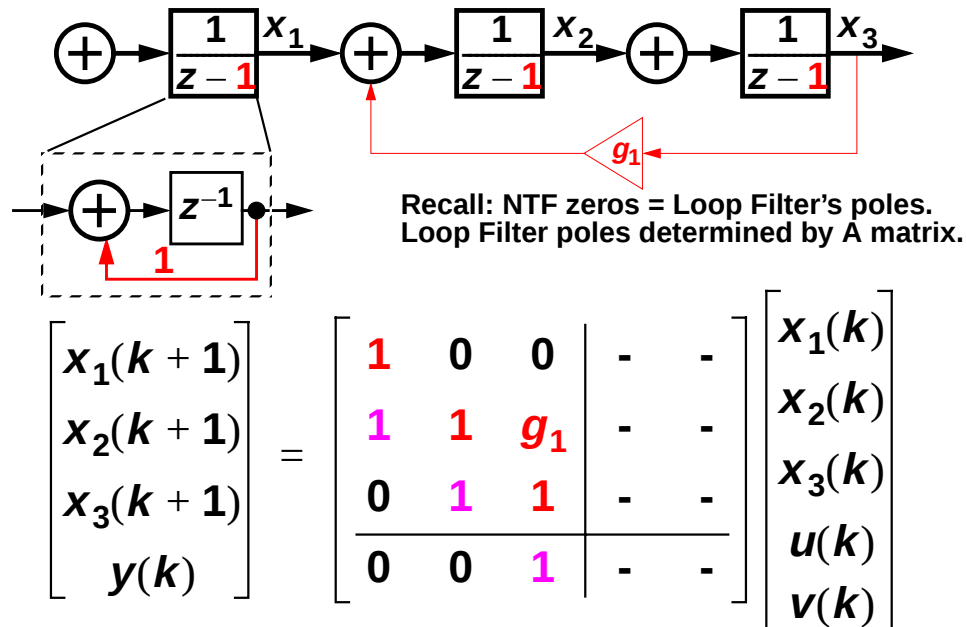

ECE1371

11-15


CIFB cont'd: a_i Control NTF & STF Poles

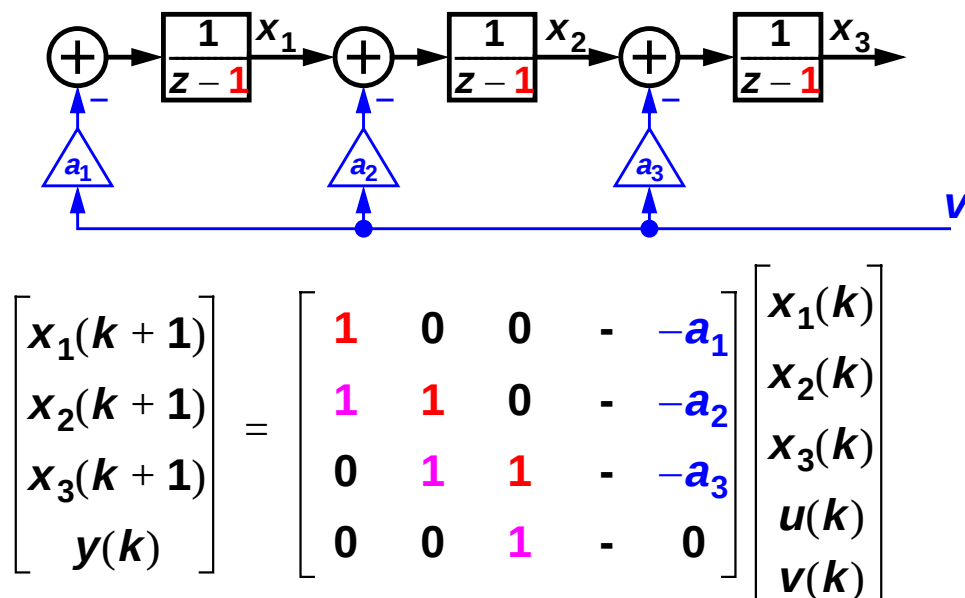

ECE1371

11-16

b_i Control STF Zeros

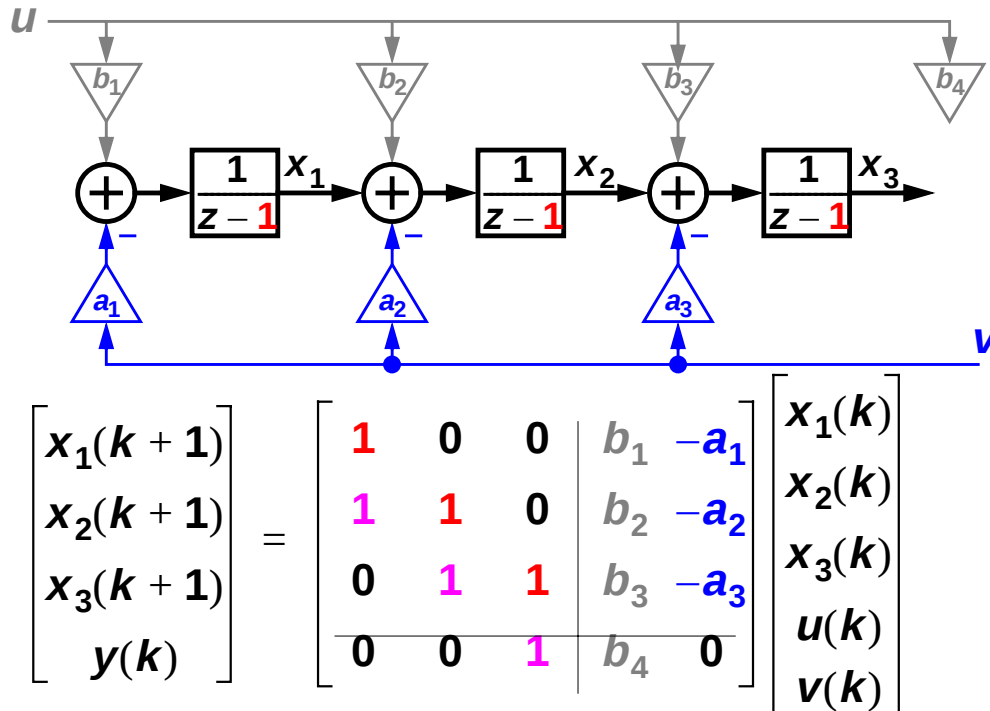

ECE1371

11-17

ABCD and the Toolbox


- `simulateDSM` simulates a modulator given an ABCD description of its loop filter
- `realizeNTF` gives (unscaled) coefficients for any of the supported topologies
- `stuffABCD` produces an ABCD matrix given the coefficients for one of the supported topologies
`mapABCD` performs the inverse operation.
- `scaleABCD` does dynamic range scaling on any ABCD matrix
- `calculateTF` calculates the NTF and STF from ABCD
 Useful for checking implementation of new topologies.

ECE1371

11-18

Cascade (MASH) Modulators

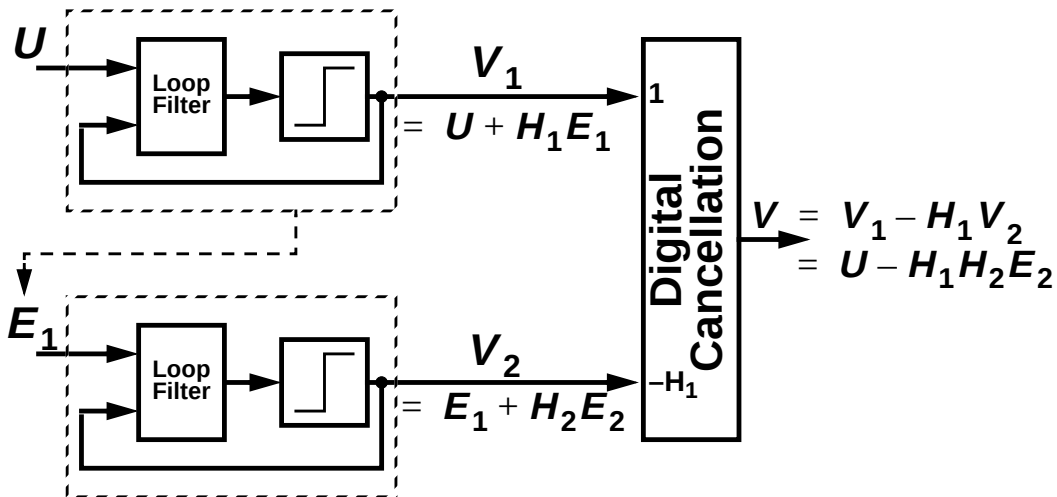- Put two (or more) modulators in “series”




- The resulting NTF is the *product* of the individual NTFs

ECE1371

11-19

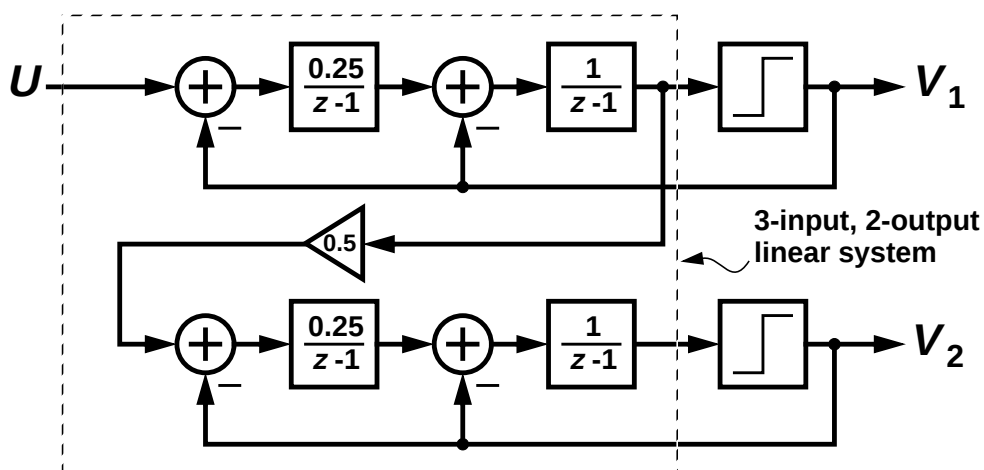Example: 2-2 Cascade

- Use Two MOD2b: $H(z) = \left(\frac{z-1}{z-0.5} \right)^2$




$$\left(V = \frac{1}{z^3} V_1 + \frac{8(z-1)^2(z-0.5)^2}{z^3(z-0.75)} V_2 \right) \Rightarrow \left(H(z) = \frac{8(z-1)^4}{(z-0.75)} \right)$$

ECE1371

11-20


Example MASH Spectra

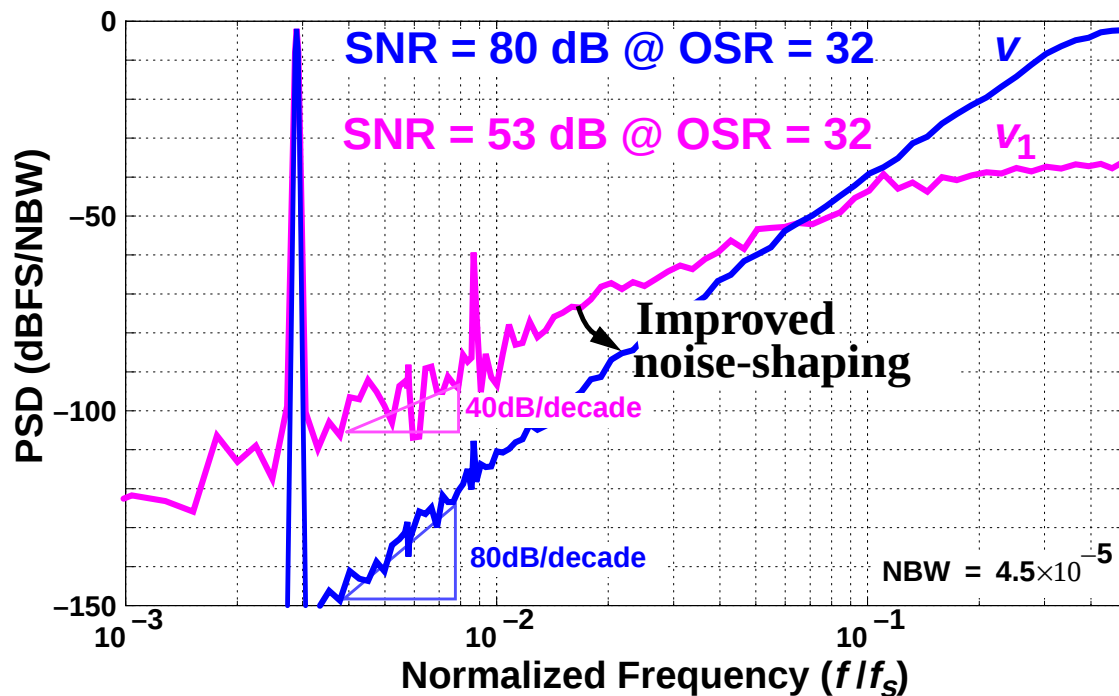

ECE1371

11-21

A Continuous-Time $\Delta\Sigma$ ADC

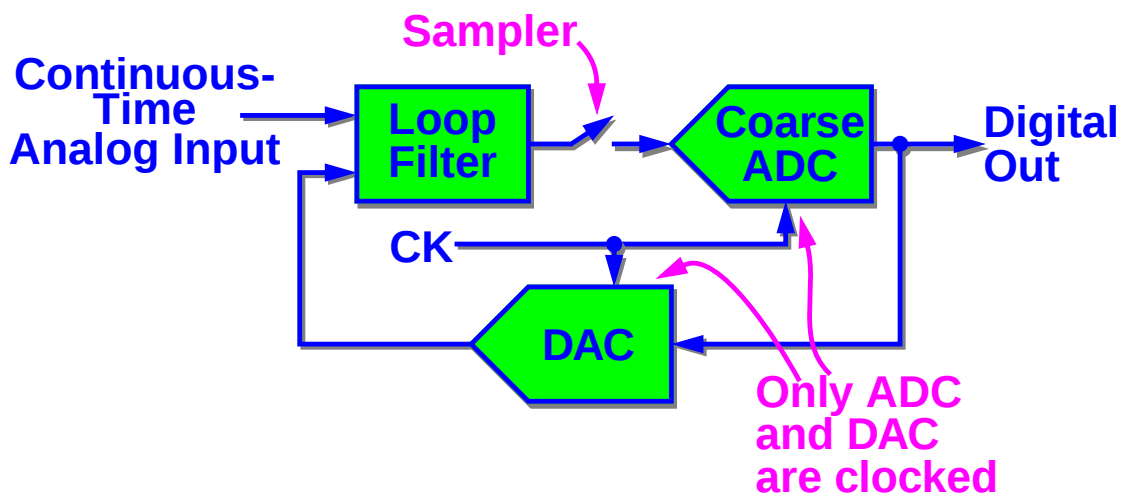


- Loop filter implemented with continuous-time circuitry
- Sampling occurs after the loop filter

ECE1371


11-22

Example: MOD1-CT

Block Diagram

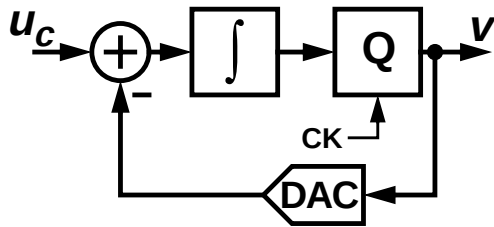

Schematic

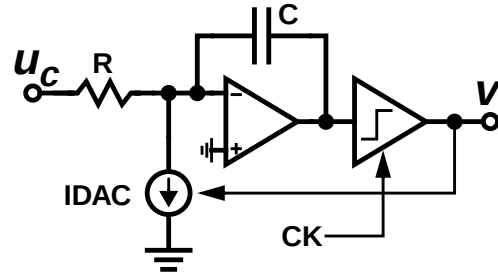


- Note: Input is a simple resistor, *not* a switched capacitor
CT ADCs are easier to drive than DT ADCs.

ECE1371


11-23

Inherent Anti-Aliasing

- $\Delta\Sigma$ ADC with CT Loop Filter

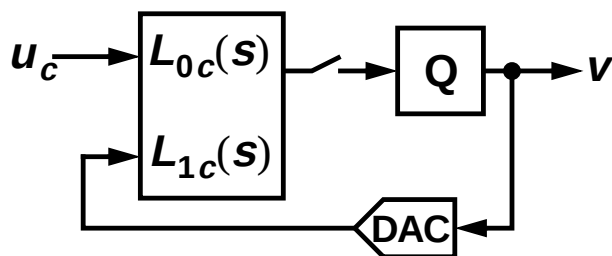


- Equivalent system with DT feedback path

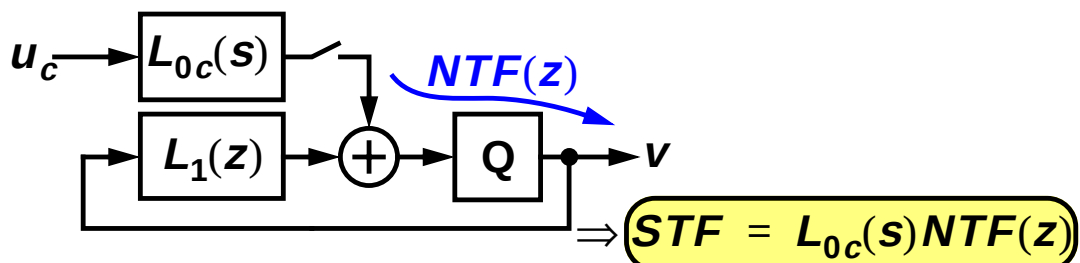

ECE1371

11-24


Example: MOD1-CT $STF = \frac{1-z^{-1}}{s}$
 Recall $z = e^s$

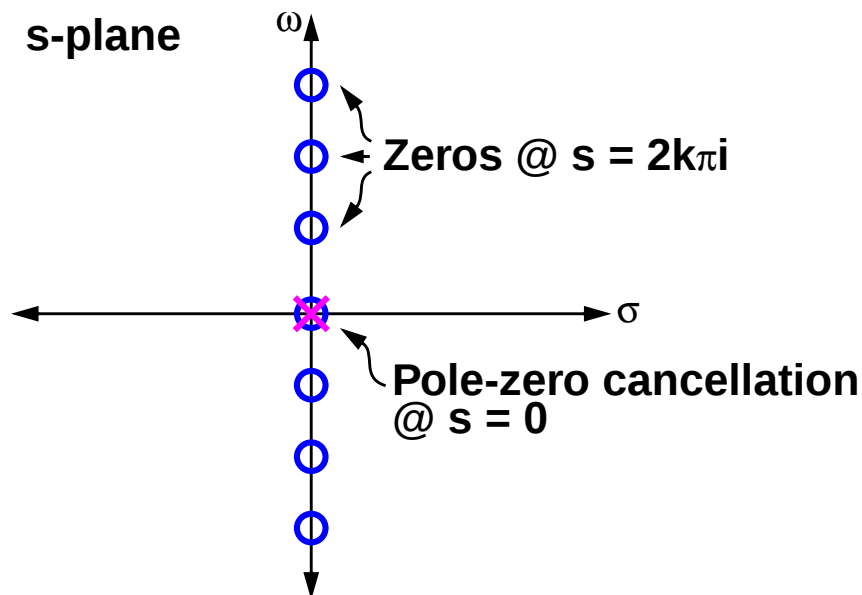

ECE1371

11-25

MOD1-CT Frequency Responses

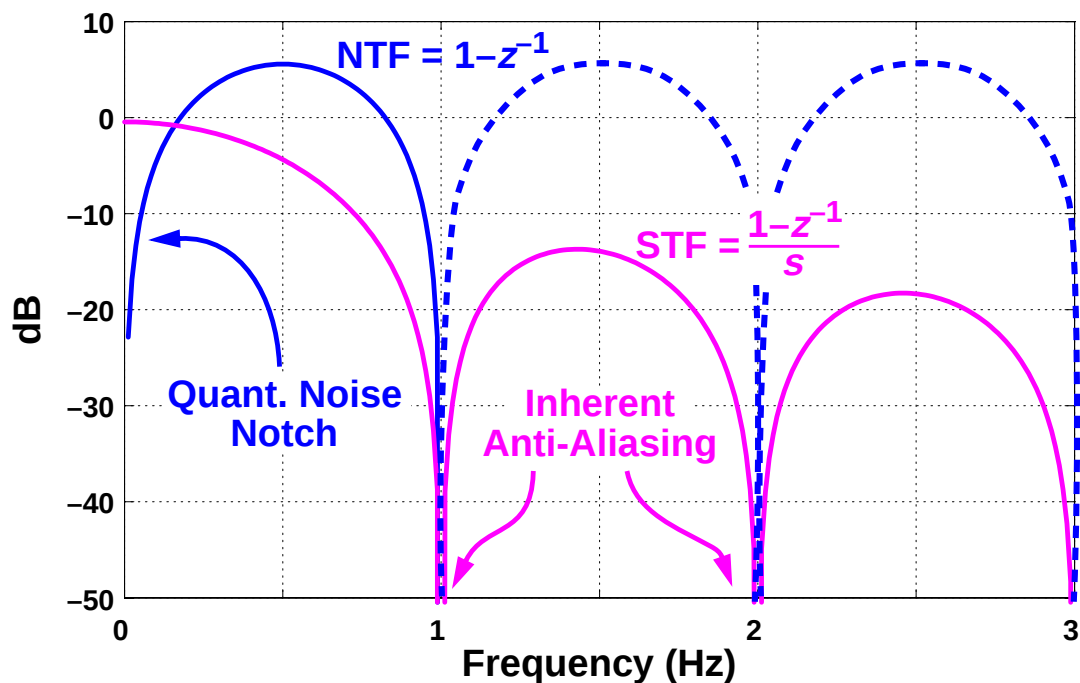

ECE1371

11-26

Inherent AAF Summary

$$STF = L_{0c}(s)NTF(z)$$

- STF contains the zeros of the NTF
- Any frequency which aliases to the passband is attenuated by at least as much as the quantization noise

Anti-alias performance tracks modulator order.
Also true for MASH systems.


- The effective anti-alias filter is

$$AAF(f) = \frac{STF(f)}{STF(f_{alias})} = \frac{L_{0c}(f)}{L_{0c}(f_{alias})}$$

ECE1371

11-27

DT $\Delta\Sigma$ vs. CT $\Delta\Sigma$

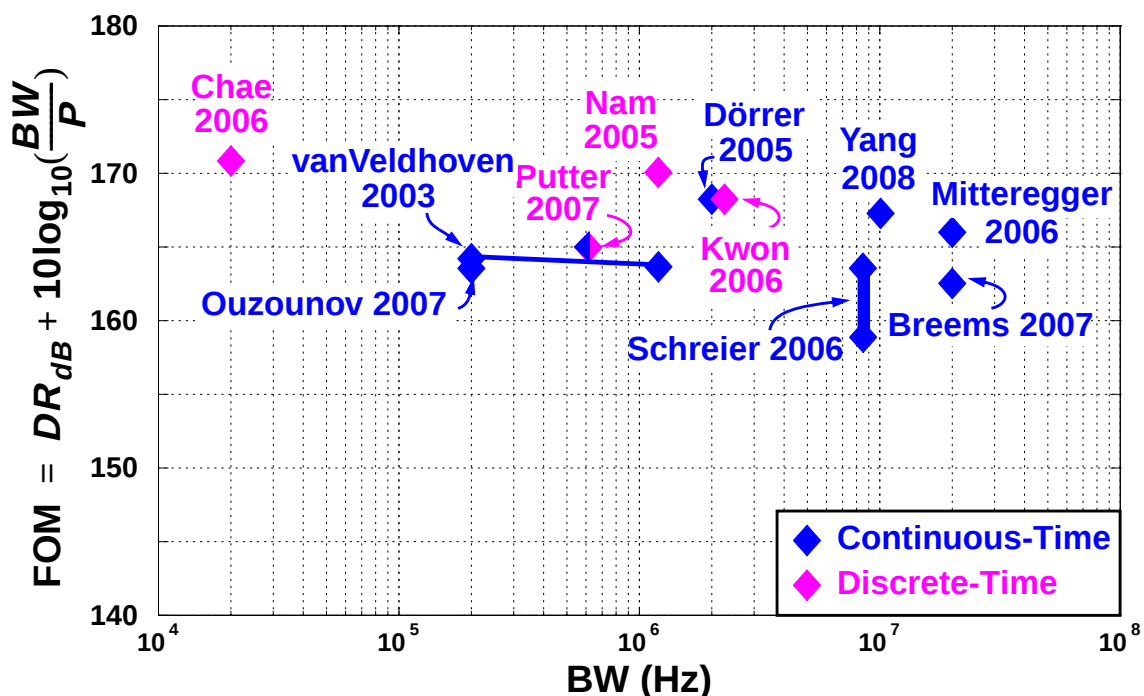

ECE1371

11-28

References— DT vs. CT

BW (Hz)	DR (dB)	P (mW)	FOM	Reference	Architecture <i>N</i> =order (<i>M</i> =#steps)
20k	85	0.036	172	Chae, ISSCC 2008:27.2	$\Delta\Sigma$ SC 3(1)
200k	82	1.4	164	Ouzounov, ISSCC 2007:13.3	$\Delta\Sigma$ A-RC 5(1)
614k	82	3.1	165	Putter, ISSCC 2007:13.4	$\Delta\Sigma$ A-RC+SC 6(1)
1.2M	82	8	164	vanVeldhoven, ISSCC 2003:3.4	$Q\Delta\Sigma$ gm-C 5(1)
1.2M	96	44	171	Nam, JSSC 2005-09	$\Delta\Sigma$ SC 2(32)-2(8)
2M	80	3.0	168	Dörrer, ISSCC 2005:27.1	$\Delta\Sigma$ A-RC 3(15)
2.2M	86	14	168	Kwon, ISSCC 2006:3.4	$\Delta\Sigma$ SC 2(4)
8.5M	88	375	162	Schreier, ISSCC 2006:3.2	$QBP\Delta\Sigma$ A-RC 4(16)
10M	87	100	167	Yang, ISSCC 2008:27.6	$\Delta\Sigma$ A-RC 5(7)
20M	76	20	166	Mitteregger, ISSCC 2006:3.1	$\Delta\Sigma$ A-RC 3(15)
20M	77	56	164	Breems, ISSCC 2007:13.1	$Q\Delta\Sigma$ A-RC 2(15)-2(15)


Advantages of Discrete-Time

- 1 Less sensitive to jitter
- 2 Accurate transfer functions regardless of f_{CK}
- 3 FF topology with no STF-peaking is possible
- 4 DAC dynamics are non-critical
- 5 Math is simpler

Advantages of Continuous-Time

- 1 Higher speed
- 2 Inherent anti-aliasing
- 3 Easier to drive (well-defined Z_{in})
- 4 Sampling is non-critical
- 5 Lower power (?)

A Bandpass $\Delta\Sigma$ ADC System

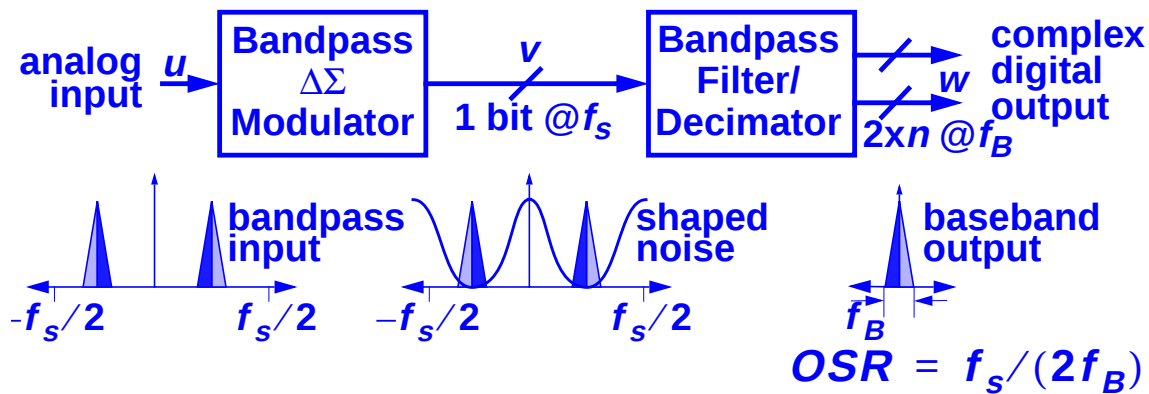


- ADC converts its analog input into a noise-shaped digital output
- DSP removes out-of-band noise (and signals) and translates the signal to baseband

ECE1371

11-31

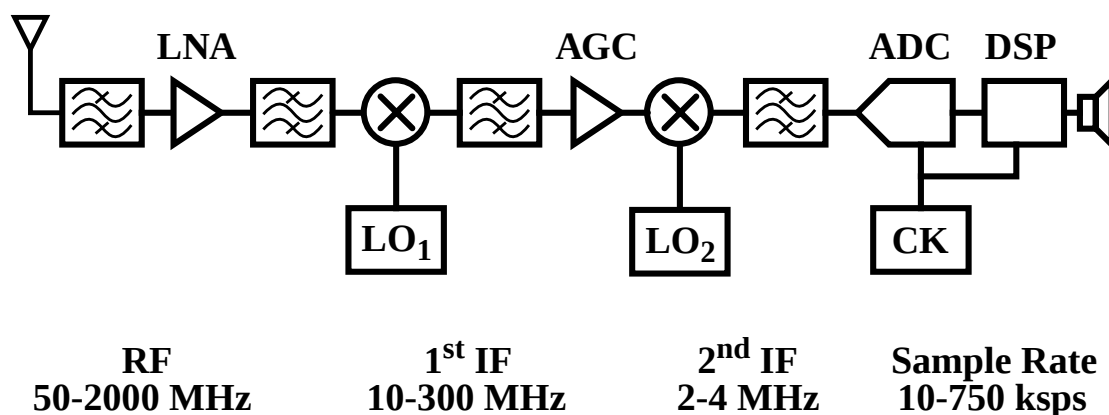A Dual-Conversion Superheterodyne Receiver




- A bandpass ADC fits naturally into this narrowband system
Perfect I/Q, high dynamic range. Low power?

ECE1371

11-32

System Partitioning

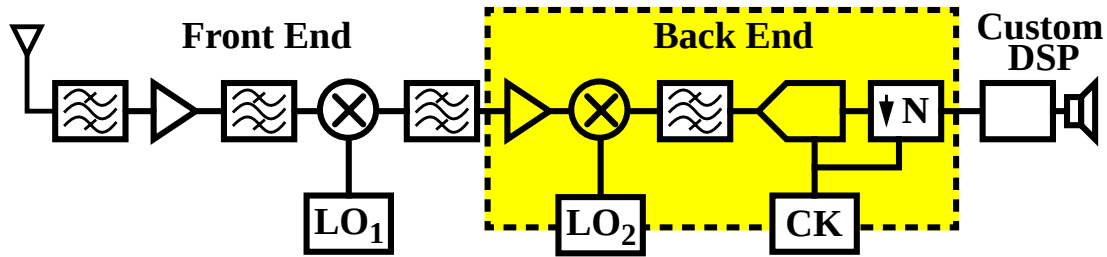


- **Goal: a general-purpose, high-performance, low-power back-end**

ECE1371

11-33

Traditional Implementation

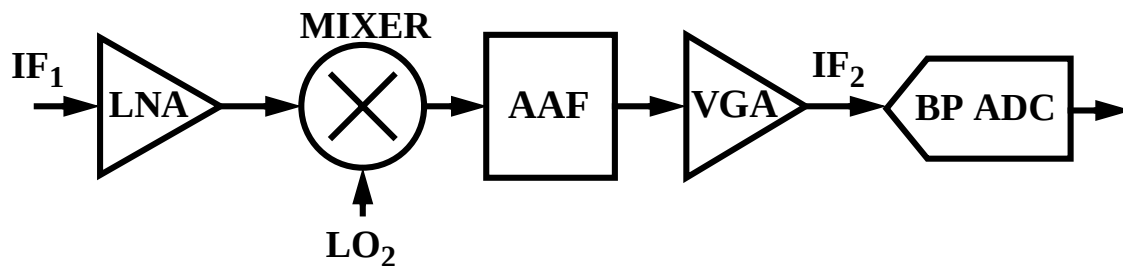


- ☹ Numerous high-dynamic range blocks
- ☹ Noise and power budgets are very tight
- ☹ Large VGA range needed

ECE1371

11-34

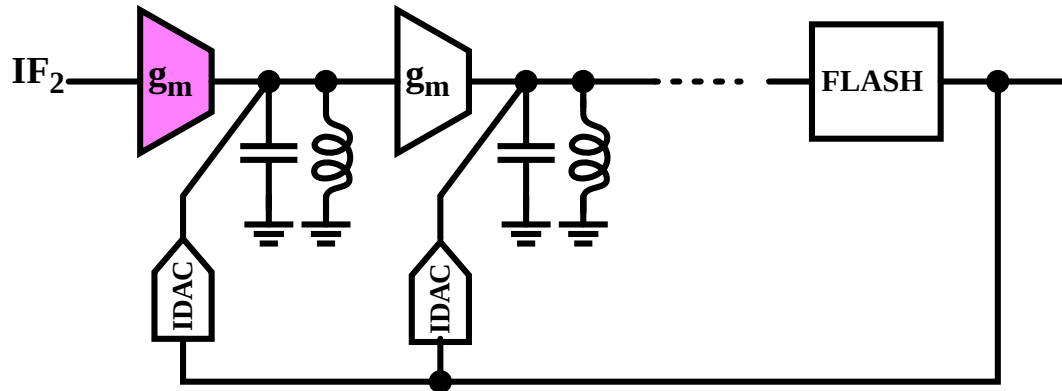
Eliminating the AAF with a Continuous-Time BP $\Sigma\Delta$ ADC



☺ Anti-alias filtering is inherent


☹ But still need a **low-noise, linear V-I converter**

Eliminating the Input g_m

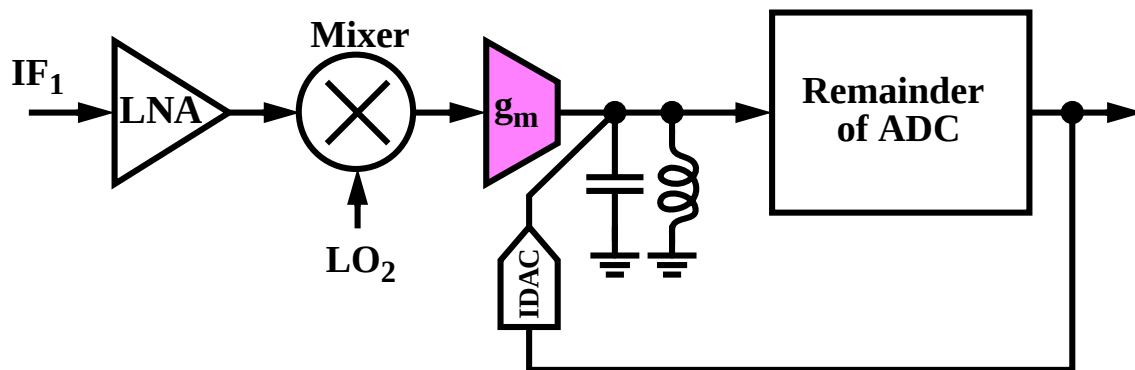

The output of the mixer is available in current form, so ...

Merge ADC with Mixer!

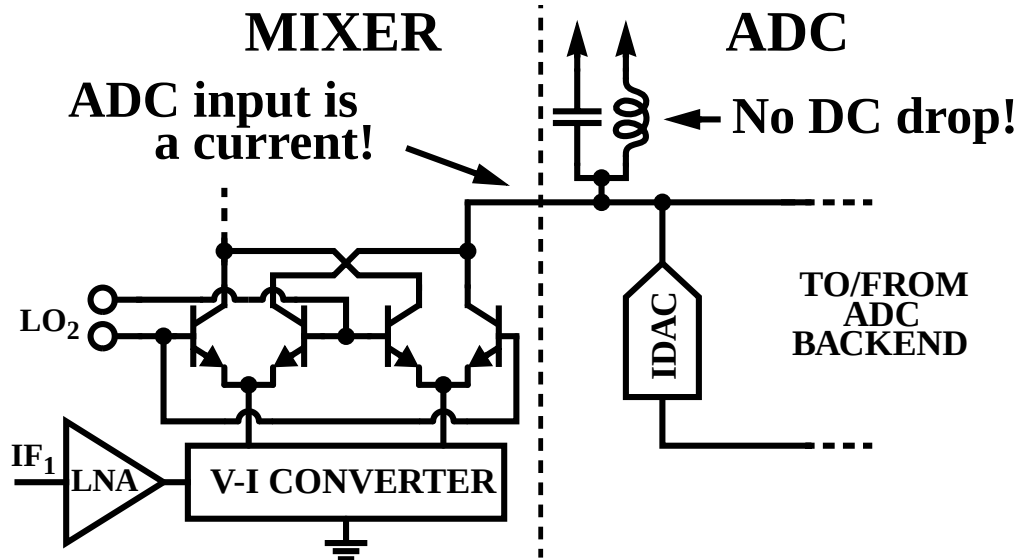


- Eliminates redundant I-V & V-I conversion
- Gives mixer and IDAC more headroom

ECE1371

11-37

Merge ADC with Mixer!

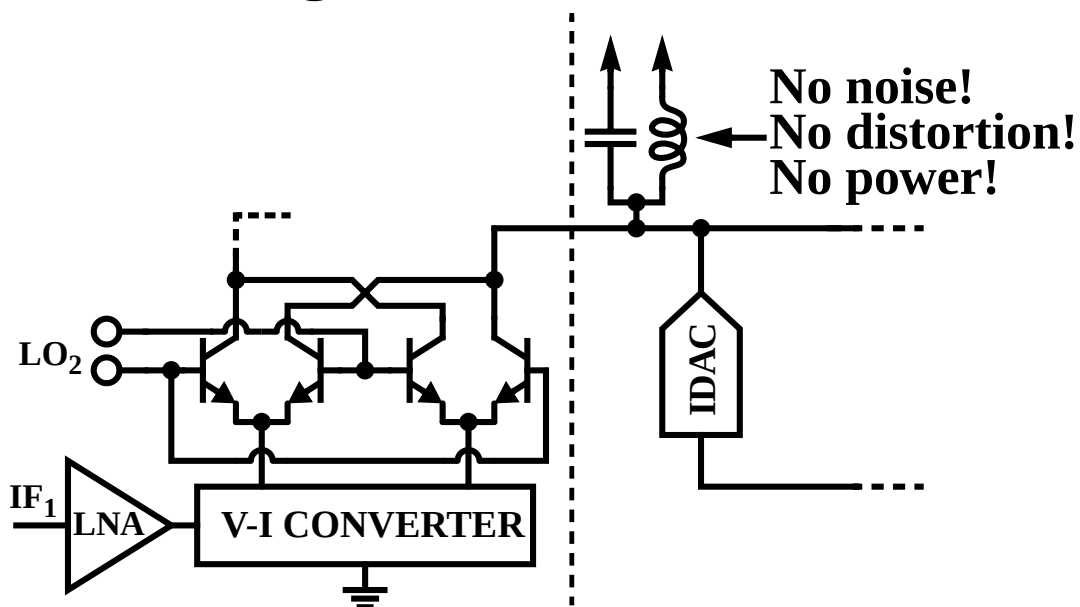


💡 LC tank effectively adds gain, without adding noise, adding distortion or consuming power

ECE1371

11-38

Noise Analysis

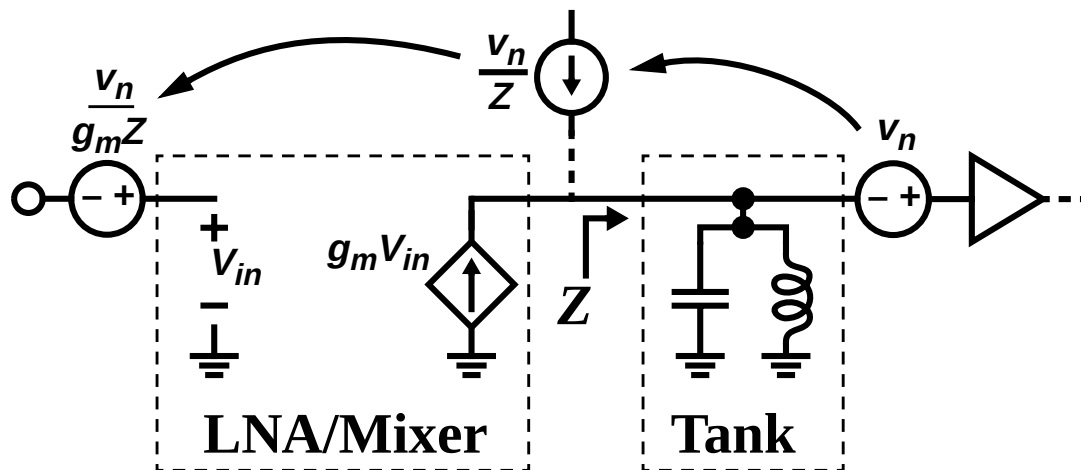

- Noise in the ADC backend is attenuated by g_m times the tank impedance
In this work, $g_m \approx 10 \text{ mA/V}$

ECE1371

11-39

$$Z_{eff}$$

- Near resonance, $|Z_L| = |Z_C|$
 $|Z_{L,C}| \approx 300\Omega$ in this design
- At resonance, $|Z| \approx Q \cdot |Z_{L,C}|$
About $6k\Omega$ for $Q = 20 \Rightarrow g_m Z \approx 60$.
- More generally, the effective tank impedance is found by integrating the input-referred noise over the band of interest:


$$\int \left(\frac{v_n}{g_m Z(\omega)} \right)^2 d\omega = \left(\frac{v_n}{g_m} \right)^2 \int Y(\omega)^2 d\omega = \left(\frac{v_n}{g_m Z_{eff}} \right)^2 \Delta\omega$$

$$\Rightarrow Z_{eff} = (Y_{rms})^{-1}$$

ECE1371


11-40

Z vs. Frequency

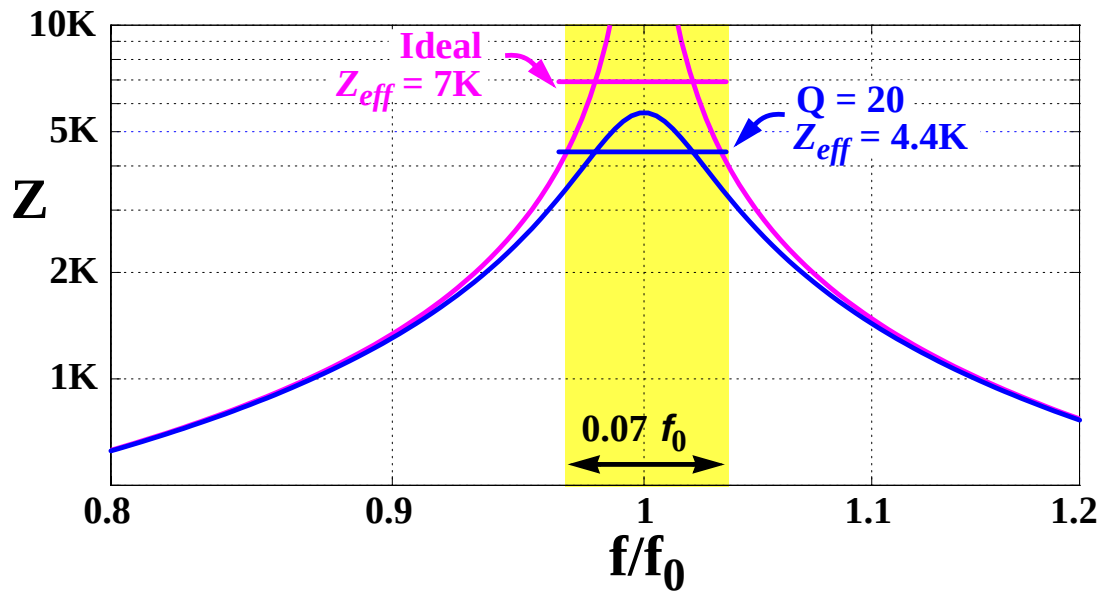


- $Q = 20$ reduces Z_{eff} by about 4 dB

Remainder of ADC?

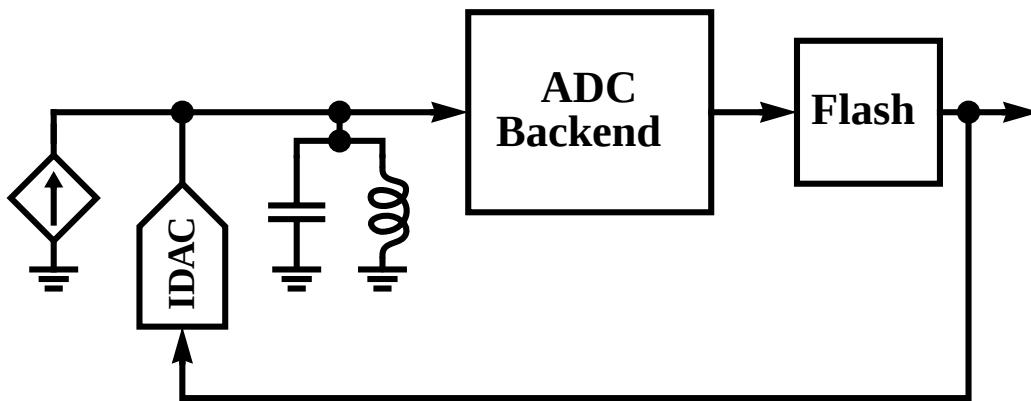

- Add resonator stages until the quantization noise of the flash is low enough

Second Resonator?

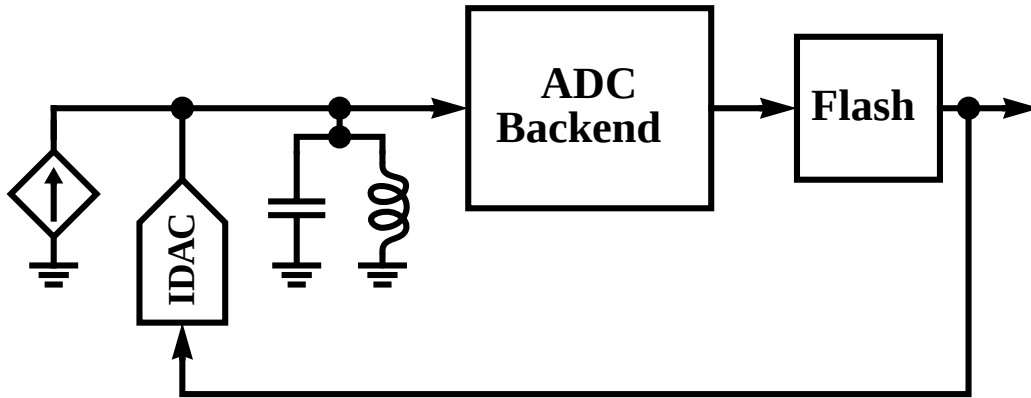


- **LC:** Needs more external components plus associated pins
- **Active-RC:** 2 mA for $50 \text{ nV}/\sqrt{\text{Hz}}$ input-referred noise
- **Switched-Cap:** est. $>10 \text{ mA}$ for same noise

ECE1371

11-43

Third Resonator?

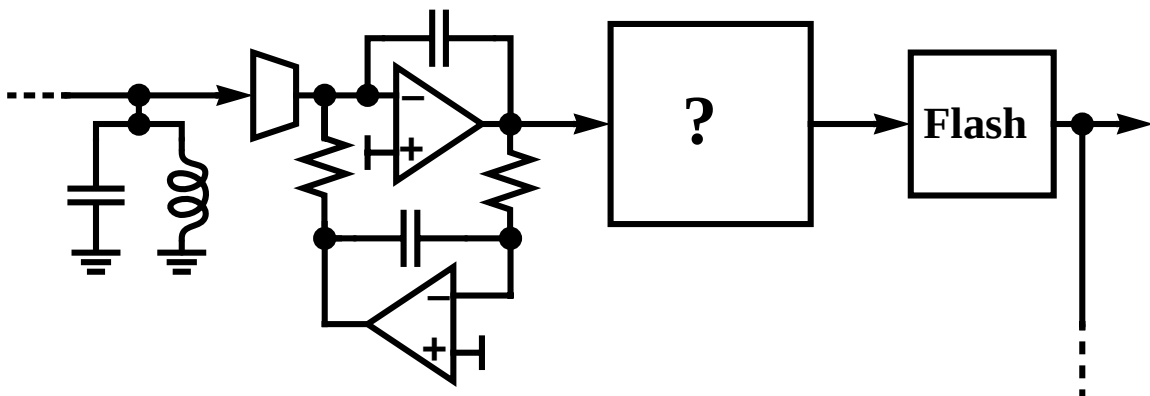


- **Active-RC:** $Q \approx 10 \Rightarrow$ Need 4th resonator
- **Switched-Cap:** Q is high & drift is low;
 $<1 \text{ mA}$ for $300 \text{ nV}/\sqrt{\text{Hz}}$ i.r.n.

ECE1371

11-44

Complete ADC

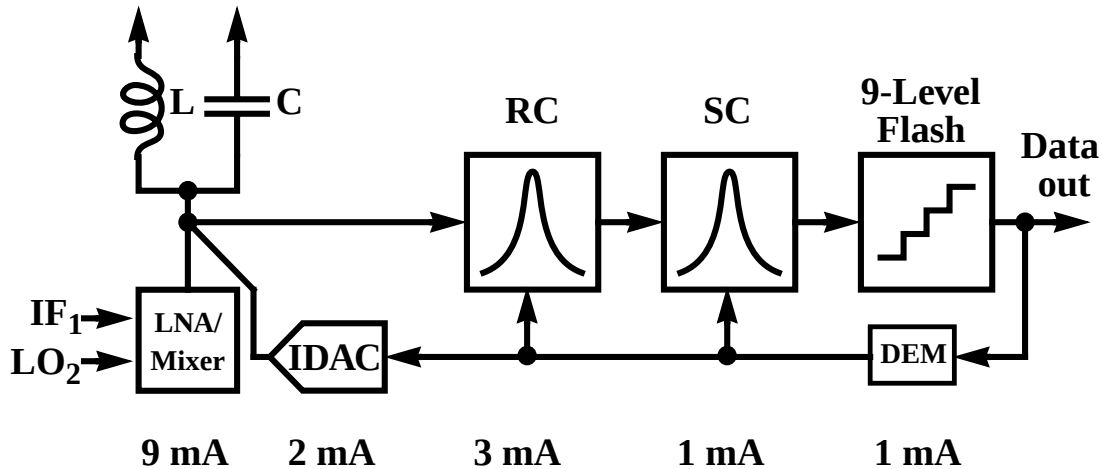


- Eliminates high-power VGA & AAF
2/3 of the total power used by LNA, Mixer & IDAC
- Uses CT and DT time elements, plus multi-bit quantization and mismatch-shaping

ECE1371

11-45

ADC in More Detail

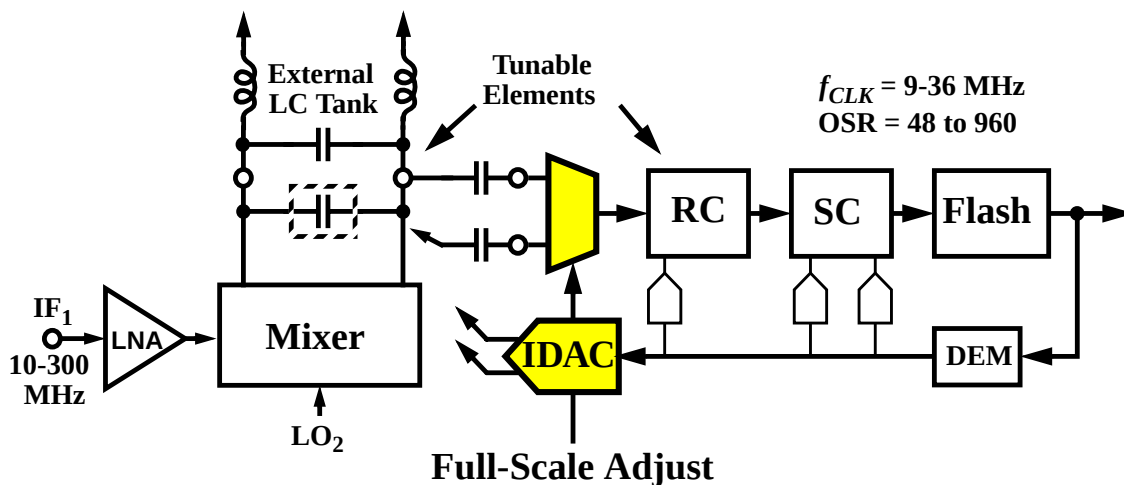


- Can save power under small-signal conditions by reducing IDAC's full-scale
By a factor of 4 in this product.

ECE1371

11-46


Noise vs. Full-Scale

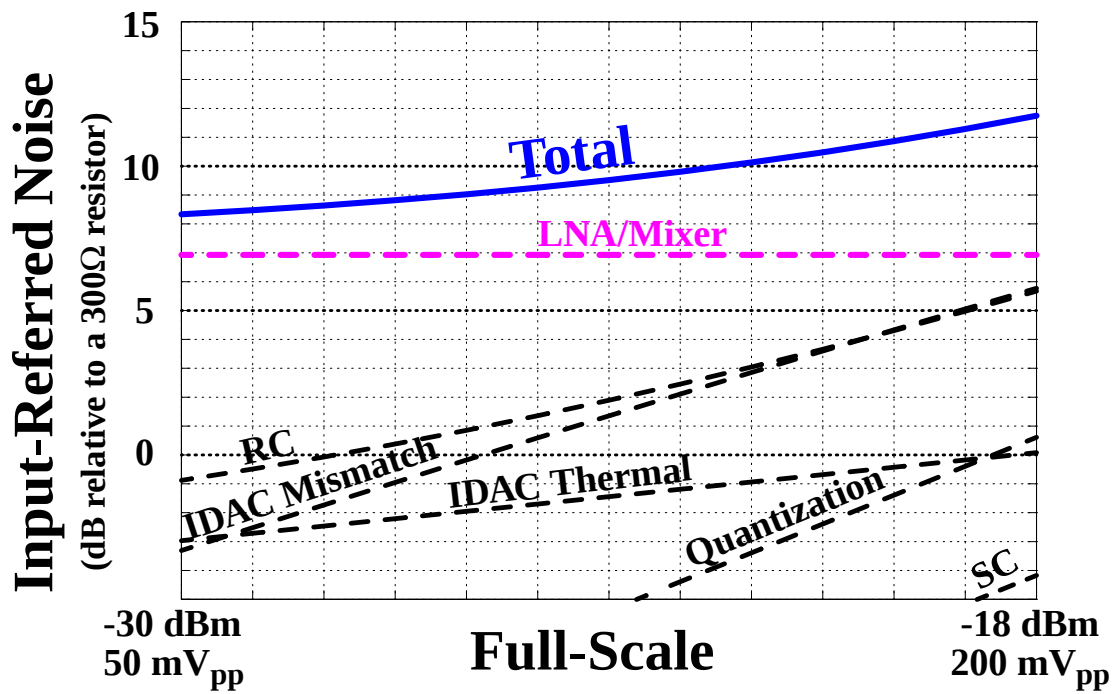

ECE1371

11-47

Die Photo

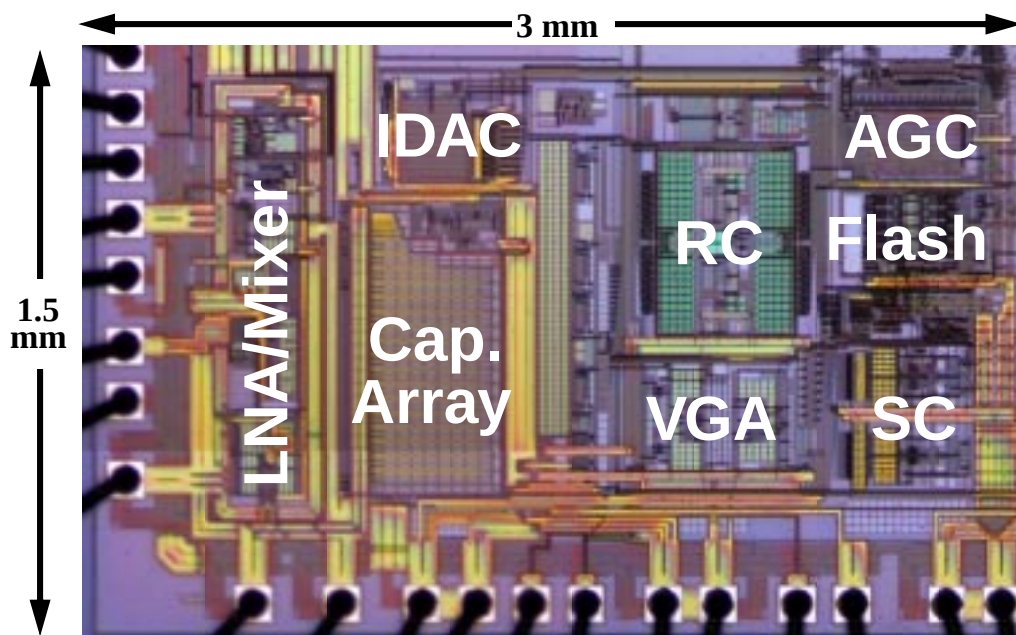


- 0.35μm BiCMOS process

ECE1371

11-48


Measured STF & NTF

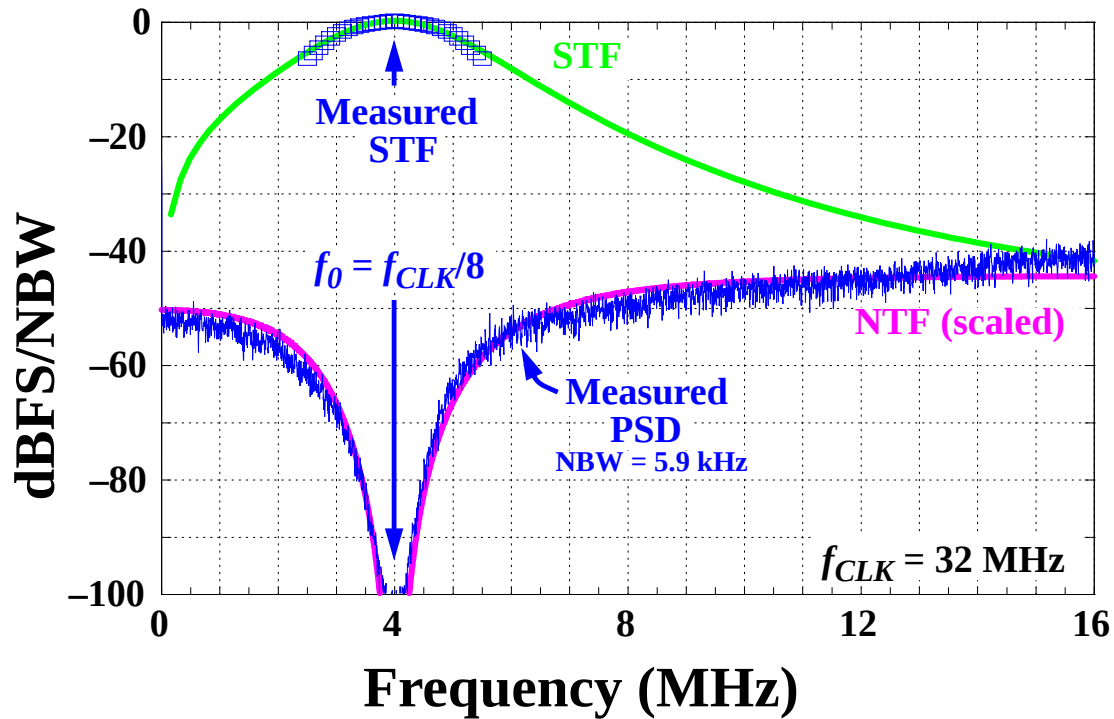

ECE1371

11-49


In-Band Spectrum (OSR=48)

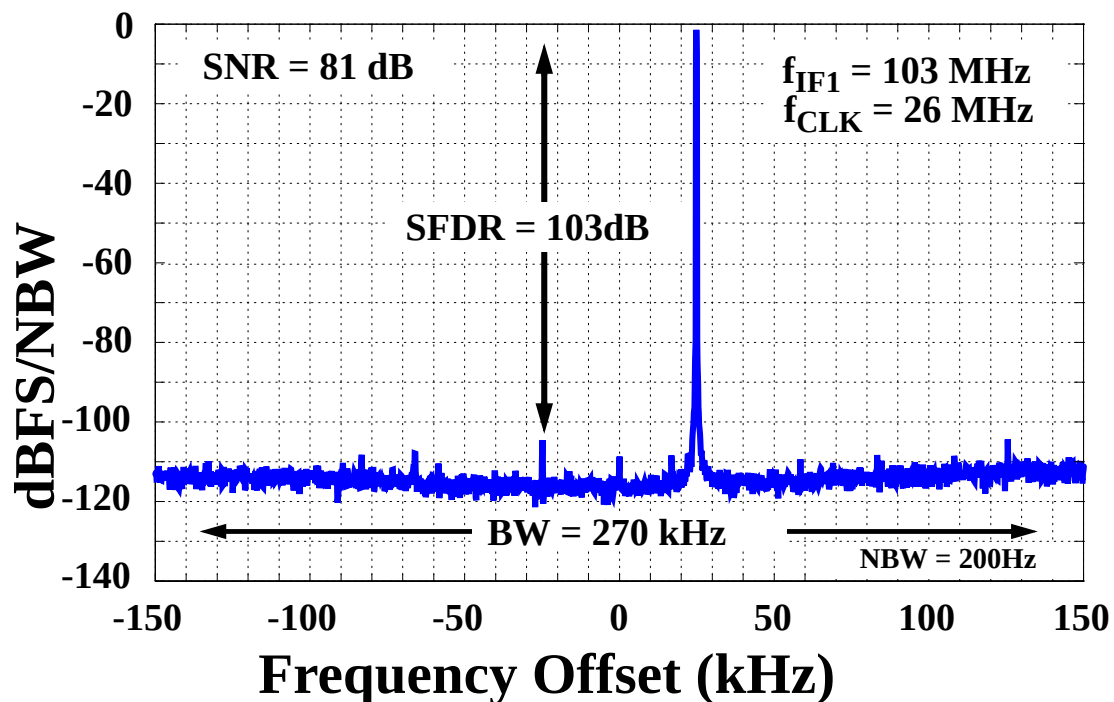

ECE1371

11-50


In-Band Spectrum (OSR=900)

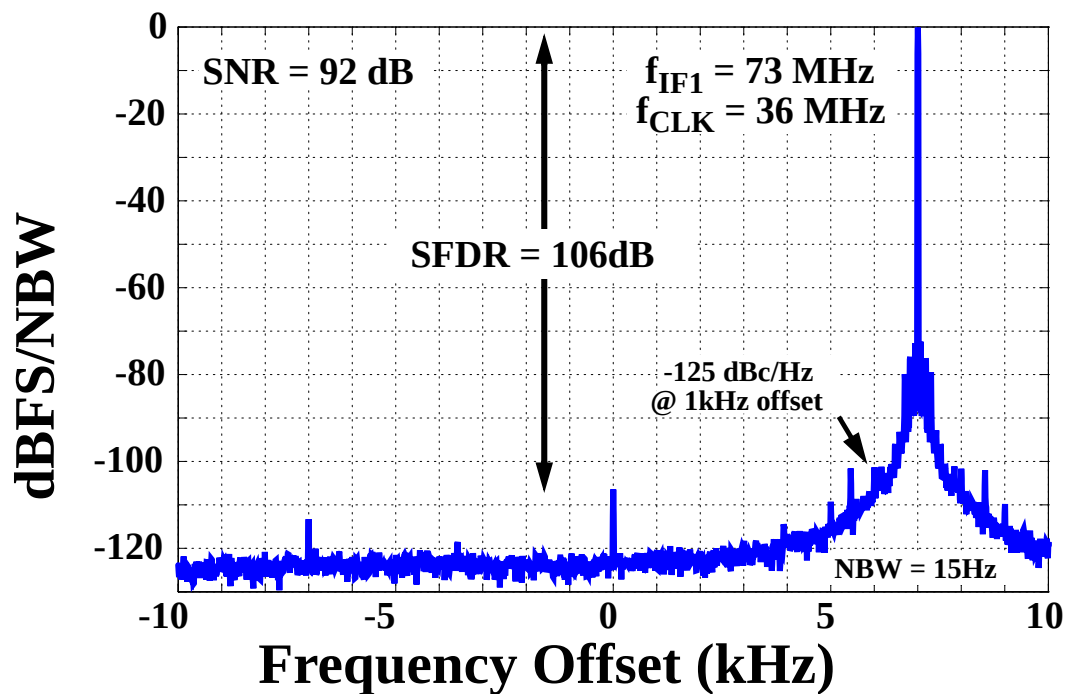

ECE1371

11-51


SNR vs. Input Power

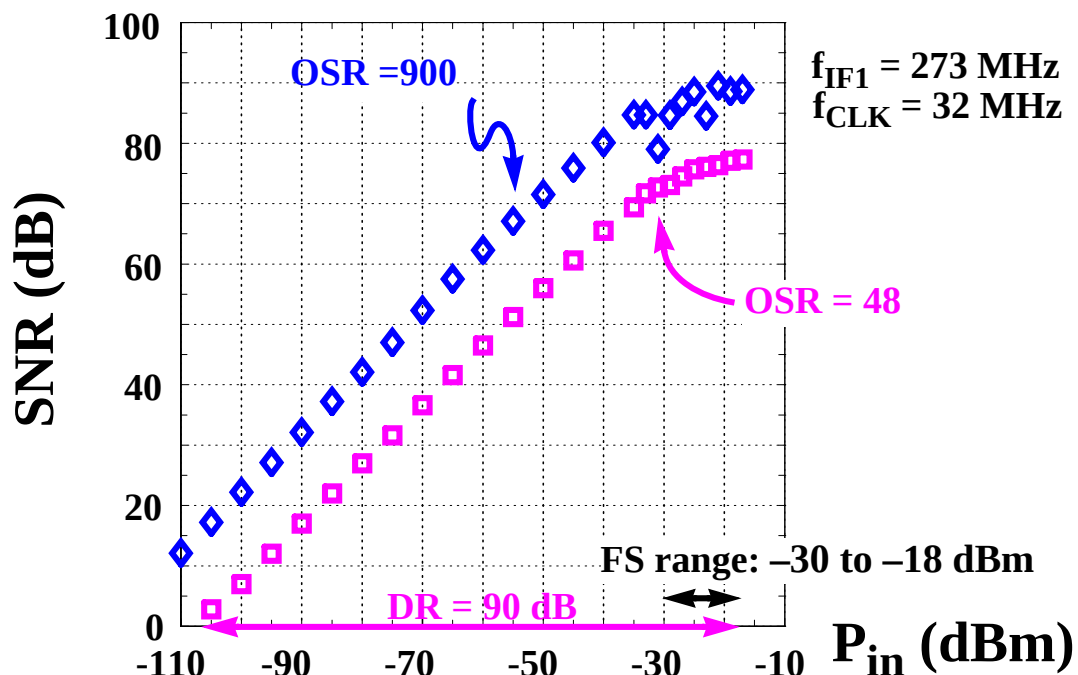

ECE1371

11-52

A Quadrature $\Delta\Sigma$ ADC System

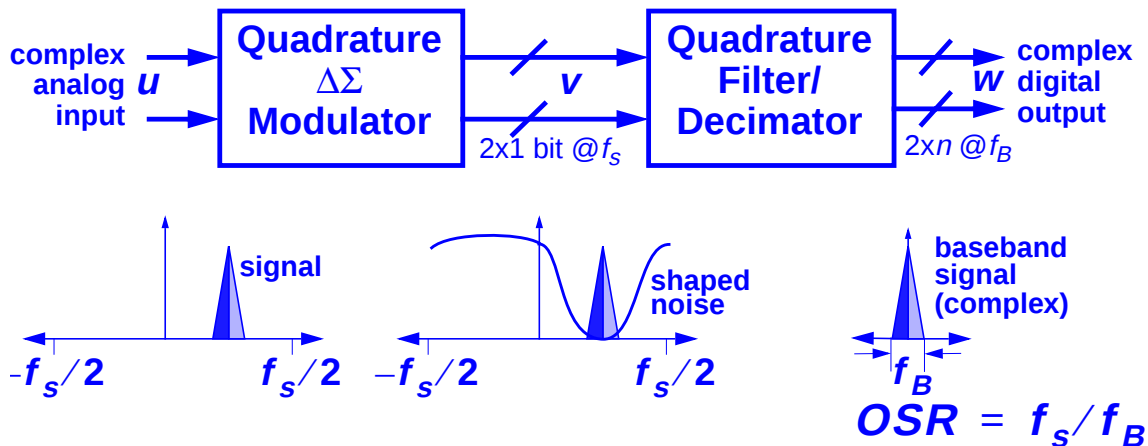


- Modulator converts its quadrature analog input into a pair of bit-stream outputs
- DSP removes out-of-band noise and translates the signal to baseband

ECE1371

11-53


Example Quadrature $\Delta\Sigma$ ADC AD9322, AD9328

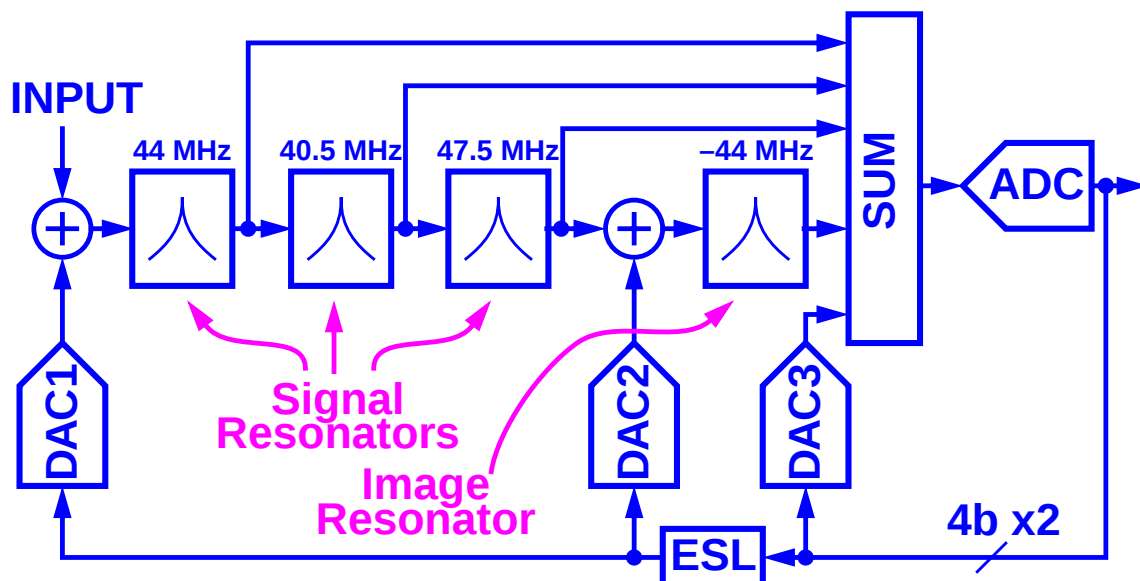

ECE1371

11-54

STF & NTF

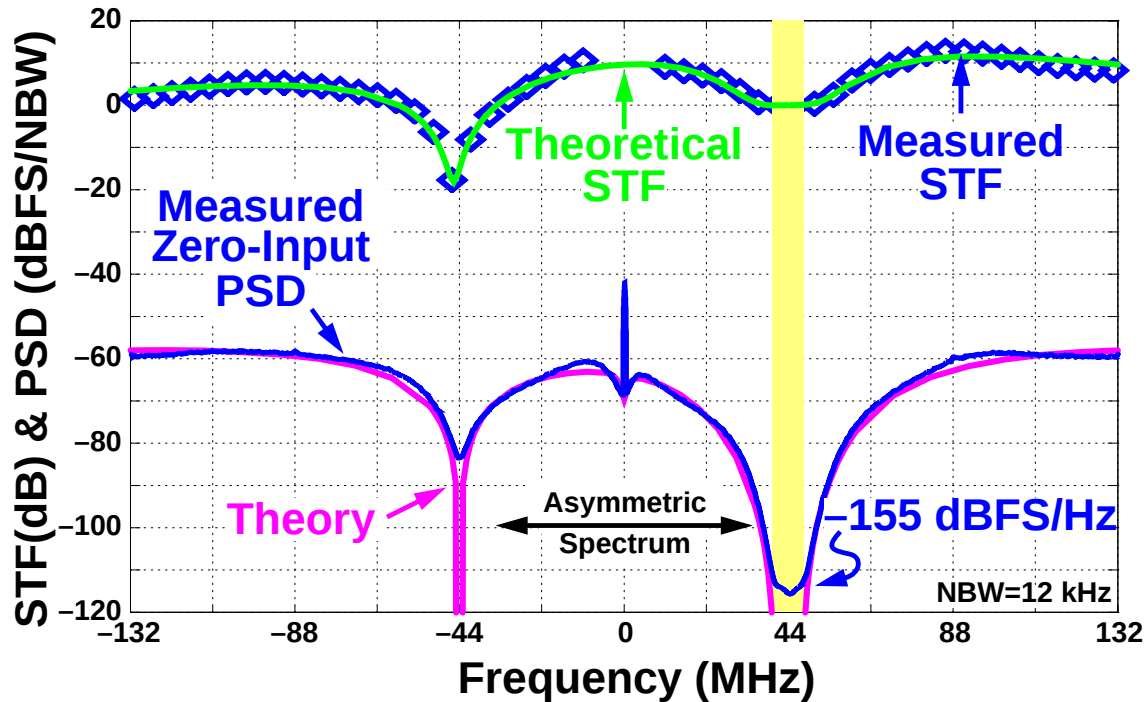

ECE1371

11-55

NLCOTD: High-Q Resonator

- Want $Q \gg \sqrt{3} \frac{f_0}{BW}$ for small SQNR degradation
- In a TV tuner ADC $f_0 = 44$ MHz and $BW = 8.5$ MHz, so we needed $Q \gg 9$


Actual requirement was $Q > 20$.

How can Q be kept high despite finite amplifier gain and bandwidth?

ECE1371

11-56

Active-RC Resonator Structure

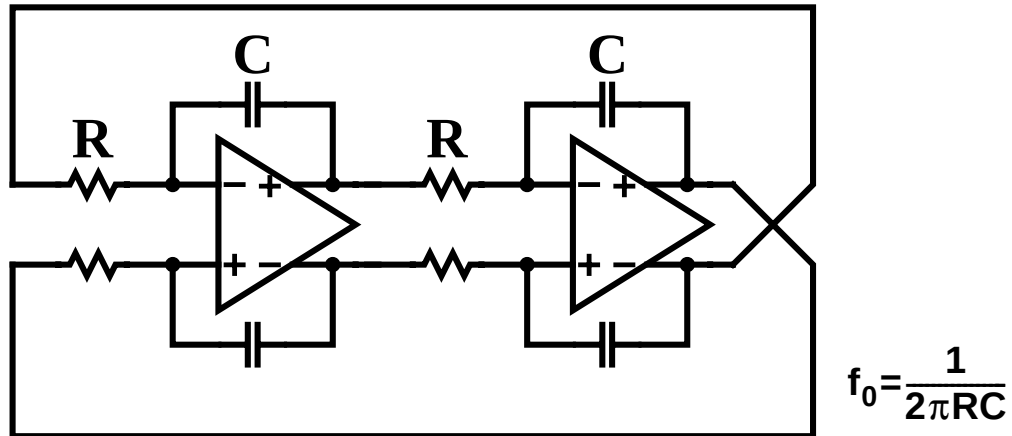


- Tuned by adding positive feedback to make an oscillator and adjusting C until the desired resonance is achieved
- Amplifier drives both R and $C \Rightarrow$ trouble?

ECE1371

11-57

Amplifier Gain and Phase


- Finite gain degrades Q
- Phase lag enhances Q
- Analysis shows $\phi = 45^\circ$ yields high Q , regardless of amplifier gain

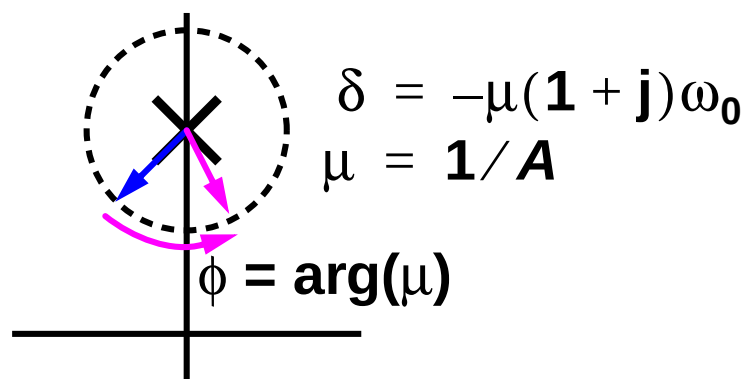

ECE1371

11-58


An Amplifier with $\phi = 45^\circ$ @ f_0 :

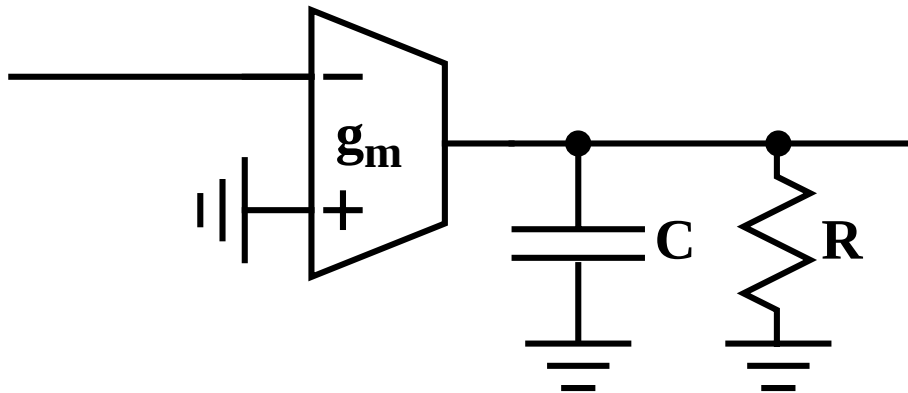

ECE1371

11-59

Resulting High-Q Resonator

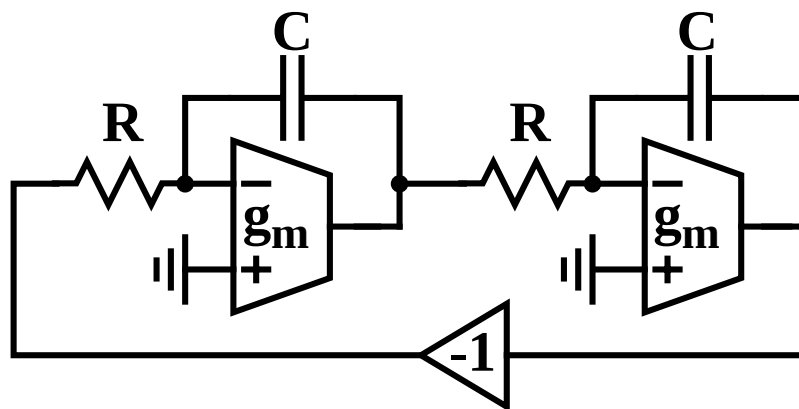


- Amplifier load yields $\phi = 45^\circ$ @ f_0
- Finite g_m shifts the pole frequency, but does not degrade Q!

ECE1371

11-60

Measured STF in an Alias Band

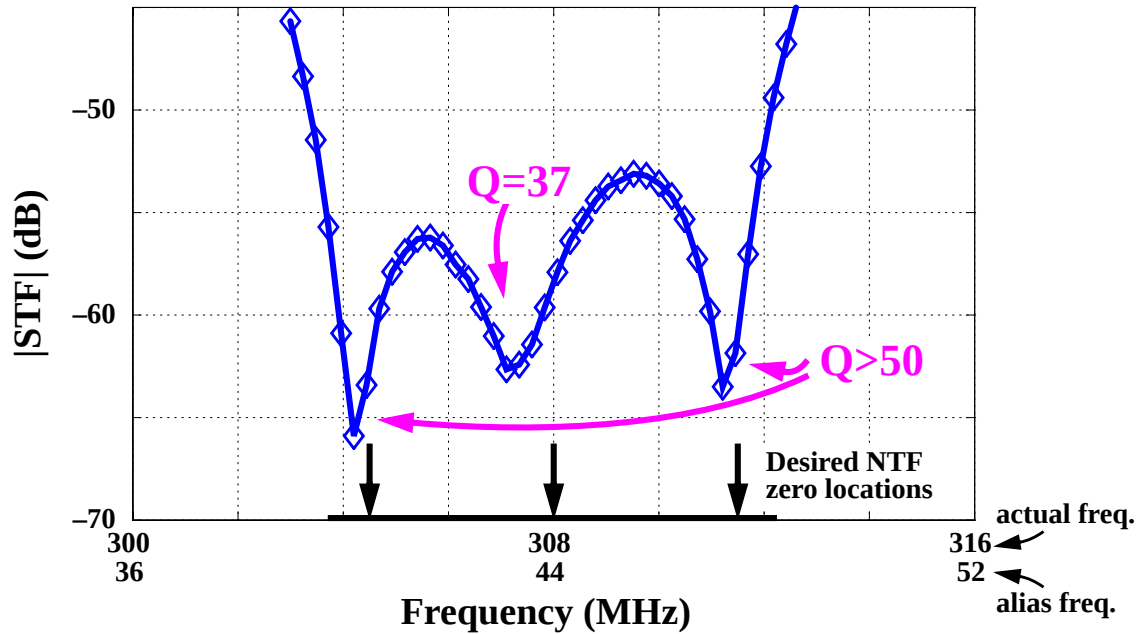

- Resonator Q is well above the design target!

ECE1371

11-61

What You Learned Today

- 1 State-space (ABCD) representation of the loop filter in the $\Delta\Sigma$ Toolbox
- 2 MASH Modulators
- 3 Continuous-Time Modulators
- 4 Bandpass and Quadrature Bandpass $\Delta\Sigma$

ECE1371

11-62