

ECE1371 Advanced Analog Circuits

Lecture 3

EXAMPLE DESIGN– PART 1

Richard Schreier
`richard.schreier@analog.com`

Trevor Caldwell
`trevor.caldwell@utoronto.ca`

Course Goals

- **Deepen understanding of CMOS analog circuit design through a top-down study of a modern analog system— a delta-sigma ADC**
- **Develop circuit insight through brief peeks at some nifty little circuits**


The circuit world is filled with many little gems that every competent designer ought to know.

Date	Lecture			Ref	Homework
2012-01-12	RS	1	Introduction: MOD1	ST 2, A	1: MOD1 in Matlab
2012-01-19	RS	2	MOD2 & MODN	ST 3, 4, B	2: MOD2 in Matlab
2012-01-26	RS	3	Example Design: Part 1	ST 9.1, CCJM 14	3: Sw.-level MOD2
2012-02-02	TC	4	SC Circuits	R 12, CCJM 14	4: SC Integrator
2012-02-09	TC	5	Amplifier Design		
2012-02-16	TC	6	Amplifier Design		5: SC Int w/ Amp
2012-02-23	Reading Week + ISSCC– No Lecture				
2012-03-01	RS	7	Example Design: Part 2	CCJM 18	Start Project
2012-03-08	RS	8	Comparator & Flash ADC	CCJM 10	
2012-03-15	TC	9	Noise in SC Circuits	ST C	
2012-03-22	TC	10	Matching & MM-Shaping	ST 6.3-6.5, +	
2012-03-29	RS	11	Advanced $\Delta\Sigma$	ST 6.6, 9.4	
2012-04-05	TC	12	Pipeline and SAR ADCs	CCJM 15, 17	
2012-04-12	No Lecture				
2012-04-19	Project Presentation				

Highlights (i.e. What you will learn today)

- 1 MOD2 implementation
- 2 Switched-capacitor integrator
Switched-C summer & DAC too
- 3 Dynamic-range scaling
- 4 kT/C noise
- 5 Verification strategy



Review: A $\Delta\Sigma$ ADC System

 

ECE1371

3-5

Review: MOD1

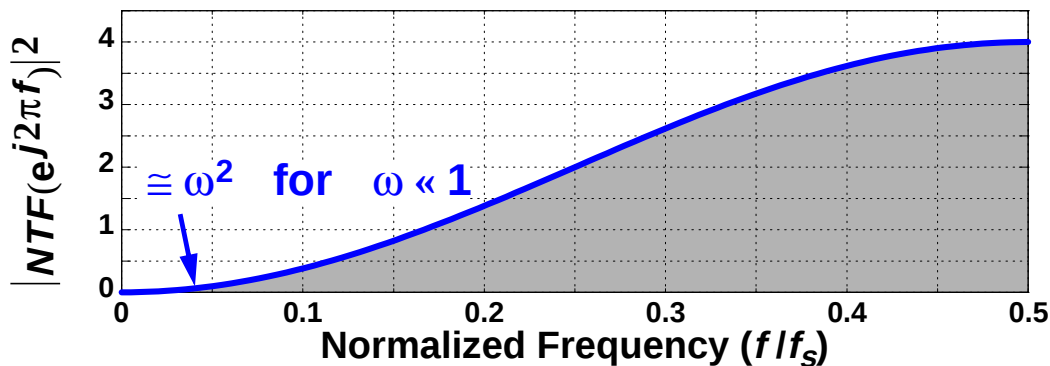
 


- Doubling OSR improves SQNR by 9 dB
 Peak SQNR $\approx \text{dbp}(9 \cdot \text{OSR}^3 / (2\pi^2))$; $\text{dbp}(x) \equiv 10\log_{10}(x)$

ECE1371


3-6

Review: MOD2

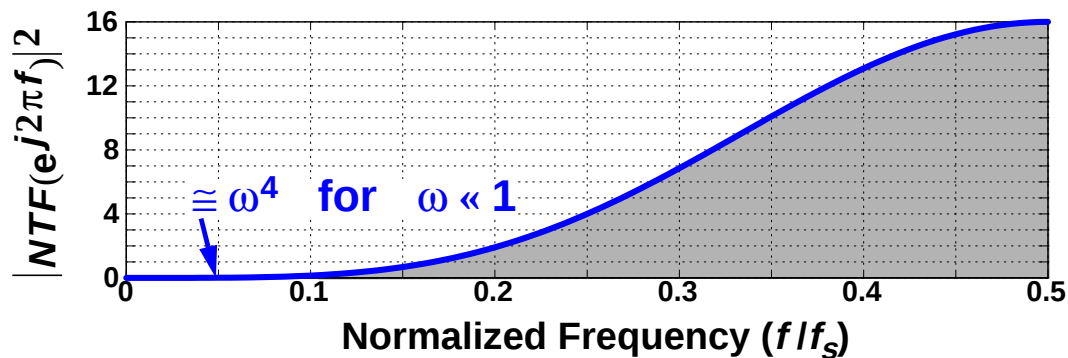 

- Doubling OSR improves SQNR by 15 dB
 Peak SQNR $\approx \text{dbp}((15 \cdot OSR^5)/(4\pi^4))$

 Review: Simulated MOD2 PSD Input at 50% of FullScale



Review: Advantages of $\Delta\Sigma$

- **ADC: Simplified Anti-Alias Filter**
Since the input is oversampled, only very high frequencies alias to the passband.
A simple RC section often suffices.
If a continuous-time loop filter is used, the anti-alias filter can often be eliminated altogether.
- **DAC: Simplified Reconstruction Filter**
The nearby images present in Nyquist-rate reconstruction can be removed digitally.
- + **Inherent Linearity**
Simple structures can yield very high SNR.
- + **Robust Implementation**
 $\Delta\Sigma$ tolerates sizable component errors.

ECE1371

3-9


Let's Try Making One!

- Clock at $f_s = 1$ MHz.
Assume BW = 1 kHz.
- $\Rightarrow OSR = f_s / (2 \cdot BW) = 500 \approx 2^9$
- MOD1: SQNR ≈ 9 dB/octave $\cdot 9$ octaves = 81 dB
 - MOD2: SQNR ≈ 15 dB/octave $\cdot 9$ octaves = 135 dB
Actually more like 120 dB.
 - SQNR of MOD1 is not bad, but SQNR of MOD2 is awesome!
In addition to MOD2's SQNR advantage, MOD2 is usually preferred over MOD1 because MOD2's quantization noise is more well-behaved.

ECE1371

3-10

What Do We Need?

 


- 1 Summation blocks
- 2 Delaying and non-delaying discrete-time integrators
- 3 Quantizer (1-bit)
- 4 Feedback DACs (1-bit)
- 5 Decimation filter (not shown)


Digital and therefore “easy.”

Switched-Capacitor Integrator


Single-ended circuit:

 


Timing:

 

$\phi 1$:

 

$\phi 2$:

 

ECE1371

3-13

$$q_2(n+1) = q_2(n) + q_1(n)$$

$$zQ_2(z) = Q_2(z) + Q_1(z)$$

$$Q_2(z) = \frac{Q_1(z)}{z-1}$$

- This circuit integrates charge
- Since $Q_1 = C_1 V_{in}$ and $Q_2 = C_2 V_{out}$

$$\frac{V_{out}(z)}{V_{in}(z)} = \frac{C_1/C_2}{z-1}$$


- Note that the voltage gain is controlled by a *ratio* of capacitors

With careful layout, 0.1% accuracy is possible.

ECE1371

3-14

Summation + Integration

 


⇒ Adding an extra input branch accomplishes addition, with weighting

ECE1371

3-15


1b DAC + Summation + Integration

 

ECE1371

3-16

Differential Integrator

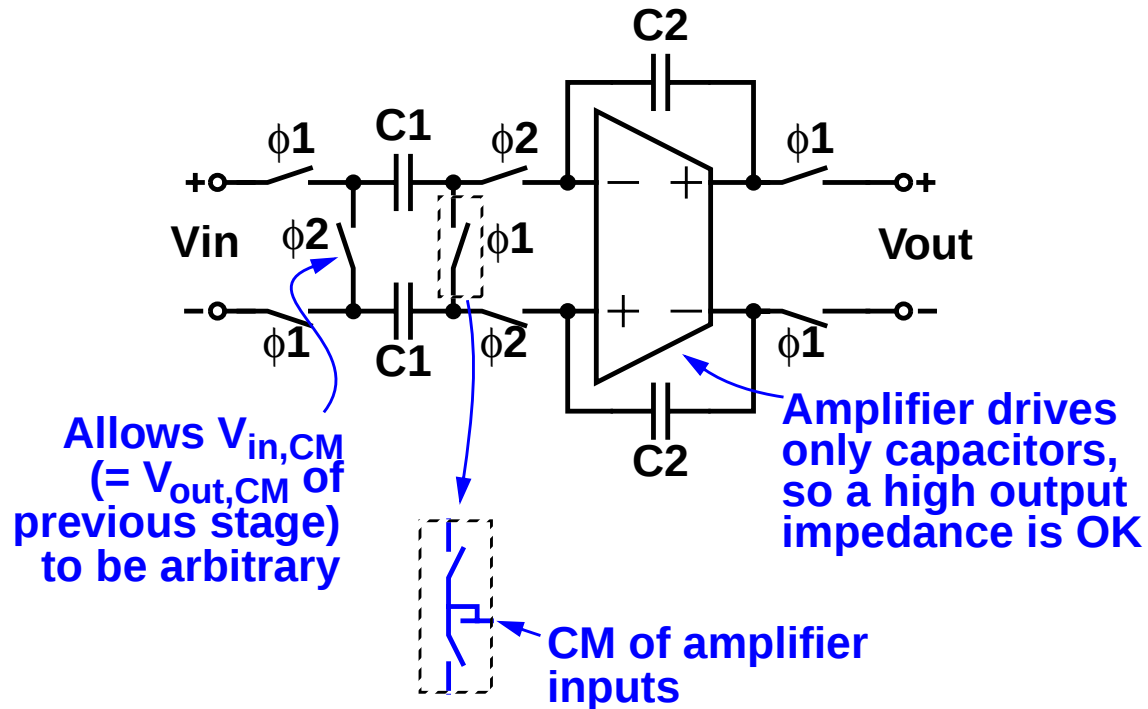


ECE1371


3-17

Non-Delaying Integrator

Single-ended circuit:

 


Timing:

 


ECE1371

3-18

$\phi 2$:

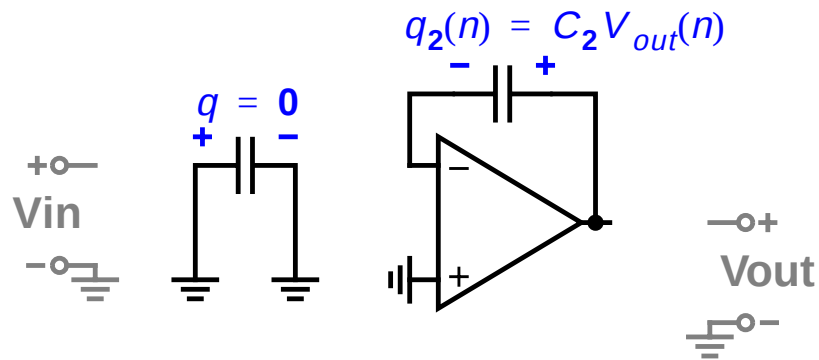

$\phi 1$:

 

ECE1371

3-19

$$q_2(n+1) = q_2(n) - q_1(n+1)$$

$$z Q_2(z) = Q_2(z) - z Q_1(z)$$

$$\frac{Q_2(z)}{Q_1(z)} = -\frac{z}{z-1}$$

$$\frac{V_{out}(z)}{V_{in}(z)} = -\left(\frac{C_1}{C_2}\right) \frac{z}{z-1}$$


- Delay-free integrator (inverting)

ECE1371


3-20

“Half-Delay” Integrator

Single-ended circuit:

 

Timing:

 

ECE1371

3-21

Half-Delay Integrator


- Output is sampled on a different phase than the input
 - Some use the notation $H(z) = \frac{z^{-1/2}}{z-1}$ to denote the shift in sampling time
I consider this an abuse of notation.
 - An alternative method is to declare that the border between time n and $n+1$ occurs at the end of a specific phase, say $\phi2$
- ⇒ A circuit which samples on $\phi1$ and updates on $\phi2$ is non-delaying, i.e. $H(z) = z/(z-1)$, whereas a circuit which samples on $\phi2$ and updates on $\phi1$ is delaying, i.e. $H(z) = 1/(z-1)$.

ECE1371

3-22

Timing in a $\Delta\Sigma$ ADC

 - The safest way to deal with timing is to construct a timing diagram and verify that the circuit implements the desired difference equations
- E.g. MOD2:



Difference Equations:

$$v(n) = Q(x_2(n)) \quad (0)$$


$$x_1(n+1) = x_1(n) - v(n) + u(n) \quad (1)$$

$$x_2(n+1) = x_2(n) - v(n) + x_1(n+1) \quad (2)$$


ECE1371

3-23

Switched-Capacitor Realization

 

Timing

 

Timing looks OK!

ECE1371

3-24

Signal Swing

- So far, we have not paid any attention to how much swing the op amps can support, or to the magnitudes of u , V_{ref} , x_1 and x_2
- For simplicity, assume:
the full-scale range of u is ± 1 V,
the op-amp swing is also ± 1 V and
 $V_{\text{ref}} = 1$ V
- We still need to know the ranges of x_1 and x_2 in order to accomplish *dynamic-range scaling*


ECE1371

3-25


Dynamic-Range Scaling

- In a linear system with known state bounds, the states can be scaled to occupy any desired range

e.g. one state of original system:

 

state scaled by $1/k$:

 


ECE1371

3-26

State Swings in MOD2

Linear Theory

 

$$V = z^{-1}U + (1 - z^{-1})^2 E$$

$$X_1 = \frac{z}{z-1}(U - V) = U - (1 - z^{-1})E$$

$$X_2 = V - E = z^{-1}U + (-2z^{-1} + z^{-2})E$$



- If u is constant and e is white with power $\sigma_e^2 = 1/3$, then $\bar{x}_1 = u$, $\sigma_{x_1}^2 = 2\sigma_e^2 = 2/3$, $\bar{x}_2 = u$ and $\sigma_{x_2}^2 = 5\sigma_e^2 = 5/3$

ECE1371



3-27

Simulated Histograms

$u = -0.1$

  

$u = 0.7$

  

ECE1371

3-28


Observations

- The match between simulations and our linear theory is fair for x_1 , but poor for x_2
 - x_1 's mean and standard deviation match theory, although x_1 's distribution does not have the triangular form that would result if e were white and uniformly-distributed in $[-1,1]$.
 - x_2 's mean is 50-100% high, its standard deviation is ~25% low, and the distribution is weird.
- ⇒ Our linear theory is not adequate for determining signal swings in MOD2
 - No real surprise. Linear theory does not handle overload, i.e. where $x_1, x_2 \rightarrow \infty$ when $u > 1$.
- Is there a better theory?
 - Yes, but it is complicated and gives minimal insight.

ECE1371

3-29

MOD2 Simulated State Bounds

 


ECE1371

3-30

Scaled MOD2


- Take $\|x_1\|_\infty = 3$ and $\|x_2\|_\infty = 9$
The first integrator should not saturate.
The second integrator will not saturate for dc inputs up to -3 dBFS and possibly as high as -1 dBFS.
- Our scaled version of MOD2 is thus

 

ECE1371

3-31

 First Integrator (INT1) Shared Input/Reference Caps




- How do we determine C?

ECE1371

3-32

kT/C Noise

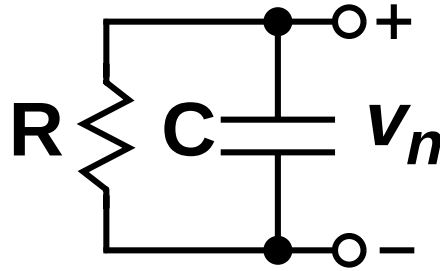

- **Fact:** Regardless of the value of R , the mean-square value of the voltage on C is

$$\overline{V_n^2} = \frac{kT}{C}$$

where $k = 1.38 \times 10^{-23}$ J/K is *Boltzmann's constant* and T is the temperature in Kelvin

The ms noise charge is $\overline{q_n^2} = C^2 \overline{V_n^2} = kTC$.

Derivation of kT/C Noise

- ***Equipartition of Energy*** physical principle:
“In a system at thermal equilibrium, the average energy associated with any degree of freedom is $\frac{1}{2}kT$.”

This applies to the kinetic energy of atoms (along each axis of motion), vibrational energy in molecules and to the potential energy in electrical components.

- **Fact:** The energy stored in a capacitor is $\frac{1}{2}CV^2$
- So, according to equipartition, $\frac{1}{2}C\overline{V^2} = \frac{1}{2}kT$,
or

$$\overline{V^2} = \frac{kT}{C}$$


Implications for an SC Integrator

- Each charge/discharge operation has a random component

The amplifier plays a role during phase 2, but we'll assume that the noise in both phases is just kT/C .

We'll revisit this assumption in Lecture 9.

- For a given cap, these random components are essentially uncorrelated, so the noise is white

 


ECE1371

3-35

Integrator Implications (cont'd)

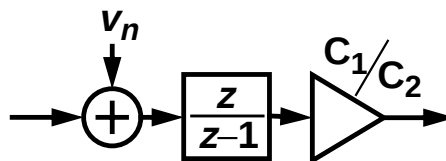- This noise charge is equivalent to a noise voltage with ms value $\overline{v_n^2} = 2kT/C_1$ added to the input of the integrator:




- This noise power is spread uniformly over all frequencies from 0 to $f_s/2$

⇒ The power in the band $[0, f_B]$ is $\overline{v_n^2}/OSR$

ECE1371

3-36

Differential Noise

 

- Twice as many switched caps
 $\Rightarrow$ twice as much noise power
- The input-referred noise power in our differential integrator is

$$\overline{v_n^2} = 4kT/C_1$$

ECE1371

3-37

INT1 Absolute Capacitor Sizes For SNR = 100 dB @ -3-dBFS input

- The signal power is

$$\overline{v_s^2} = \underbrace{\frac{1}{2}}_{-3 \text{ dBFS}} \cdot \underbrace{\frac{(1 \text{ V})^2}{2}}_{\frac{A^2}{2}} = 0.25 \text{ V}^2$$

- Therefore we want $\overline{v_{n, \text{in-band}}^2} = 0.25 \times 10^{-10} \text{ V}^2$
- Since $\overline{v_{n, \text{in-band}}^2} = \overline{v_n^2} / \text{OSR}$

$$C_1 = \frac{4kT}{\overline{v_n^2}} = 1.33 \text{ pF}$$


- If we want 10 dB more SNR, we need 10x caps

ECE1371

3-38

Second Integrator (INT2)

Separate Input and Feedback Caps

 


ECE1371

3-39

INT2 Absolute Capacitor Sizes

 - In-band noise of second integrator is greatly attenuated



⇒ Capacitor sizes not dictated by thermal noise


- Charge injection errors and desired ratio accuracy set absolute size

A reasonable size for a small cap is currently ~10 fF.

ECE1371

3-40

Behavioral Schematic

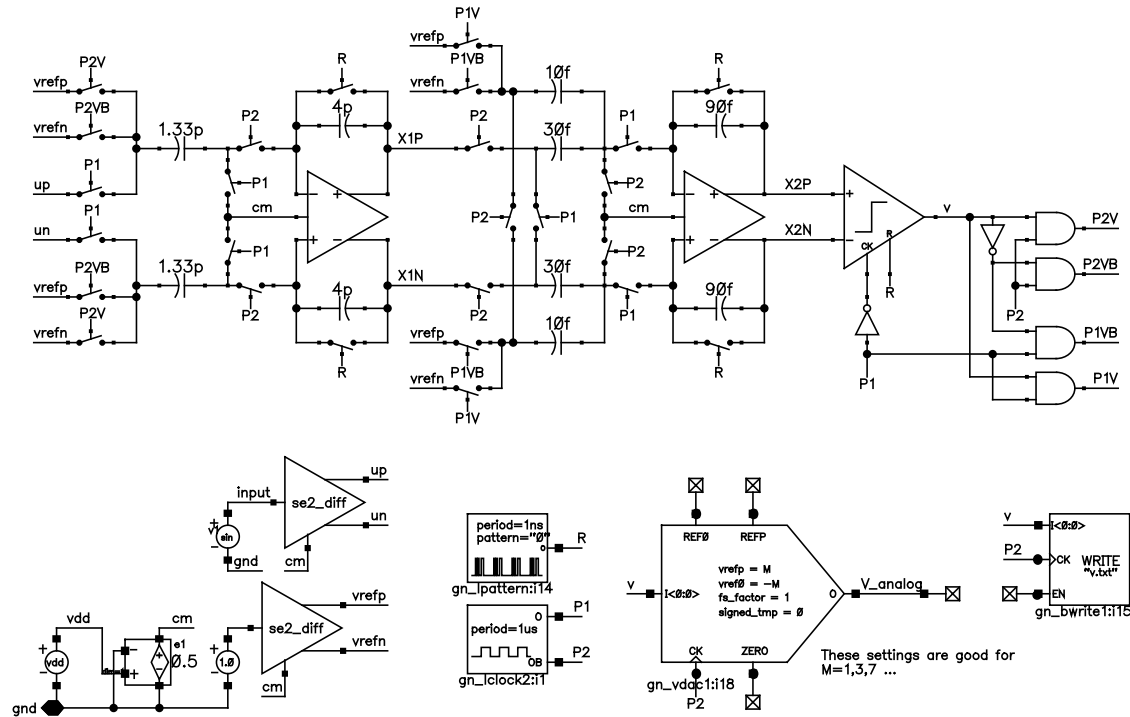

ECE1371

3-41

Verification

Open-loop verification

- 1 Loop filter
- 2 Comparator

Since MOD2 is a 1-bit system, all that can go wrong is the polarity and the timing. Usually the timing is checked by (1), so this verification step is not needed.

Closed-loop verification


- 3 Swing of internal states
- 4 Spectrum: SQNR, STF gain
- 5 Sensitivity, start-up, overload recovery, ...

ECE1371

3-42

Loop-Filter Check— Theory

 - Open the feedback loop, set $u = 0$ and drive an impulse through the feedback path



$$X_2 = \frac{-1}{z-1} \left(1 + \frac{z}{z-1} \right) Y$$


$$\therefore y(n) = \{1, 0, 0, \dots\} \Rightarrow x_2(n) = \{-2, -3, -4, \dots\}$$

- If x_2 is as predicted then the loop filter is correct
At least for the feedback signal, which implies that the NTF will be as designed.

ECE1371

3-43

Loop Filter Check— Practice*

 

*. "In theory there is no difference between theory and practice.
But in practice there is."

ECE1371

3-44

Hey! You Cheated!

- An impulse is $\{1,0,0,\dots\}$, but a binary DAC can only output ± 1 , i.e. it cannot produce a 0

Q: So how can we determine the impulse response of the loop filter through simulation?


A: Do two simulations: one with $v = \{-1,-1,-1,\dots\}$ and one with $v = \{+1,-1,-1,\dots\}$.

Then take the difference.


According to superposition, the result is the response to $v = \{2,0,0,\dots\}$, so divide by 2.

To keep the integrator states from growing too quickly, you could also use $v = \{-1,-1,+1,-1,\dots\}$ and then $v = \{+1,-1,+1,-1,\dots\}$.

 Simulated State Swings –3-dBFS ~300-Hz sine wave




Unclear Spectrum

 

ECE1371

3-47

Professional Spectrum

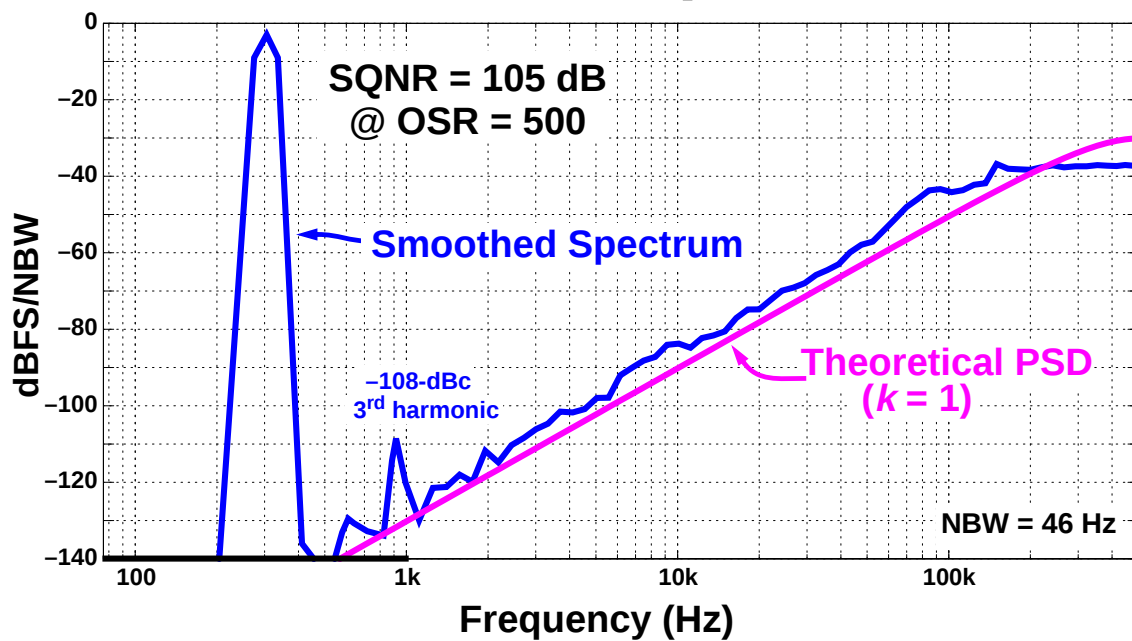

- SQNR dominated by -109-dBFS 3rd harmonic

ECE1371

3-48

Implementation Summary


- 1 Choose a viable SC topology and manually verify timing
- 2 Do dynamic-range scaling
You now have a set of capacitor ratios.
Verify operation: loop filter, timing, swing, spectrum.
- 3 Determine absolute capacitor sizes
Verify noise.
- 4 Determine op-amp specs and construct a transistor-level schematic
Verify everything.
- 5 Layout, fab, debug, document, get customers, sell by the millions, go public, ...

ECE1371


3-49

Differential vs. Single-Ended

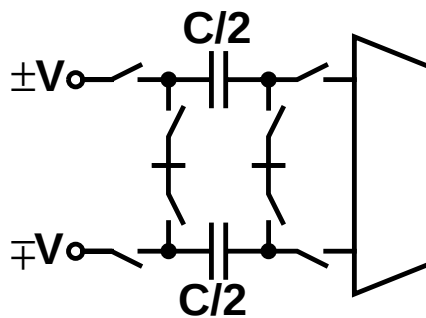- Differential is more complicated and has more caps and more noise $\Rightarrow$ single-ended is better?


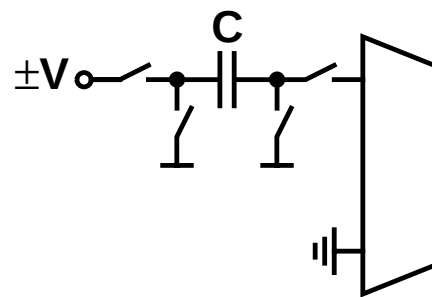
$$SNR = \frac{(2V)^2/2}{4kT/(C/2)} = \frac{CV^2}{4kT}$$




$$SNR = \frac{V^2/2}{2kT/C} = \frac{CV^2}{4kT}$$

- Same capacitor area $\Rightarrow$ same SNR
Differential is generally preferred due to rejection of even-order distortion and common-mode noise/interference.

ECE1371

3-50

Double-Sampled Input

 


- Doubles the effective input signal
- Allows C_1 to be 1/4 the size for the same SNR
- Doubles the sampling rate of the signal, thereby easing AAF further

ECE1371

3-51

Shared vs. Separate Input Caps

 - Separate caps $\Rightarrow$ More noise:




- But using separate caps allows input CM to be different from reference CM, and so is often preferred in a general-purpose ADC

ECE1371

3-52

Signal-Dependent Ref. Loading

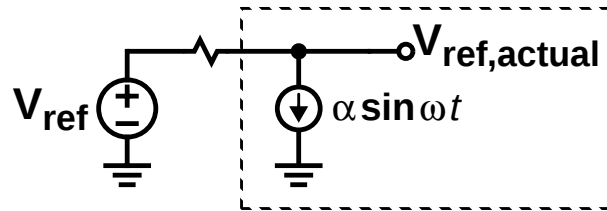- Another practical concern is the current draw from the reference




$$\text{ADC Output} \propto \frac{V_{in}}{V_{ref}(1 - \epsilon \sin \omega t)} \approx \frac{V_{in}}{V_{ref}}(1 + \epsilon \sin \omega t)$$

- If the reference current is signal-related, harmonic distortion can result

ECE1371

3-53

Shared Caps and Ref. Loading

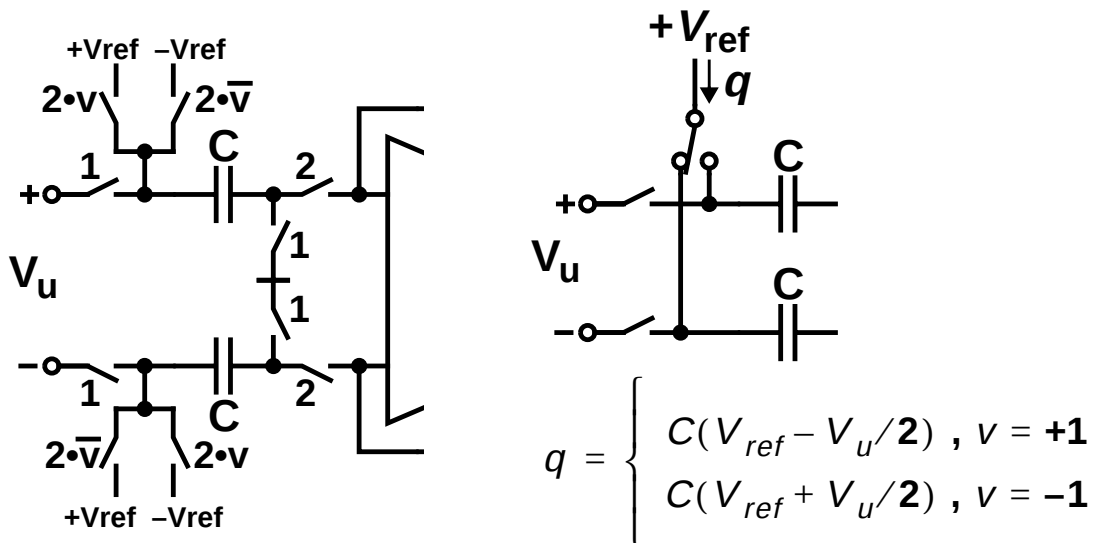

ECE1371

3-54

Thus

$$\bar{i} = \frac{C}{T}(V_{ref} - v \cdot V_u/2)$$

- If $u = A\sin\omega_u t$, then $v = u + \text{error}$ also contains a component at ω_u and thus i contains a component at $\omega = 2\omega_u$.
- Since ADC Output $\propto V_{in}(1 + \varepsilon \sin\omega t)$, the signal-dependent reference current in our circuit can produce 3rd-harmonic distortion

Also, the load presented to the driving circuit is dependent on v and this noisy load can cause trouble.


- With separate caps, the reference current is signal-independent

Yet another reason for using separate caps.

ECE1371

3-55

Unipolar Reference

 


- Be careful of the timing of v relative to the integration phase!

ECE1371

3-56

Single-Ended Input Shared Caps

 

ECE1371

3-57

Homework #3

Construct a differential switched-capacitor implementation of MOD2 using ideal elements (switches, capacitors, amplifiers, comparator) and verify it.

Scale the circuit such that the full-scale differential input range is $[-1, +1]$ V and the op amp swing is $0.5 V_{p,diff}$ at -6 dBFS. You may assume that -0.5 -V and $+0.5$ -V references are available and that the input is available in differential form.

Choose capacitor values such that the SNR with a -6 dBFS input will be ~ 85 dB when $OSR = 128$. You may assume that the only source of noise is kT/C noise.

ECE1371

3-58

Homework Deliverables

- 1 Schematic of MOD2 with annotated DC node voltages
- 2 Open-loop impulse response plot
- 3 Transient of input signal and integrator outputs for a -6 -dBFS input
- 4 Spectrum of output data for a -6 -dBFS input, with SNDR calculated
- 5 SNDR vs. input amplitude plot
- 6 kT/C noise calculation (justify your choice of C)

What You Learned Today And what the homework should solidify

- 1 MOD2 implementation
- 2 Switched-capacitor integrator
Switched-C summer & DAC too
- 3 Dynamic-range scaling
- 4 kT/C noise
- 5 Verification strategy