

ECE1371 Advanced Analog Circuits

Lecture 8

COMPARATOR & FLASH ADC DESIGN

Richard Schreier
richard.schreier@analog.com

Trevor Caldwell
trevor.caldwell@utoronto.ca

| Date | | Lecture | Ref | Homework |
|------------|-------|----------------------------------|-----------------|-------------------|
| 2012-01-12 | RS 1 | Introduction: MOD1 | ST 2, A | 1: MOD1 in Matlab |
| 2012-01-19 | RS 2 | MOD2 & MODN | ST 3, 4, B | 2: MOD2 in Matlab |
| 2012-01-26 | RS 3 | Example Design: Part 1 | ST 9.1, CCJM 14 | 3: Sw.-level MOD2 |
| 2012-02-02 | TC 4 | SC Circuits | R 12, CCJM 14 | 4: SC Integrator |
| 2012-02-09 | TC 5 | Amplifier Design | | |
| 2012-02-16 | TC 6 | Amplifier Design | | 5: SC Int w/ Amp |
| 2012-02-23 | | Reading Week + ISSCC— No Lecture | | |
| 2012-03-01 | RS 7 | Example Design: Part 2 | CCJM 18 | Start Project |
| 2012-03-08 | RS 8 | Comparator & Flash ADC | CCJM 10 | |
| 2012-03-15 | TC 9 | Noise in SC Circuits | ST C | |
| 2012-03-22 | TC 10 | Matching & MM-Shaping | ST 6.3-6.5, + | |
| 2012-03-29 | RS 11 | Advanced $\Delta\Sigma$ | ST 6.6, 9.4 | |
| 2012-04-05 | TC 12 | Pipeline and SAR ADCs | CCJM 15, 17 | |
| 2012-04-12 | | No Lecture | | |
| 2012-04-19 | | Project Presentation | | |

ECE1371

8-3

Course Goals


- Deepen understanding of CMOS analog circuit design through a top-down study of a modern analog system— a delta-sigma ADC
- Develop circuit insight through brief peeks at some nifty little circuits

The circuit world is filled with many little gems that every competent designer ought to know.

ECE1371

8-2

NLCOTD: Linear Transconductor

 

- Useful in
 - 1 gm-C filter
 - 2 LNA
 - 3 mixer
 - 4 CT $\Delta\Sigma$ ADC

ECE1371

8-4

Highlights


(i.e. What you will learn today)

- 1 Operation of Example Comparator Circuit
- 2 Regeneration Time Constant
- 3 Metastability, Probability of Error
- 4 Dynamic Offset
- 5 Other Comparator Circuits
- 6 A Bunch of Transconductor Circuits

ECE1371

8-5

Background: Filtered White Noise

 


- The power of the output is the product of the PSD and the power gain of the filter
- Example: $h(t) = \begin{cases} 1 & 0 \leq t \leq T \\ 0 & \text{otherwise} \end{cases}$

$$\Rightarrow \sigma_y^2 = ST$$

ECE1371


8-6

 Circuits Application: Integrated White Noise



- Variance of V increases linearly with time
- “Random Walk” or “Brownian Motion”
For any given increment of time Δt , the change in V is a random variable with constant variance
 $\delta(t) \equiv V(t) - V(t - \Delta t) \Rightarrow \sigma_{\delta}^2 = \text{constant}$

Today's Application

 

$$h(t) = \begin{cases} e^{t/\tau} & 0 \leq t \leq T \\ 0 & \text{otherwise} \end{cases}$$

$$\sigma_y^2 = \frac{S\tau}{4} \left(e^{\frac{2T}{\tau}} - 1 \right)$$

ECE1371

8-7

ECE1371

8-8

Background: PDF of a Sum


- Suppose x and y are two independent random variables with probability density functions (PDFs) $\rho_x(x)$ and $\rho_y(y)$
- Then the PDF of their sum is the convolution of the individual PDFs

$$z = x + y \Rightarrow \rho_z(z) = \int_{-\infty}^{\infty} \rho_x(x) \rho_y(z - x) dx$$

ECE1371

8-9

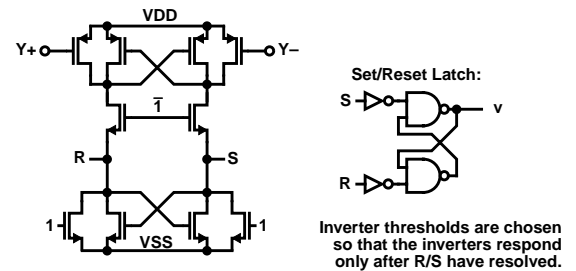Review: Latched Comparator From Lecture #7's 1-MHz MOD2




- Falling phase 1 initiates regenerative action
S and R connected to a Set/Reset latch.

ECE1371

8-10

Phase 1 = High: “Reset” Mode

 


- Grayed-out devices are off
=> the active part of the comparator is reset
- R and S are low => the SR latch is in hold mode

ECE1371

8-11

Phase 1 Goes Low: “Latch” Mode

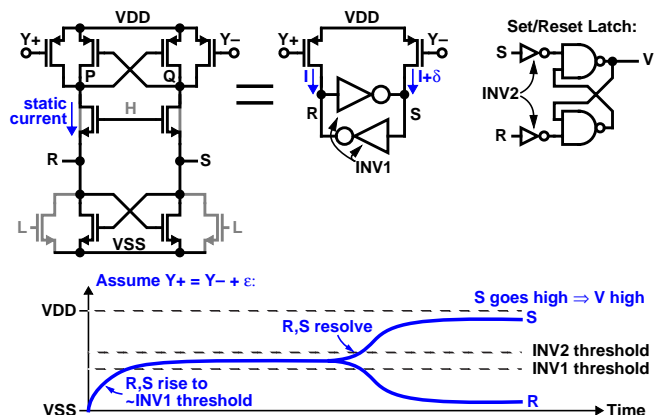


ECE1371

8-12

Example Waveforms


Quick Design in 65nm (VDD = 1V)

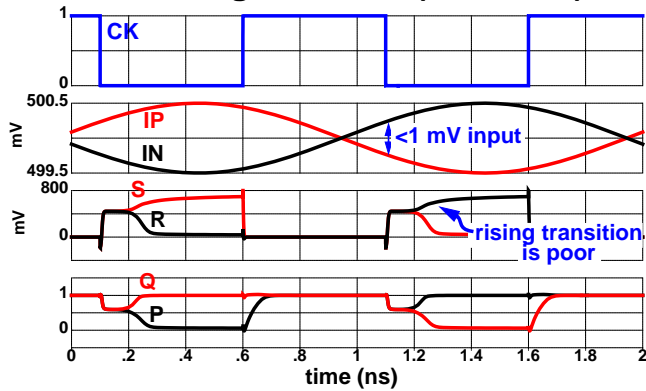

ECE1371

8-13


Better Design

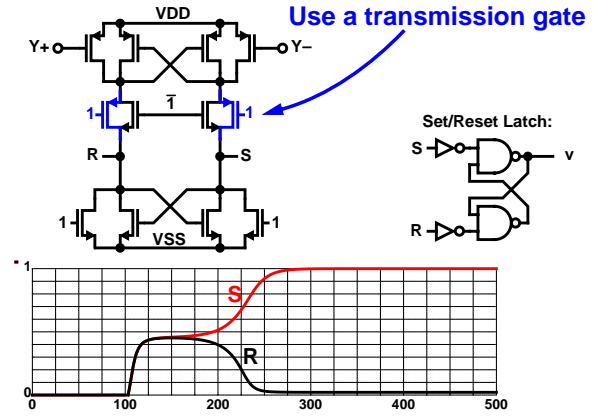

ECE1371

8-14


Responses for Various V_{in}

 

ECE1371

8-15

Delay vs. V_{in}

 


ECE1371


8-16

Latch Mode Dynamics

 - For V_{in} near the trip point, an inverter is essentially just a transconductor:




- So near balance the comparator looks like this:

 

ECE1371

8-17


Small-Signal Analysis

 

ECE1371

8-18

State-Space

 


- $v_{cm} \rightarrow VDD/2, v_d \rightarrow \pm VDD$

ECE1371

8-19

Metastability

- Metastability is fundamentally unavoidable
- Assuming the universe is continuous and deterministic, a comparator can be unresolved for any length of time

 

ECE1371

8-20

Probability of Error, P_E

$$P_E = P\{\text{not resolved by time } t\}$$

$$= P\left\{V_{in} < \exp\left(-\frac{t-t_0}{\tau}\right)\right\}$$

- Take $t_0 = 100$ ps and $\tau = 20$ ps
- Then for $t = 500$ ps (1 GHz clock with a half-cycle between the comparator's clock and the clock of the subsequent latch),


$$P_E = P\{|V_{in}| < 2 \text{ nV}\}$$
- Assuming V_{in} is uniformly distributed in $[-0.5, +0.5]$ V, $P_E = 2 \times 10^{-9}$
 Metastability occurs twice a second!

ECE1371

8-21

Quantized Charge Helps?

 - If $C = 20$ fF, then 1 electron yields $8 \mu\text{V}$
- $V_{in} = 2$ nV and hence metastability impossible?



- + Unless V_{offset} is within 2 nV of one of the discrete V_{in} levels, metastability can't happen
- But if V_{offset} is within 2 nV of an allowed V_{in} level, metastability will be abnormally frequent
- Offset drift will tend to make metastability appear/disappear sporadically (?)

ECE1371

8-22


Noise Helps?

- $kT/C = 500 \mu\text{V}$, so it is impossible to guarantee that metastability will result even if $V_{in} = 0$
- + Noise does help a comparator resolve if it is metastable
- But for any given noise (random initial condition), there is always an input which results in metastability
- Noise makes it hard to set initial conditions that will result in metastability, but does not reduce the probability of error

ECE1371

8-23

What About Noise During Regeneration?

 


- Noise from the g_m s prevents metastability?

ECE1371

8-24

Differential Circuit

 

ECE1371

8-25


Let's "Make Numbers"

- Assume $g_m = 1 \text{ mA/V}$, $C = 20 \text{ fF}$, $t = 400 \text{ ps}$
 $\Rightarrow \tau = 20 \text{ ps}$; 20τ to resolve
- If v_0 uniformly distributed in $[-2, +2] \text{ mV}$, then 1st term is uniformly distributed in $[-1, +1] \text{ MV}$
- Standard deviation of 2nd term is 250 kV
 Equivalent to a 0.5-mV initial condition
- Noise during regeneration helps when the input is known to be small, but is usually negligible compared to the exponential growth of the initial conditions

ECE1371

8-26

Offset

 


- Obvious sources of offset include mismatch in the input differential pair as well as mismatch in the regenerating devices

ECE1371

8-27

Dynamic Offset

 


- Mismatched parasitic capacitance also causes offset
 20 mV/fF for this comparator!
- Bad design– Can fix this!

ECE1371

8-28

Improved Comparator [S&T Fig. 9.36]

 


- Reset when $CK = 1$; regenerates when $CK = 0$
- x & y don't step if biased properly
 Mismatch in overlap capacitance still a problem.

ECE1371

8-29

Reducing Offset with a Preamp

 


$$V_{\text{off,tot}} = V_{\text{off,amp}} + V_{\text{off,comp}}/A$$

- Comparator offset is reduced by preamp gain
 Amplifier offset dominates.
- Amplifier also isolates driving stage from "charge kickback"
- Amplifier bandwidth limits speed, especially recovery from overload

ECE1371

8-30

 Auto-zeroed SC Comparator [J&M Fig 13.17]




- During P1, the inverter/amplifier is biased at its threshold/offset voltage
- During P2, the difference between V_{in} and V_{ref} is amplified

ECE1371

8-31


Comparator with Preamp [J&M Fig. 7.16]

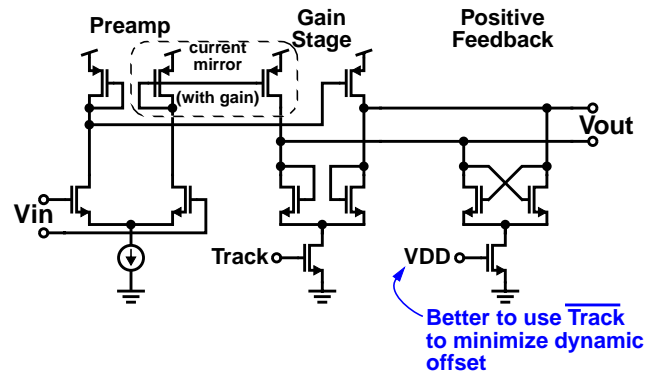

ECE1371

8-32

Two-Stage Comparator [J&M Fig 7.17]

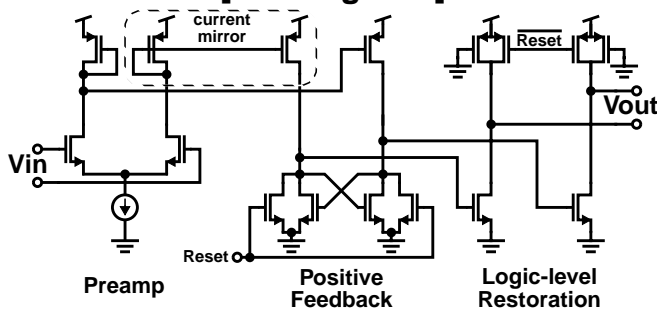


- Precharges regeneration nodes low & digital output nodes high

ECE1371

8-33


Flash ADC

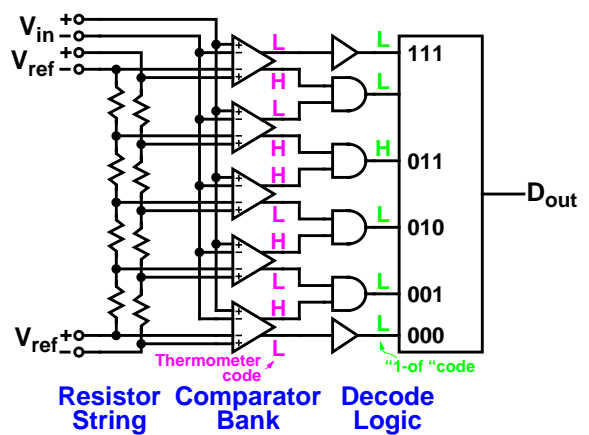

ECE1371

8-34


Flash Bubbles

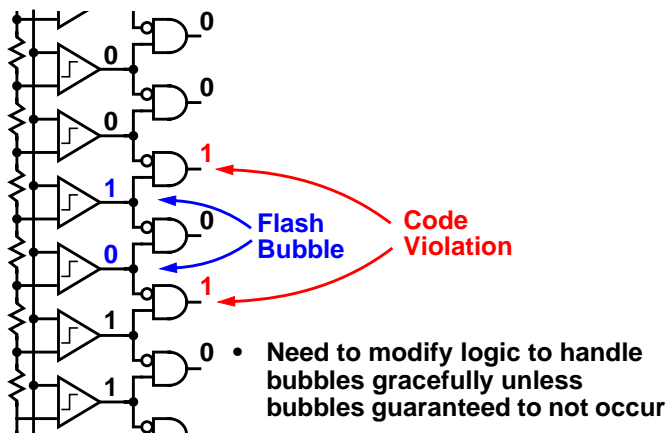

ECE1371

8-35


Averaging and Interpolation

 

ECE1371


8-36

 NLCOTD: Linear Transconductors Degenerated Differential Pair



- + Simple!
- V_{gs} varies nonlinearly with $I_{out} \Rightarrow g_m$ is nonlinear

Force Constant V_{gs}

 

- I_d constant $\Rightarrow V_{gs}$ constant
- Linearity dependent on current-mirror linearity


ECE1371

8-37

ECE1371

8-38

Cascomp

 


- V_{gs} of input devices replicated in cascodes and distortion-cancelling current injected into output
- + All NMOS \Rightarrow fast
- Cancellation depends on matching
Should tie bulk to source?

ECE1371

8-39

Add Op Amps

 


- + Linearity limited only by op amp gain and BW
- + High output resistance
- Output compliance depends on input swing

ECE1371

8-40

Mirror the Output Current

 


- + Output compliance is $V_{DD} - 2 V_{dsat}$
- Top of differential pair at $V_{DD} - V_{gs}$

ECE1371

8-41

Fold the Output Current

 


- + Increased headroom for differential pair
- + Increased output resistance

ECE1371

8-42

Multi-Tanh Doublet

[Gilbert JSSC Dec. 1998]

 


- With BJTs, ratioing the emitter areas creates a well-controlled offset
- With the right offset, the cubic term in the nonlinearity is zero!

$$n = 2 + \sqrt{3} = 3.73 \approx 15/4$$

ECE1371

8-43

MOS Quad

 

- Supposedly can get less distortion than a degenerated differential pair by fiddling with W/L

ECE1371

8-44

What You Learned Today

- 1 Operation of Example Comparator Circuit
- 2 Regeneration Time Constant
- 3 Metastability, Probability of Error
- 4 Dynamic Offset
- 5 Other Comparator Circuits
- 6 A Bunch of Transconductor Circuits

ECE1371

8-45