

ECE1371 Advanced Analog Circuits

Lecture 10

ADVANCED $\Delta\Sigma$

Richard Schreier

`richard.schreier@analog.com`

Trevor Caldwell

`trevor.caldwell@utoronto.ca`

Course Goals

- **Deepen understanding of CMOS analog circuit design through a top-down study of a modern analog system— a delta-sigma ADC**
- **Develop circuit insight through brief peeks at some nifty little circuits**

The circuit world is filled with many little gems that every competent designer ought to know.

NLCOTD: High-Q Resonator

- Want $Q \gg \sqrt{3} \frac{f_0}{BW}$ for small SQNR degradation
- In a TV tuner ADC $f_0 = 44$ MHz and $BW = 8.5$ MHz, so we needed $Q \gg 9$
In actuality the requirement was $Q > 20$.
- How can Q be kept high despite finite amplifier gain and bandwidth?

ECE1371


10-3

Date	Lecture (M 13:00-15:00)		Ref	Homework	
2015-01-05	RS	1	MOD1 & MOD2	ST 2, 3, A	1: Matlab MOD1&2
2015-01-12	RS	2	MODN + $\Delta\Sigma$ Toolbox	ST 4, B	2: $\Delta\Sigma$ Toolbox
2015-01-19	RS	3	Example Design: Part 1	ST 9.1, CCJM 14	3: Sw.-level MOD2
2015-01-26	RS	4	Example Design: Part 2	CCJM 18	
2015-02-02	TC	5	SC Circuits	R 12, CCJM 14	4: SC circuit
2015-02-09	TC	6	Amplifier Design		
2015-02-16	Reading Week– No Lecture				
2015-02-23	TC	7	Amplifier Design		5: SC Int w/ Amp
2015-03-02	RS	8	Comparator & Flash ADC	CCJM 10	Project
2015-03-09	TC	9	Noise in SC Circuits	ST C	
2015-03-16	RS	10	Advanced $\Delta\Sigma$	ST 6.6, 9.4	
2015-03-23	TC	11	Matching & MM-Shaping	ST 6.3-6.5, +	
2015-03-30	TC	12	Pipeline and SAR ADCs	CCJM 15, 17	
2015-04-06	Exam		Proj. Report Due Friday April 10		
2015-04-13	Project Presentation				

ECE1371

10-4

Active-RC Resonator Structure

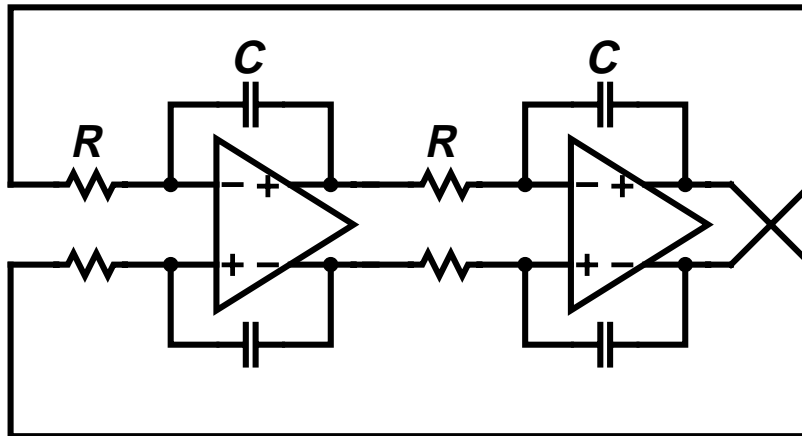

$$f_0 = \frac{1}{2\pi RC}$$

- **Frequency-tuning: adjust C until the desired resonant frequency is achieved**
 - No Q-tuning.
- **Amplifier drives both R and C \Rightarrow Q trouble?**

ECE1371

10-5


Highlights (i.e. What you will learn today)

- 1 **Feedback vs. Feedforward topology**
- 2 **State-space (ABCD) representation of the loop filter in the $\Delta\Sigma$ Toolbox**
- 3 **MASH Modulators**
- 4 **Continuous-Time Modulators**
- 5 **Bandpass and Quadrature Bandpass $\Delta\Sigma$**

ECE1371

10-6

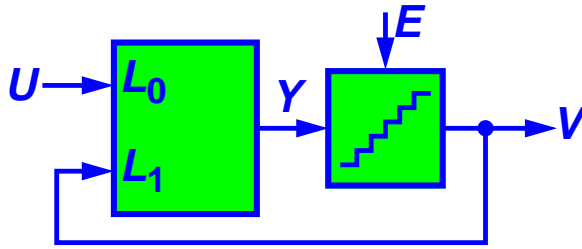Review: Generic Single-Loop $\Delta\Sigma$ ADC



$$\begin{aligned}
 Y &= L_0 U + L_1 V \\
 V &= Y + E
 \end{aligned}
 \Rightarrow V = STF \cdot U + NTF \cdot E, \text{ where}$$

$$NTF = \frac{1}{1 - L_1} \quad \& \quad STF = L_0 \cdot NTF$$

Inverse Relations:


$$L_1 = 1 - 1/NTF, \quad L_0 = STF / NTF$$

ECE1371

10-7

Review: $\Delta\Sigma$ Toolbox Model

Modulator:


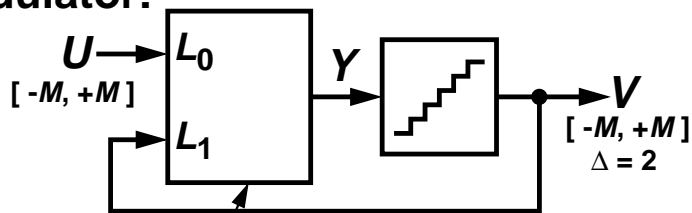


$$NTF = \frac{1}{1 - L_1}$$


$$STF = \frac{L_0}{1 - L_1}$$

Loop filter can be specified by NTF or by ABCD, a state-space representation

Quantizer:

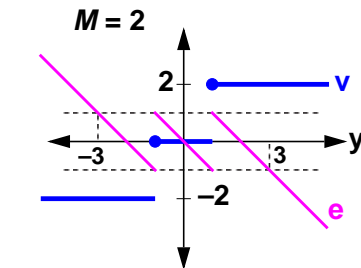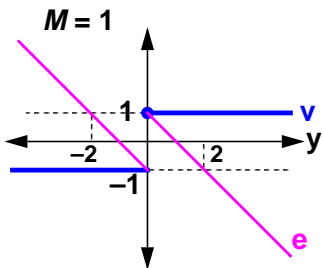

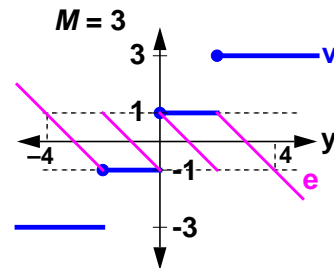Mid-tread quantizer;
v: even integers $[-M, +M]$




Mid-rise quantizer;
v: odd integers $[-M, +M]$

ECE1371

10-8

Feedback Topology

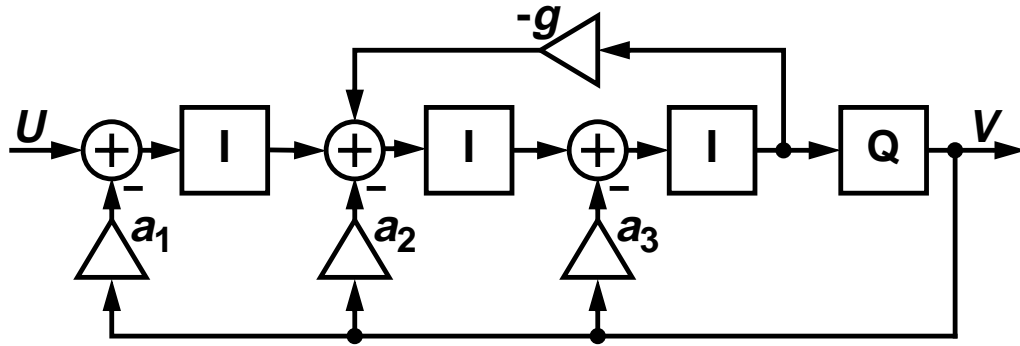


- N integrators precede the quantizer
- Feedback from the quantizer to the input of each integrator (via a DAC)
- Local feedback around pairs of integrators to set the NTF's zeros
- Multiple input feed-in branches are possible

ECE1371

10-9

Feedforward Topology

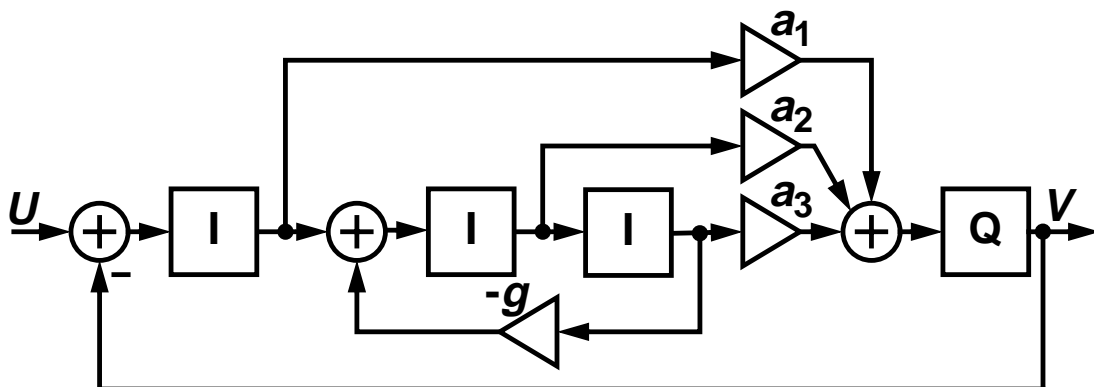


- N integrators in a row
- Each integrator output is fed forward to the quantizer
- Local feedback around pairs of integrators to control NTF zeros
- Multiple input feed-in branches also possible

ECE1371

10-10

Feedback vs. Feedforward STF

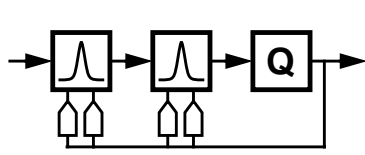


$$L_0(z) = \frac{N_0(z)}{D(z)} \quad L_1(z) = \frac{N_1(z)}{D(z)}$$

$$NTF(z) = \frac{1}{1 - L_1(z)} = \frac{D(z)}{N_1(z) - D(z)}$$

poles of LF are zeros of NTF

$$STF(z) = \frac{L_0(z)}{1 - L_1(z)} = \frac{N_0(z)}{N_1(z) - D(z)}$$

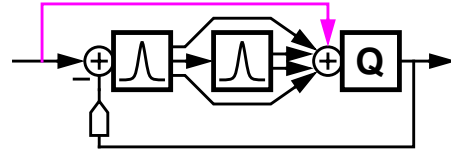
same poles as NTF
zeros = zeros of L_0
STF often has no zeros, only poles.



$$L_0(z) = -L_1(z) = L(z)$$

$$NTF(z) = \frac{1}{1 - L_1(z)} = \frac{1}{1 + L(z)}$$

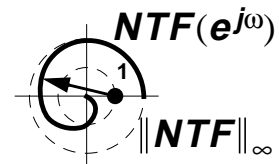
$$STF(z) = \frac{L(z)}{1 + L(z)} = 1 - NTF(z)$$



$$\|STF\|_{\infty} \approx \|NTF\|_{\infty} + 1$$

With extra feed-in to Q, $STF(z) = 1$.

STF Comparison 5th-Order; Single Feed-In

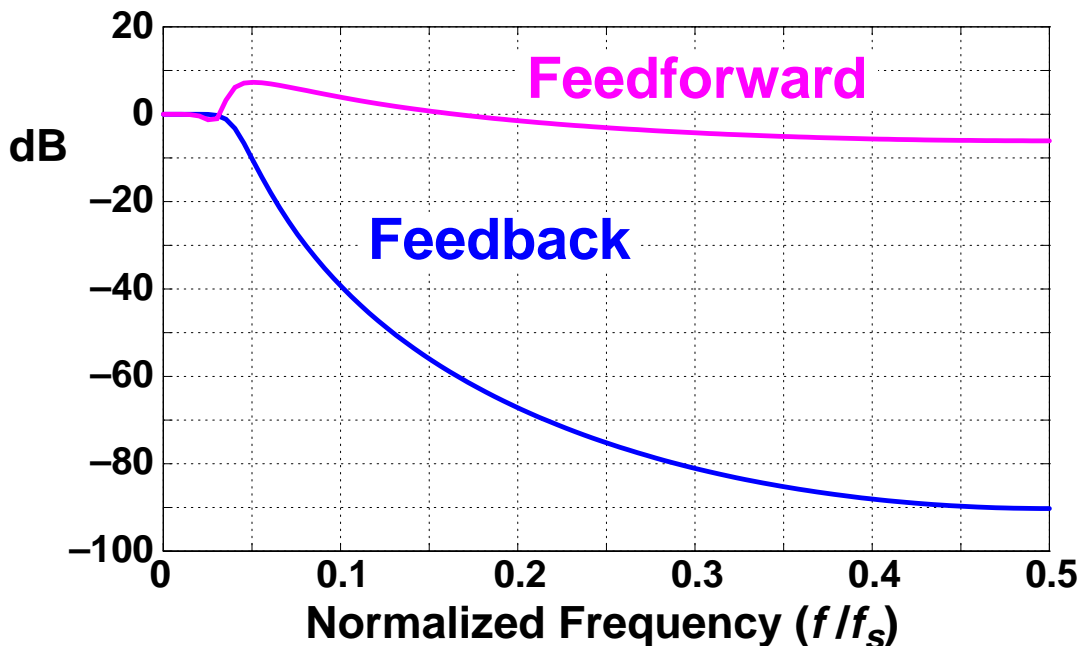


Feedforward vs. Feedback

- FF has relaxed dynamic range requirements
 “All stages except the last have attenuated signal components.”
- FB has better STF and, for CT modulators, a better AAF
 In a discrete-time modulator, the STF of FF can be made unity by adding a signal feedforward term to the input of the quantizer.
- FB needs many DACs;
 FF needs a summation block
 Can do partial summation before the last integrator.
- FF with signal to quantizer: timing can be tricky
 Need to quantize u and feed it back in zero time.

ECE1371

10-13


ABCD: A *State-Space* Representation of the Loop Filter

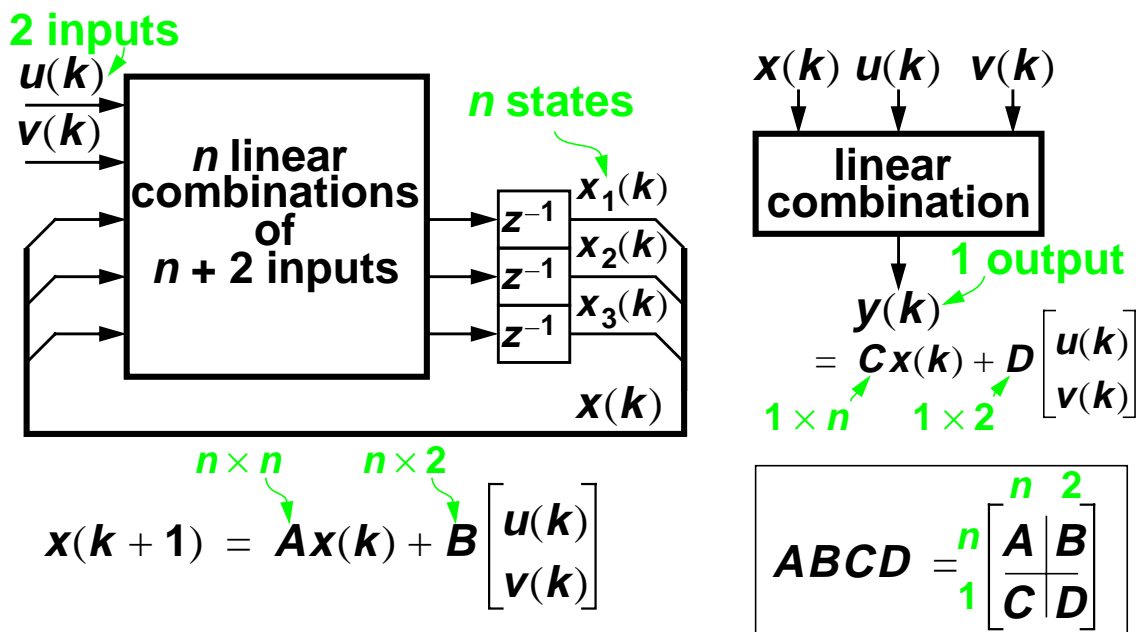

ECE1371

10-14


Ex.: Cascade of Integrators Feedback (CIFB) Topology

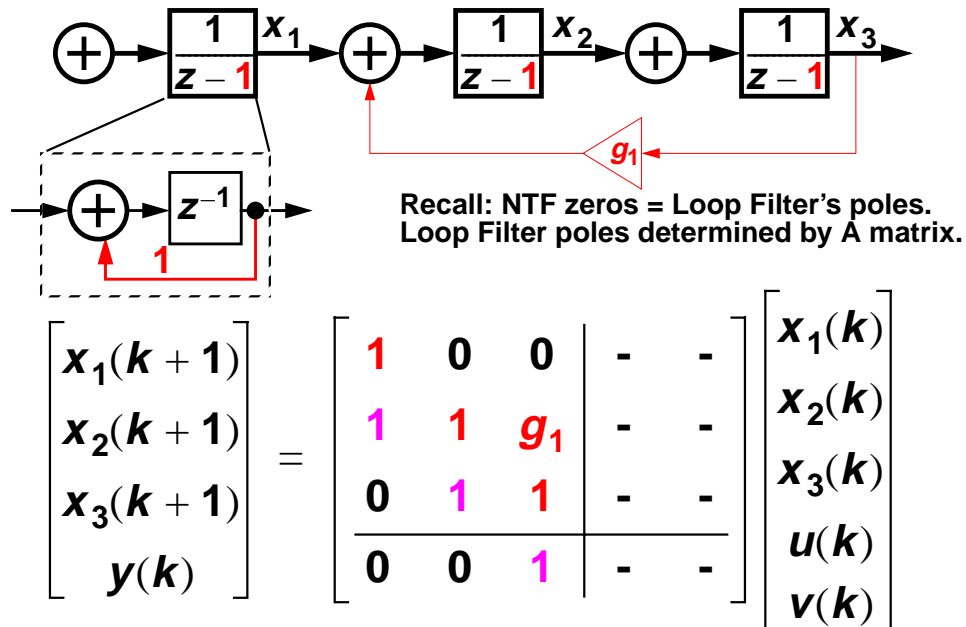

ECE1371

10-15


CIFB cont'd: a_i Control NTF & STF Poles

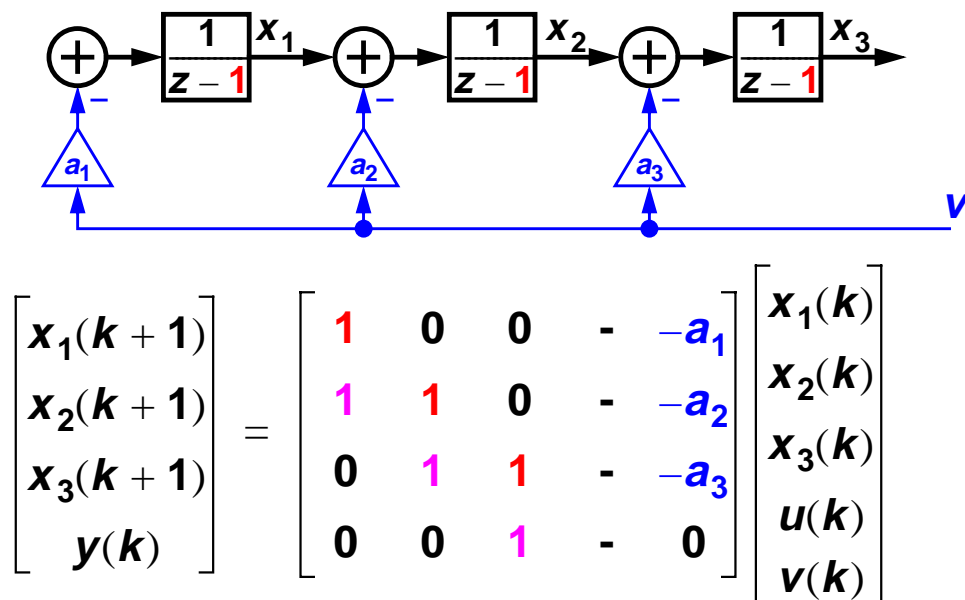

ECE1371

10-16

b_i Control STF Zeros

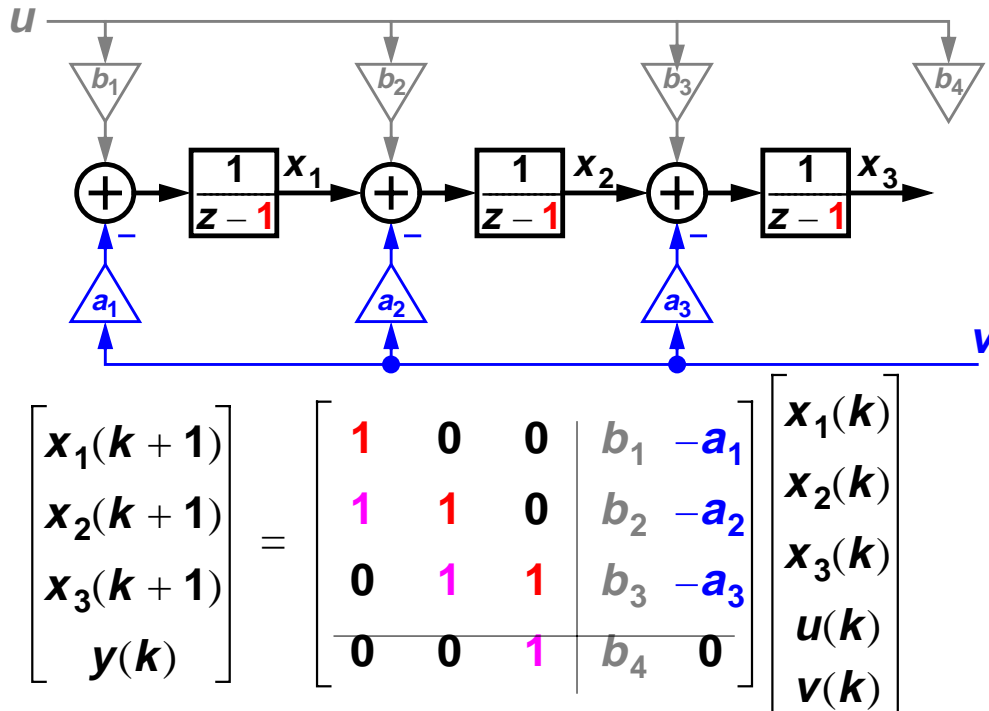

ECE1371

10-17

ABCD and the Toolbox


- `simulateDSM` simulates a modulator given an ABCD description of its loop filter
- `realizeNTF` gives (unscaled) coefficients for any of the supported topologies
- `stuffABCD` produces an ABCD matrix given the coefficients for one of the supported topologies
`mapABCD` performs the inverse operation.
- `scaleABCD` does dynamic range scaling on any ABCD matrix
- `calculateTF` calculates the NTF and STF from ABCD
 Useful for checking implementation of new topologies.

ECE1371

10-18

Cascade (MASH) Modulators

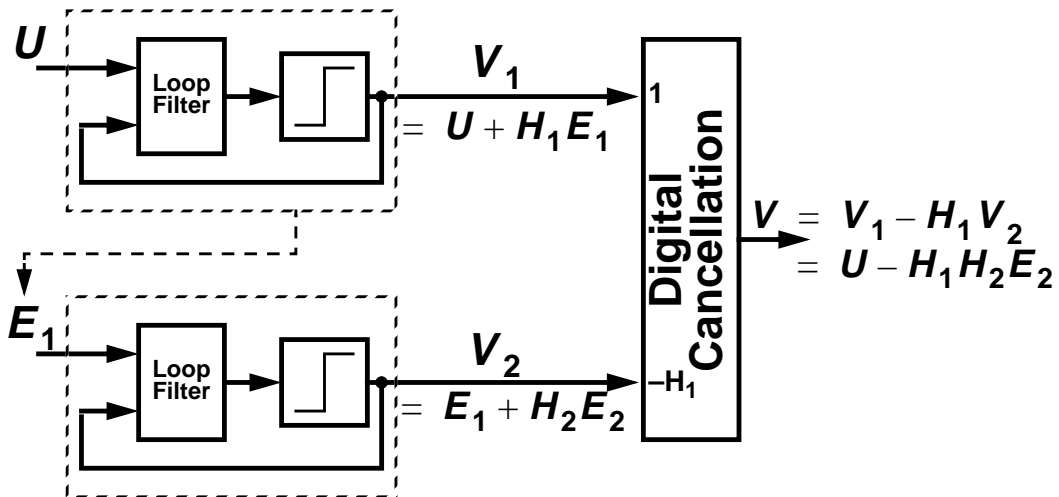- Put two (or more) modulators in “series”




- The resulting NTF is the *product* of the individual NTFs

ECE1371

10-19

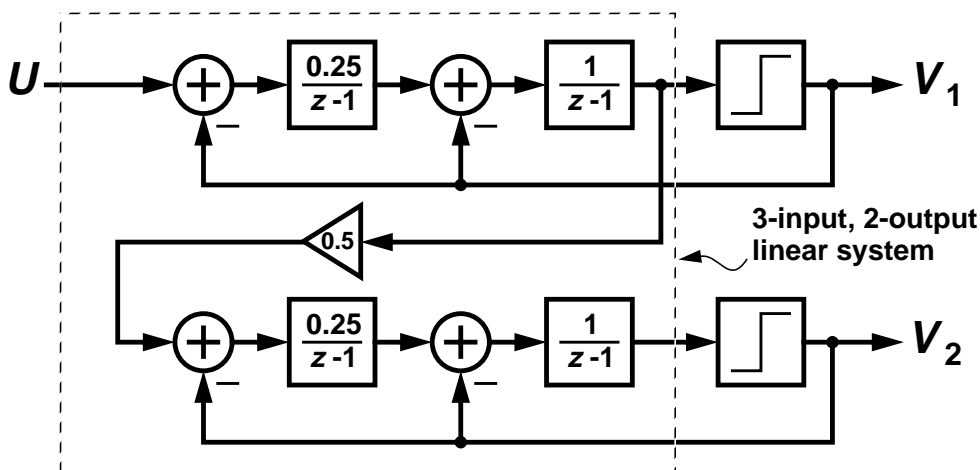Example: 2-2 Cascade

- Use Two MOD2b: $H(z) = \left(\frac{z-1}{z-0.5}\right)^2$




$$\left(V = \frac{1}{z^3} V_1 + \frac{8(z-1)^2(z-0.5)^2}{z^3(z-0.75)} V_2 \right) \Rightarrow \left(H(z) = \frac{8(z-1)^4}{(z-0.75)} \right)$$

ECE1371

10-20


Example MASH Spectra

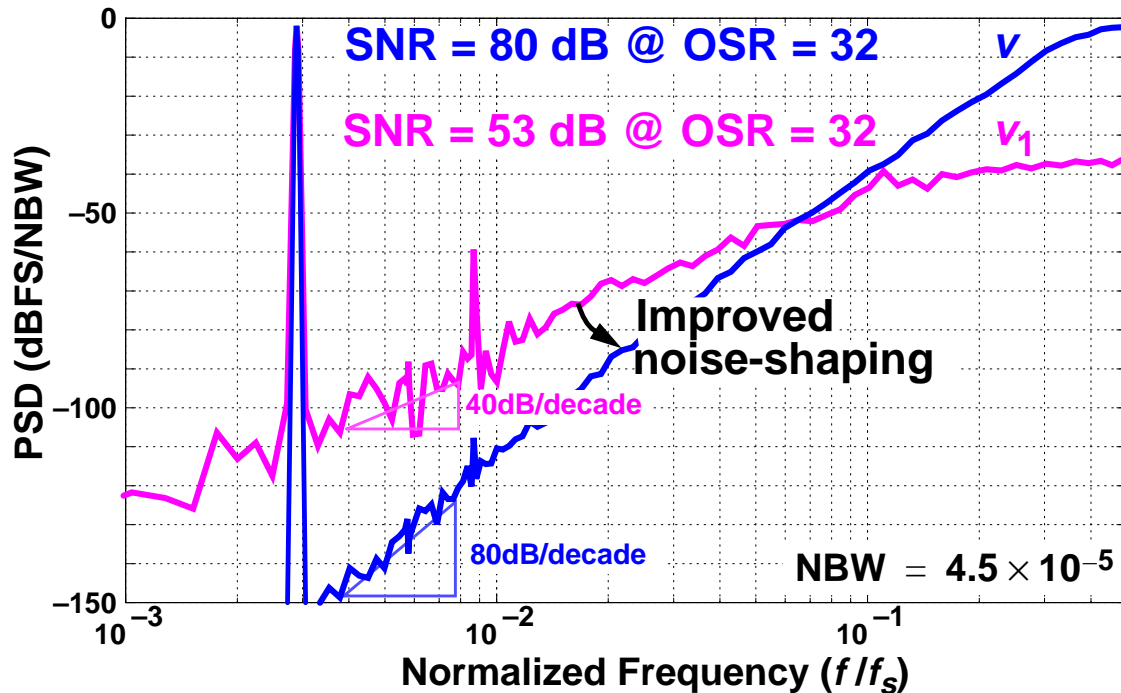

ECE1371

10-21

A Continuous-Time $\Delta\Sigma$ ADC

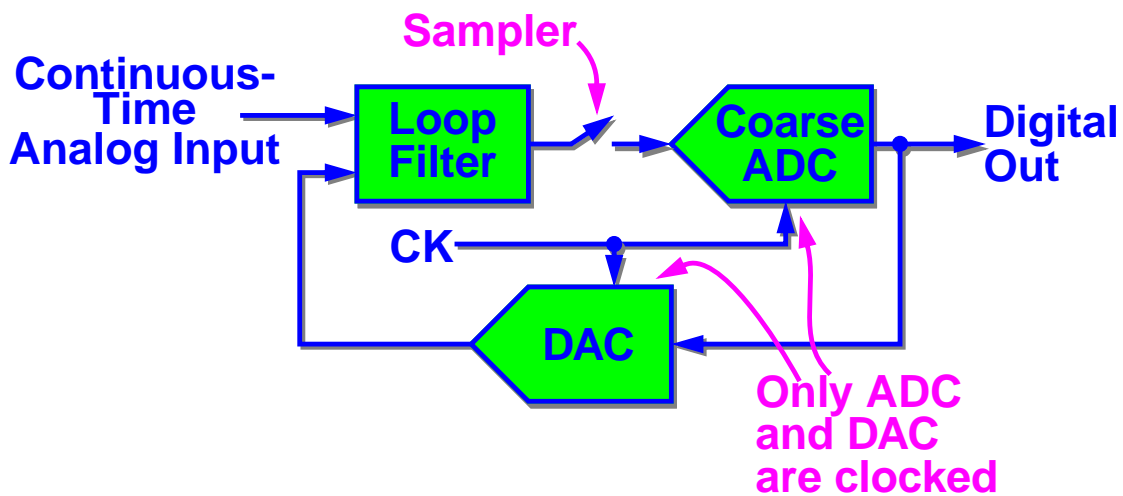


- Loop filter implemented with continuous-time circuitry
- Sampling occurs after the loop filter

ECE1371


10-22

Example: MOD1-CT

Block Diagram

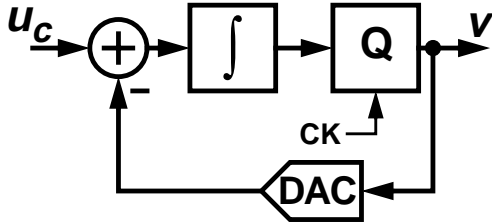


Schematic

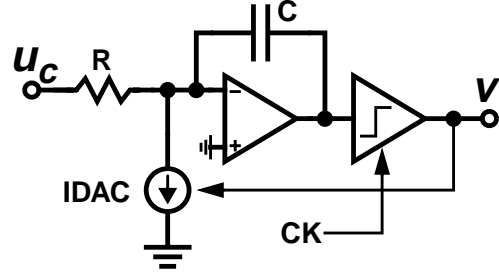


- **Note: Input is a simple resistor, *not* a switched capacitor**
CT ADCs are easier to drive than DT ADCs.

Inherent Anti-Aliasing

- $\Delta\Sigma$ ADC with CT Loop Filter

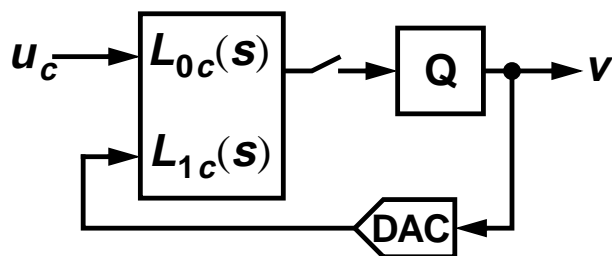


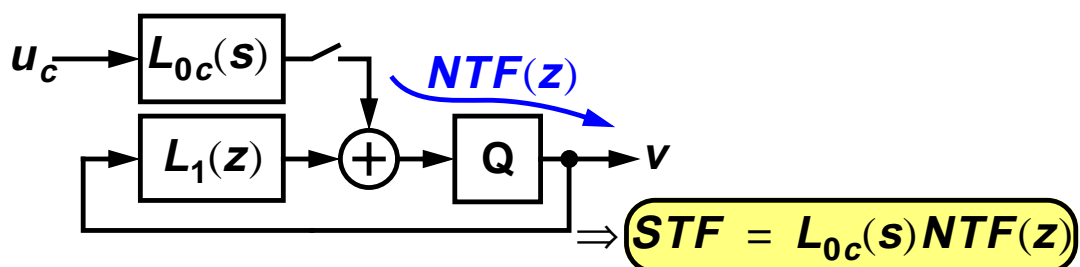- Equivalent system with DT feedback path




Example: MOD1-CT STF = $\frac{1-z^{-1}}{s}$

Recall $z = e^s$

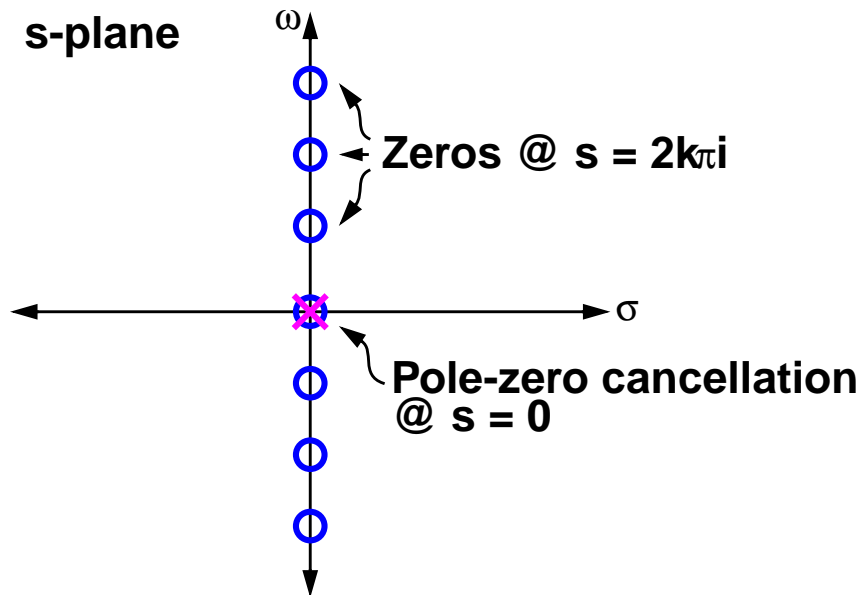

MOD1-CT Frequency Responses

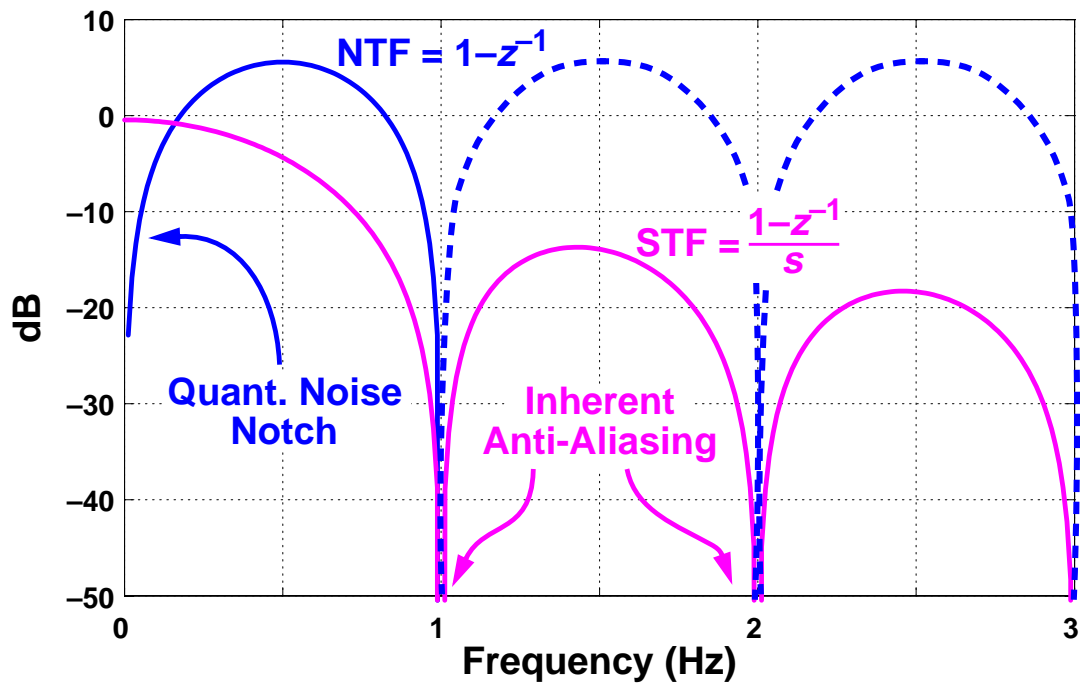

Inherent AAF Summary

$$STF = L_{0c}(s)NTF(z)$$

- STF contains the zeros of the NTF
- Any frequency which aliases to the passband is attenuated by at least as much as the quantization noise
 - Anti-alias performance tracks modulator order.
 - Also true for MASH systems.


- The effective anti-alias filter is

$$AAF(f) = \frac{STF(f)}{STF(f_{alias})} = \frac{L_{0c}(f)}{L_{0c}(f_{alias})}$$

ECE1371

10-27

Effect of Quantizer/DAC Delay

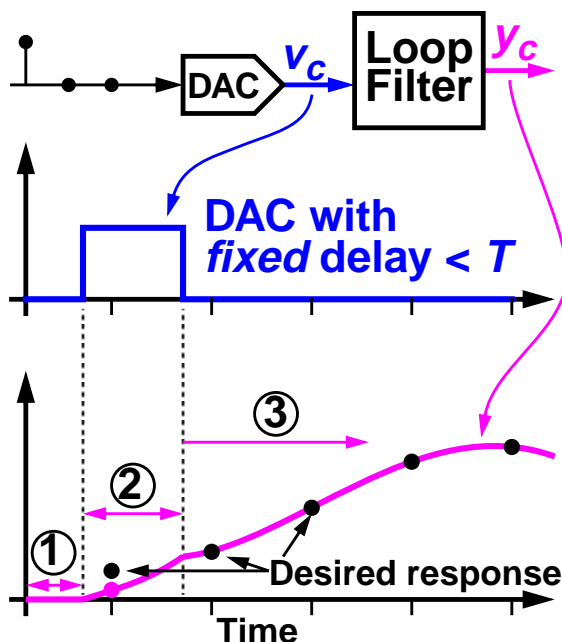


- 1 Loop outputs zero until DAC pulse begins
 - 2 Loop responds as if input were a step
 - 3 Loop follows trajectory of an n^{th} -order linear system with zero input but non-zero initial conditions
- ⇒ At best, samples of the pulse response will match the desired impulse response except at the first point.
The NTF will be wrong.

ECE1371

10-28

Compensating for Feedback Delay

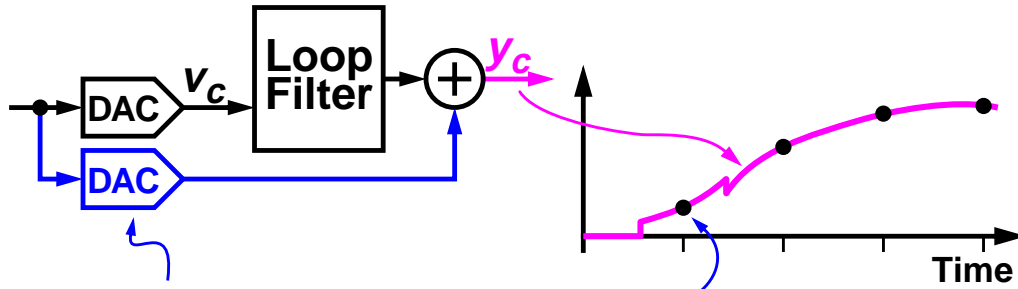- To fix the first sample, add a *direct feedback* DAC




Direct Feedback DAC corrects the first sample

- With enough DACs, one for each errant sample, any finite number of points can be repaired

In principle, the delay of the main feedback path can be anything, but the system becomes sensitive to coefficient errors.

DT $\Delta\Sigma$ vs. CT $\Delta\Sigma$

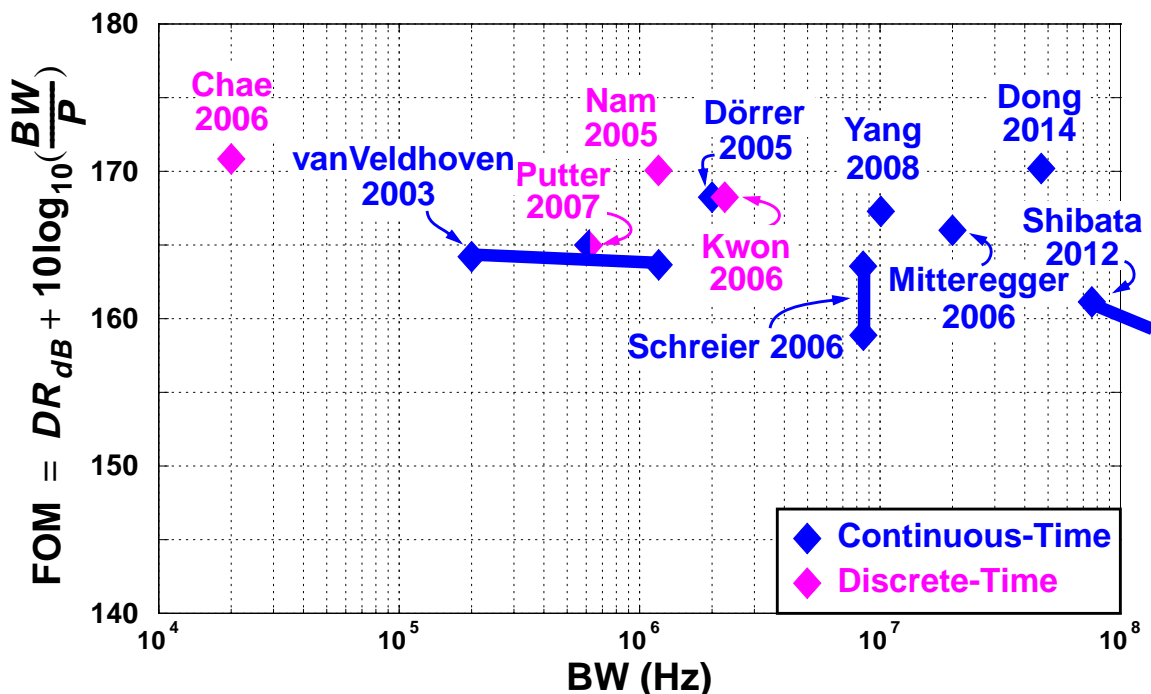

References— DT vs. CT

BW (Hz)	DR (dB)	P (mW)	FOM	Reference	Architecture <i>N</i> =order (<i>M</i> =#steps)
20k	85	0.036	172	Chae, ISSCC 2008:27.2	$\Delta\Sigma$ SC 3(1)
614k	82	3.1	165	Putter, ISSCC 2007:13.4	$\Delta\Sigma$ A-RC+SC 6(1)
1.2M	82	8	164	vanVeldhoven, ISSCC 2003:3.4	$Q\Delta\Sigma$ gm-C 5(1)
1.2M	96	44	171	Nam, JSSC 2005-09	$\Delta\Sigma$ SC 2(32)-2(8)
2M	80	3.0	168	Dörrer, ISSCC 2005:27.1	$\Delta\Sigma$ A-RC 3(15)
2.2M	86	14	168	Kwon, ISSCC 2006:3.4	$\Delta\Sigma$ SC 2(4)
8.5M	88	375	162	Schreier, ISSCC 2006:3.2	$QB\Delta\Sigma$ A-RC 4(16)
10M	87	100	167	Yang, ISSCC 2008:27.6	$\Delta\Sigma$ A-RC 5(7)
20M	76	20	166	Mitteregger, ISSCC 2006:3.1	$\Delta\Sigma$ A-RC 3(15)
53M	88	235	172	Dong, JSSC 2014-12	$\Delta\Sigma$ A-RC 0(16)-3(16)
75M	80	550	161	Shibata, JSSC 2012-12	$BP\Delta\Sigma$ LC/A-RC 6(16)


Advantages of Discrete-Time

- 1 Less sensitive to jitter
- 2 Accurate transfer functions regardless of f_{CK}
- 3 FF topology with no STF-peaking is possible
- 4 DAC dynamics are non-critical
- 5 Math is simpler

Advantages of Continuous-Time

- 1 Higher speed
- 2 Inherent anti-aliasing
- 3 Easier to drive (well-defined Z_{in})
- 4 Sampling is non-critical
- 5 Lower power (?)

A Bandpass $\Delta\Sigma$ ADC System

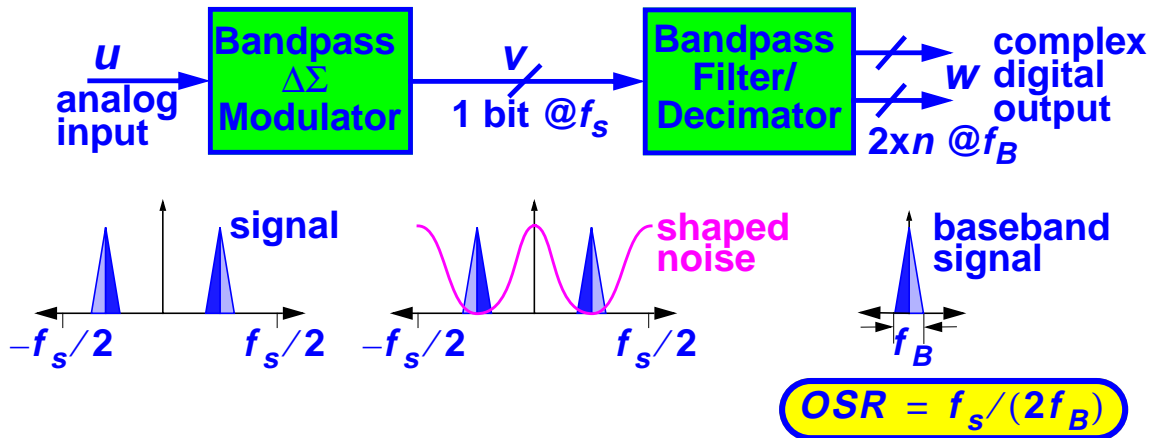


- ADC converts its analog input into a noise-shaped digital output
- DSP removes out-of-band noise (and signals) and translates the signal to baseband

ECE1371

10-33

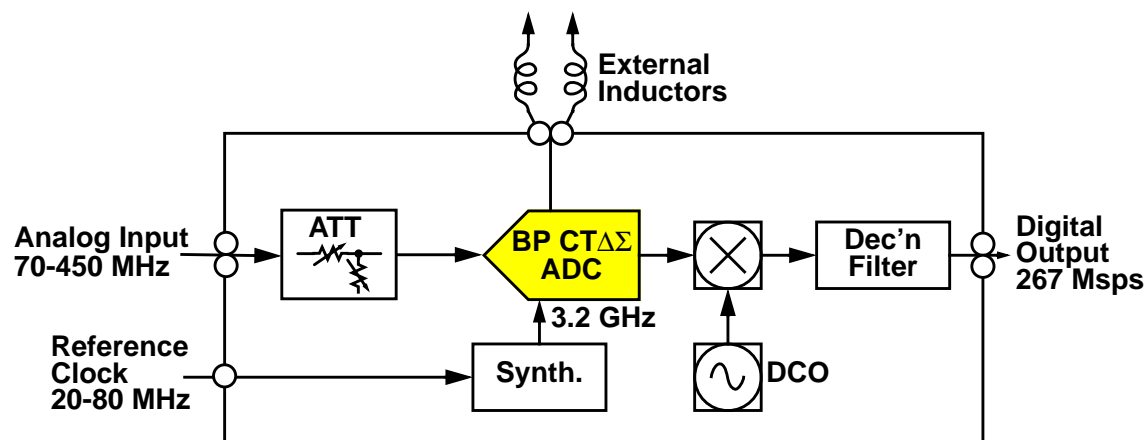Example CT Bandpass $\Delta\Sigma$ ADC: The AD6676 [Shibata 2012]



- IF subsystem containing attenuator, synthesizer, CT BP $\Delta\Sigma$ ADC and digital filter

ECE1371

10-34


AD6676 Specs

Parameter	Value	Notes
Z_{in}	50 Ω	
ADC FS	-16 to -4 dBm	
Attenuation	0 to +27 dB	
NSD	< -157 dBFS/Hz	BW = 75 MHz; 12-dB att.
IF	70-450 MHz	
BW	up to 100 MHz	<3-dB NSD degradation
F_{ck}	2-3.2 GHz	
Power	1.25 W	Includes digital filter & JESD204B interface

ECE1371

10-35

ADC Schematic

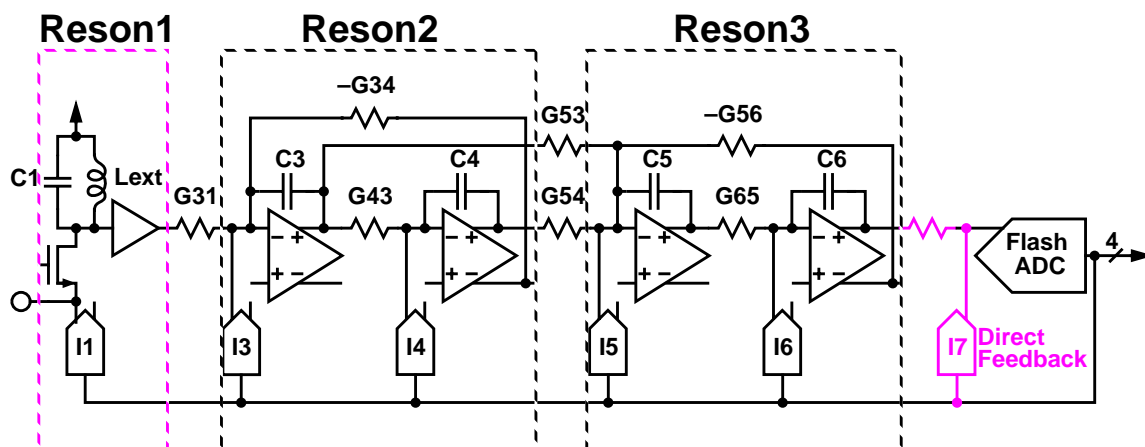


- **6th-order FB-style loop filter**
One LC resonator plus two active-RC resonators.
G53 makes up for missing DAC2.
- **16-step quantization, [1 2] DAC timing**

ECE1371

10-36

Programmable Everything

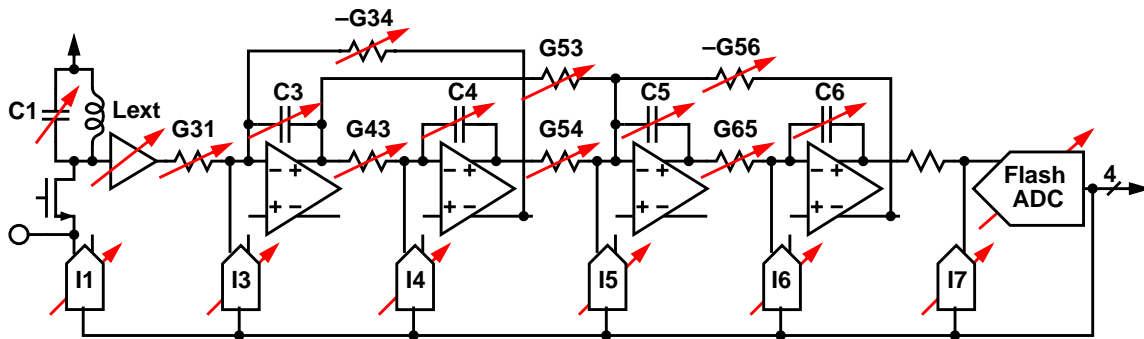


- **Feedback currents, integrating capacitors, inter-stage conductances, flash LSB**
The inductors were also selectable via the cascode (2 choices).

ECE1371

10-37

Attenuator Schematic

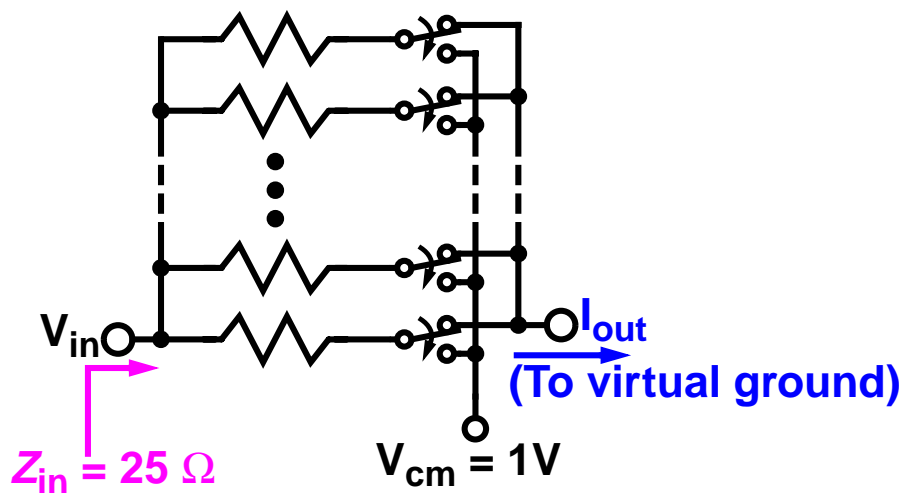


- **Resistors switched between virtual ground provided by cascode and V_{cm}**
Maintains matching independent of attenuation.

ECE1371

10-38

Feed-Forward Amplifier Concept

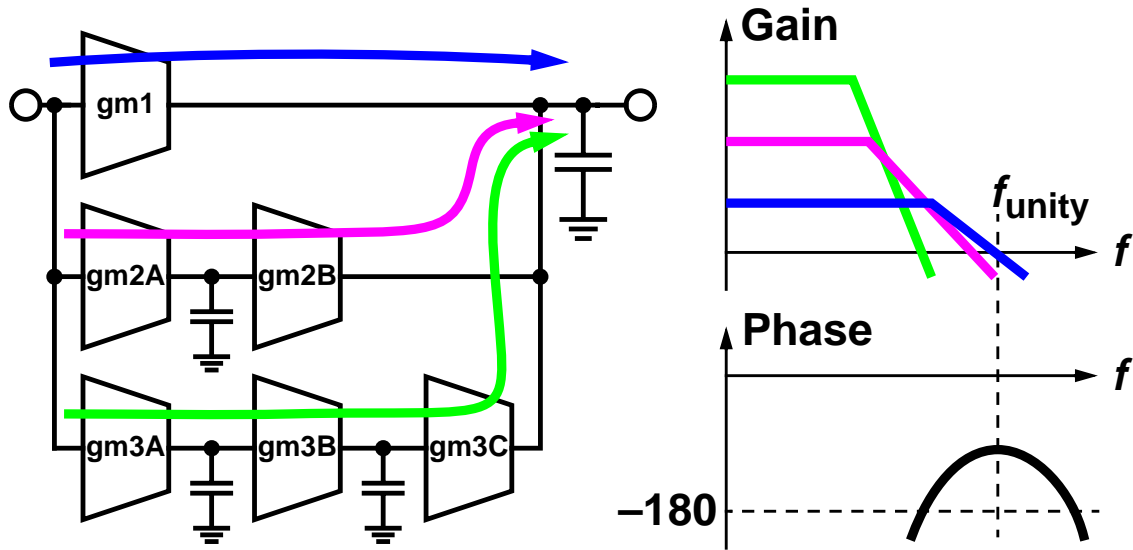


- High gain provided by longest path
- Stability by shorter, higher-bandwidth paths

ECE1371

10-39

FF Amp— Stage-Sharing


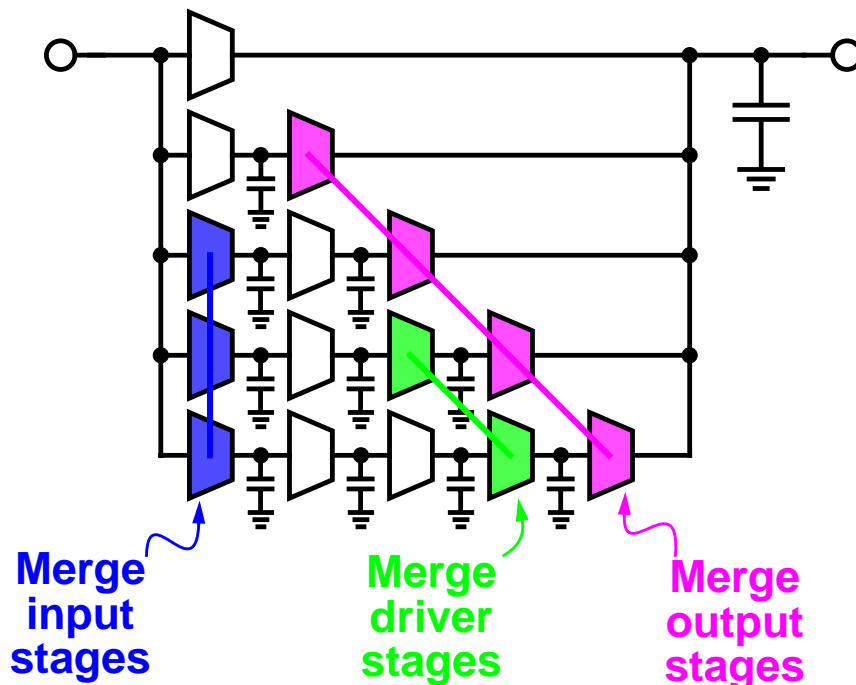


ECE1371


10-40

FF Amp— A1 Architecture

Built up by adding L-sections:

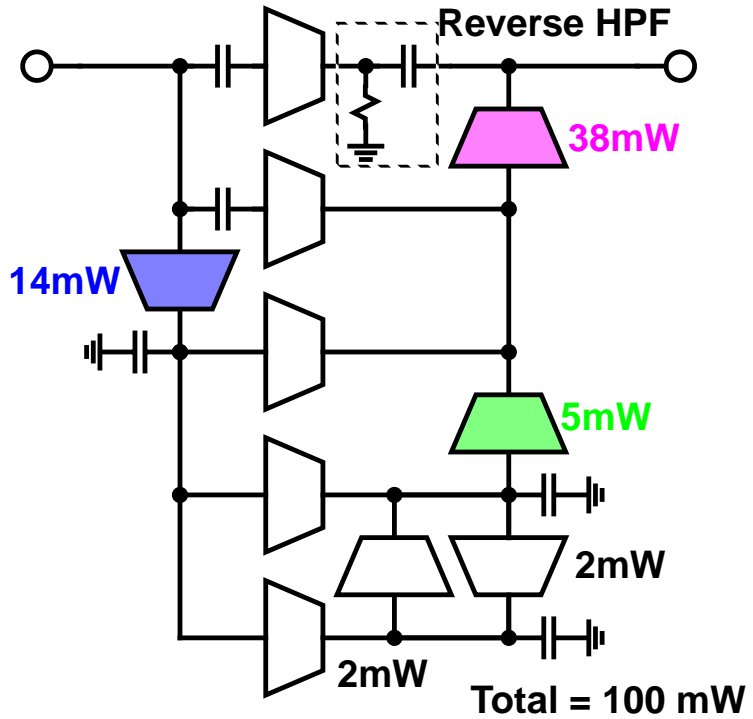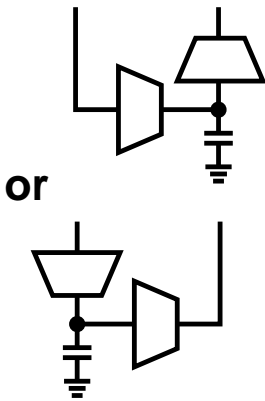


$F_0 = 150\text{-}400\text{ MHz}; F_s = 3\text{ GHz}$

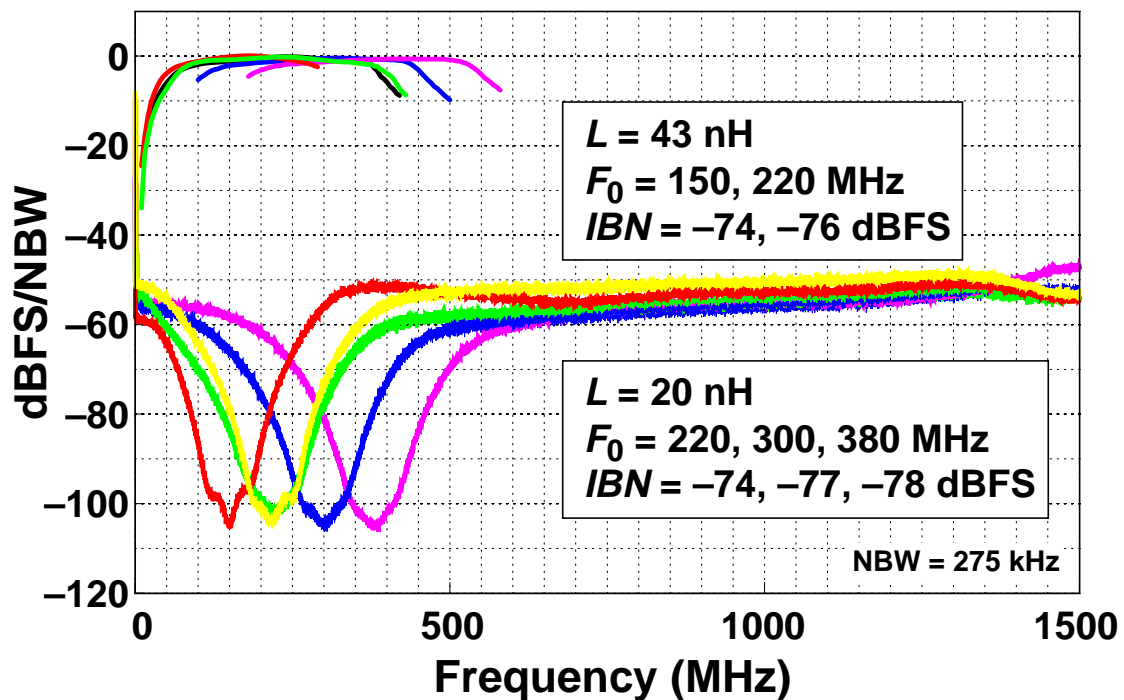


Example In-Band Spectrum

IF = 400 MHz, BW = 75 MHz

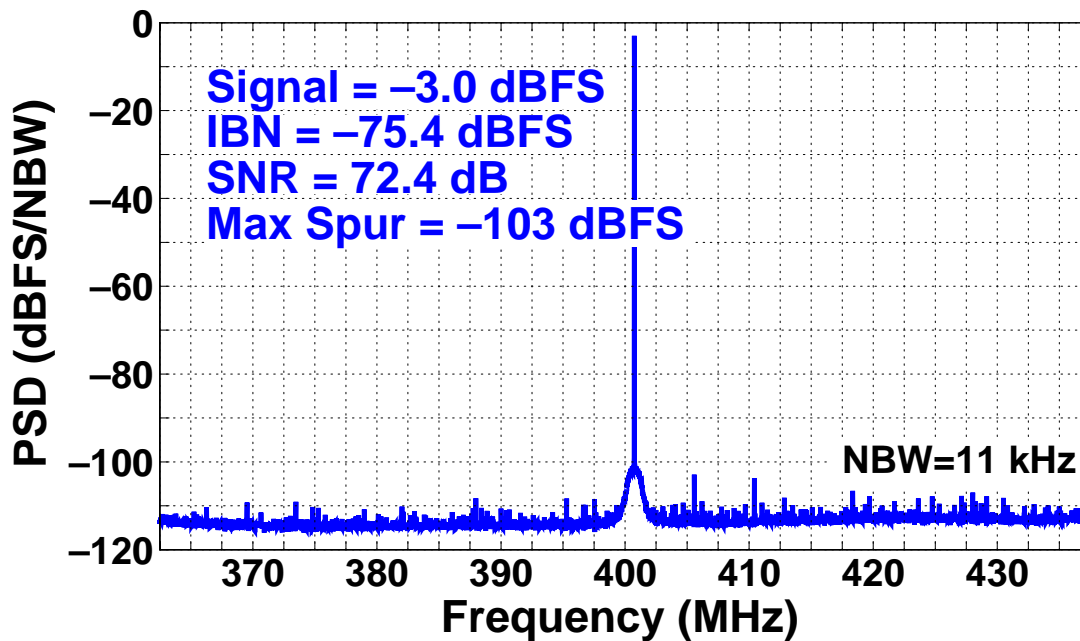


A Quadrature $\Delta\Sigma$ ADC System

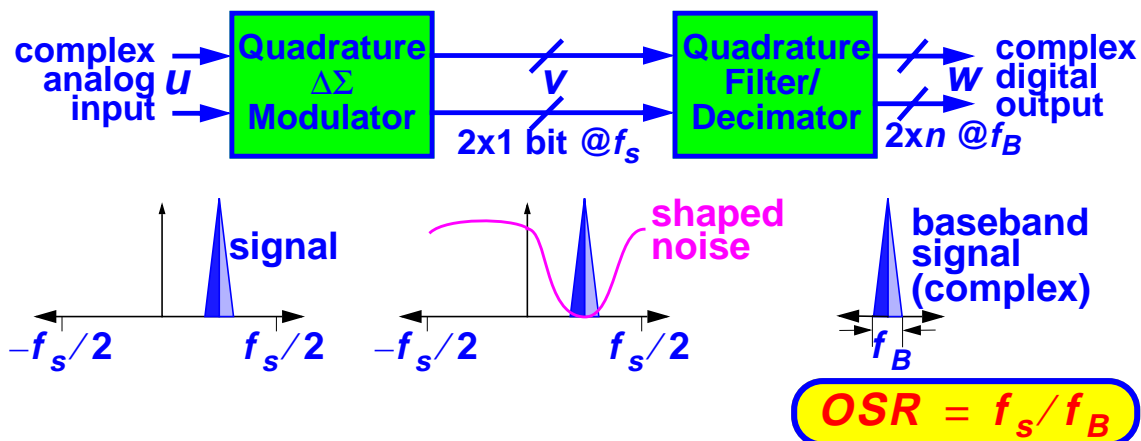

- Modulator converts its quadrature analog input into a pair of bit-stream outputs
- DSP removes out-of-band noise and translates the signal to baseband

A Quadrature $\Delta\Sigma$ Modulator

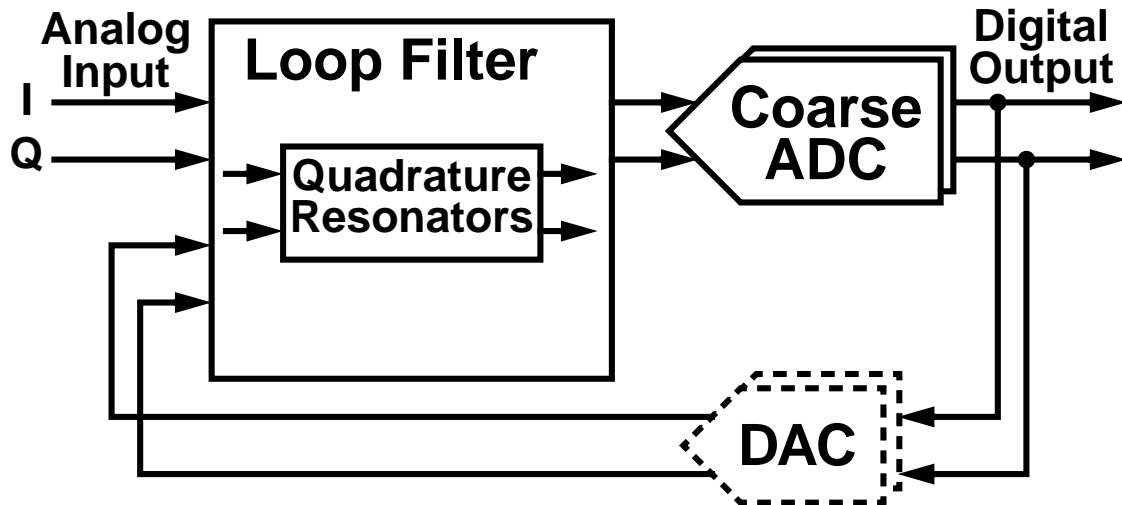


- A $\Delta\Sigma$ ADC with quadrature everything
NTF and STF are complex.

ECE1371

10-45

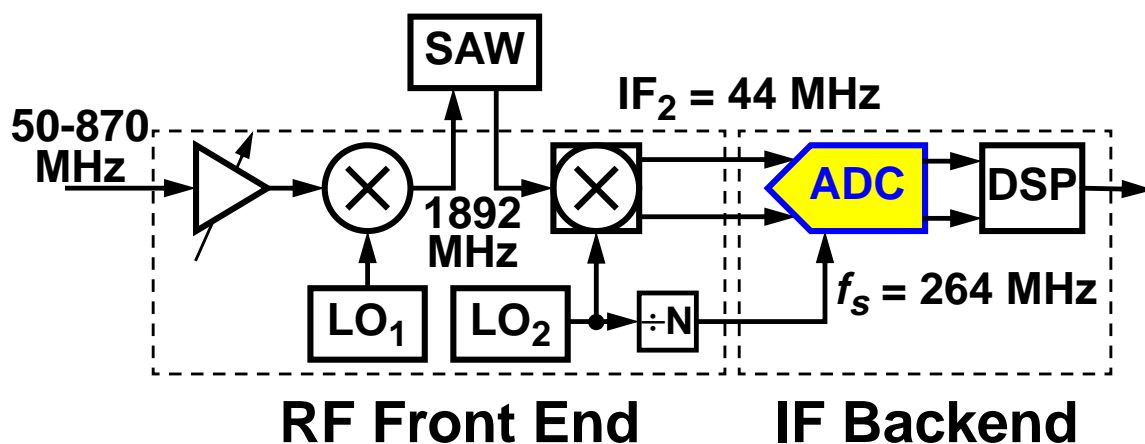Example: A Quadrature $\Delta\Sigma$ ADC for a TV Tuner System




- Dual-conversion super-heterodyne receiver containing a quadrature bandpass $\Delta\Sigma$ ADC

ECE1371


10-46

ADC Architecture

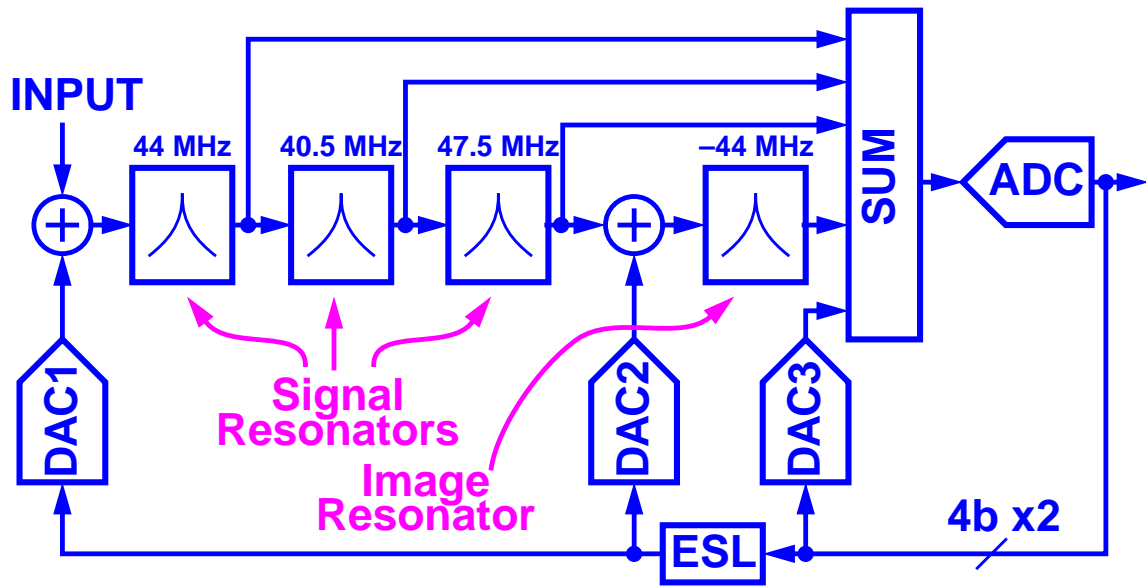


- $(3+1)^{\text{th}}$ -order, 4-b, feedforward A-RC modulator


Quadrature ADC Front-End

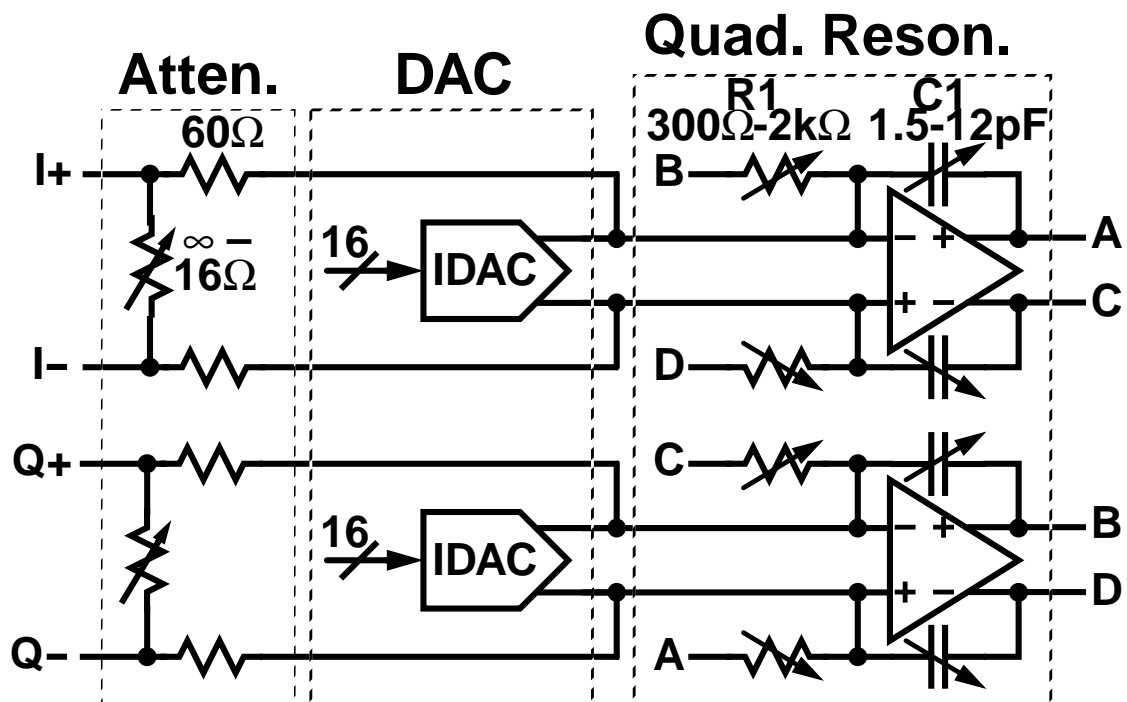

STF & NTF

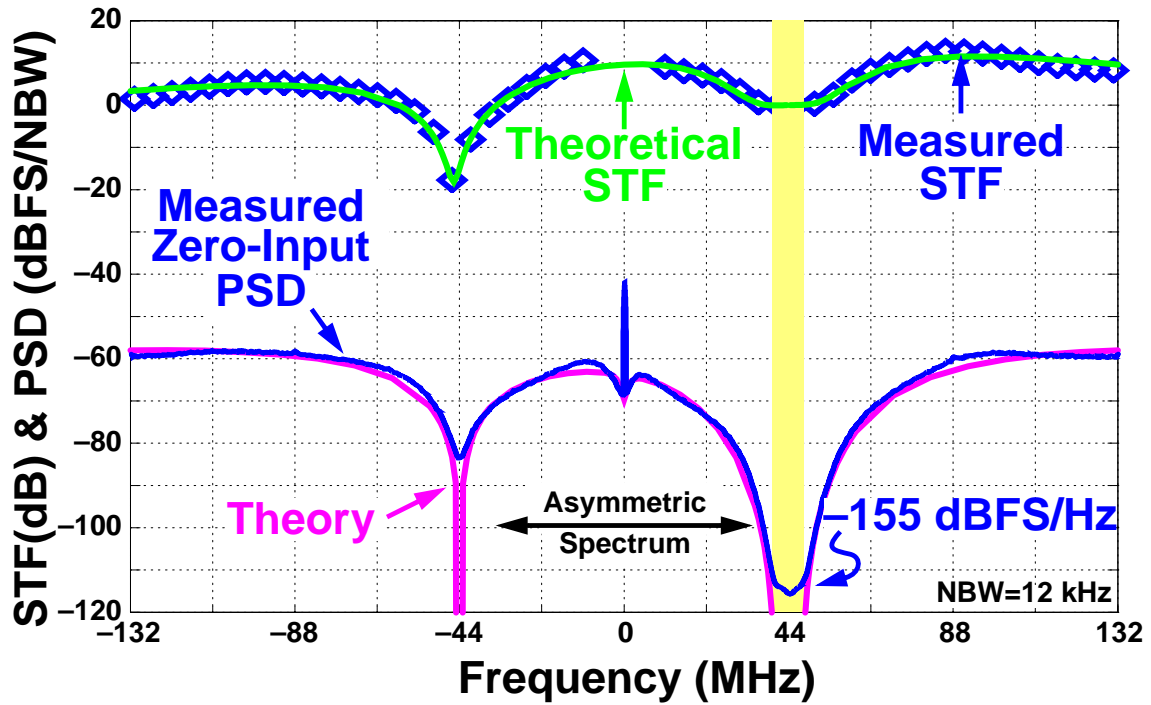

FOM Comparison

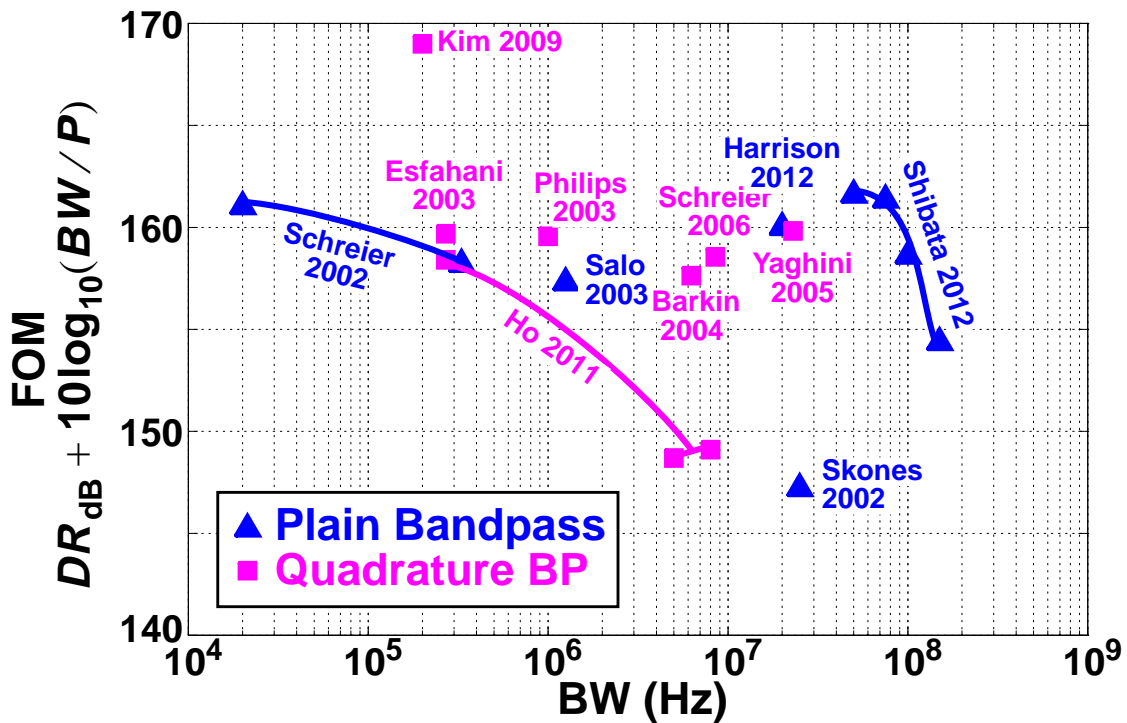

NLCOTD: High-Q Resonator

- Want $Q \gg \sqrt{3} \frac{f_0}{BW}$ for small SQNR degradation
- In a TV tuner ADC $f_0 = 44$ MHz and $BW = 8.5$ MHz, so we needed $Q \gg 9$


Actual requirement was $Q > 20$.

How can Q be kept high despite finite amplifier gain and bandwidth?

ECE1371

10-51

Active-RC Resonator Structure

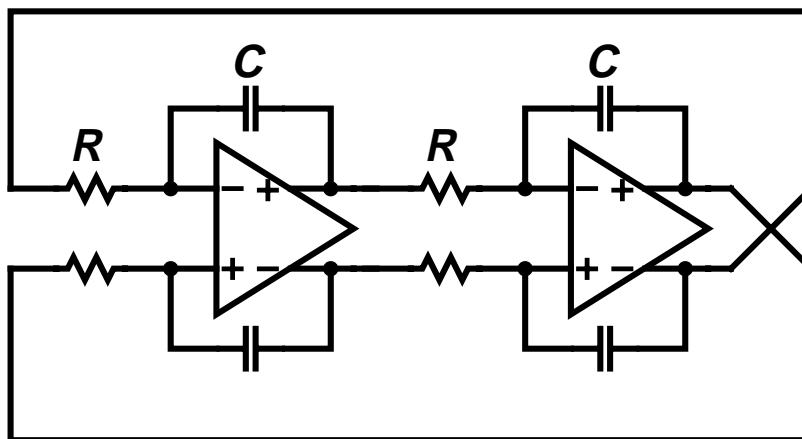

$$f_0 = \frac{1}{2\pi RC}$$


- Tuned by adding positive feedback to make an oscillator and adjusting C until the desired resonance is achieved
- Amplifier drives both R and $C \Rightarrow$ trouble?

ECE1371

10-52

Amplifier Gain and Phase


- Finite gain degrades Q
- Phase lag enhances Q
- Analysis shows $\phi = 45^\circ$ yields high Q , regardless of amplifier gain

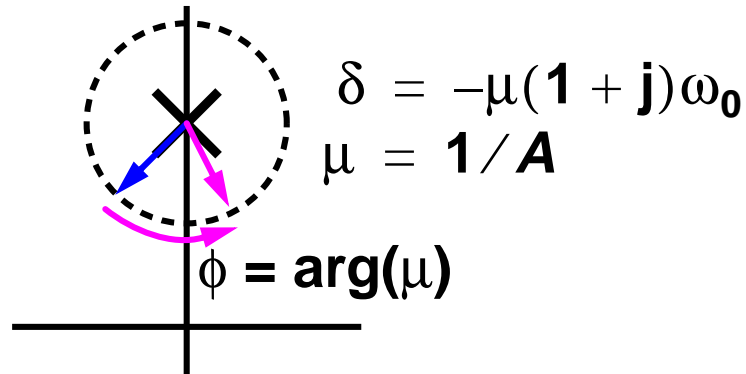

ECE1371

10-53


An Amplifier with $\phi = 45^\circ$ @ f_0 :

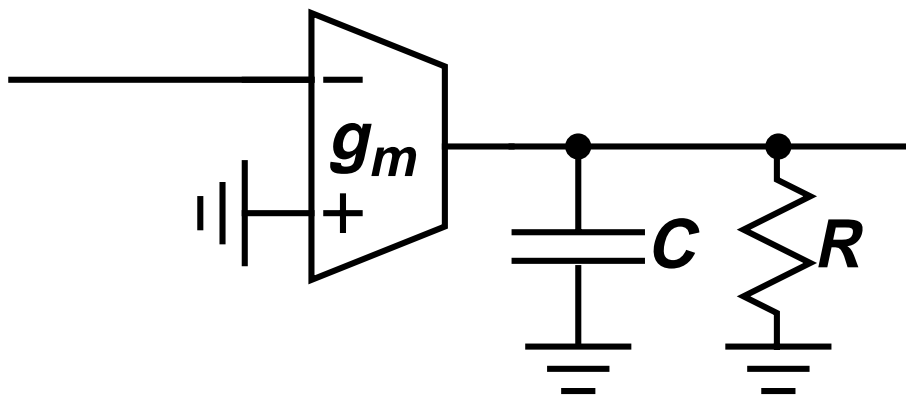

ECE1371

10-54

Resulting High-Q Resonator

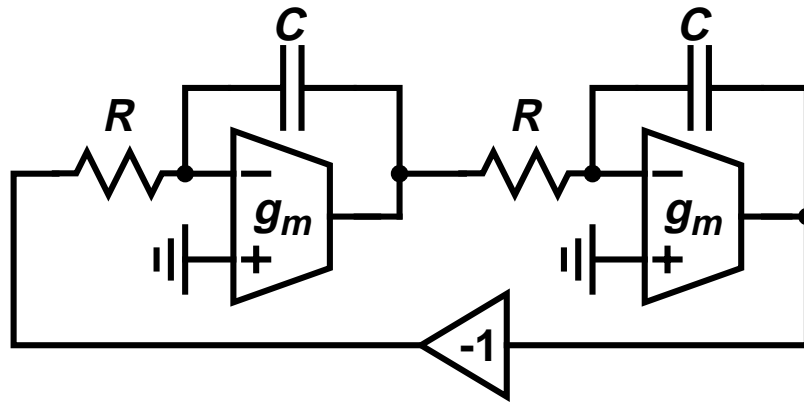


- Amplifier load yields $\phi = 45^\circ @ f_0$
- Finite g_m shifts the pole frequency, but does not degrade Q!

ECE1371

10-55

Measured STF in an Alias Band

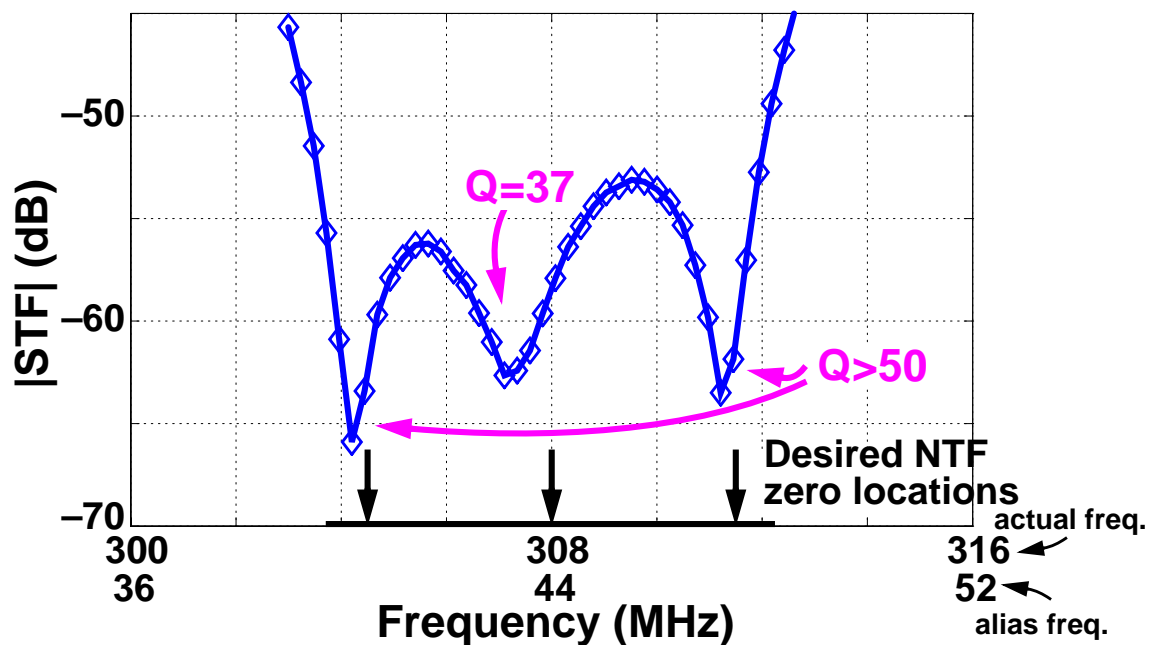

- Resonator Q is well above the design target!

ECE1371

10-56

What You Learned Today

- 1 **Feedback vs. Feedforward topology**
- 2 **State-space (ABCD) representation of the loop filter in the $\Delta\Sigma$ Toolbox**
- 3 **MASH Modulators**
- 4 **Continuous-Time Modulators**
- 5 **Bandpass and Quadrature Bandpass $\Delta\Sigma$**