

# **ECE1371 Advanced Analog Circuits**

## **Lecture 4**

# **EXAMPLE DESIGN– PART 2**

**Richard Schreier**

**`richard.schreier@analog.com`**

**Trevor Caldwell**

**`trevor.caldwell@utoronto.ca`**


# Course Goals

- **Deepen understanding of CMOS analog circuit design through a top-down study of a modern analog system— a delta-sigma ADC**
- **Develop circuit insight through brief peeks at some nifty little circuits**
  - The circuit world is filled with many little gems that every competent designer ought to know.**

Date	Lecture (M 13:00-15:00)			Ref	Homework
2015-01-05	RS	1	MOD1 & MOD2	ST 2, 3, A	1: Matlab MOD1&2
2015-01-12	RS	2	MODN + $\Delta\Sigma$ Toolbox	ST 4, B	2: $\Delta\Sigma$ Toolbox
2015-01-19	RS	3	Example Design: Part 1	ST 9.1, CCJM 14	3: Sw.-level MOD2
2015-01-26	RS	4	Example Design: Part 2	CCJM 18	
2015-02-02	TC	5	SC Circuits	R 12, CCJM 14	4: SC Integrator
2015-02-09	TC	6	Amplifier Design		
2015-02-16	Reading Week– No Lecture				
2015-02-23	TC	7	Amplifier Design		5: SC Int w/ Amp
2015-03-02	RS	8	Comparator & Flash ADC	CCJM 10	Project
2015-03-09	TC	9	Noise in SC Circuits	ST C	
2015-03-16	RS	10	Advanced $\Delta\Sigma$	ST 6.6, 9.4	
2015-03-23	TC	11	Matching & MM-Shaping	ST 6.3-6.5, +	
2015-03-30	TC	12	Pipeline and SAR ADCs	CCJM 15, 17	
2015-04-06	Exam			Proj. Report Due Friday April 10	
2015-04-13	Project Presentation				
 
# NLCOTD: Non-Overlapping Clock Generator

- Our SC circuits require two non-overlapping clocks. How do we generate them?




# **Highlights**

**(i.e. What you will learn today)**


- 1 Transistor-level implementation of MOD2  
op-amp, SC CMFB, comparator, clock generator**
- 2 MOD2 variants**
- 3 Variable quantizer gain**

# Review: MOD2


## Standard Block Diagram

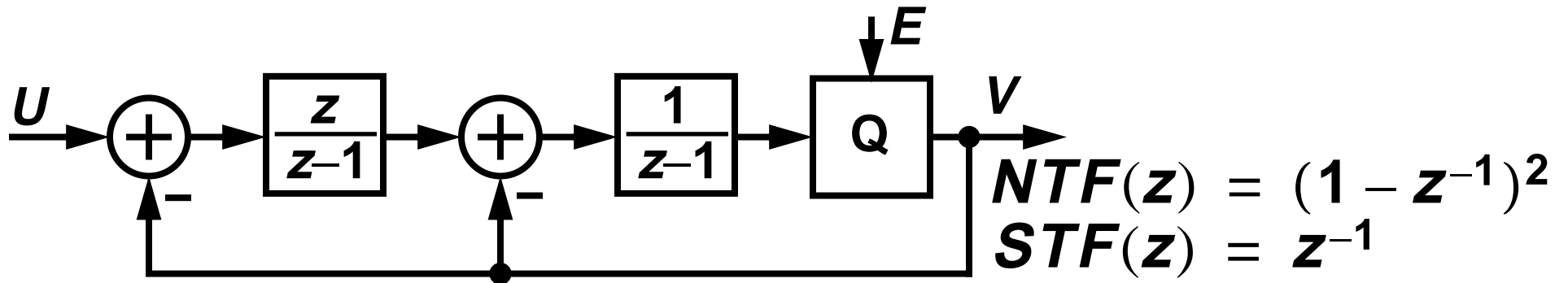

## Scaled Block Diagram

 


# Review: Schematic

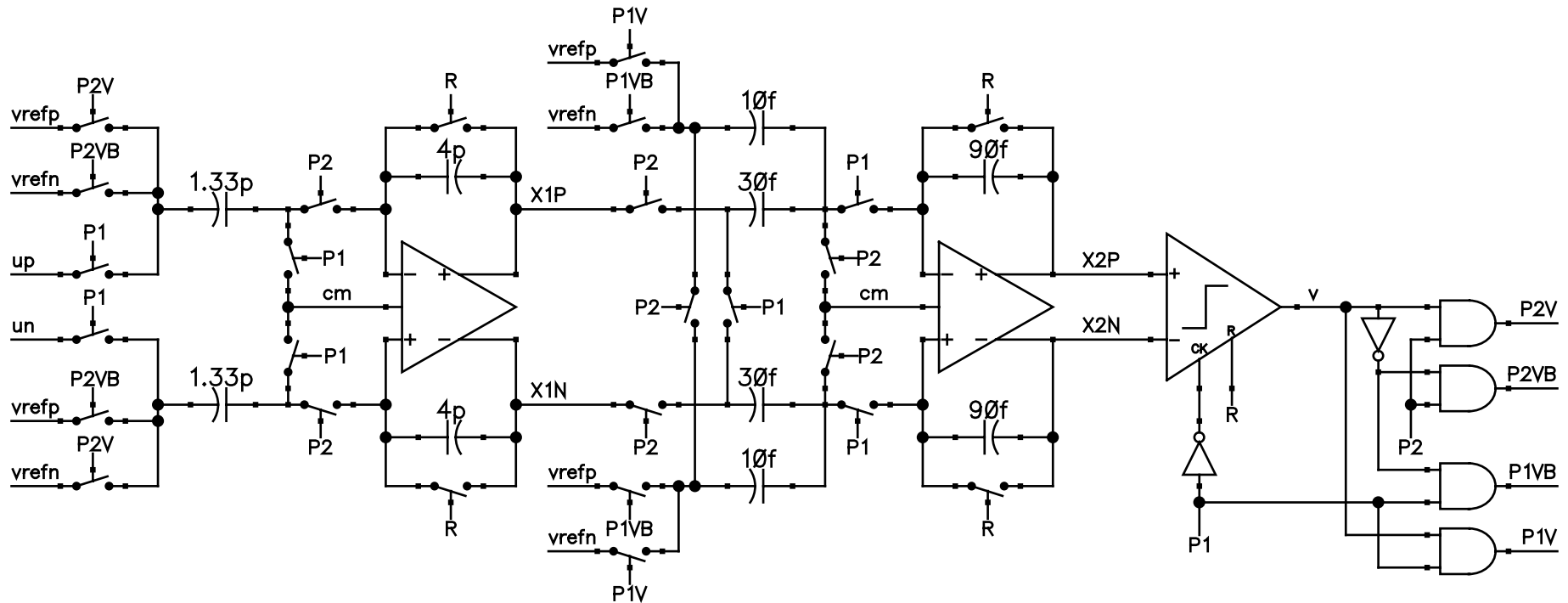

- **1<sup>st</sup>-stage capacitor sizes set for SNR = 100 dB @ OSR = 500 and -3-dBFS input**  
 $V_{ref} = 1V$  and the full-scale input range is  $\pm 1 V$ .
- **2<sup>nd</sup>-stage capacitor sizes set by minimum allowable capacitance**

# Review: Simulated Spectrum

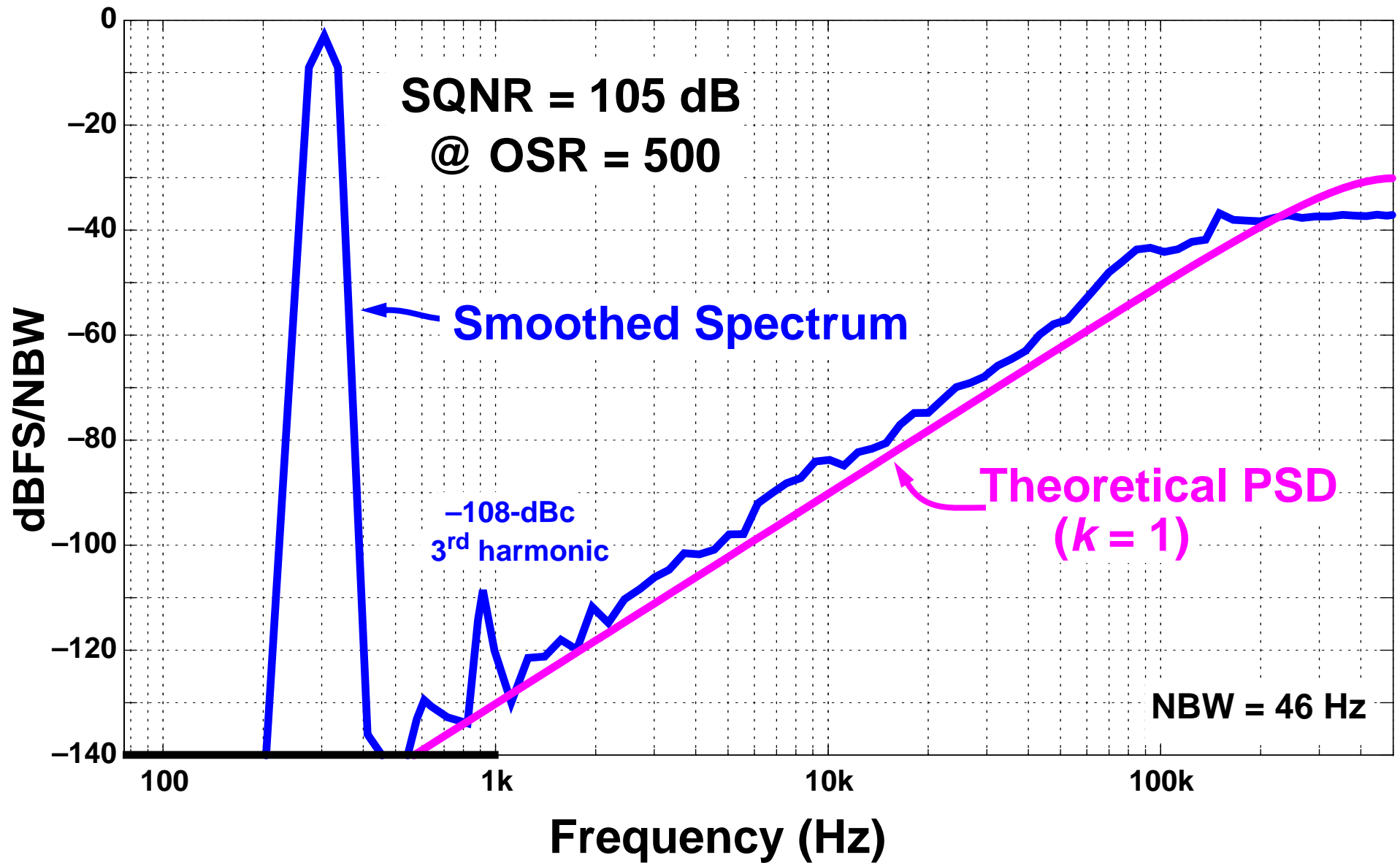




# Review: Implementation Summary

- ✓ 1 **Choose a viable SC topology and manually verify timing**
- ✓ 2 **Do dynamic-range scaling**  
You now have a set of capacitor ratios.  
Verify operation.
- ✓ 3 **Determine absolute capacitor sizes**  
Verify noise.
- 4 **Determine op-amp specs and construct a transistor-level schematic**  
Verify.
- 5 **Layout, fab, debug, document, get customers, sell by the millions, go public, ...**

# Effect of Finite Op Amp Gain
 
## Linear Theory

- Suppose that the amplifier has finite DC gain  $A$ . Define  $\mu = 1/A$ .
- To determine the effect on the integrator pole, let's look at our SC integrator with zero input:




- A fraction of  $q_2$  leaks away each clock cycle:

$$q_2(n+1) = (1 - \varepsilon)q_2(n),$$

$$\text{where } \varepsilon = \mu C_1 / C_2$$

- Thus, the integrator is lossy, with a pole at  $z = 1 - \varepsilon$

 **Q: How big can  $\varepsilon$  get before the effect becomes significant?**



# Op Amp Gain Requirement

## Linear Theory

- According to the linear theory, finite op amp gain should not degrade the noise significantly as long as


$$A > (C_1 / C_2)(OSR / \pi)$$

- For our implementation of MOD2, in which  $C_1 / C_2 = 1/4$  and  $OSR = 500$ , this leads to
$$A > 40 = 32 \text{ dB},$$
which is quite a lax requirement!
- As OSR is decreased, the gain requirement goes down

# Op Amp Transconductance

## Settling time

- Model the op amp as a simple  $g_m$ :

 

$$\beta = C_2 / (C_1 + C_2)$$

$$C_{eff} = C_3 + C_1 C_2 / (C_1 + C_2)$$

- This is a single-time-constant-circuit with  $\tau = C_{eff} / (\beta g_m)$

# Settling Requirements

- If  $g_m$  is linear, incomplete settling has the same effect as a coefficient error and thus  $g_m$  can be very low
- In practice, the  $g_m$  is not linear and we need to ensure nearly complete settling
- As a worst case scenario, let's require transients to settle to 1 part in  $10^5$   
This should be more than enough for  $-100$  dBc distortion.

# Settling Requirements (cont'd)

- If linear settling is allocated 1/4 of a clock period,

$$\text{we want } \exp\left(-\frac{T/4}{\tau}\right) = 10^{-5}, \text{ or } \tau = \frac{T}{4 \ln 10^5} = 20 \text{ ns}$$

$$\text{and thus } g_m = \frac{C_{eff}}{\beta \tau} = \frac{C_{eff}}{\beta} 4 f_s \ln 10^5$$

- For INT1 of our MOD2:

$$C_{eff} = 0.5 \left( \frac{4\text{p} \cdot 1.33\text{p}}{4\text{p} + 1.33\text{p}} + 30\text{f} \right) = 0.5 \text{ pF}^*$$

$$\beta = 3/4$$

$$f_s = 1 \text{ MHz}$$


$$\Rightarrow g_m = 30 \mu\text{A/V}$$

---

\*. 0.5 comes from the single-ended to differential translation.
 
# Slewing

- The maximum charge transferred through C1 is




- If we require the slew current to be enough to transfer  $q_{max}$  in 1/4 of a clock period, then

$$I_{slew} = \frac{q_{max}}{T/4} \approx 5 \mu\text{A}$$



# Building Block– Op Amp

 


- **Folded-cascode op-amp with switched-capacitor common-mode feedback**

# Op-Amp Design— Bias Current


Bias Currents

Slew Currents

 


- Slew constraint dictates  $I > 5 \mu\text{A}$

# Op-Amp Design— $g_m$

 


- **Square-law MOSFET model:  $g_{m1} = (2I_D)/(\Delta V)$**
- **$I_D = 5 \mu\text{A}$ ,  $g_m \geq 30 \mu\text{A/V} \Rightarrow \Delta V \leq 0.33 \text{ V}$**   
 Usually  $\Delta V \approx 200 \text{ mV}$ , so we should be able to get high enough  $g_m$ .

# Transistor Sizes & Bias Point

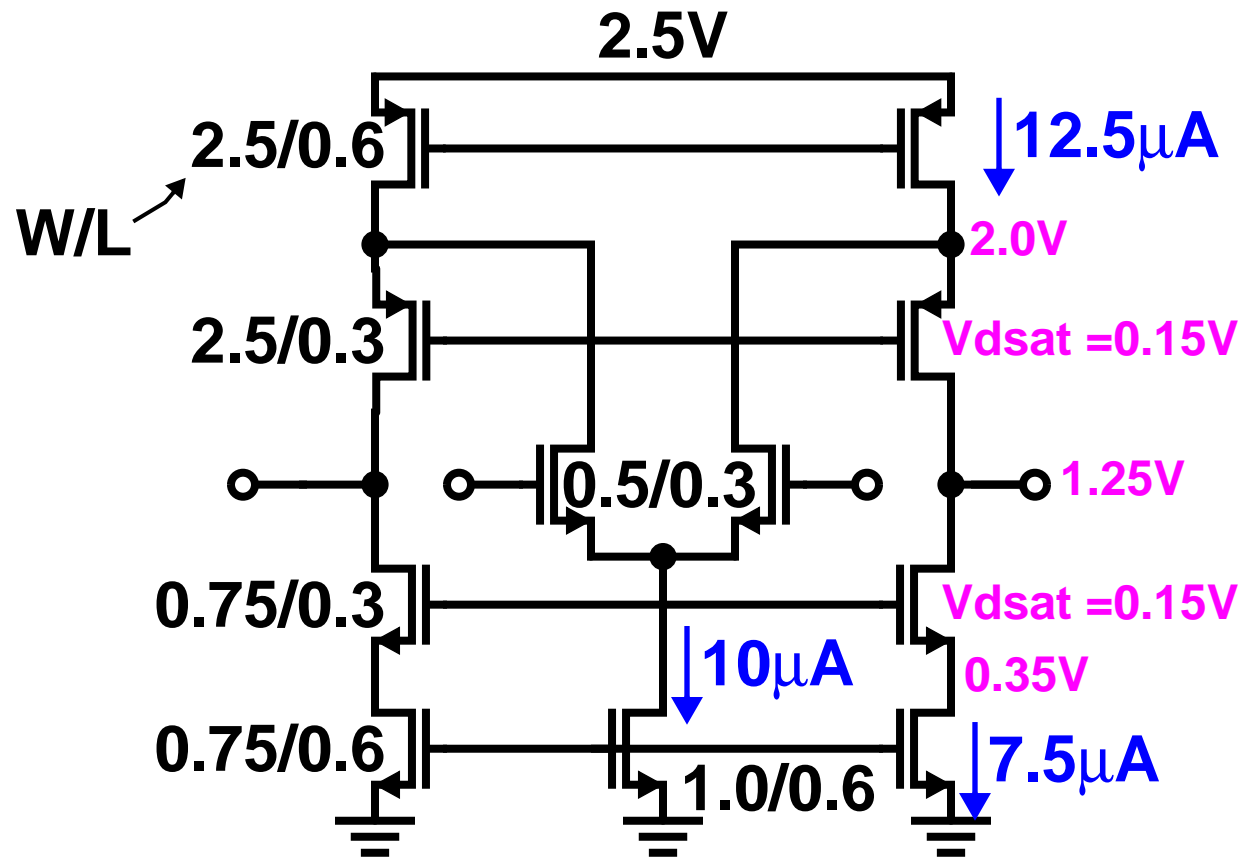


- Allowable swing is +0.6 V, -0.75 V
- Simulated  $g_m = 36 \mu A/V$ ,  $A = 48$  dB  
 $g_m$  is high enough and the gain is 6× required.

# Ideal Common-Mode Feedback

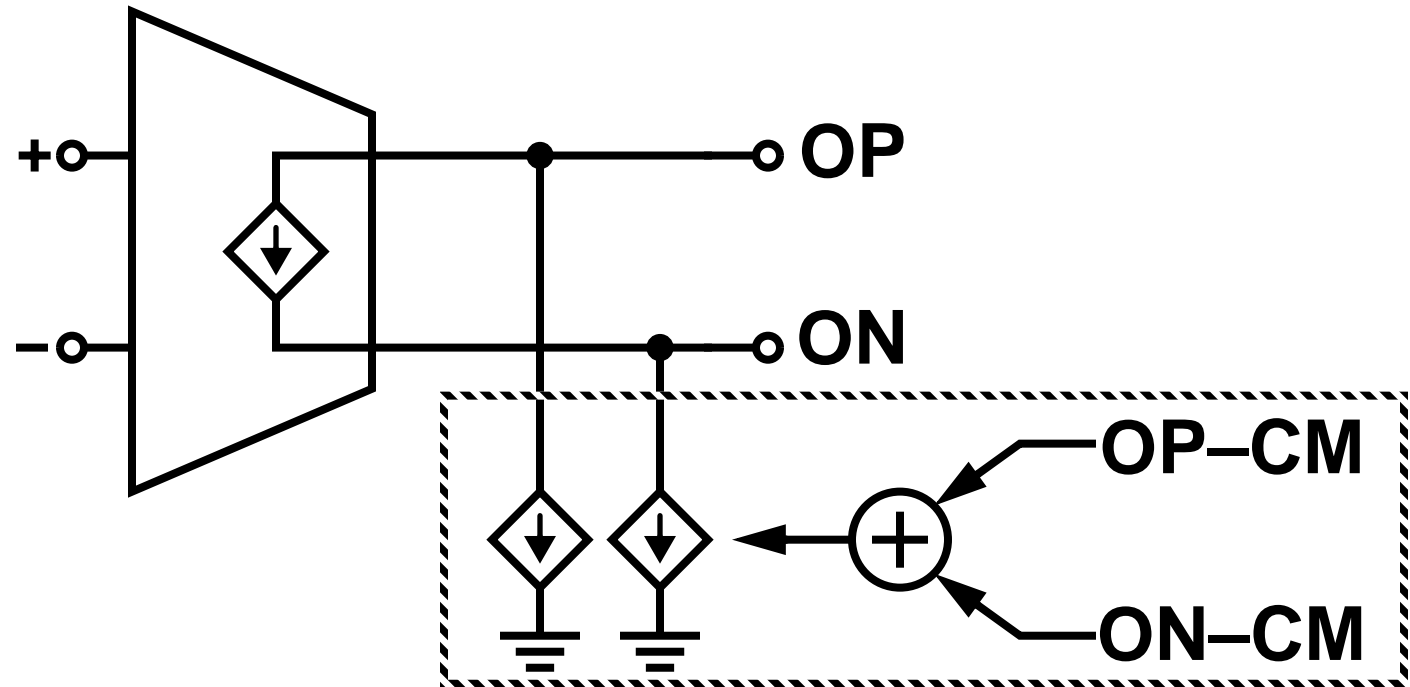


- Can use this circuit to speed up the simulation


# Simulated Waveforms

 

# Expanded Waveforms

 

# Simulated Spectrum

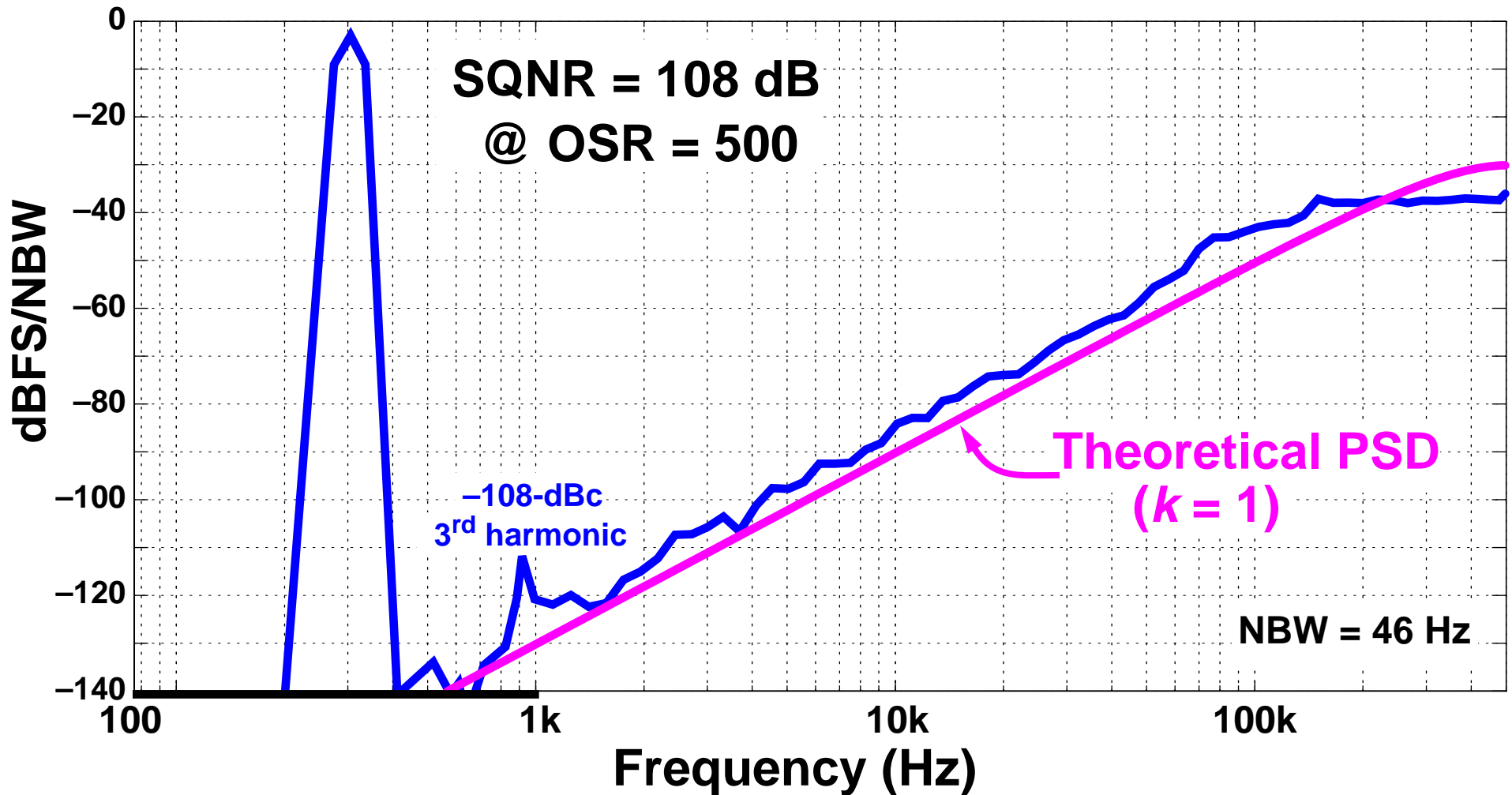


- **This was too easy!**  
Although this one simulation *did* take an hour.





# SC Common-Mode Feedback

## Common-Mode 1/2-Circuit

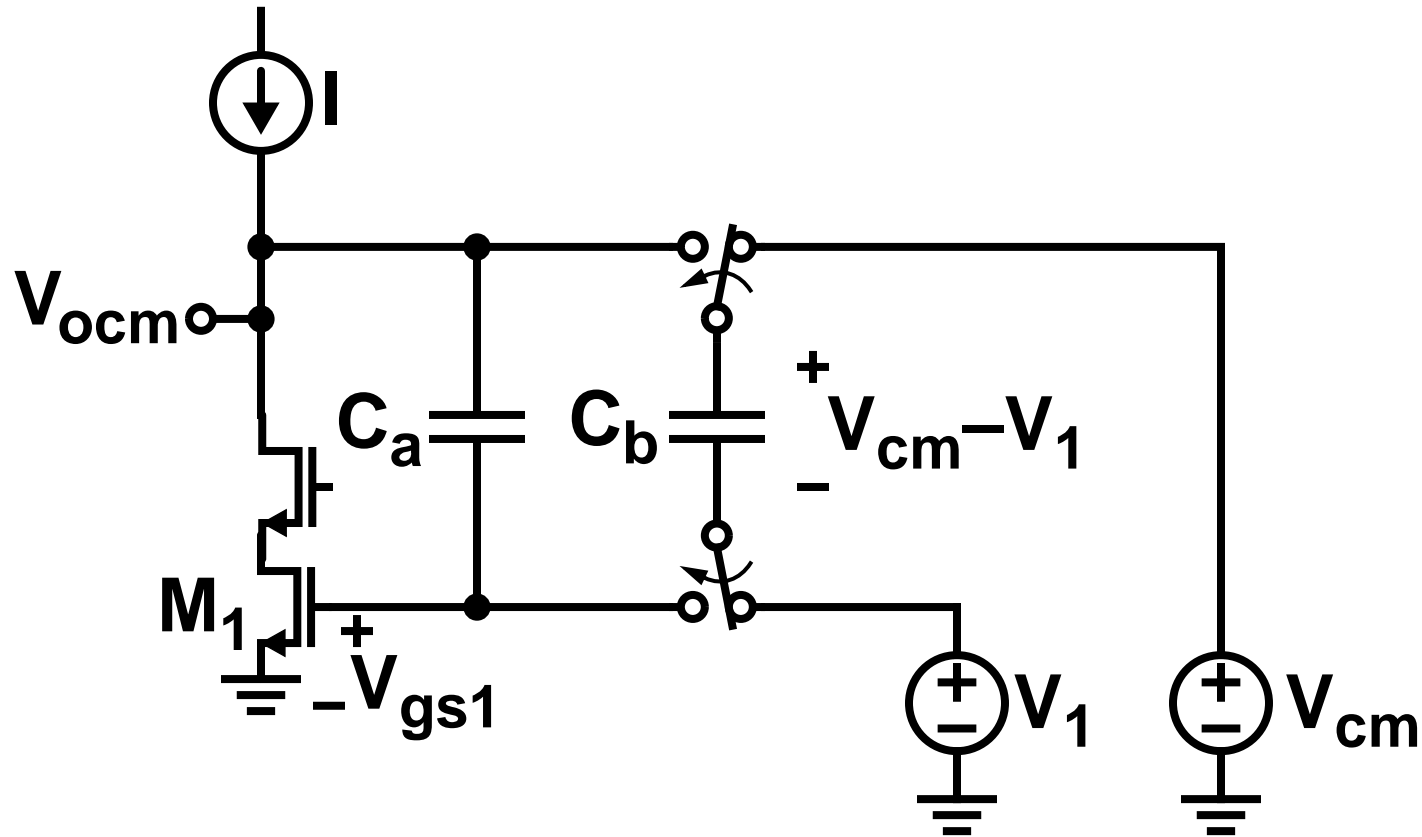

- $V_{ocm} = V_{cm} + V_{gs1} - V_1$   
 If  $V_1 = V_{gs1}$ , then  $V_{ocm} = V_{cm}$ .

# Latched Comparator

 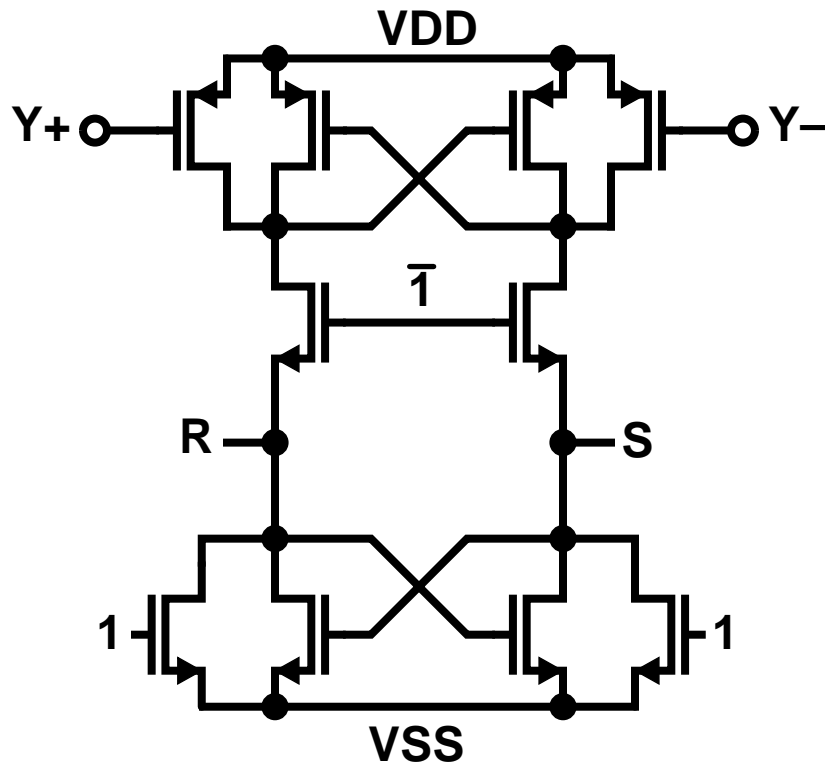


Inverter thresholds are chosen so that the inverters respond only after R/S have resolved.

- **Falling phase 1 initiates regenerative action**  
**S and R connected to a Set/Reset latch.**

# Switch Resistance

## Sampling Phase

 


- If  $R_{sw}$  is constant, it has only a filtering (linear) effect, which is benign
  - Unfortunately, the on-resistance of MOS switches varies with  $V_{gs}$  (and hence  $V_{in}$ )
- ⇒ Must make MOS switches large enough

# Switch Resistance


## Integration Phase

Differential  
Half-Circuit:


 


- $R_{sw}$  increases the settling time by a factor of  $1 + 4g_m R_{sw}$
- ⇒ Set  $R_{sw} \leq \frac{1}{40g_m}$  to make the increase in  $\tau$  small
- So in our MOD2, we want  $R_{sw} \leq 0.75 \text{ k}\Omega$ .  
BTW, my simulation used  $R_{sw} = 1 \text{ k}\Omega$  and was OK.
 
# NLCOTD: Non-Overlapping Clock Generator




# Non-Overlapping Clock Generator

  


- Non-overlap time set by NOR's  $t_{PLH}$

# Clocking Details— Early/Late Phases

 

- **Charge injected via M1 is (non-linearly) signal-dependent, whereas charge injection from M2 is signal-independent**
- ⇒ **Open M2 (early) then open M1 (late) so that charge injected from  $C_{gs1}$  cannot enter C1**
 
# Clocking Details— Bottom-plate sampling



- Parasitic capacitance on the right terminal of  $C1$  degrades the effectiveness of early/late clocking
- $C_p$  for the top plate is smaller, so use the top plate for the right terminal and the bottom plate for the left




# Complementary Clock Alignment


- We need complementary clocks if transmission gates are used for the switches

**Q: How do we align them?**

 
**A: Carefully size the inverters relative to their capacitive loads, or use a transmission gate to mimic an inverter delay:**



 **Need to match delay  
of 3 INVs to 2 INVs**



# Professional Clock Generator

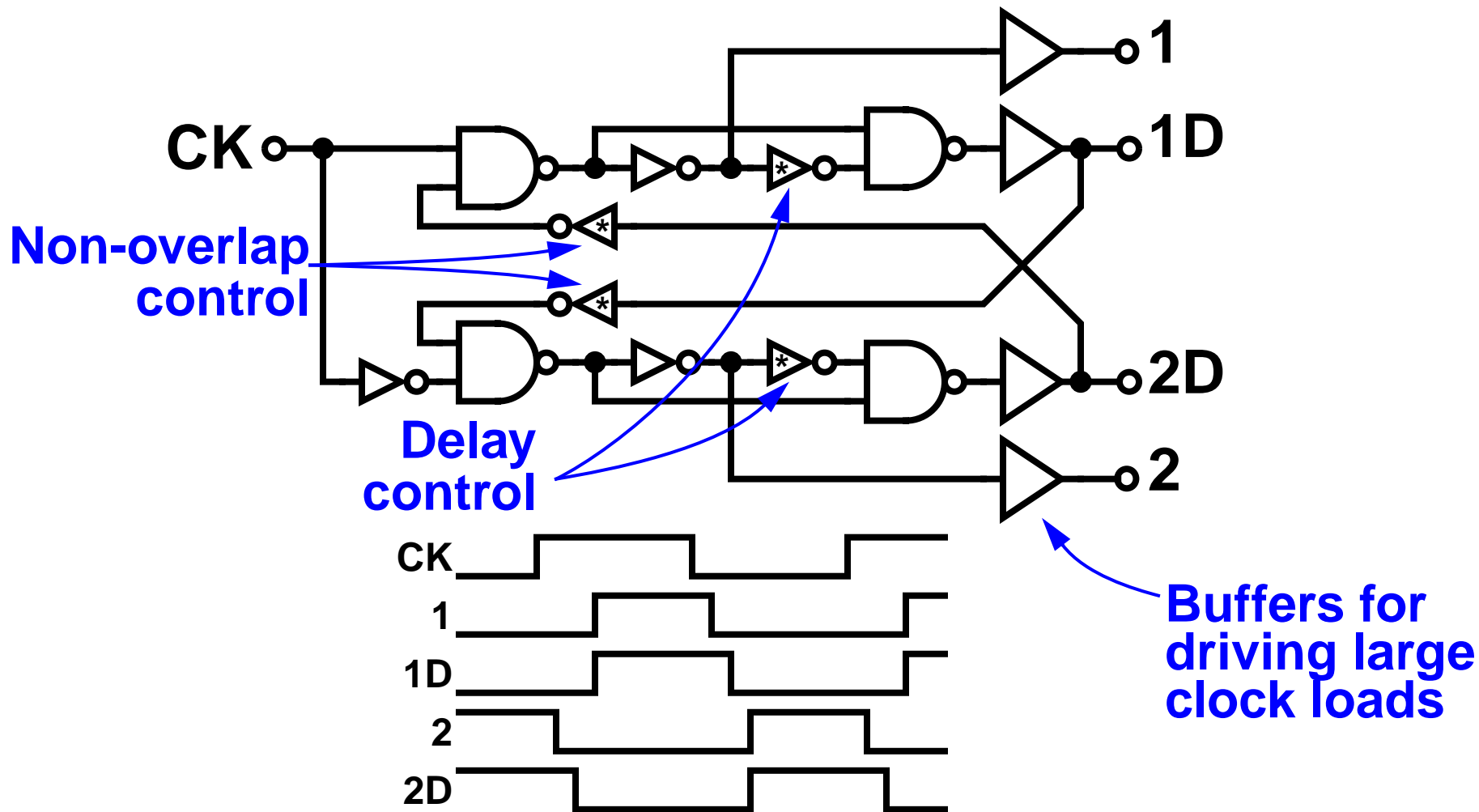


- To maximize the time available for settling, make the early and late phases start at the same time

# Review: Implementation Summary


- ✓ 1 Choose a viable SC topology and manually verify timing
- ✓ 2 Do dynamic-range scaling
- ✓ 3 Determine absolute capacitor sizes
- ✓ 4 Determine op-amp specs and construct a transistor-level schematic
  - Verify. Verify. Verify.
- 5 Layout, fab, debug, document, get customers, sell by the millions, go public, ...
  - This last step is an “exercise for the reader.”

# Topological Variant– Feed-Forward

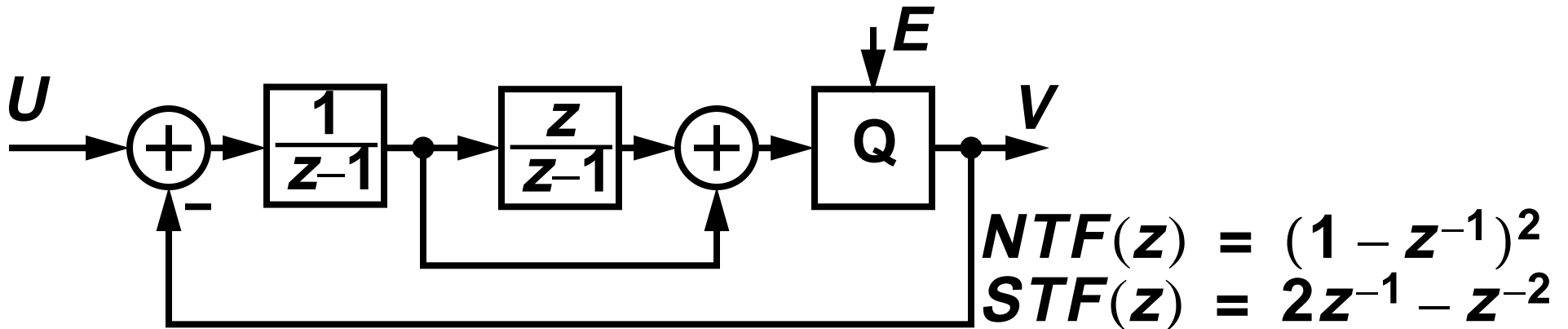


- + **Output of first integrator has no DC component**  
Dynamic range requirements of this integrator are relaxed.
- **Although  $|STF| \approx 1$  near  $\omega = 0$ ,**  
 **$|STF| = 3$  for  $\omega = \pi$**   
Instability is more likely.
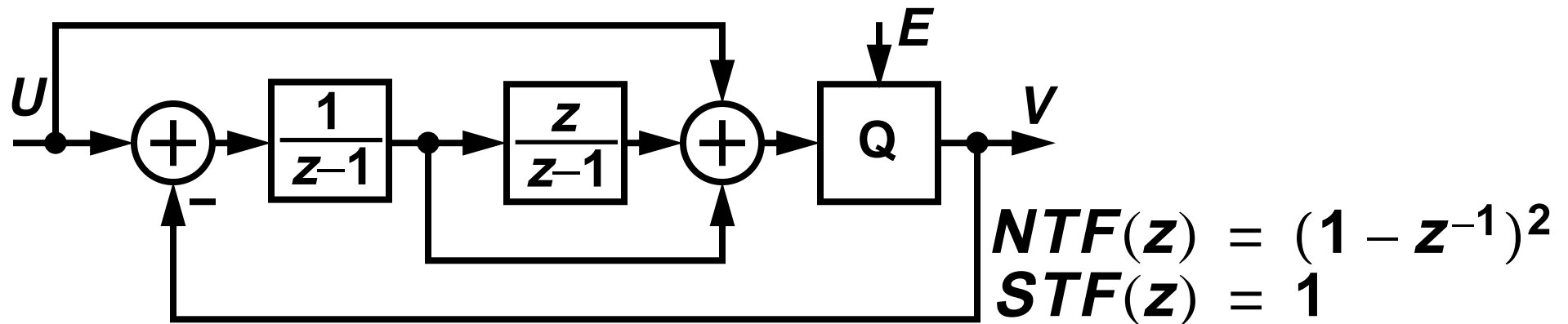
# Topological Variant– Feed-Forward with Extra Feed-In



- + **No DC component in either integrator's output**  
Reduced dynamic range requirements in both integrators, esp. for multi-bit modulators.
- + **Perfectly flat STF**  
No increased risk of instability.
- **Timing is tricky**

# Topological Variant– Error Feedback

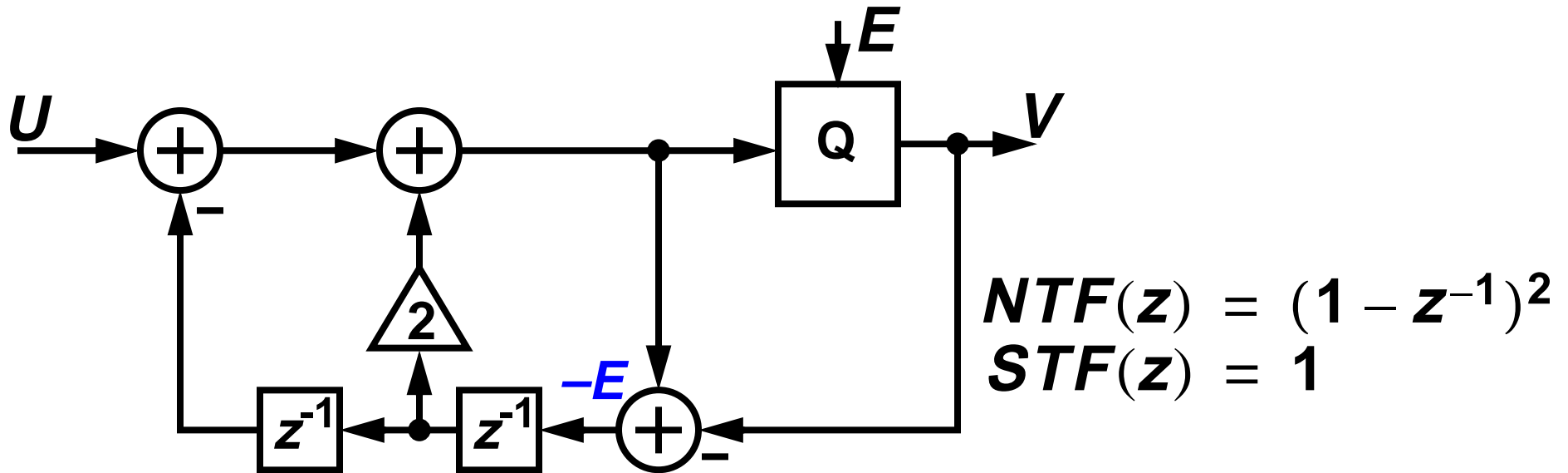

- + Simple
- Very sensitive to gain errors  
Only suitable for digital implementations.

# Is MOD2 The Only 2<sup>nd</sup>-Order Modulator?


- Except for the filtering provided by the STF, any modulator with the same NTF as MOD2 has the same input-output behavior as MOD2
  - SQNR curve is the same.
  - Tonality of the quantization noise is unchanged.
- Internal states, sensitivity, thermal noise etc. can differ from realization to realization

**BUT, in terms of input-output behavior,**


- A 2<sup>nd</sup>-order modulator is truly different only if it possesses a truly different (2<sup>nd</sup>-order) NTF

# A Better 2<sup>nd</sup>-Order NTF

## Pole-Zero Plot

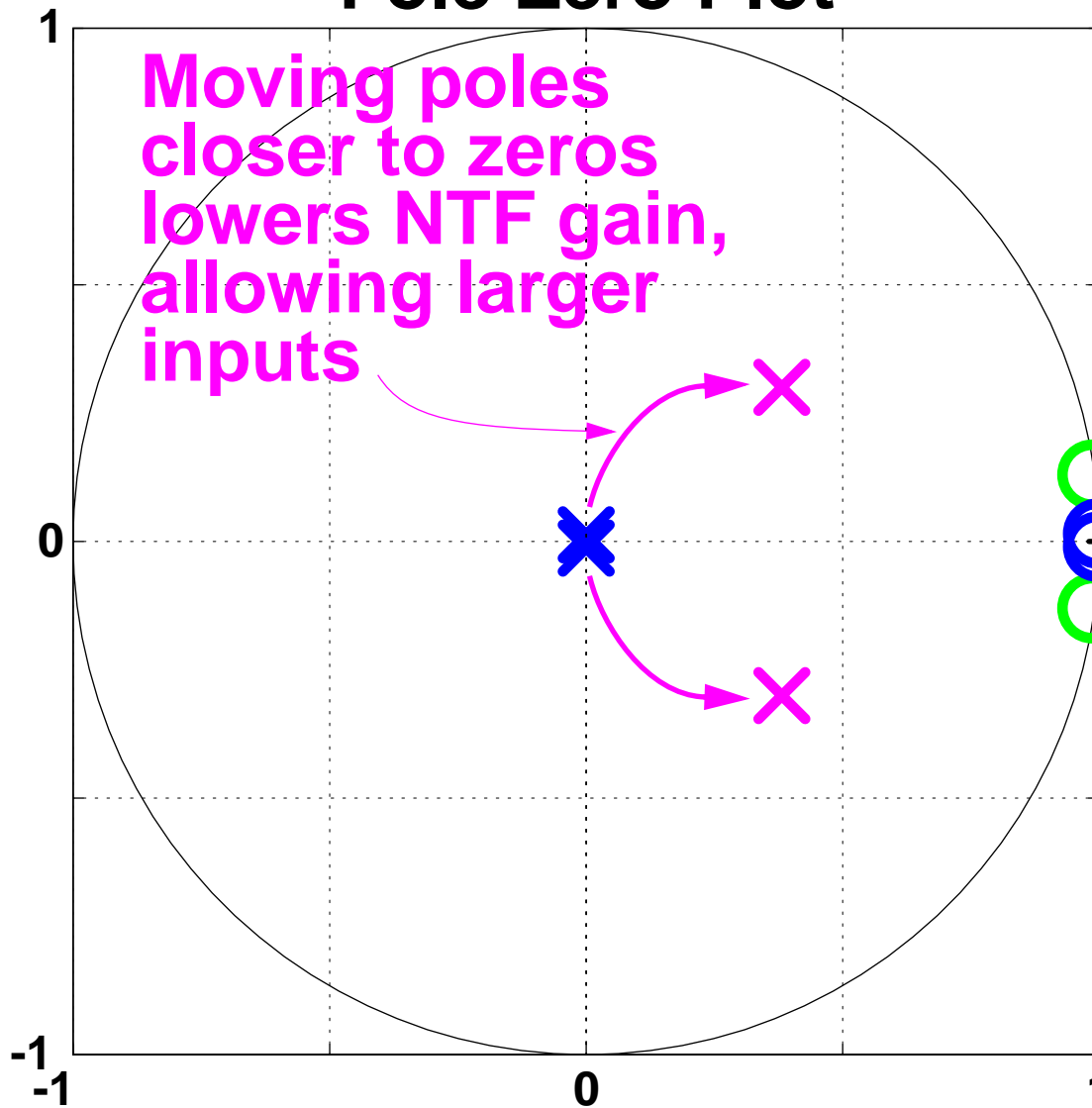


 Separating the zeros reduces in-band noise:






# NTF Comparison


 


# SNR vs. Amp Comparison

 

# MOD2 Internal Waveforms


## Input @ 75% of FS

  


# MOD2b Internal Waveforms

Input @ 75% of FS


$x_1$

 

$y = x_2$

 

# Gain of a Binary Quantizer

 

- The effective gain of a binary quantizer is not known a priori
- The gain ( $k$ ) depends on the statistics of the quantizer's input  
Halving the signal doubles the gain.


# Gain of the Quantizer in MOD2

- The effective gain of a binary quantizer can be computed from the simulation data using


$$k = \frac{E[|y|]}{E[y^2]} \text{ [S\&T Eq. 2.5]}$$

- For the simulation of 2-14,  $k = 0.63$
- $k \neq 1$  alters the NTF:
 
$$NTF_k(z) = \frac{NTF_1(z)}{k + (1 - k)NTF_1(z)}$$



# Revised PSD Prediction

 

- Agreement is now excellent

# Variable Quantizer Gain

- When the input is small (below  $-12$  dBFS), the effective gain of MOD2's quantizer is  $k = 0.75$
- MOD2's "small-signal NTF" is thus
$$NTF(z) = \frac{(z - 1)^2}{z^2 - 0.5z + 0.25}$$
- This NTF has 2.5 dB less quantization noise suppression than the  $(1 - z^{-1})^2$  NTF derived from the assumption that  $k = 1$ 

Thus the SQNR should be about 2.5 dB lower than ✕.
- As the input signal increases,  $k$  decreases and the suppression of quantization noise degrades  
SQNR increases less quickly than the signal power. Eventually the SQNR saturates and then decreases as the signal power reaches full-scale.



# What You Learned Today

- 1 Transistor-level implementation of MOD2  
op-amp, SC CMFB, comparator, clock generator**
- 2 MOD2 variants**
- 3 Variable quantizer gain**

# Op Amp Gain Requirement

## Nonlinear Theory 1

- MOD2 has a “deadband” around  $u = 0$  whose width is approximately

$$\frac{0.5(a_1 c_1) + a_2}{A^2} = \frac{0.5((1/3) \cdot (1/3)) + (1/9)}{A^2} = \frac{1}{6A^2}$$

- To make the deadband less than 1 “LSB” wide,

$$\frac{1}{6A^2} < \text{undbv}(-100) = 10^{-5},$$

$$\text{or } A > 400 = 52 \text{ dB}$$

- Since we didn't need so much gain to get excellent AC performance, this calculation looks like it is conservative

# Op Amp Gain Requirements

## Nonlinear Theory 2

- **Finite DC gain  $\Rightarrow$  incomplete charge transfer**
- **The gain is a nonlinear function, so the residual charge is nonlinearly related to the output voltage of the amplifier**
  - The residual charge is akin to noise.**
- **However, if the amplifier output contains signal components, then nonlinear gain can result in harmonic distortion**
  - The feedforward topology is known to yield low distortion even when the amplifier gain is low.**
- **The effects are difficult to quantify analytically, and so we typically rely on simulations**