

ECE1371 Advanced Analog Circuits

Lecture 8

COMPARATOR & FLASH ADC DESIGN

Richard Schreier
richard.schreier@analog.com

Trevor Caldwell
trevor.caldwell@utoronto.ca

Course Goals

- Deepen understanding of CMOS analog circuit design through a top-down study of a modern analog system—a delta-sigma ADC
- Develop circuit insight through brief peeks at some nifty little circuits


The circuit world is filled with many little gems that every competent designer ought to know.

ECE1371

8-2

Date	Lecture (M 13:00-15:00)	Ref	Homework
2015-01-05	RS 1	MOD1 & MOD2	ST 2, 3, A
2015-01-12	RS 2	MODN + $\Delta\Sigma$ Toolbox	ST 4, B
2015-01-19	RS 3	Example Design: Part 1	ST 9.1, CCJM 14
2015-01-26	RS 4	Example Design: Part 2	CCJM 18
2015-02-02	TC 5	SC Circuits	R 12, CCJM 14
2015-02-09	TC 6	Amplifier Design	
2015-02-16	Reading Week— No Lecture		
2015-02-23	TC 7	Amplifier Design	
2015-03-02	RS 8	Comparator & Flash ADC	CCJM 10
2015-03-09	TC 9	Noise in SC Circuits	ST C
2015-03-16	RS 10	Advanced $\Delta\Sigma$	ST 6.6, 9.4
2015-03-23	TC 11	Matching & MM-Shaping	ST 6.3-6.5, +
2015-03-30	TC 12	Pipeline and SAR ADCs	CCJM 15, 17
2015-04-06	Exam		Proj. Report Due Friday April 10
2015-04-13	Project Presentation		

NLCOTD: Linear Transconductor

 

- Useful in
 - 1 gm-C filter
 - 2 LNA
 - 3 mixer
 - 4 CT $\Delta\Sigma$ ADC

ECE1371

8-3

ECE1371

8-4



Highlights

(i.e. What you will learn today)

- 1 Operation of Example Comparator Circuit
- 2 Regeneration Time Constant τ
- 3 Metastability, Probability of Error
- 4 Offset, Dynamic Offset, Auto-zeroing
- 5 Flash ADC
- 6 A Bunch of Transconductor Circuits

Review: Latched Comparator

From Lecture #4's 1-MHz MOD2

  

Inverter thresholds are chosen so that the inverters respond only after R/S have resolved.

- Falling phase 1 initiates regenerative action
S and R connected to a Set/Reset latch.


ECE1371

8-5

ECE1371

8-6

Phase 1 = High: "Reset" Mode


 


- Grayed-out devices are off
⇒ the active part of the comparator is reset
- R and S are low ⇒ the SR latch is in hold mode

ECE1371

8-7


Phase 1 Goes Low: "Latch" Mode

  

ECE1371

8-8



Example Waveforms Quick Design in 65nm (VDD = 1V)

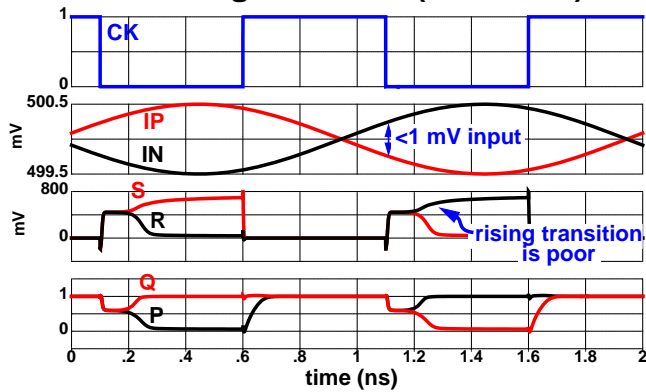

ECE1371

8-9


Better Design

  

ECE1371

8-10


Responses for Various V_{in}

 

ECE1371

8-11

Delay vs. V_{in}

 


ECE1371


8-12

Latch Mode Dynamics

 - For V_{in} near the trip point, an inverter is essentially just a transconductor:




- So near balance the comparator looks like this:

 

ECE1371

8-13

Small-Signal Analysis

 


$$\begin{aligned}
 C\dot{x} &= -g_m y \\
 C\dot{y} &= -g_m x \\
 v_d &= x - y \\
 v_{cm} &= \frac{x + y}{2} \\
 C\dot{v}_d &= g_m v_d & C\dot{v}_{cm} &= -g_m v_{cm} \\
 v_d(t) &= v_{d0} e^{t/\tau} & v_{cm}(t) &= v_{cm0} e^{-t/\tau} \\
 \tau &= \frac{C}{g_m}
 \end{aligned}$$

- Differential component grows exponentially
- CM component decays exponentially

ECE1371

8-14

State-Space

 


- $v_{cm} \rightarrow VDD/2, v_d \rightarrow \pm VDD$

ECE1371

8-15

Metastability

- Metastability is fundamentally unavoidable
- Assuming the universe is continuous and deterministic, a comparator can be unresolved for any length of time

 

ECE1371

8-16

Probability of Error, P_E

$$\begin{aligned}
 P_E &= P\{\text{not resolved by time } t\} \\
 &= P\left\{V_{in} < \exp\left(-\frac{t-t_0}{\tau}\right)\right\}
 \end{aligned}$$

- Take $t_0 = 100$ ps and $\tau = 20$ ps
- Then for $t = 500$ ps (1 GHz clock with a half-cycle between the comparator's clock and the clock of the subsequent latch),

$$P_E = P\{|V_{in}| < 2 \text{ nV}\}$$

- Assuming V_{in} is uniformly distributed in $[-0.5, +0.5]$ V, $P_E = 2 \times 10^{-9}$
Metastability occurs twice a second!

ECE1371

8-17


Metastability Summary

- Metastability is unavoidable
All you can do is make τ small and give enough time for regeneration to make P_E small.
- Supplementary Slides examine the effects of quantized charge and noise
Noise helps a comparator resolve when $V_{in} = 0$ but usually does not reduce P_E
- At best, metastability causes SNR degradation
At worst, it causes a system failure.

ECE1371

8-18

Offset

 


- Obvious sources of offset include mismatch in the input differential pair as well as mismatch in the regenerating devices

ECE1371

8-19

Dynamic Offset

 


- Mismatched parasitic capacitance also causes offset
20 mV/fF for this comparator!
- Bad design– Can fix this!

ECE1371

8-20

Improved Comparator

[S&T Fig. 9.36]

 


- Reset when CK = 1; regenerates when CK = 0
- x & y don't step if biased properly
Mismatch in overlap capacitance still a problem.

ECE1371

8-21

Reducing Offset with a Preamp

 

$$V_{\text{off,tot}} = V_{\text{off,amp}} + V_{\text{off,comp}}/A$$


- + Comparator offset is reduced by preamp gain
Amplifier offset dominates.
- + Amplifier also isolates driving stage from "charge kickback"
- Amplifier bandwidth limits speed, especially recovery from overload

ECE1371

8-22

Auto-zeroed SC Comparator

[J&M Fig 13.17]

 


- During P1, the inverter/amplifier is biased at its threshold/offset voltage
- During P2, the difference between V_{in} and V_{ref} is amplified

ECE1371

8-23

Comparator with Preamp

[J&M Fig. 7.16]

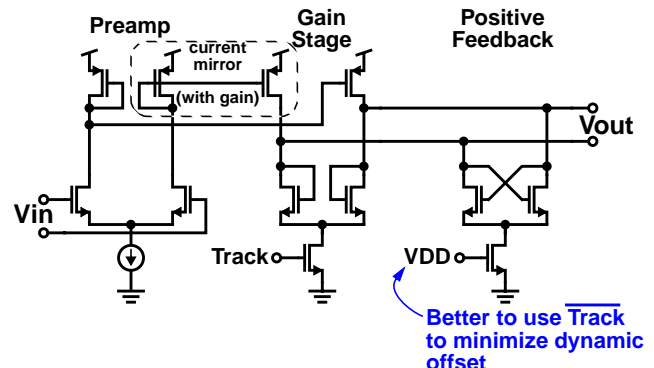


ECE1371

8-24

Two-Stage Comparator

[J&M Fig 7.17]

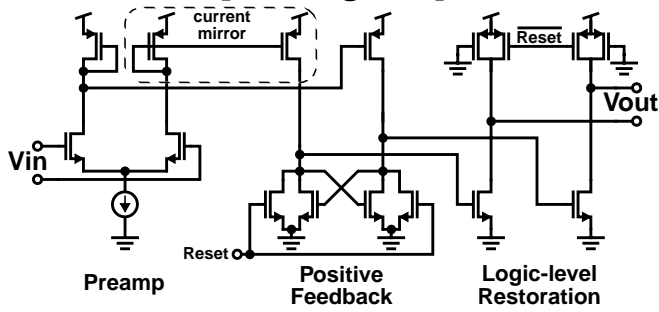


- Precharges regeneration nodes low & digital output nodes high

ECE1371

8-25

StrongArm Flip Flop

 


- + No static current
 - + Can be used as a comparator
- Note that input CM voltage defines the bias point during regeneration.

ECE1371

8-26

Improved StrongArm Design

 


- MX provides DC path to ground for leakage currents in case D changes after CK goes high
MX is needed to make latch static.

ECE1371

8-27

Alternative Arrangement

 


- Well-defined initial state \Rightarrow less hysteresis
[Abidi 2014CICC] "Understanding the Regenerative Comparator Circuit"

ECE1371

8-28

Symmetric Latch

 


- Faster than cross-coupled NAND gates

ECE1371

8-29

Yang's High-Speed Comparator

 


- $\tau_{nom} = 6 \text{ ps (!)}$ in 65nm CMOS
Used in a CT $\Delta\Sigma$ ADC clocked at 4 GHz [Shibata2012].


ECE1371

8-30

Dual-Difference Comparator

 


 In any of our comparator circuits, replace:




Q: Where should Va- go?


Flash ADC

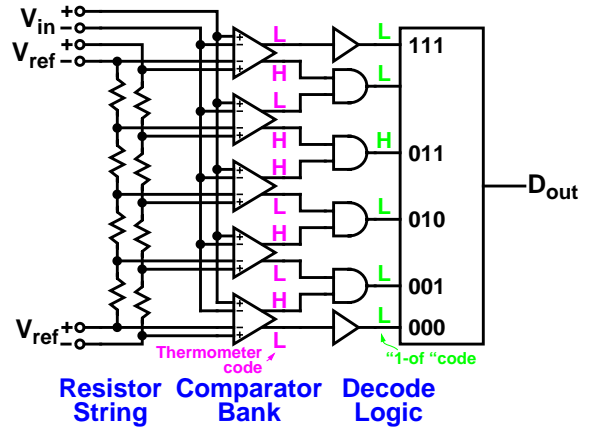


Flash Bubbles

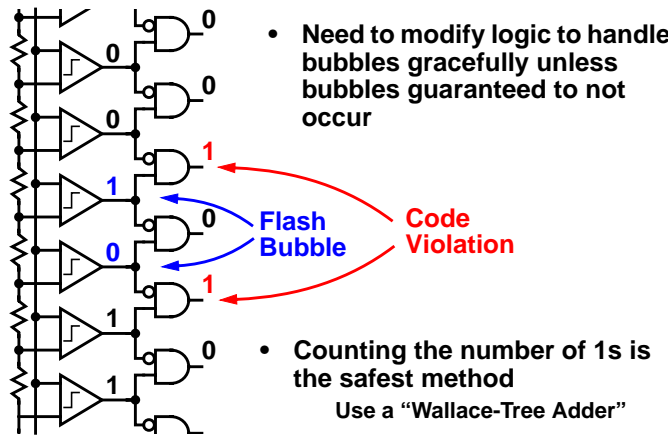

Averaging and Interpolation

 


VCO as a Quantizer— Concept

 


- + Simple
- + Monotonic
- Not linear
- Ill-defined full-scale

 Current-Controlled Ring Oscillator (CCRO)



- Oscillation frequency is proportional to current
- ⇒ Can make a fairly linear quantizer

CCRO + Phase latch + EXOR = Q!

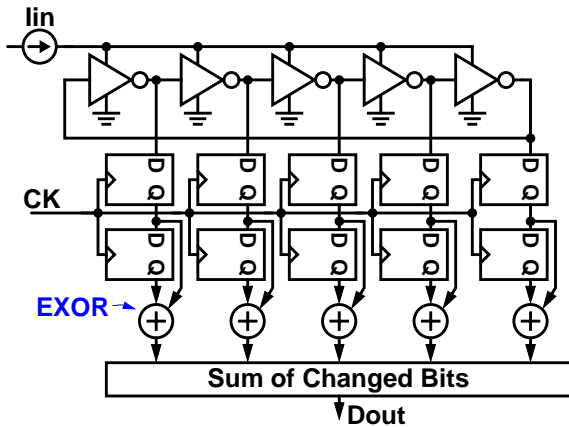

ECE1371

8-37


Improvements to CCRO Quantizer

- Put EXOR before 1st FF and remove 2nd FF
To eliminate unnecessary delay.
- Add inverters to increase resolution
Must keep f_{osc} constant to maintain full-scale.
- Use 2 rings in a pseudo-differential arrangement
To cancel even-order distortion and make mid-scale self-referenced.
- Use multiple rings with phase interpolation to increase resolution without hitting f_{osc} ceiling
- Driving the elements of the DACs with the EXOR outputs directly results in *mismatch-shaping*

ECE1371

8-38

 NLCOTD: Linear Transconductors Degenerated Differential Pair




- + Simple!
- V_{gs} varies nonlinearly with $I_{out} \Rightarrow g_m$ is nonlinear

ECE1371

8-39

Force Constant V_{gs}

 


- I_d constant $\Rightarrow V_{gs}$ constant
- Linearity dependent on current-mirror linearity

ECE1371

8-40

Cascomp

 


- V_{gs} of input devices replicated in cascodes and distortion-cancelling current injected into output
- + All NMOS \Rightarrow fast
- Cancellation depends on matching
Should tie bulk to source?

ECE1371

8-41

Add Op Amps

 


- + Linearity limited only by op amp gain and BW
- + High output resistance
- Output compliance depends on input swing

ECE1371

8-42

Mirror the Output Current

 


- + Output compliance is $V_{DD} - 2 V_{dsat}$
- Top of differential pair at $V_{DD} - V_{gs}$

ECE1371

8-43

Fold the Output Current

 


- + Increased headroom for differential pair
- + Increased output resistance

ECE1371

8-44

 Multi-Tanh Doublet [Gilbert JSSC Dec. 1998]




- With BJTs, ratioing the emitter areas creates a well-controlled offset
- With the right offset, the cubic term in the nonlinearity is zero!

$$n = 2 + \sqrt{3} = 3.73 \approx 15/4$$

ECE1371

8-45

MOS Quad

 

- Supposedly can get less distortion than a degenerated differential pair by fiddling with W/L

ECE1371

8-46

What You Learned Today

- 1 Operation of Example Comparator Circuit
- 2 Regeneration Time Constant τ
- 3 Metastability, Probability of Error
- 4 Offset, Dynamic Offset, Auto-zeroing
- 5 Flash ADC
- 6 A Bunch of Transconductor Circuits

Supplementary Slides (Regarding Metastability)

ECE1371


8-47

ECE1371

8-48

Quantized Charge Helps?

 - If $C = 20 \text{ fF}$, then 1 electron yields $8 \mu\text{V}$
- $V_{\text{in}} = 2 \text{ nV}$ and hence metastability impossible?



- + Unless V_{offset} is within 2 nV of one of the discrete V_{in} levels, metastability can't happen
- But if V_{offset} is within 2 nV of an allowed V_{in} level, metastability will be abnormally frequent
- Offset drift will tend to make metastability appear/disappear sporadically (?)

ECE1371

8-49


Noise Helps?

- $kT/C = 500 \mu\text{V}$, so it is impossible to guarantee that metastability will result even if $V_{\text{in}} = 0$
- + Noise does help a comparator resolve if it is metastable
- But for any given noise (random initial condition), there is always an input which results in metastability
- Noise makes it hard to set initial conditions that will result in metastability, but does not reduce the probability of error

ECE1371

8-50

What About Noise During Regeneration?

 


- Noise from the g_m s prevents metastability?

ECE1371

8-51

Math Break: Filtered White Noise

 


- The power of the output is the product of the PSD and the power gain of the filter
- Example: $h(t) = \begin{cases} 1 & 0 \leq t \leq T \\ 0 & \text{otherwise} \end{cases}$

$$\Rightarrow \sigma_y^2 = ST$$

ECE1371

8-52

 Circuits Application: Integrated White Noise




- Variance of V increases linearly with time
- "Random Walk" or "Brownian Motion"
For any given increment of time Δt , the change in V is a random variable with constant variance
 $\delta(t) \equiv V(t) - V(t - \Delta t) \Rightarrow \sigma_{\delta}^2 = \text{constant}$

ECE1371

8-53

Today's Application

 

$$h(t) = \begin{cases} e^{t/\tau} & 0 \leq t \leq T \\ 0 & \text{otherwise} \end{cases}$$

$$\sigma_y^2 = \frac{S\tau}{4} (e^{2T/\tau} - 1)$$

ECE1371

8-54

Another Math Fact: PDF of a Sum


- Suppose x and y are two independent random variables with probability density functions (PDFs) $\rho_x(x)$ and $\rho_y(y)$
- Then the PDF of their sum is the convolution of the individual PDFs

$$z = x + y \Rightarrow \rho_z(z) = \int_{-\infty}^{\infty} \rho_x(x)\rho_y(z-x) dx$$

ECE1371

8-55

Back to Circuits

 


- Noise from the g_m s prevents metastability?

ECE1371

8-56

Differential Circuit

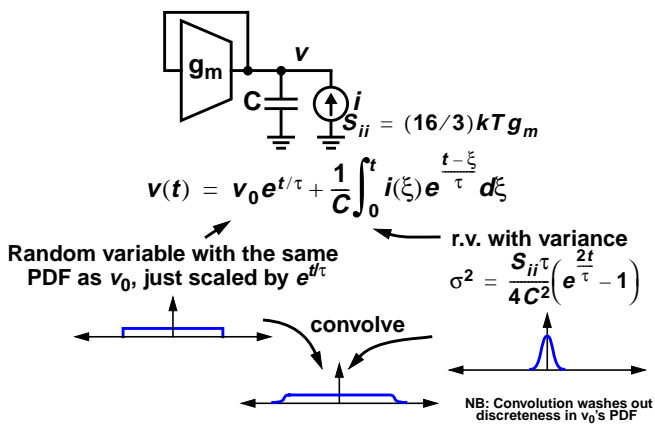

ECE1371

8-57

Making Numbers...

- Assume $g_m = 1$ mA/V, $C = 20$ fF, $t = 400$ ps
 $\Rightarrow \tau = 20$ ps; 20τ to resolve
- If v_0 uniformly distributed in $[-2,+2]$ mV, then 1st term is uniformly distributed in $[-1,+1]$ MV
- Standard deviation of 2nd term is 250 kV
 Equivalent to a 0.5-mV initial condition
- Noise during regeneration helps when the input is known to be small, but is usually negligible compared to the exponential growth of the initial conditions

ECE1371

8-58