

EXAMPLE DESIGN– PART 2

Richard Schreier
richard.schreier@analog.com

Trevor Caldwell
trevor.caldwell@utoronto.ca

- Deepen understanding of CMOS analog circuit design through a top-down study of a modern analog system
The lectures will focus on Delta-Sigma ADCs, but you may do your project on another analog system.
- Develop circuit insight through brief peeks at some nifty little circuits
The circuit world is filled with many little gems that every competent designer ought to know.

ECE1371

3-2


Date	Lecture	Ref	Homework
2008-01-07	RS 1 Introduction: MOD1 & MOD2	S&T 2-3, A	Matlab MOD2
2008-01-14	RS 2 Example Design: Part 1	S&T 9.1, J&M 10	Switch-level sim
2008-01-21	RS 3 Example Design: Part 2	J&M 14	Q-level sim
2008-01-28	TC 4 Pipeline and SAR ADCs		Arch. Comp.
2008-02-04	ISSCC– No Lecture		
2008-02-11	RS 5 Advanced $\Delta\Sigma$	S&T 4, 6.6, 9.4, B	$\Delta\Sigma$ Toolbox; Proj.
2008-02-18	Reading Week– No Lecture		
2008-02-25	RS 6 Comparator & Flash ADC	J&M 7	
2008-03-03	TC 7 SC Circuits	J&M 10	
2008-03-10	TC 8 Amplifier Design		
2008-03-17	TC 9 Amplifier Design		
2008-03-24	TC 10 Noise in SC Circuits	S&T C	
2008-03-31	Project Presentation		
2008-04-07	TC 11 Matching & MM-Shaping		Project Report
2008-04-14	RS 12 Switching Regulator		Q-level sim

ECE1371

3-3

NLCOTD: Non-Overlapping Clock Generator

- Our SC circuits require two non-overlapping clocks. How do we generate them?

 

ECE1371


3-4

Highlights


(i.e. What you will learn today)

- 1 Transistor-level implementation of MOD2 op-amp, SC CMFB, comparator, clock generator
- 2 MOD2 variants
- 3 Variable quantizer gain

Review: MOD2 Standard Block Diagram

 

Scaled Block Diagram

 


ECE1371

3-5

ECE1371

3-6

Review: Schematic

 


- 1st-stage capacitor sizes set for SNR = 100 dB @ OSR = 500 and -3-dBFS input
 $V_{ref} = 1V$ and the full-scale input range is $\pm 1V$.
- 2nd-stage capacitor sizes set by minimum allowable capacitance

ECE1371

3-7

Review: Simulated Spectrum

 

ECE1371

3-8

Review: Implementation Summary


- ✓ 1 Choose a viable SC topology and manually verify timing
- ✓ 2 Do dynamic-range scaling
 You now have a set of capacitor ratios.
 Verify operation.
- ✓ 3 Determine absolute capacitor sizes
 Verify noise.
- 4 Determine op-amp specs and construct a transistor-level schematic
 Verify.
- 5 Layout, fab, debug, document, get customers, sell by the millions, go public, ...

ECE1371

3-9

Effect of Finite Op Amp Gain Linear Theory

- Suppose that the amplifier has finite DC gain A . Define $\mu = 1/A$.
- To determine the effect on the integrator pole, let's look at our SC integrator with zero input:

 

ECE1371

3-10


- A fraction of q_2 leaks away each clock cycle:

$$q_2(n+1) = (1 - \epsilon)q_2(n),$$

$$\text{where } \epsilon = \mu C_1 / C_2$$

- Thus, the integrator is lossy, with a pole at $z = 1 - \epsilon$

Q: How big can ϵ get before the effect becomes significant?

 

ECE1371

3-11

Op Amp Gain Requirement Linear Theory

- According to the linear theory, finite op amp gain should not degrade the noise significantly as long as

$$A > (C_1 / C_2)(OSR / \pi)$$

- For our implementation of MOD2, in which $C_1 / C_2 = 1/4$ and $OSR = 500$, this leads to $A > 40 = 32 \text{ dB}$, which is quite a lax requirement!

- As OSR is decreased, the gain requirement goes down


ECE1371

3-12

Op Amp Transconductance

Settling time

- Model the op amp as a simple g_m :

 

- This is a single-time-constant-circuit with $\tau = C_{eff}/(\beta g_m)$

Settling Requirements

- If g_m is linear, incomplete settling has the same effect as a coefficient error and thus g_m can be very low
- In practice, the g_m is not linear and we need to ensure nearly complete settling
- As a worst case scenario, let's require transients to settle to 1 part in 10^5
This should be more than enough for -100 dBc distortion.

Settling Requirements (cont'd)

- If linear settling is allocated 1/4 of a clock period, we want $\exp(-\frac{T/4}{\tau}) = 10^{-5}$, or $\tau = \frac{T}{4 \ln 10^5} = 20 \text{ ns}$

and thus $g_m = \frac{C_{eff}}{\beta \tau} = \frac{C_{eff}}{\beta} 4 f_s \ln 10^5$

- For INT1 of our MOD2:


$C_{eff} = 0.5 \left(\frac{4p \cdot 1.33p}{4p + 1.33p} + 30f \right) = 0.5 \text{ pF}^*$
 $\beta = 3/4$
 $f_s = 1 \text{ MHz}$

$\Rightarrow g_m = 30 \mu\text{A/V}$

*. 0.5 comes from the single-ended to differential translation.

Slewing

 
- The maximum charge transferred through C1 is



- If we require the slew current to be enough to transfer q_{max} in 1/4 of a clock period, then

$I_{slew} = \frac{q_{max}}{T/4} \approx 5 \mu\text{A}$


Building Block– Op Amp

 

- Folded-cascode op-amp with switched-capacitor common-mode feedback


Op-Amp Design— Bias Current

Bias Currents

 

- Slew constraint dictates $I > 5 \mu\text{A}$

Op-Amp Design— gm

 


- Square-law MOSFET model: $g_{m1} = (2I_D)/(\Delta V)$
- $I_D = 5 \mu\text{A}$, $g_m \geq 30 \mu\text{A/V} \Rightarrow \Delta V \leq 0.33 \text{ V}$
 Usually $\Delta V \approx 200 \text{ mV}$, so we should be able to get high enough g_m .

ECE1371

3-19

Transistor Sizes & Bias Point

 


- Allowable swing is $+0.6 \text{ V}$, -0.75 V
- Simulated $g_m = 36 \mu\text{A/V}$, $A = 48 \text{ dB}$
 g_m is high enough and the gain is $6\times$ required.

ECE1371

3-20

Ideal Common-Mode Feedback

 


- Can use this circuit to speed up the simulation

ECE1371

3-21


Simulated Waveforms

 

ECE1371

3-22


Expanded Waveforms

 

ECE1371

3-23

Simulated Spectrum

 


- This was too easy!
 Although this one simulation *did* take an hour.

ECE1371

3-24

 SC Common-Mode Feedback Common-Mode 1/2-Circuit




- $V_{ocrm} = V_{cm} + V_{gs1} - V_1$
If $V_1 = V_{gs1}$, then $V_{ocrm} = V_{cm}$.

ECE1371

3-25

Latched Comparator

 


- Falling phase 1 initiates regenerative action
S and R connected to a Set/Reset latch.

ECE1371

3-26

Switch Resistance Sampling Phase

 


- If R_{sw} is constant, it has only a filtering (linear) effect, which is benign
 - Unfortunately, the on-resistance of MOS switches varies with V_{gs} (and hence V_{in})
- ⇒ Must make MOS switches large enough

ECE1371

3-27

Switch Resistance Integration Phase

 


- R_{sw} increases the settling time by a factor of $1 + 4g_m R_{sw}$
- ⇒ Set $R_{sw} \leq \frac{1}{40g_m}$ to make the increase in τ small
- So in our MOD2, we want $R_{sw} \leq 0.75 \text{ k}\Omega$
BTW, my simulation used $R_{sw} = 1 \text{ k}\Omega$ and was OK.

ECE1371

3-28


NLCOTD: Non-Overlapping Clock Generator

 

ECE1371

3-29

State Diagram

 

Truth Table

CK	P1	P2	P1'	P2'
0	0	1	0	1
1	0	1	0	0
1	0	0	1	0
1	1	0	1	0
0	1	0	0	0
0	0	0	0	1

ECE1371

3-30

Karnaugh Maps

P1':

P1P2 \ CK	00	01	11	10
0	0	0	X	0
1	1	0	X	1

$$P1' = CK \cdot \overline{P2} \\ = \overline{\overline{CK} + P2}$$

P2':



P1P2 \ CK	00	01	11	10
0	1	1	X	0
1	0	0	X	0

$$P2' = \overline{CK} \cdot \overline{P1} \\ = \overline{CK + P1}$$

ECE1371

3-31

Non-Overlapping Clock Generator

  


- Non-overlap time set by NOR's t_{PLH}

ECE1371

3-32

Clocking Details— Early/Late Phases

 


- Charge injected via M1 is (non-linearly) signal-dependent, whereas charge injection from M2 is signal-independent
- ⇒ Open M2 (early) then open M1 (late) so that charge injected from C_{gs1} cannot enter C1

ECE1371

3-33

Clocking Details— Bottom-plate sampling

 

- Parasitic capacitance on the right terminal of C1 degrades the effectiveness of early/late clocking
- C_p for the top plate is smaller, so use the top plate for the right terminal and the bottom plate for the left

ECE1371

3-34

Complementary Clock Alignment

- We need complementary clocks if transmission gates are used for the switches

Q: How do we align them?


A: Carefully size the inverters relative to their capacitive loads, or use a transmission gate to mimic an inverter delay:



ECE1371

3-35

Professional Clock Generator

 

- To maximize the time available for settling, make the early and late phases start at the same time

ECE1371

3-36


Review: Implementation Summary

- ✓ 1 Choose a viable SC topology and manually verify timing
- ✓ 2 Do dynamic-range scaling
- ✓ 3 Determine absolute capacitor sizes
- ✓ 4 Determine op-amp specs and construct a transistor-level schematic
Verify. Verify. Verify.
- 5 Layout, fab, debug, document, get customers, sell by the millions, go public, ...
This last step is an "exercise for the reader."

ECE1371

3-37

Topological Variant– Feed-Forward

 


- + Output of first integrator has no DC component
Dynamic range requirements of this integrator are relaxed.
- Although $|STF| \approx 1$ near $\omega = 0$,
 $|STF| = 3$ for $\omega = \pi$
Instability is more likely.

ECE1371

3-38

 Topological Variant– Feed-Forward with Extra Feed-In




- + No DC component in either integrator's output
Reduced dynamic range requirements in both integrators, esp. for multi-bit modulators.
- + Perfectly flat STF
No increased risk of instability.
- Timing is tricky

ECE1371

3-39

Topological Variant– Error Feedback

 

- + Simple
- Very sensitive to gain errors
Only suitable for digital implementations.

ECE1371

3-40


Is MOD2 The Only 2nd-Order Modulator?

- Except for the filtering provided by the STF, any modulator with the same NTF as MOD2 has the same input-output behavior as MOD2
SQNR curve is the same.
Tonality of the quantization noise is unchanged.
 - Internal states, sensitivity, thermal noise etc. can differ from realization to realization
- BUT, in terms of input-output behavior,
- A 2nd-order modulator is truly different only if it possesses a truly different (2nd-order) NTF

ECE1371

3-41


A Better 2nd-Order NTF

 

ECE1371

3-42


NTF Comparison

 

ECE1371

3-43


SNR vs. Amp Comparison

 

ECE1371

3-44


MOD2 Internal Waveforms Input @ 75% of FS

 

ECE1371

3-45


MOD2b Internal Waveforms Input @ 75% of FS

 

ECE1371

3-46

Gain of a Binary Quantizer

 

- The effective gain of a binary quantizer is not known a priori
- The gain (k) depends on the statistics of the quantizer's input
Halving the signal doubles the gain.

ECE1371

3-47


Gain of the Quantizer in MOD2

- The effective gain of a binary quantizer can be computed from the simulation data using

$$k = \frac{E[|y|]}{E[y^2]} \text{ [S\&T Eq. 2.5]}$$

- For the simulation of 1-35, $k = 0.63$
- $k \neq 1$ alters the NTF:


$$NTF_k(z) = \frac{NTF_1(z)}{k + (1-k)NTF_1(z)}$$

 

ECE1371

3-48

Revised PSD Prediction

 

- Agreement is now excellent

ECE1371

3-49

Variable Quantizer Gain

- When the input is small (below -12 dBFS), the effective gain of MOD2's quantizer is $k = 0.75$
- MOD2's "small-signal NTF" is thus

$$NTF(z) = \frac{(z-1)^2}{z^2 - 0.5z + 0.25}$$
- This NTF has 2.5 dB less quantization noise suppression than the $(1-z^{-1})^2$ NTF derived from the assumption that $k = 1$
 - Thus the SQNR should be about 2.5 dB lower than ✕.
- As the input signal increases, k decreases and the suppression of quantization noise degrades
 - SQNR increases less quickly than the signal power. Eventually the SQNR saturates and then decreases as the signal power reaches full-scale.

ECE1371

3-50

Homework #3

- 1 Design amplifiers for your MOD2 of Homework #2 and verify your ADC. Use $f_s = 10$ MHz. You may assume ideal comparator, switches, biasing and common-mode feedback.
- 2 Using your MOD2 model from Homework #1, compute and plot the effective gain of the quantizer as a function of the DC input. Also compare the simulated spectrum for MOD2 with the "predicted" spectrum for a -3 -dBFS sine-wave.
- 3 Bonus: Create a circuit which generates 3 non-overlapping phases of width $\sim T$ given a clock of period T . See if you can do the same for a clock of period $2T$. Demonstrate that your circuit works in simulation.

ECE1371

3-51

What You Learned Today And what the homework should solidify

- 1 Transistor-level implementation of MOD2 op-amp, SC CMFB, comparator, clock generator
- 2 MOD2 variants
- 3 Variable quantizer gain

ECE1371

3-52

Op Amp Gain Requirement Nonlinear Theory 1

- MOD2 has a "deadband" around $u = 0$ whose width is approximately

$$\frac{0.5(a_1 c_1) + a_2}{A^2} = \frac{0.5((1/3) \cdot (1/3)) + (1/9)}{A^2} = \frac{1}{6A^2}$$

- To make the deadband less than 1 "LSB" wide,

$$\frac{1}{6A^2} < \text{undbv}(-100) = 10^{-5},$$

or $A > 400 = 52$ dB

- Since we didn't need so much gain to get excellent AC performance, this calculation looks like it is conservative

ECE1371

3-53

Op Amp Gain Requirements Nonlinear Theory 2

- Finite DC gain \Rightarrow incomplete charge transfer
- The gain is a nonlinear function, so the residual charge is nonlinearly related to the output voltage of the amplifier
 - The residual charge is akin to noise.
- However, if the amplifier output contains signal components, then nonlinear gain can result in harmonic distortion
 - The feedforward topology is known to yield low distortion even when the amplifier gain is low.
- The effects are difficult to quantify analytically, and so we typically rely on simulations

ECE1371

3-54