

ECE1371 Advanced Analog Circuits  
Lecture 7

# SWITCHED CAPACITOR CIRCUITS

Richard Schreier  
richard.schreier@analog.com

Trevor Caldwell  
trevor.caldwell@utoronto.ca

Date		Lecture	Ref	Homework
2008-01-07	RS 1	Introduction: MOD1 & MOD2	S&T 2-3, A	Matlab MOD2
2008-01-14	RS 2	Example Design: Part 1	S&T 9.1, J&M 10	Switch-level sim
2008-01-21	RS 3	Example Design: Part 2	J&M 14, S&T B	Q-level sim
2008-01-28	TC 4	Pipeline and SAR ADCs	J&M 11,13	Pipeline DNL
2008-02-04		ISSCC – No Lecture		
2008-02-11	RS 5	Advanced $\Delta\Sigma$	S&T 4, 6.6, 9.4, B	CTMOD2; Proj.
2008-02-18		Reading Week – No Lecture		
2008-02-25	RS 6	Comparator and Flash ADC	J&M 7	
2008-03-03	TC 7	SC Circuits	Raz 12, J&M 10	
2008-03-10	TC 8	Amplifier Design		
2008-03-17	TC 9	Amplifier Design		
2008-03-24	TC 10	Noise in SC Circuits	S&T C	
2008-03-31		Project Presentations		
2008-04-07	TC 11	Matching & MM-Shaping		
2008-04-14	RS 12	Switching Regulator		Project Report

ECE1371

7-3

## Highlights

(i.e. What you will learn today)

1. Motivation for SC Circuits
2. Basic sampling switch and charge injection errors
3. Fundamental SC Circuits  
Sample & Hold, Gain and Integrator
4. Other Circuits  
Bootstrapping, SC CMFB

ECE1371

7-5

## Course Goals


- Deepen Understanding of CMOS analog circuit design through a top-down study of a modern analog system  
The lectures will focus on Delta-Sigma ADCs, but you may do your project on another analog system.
- Develop circuit insight through brief peeks at some nifty little circuits  
The circuit world is filled with many little gems that every competent designer ought to recognize.

ECE1371

7-2

## NLCOTD: Schmitt Trigger

 Problem: Input is noisy or slowly varying



How do we turn this into a clean digital output?

ECE1371

7-4

## Why Switched Capacitor?

- Used in discrete-time or sampled-data circuits  
Alternative to continuous-time circuits
- Capacitors instead of resistors  
Capacitors won't reduce the gain of high output impedance OTAs  
No need for low output impedance buffer to drive resistors
- Accurate frequency response  
Filter coefficients determined by capacitor ratios (rather than RC time constants) and clock frequencies  
Capacitor matching on the order of 0.1% - when the transfer characteristics are a function of only a capacitor ratio, it can be very accurate  
RC time constants vary by up to 20%

ECE1371

7-6

## Basic Building Blocks


- **Opamps**  
Ideal usually assumed  
Some important non-idealities to consider include:
  1. DC Gain: sets the accuracy of the charge transfer, how 'grounded' the virtual ground is
  2. Unity-gain freq, Phase Margin & Slew Rate: determines maximum clock frequency
  3. DC Offsets: circuit techniques to combat this and 1/f noise – Correlated Double Sampling, Chopping
- **Capacitors**  
Large absolute variation, good matching  
Large bottom plate capacitor adds parasitic cap

ECE1371

7-7

## Basic Building Blocks

- **Switches**  
MOSFET switches are good – large off resistance ( $G\Omega$ ), small on resistance ( $100\Omega - 5k\Omega$ , depending on transistor sizing)  
MOSFET switches have non-linear parasitic capacitors
- **Non-Overlapping Clocks**  
Clocks are never on at the same time  
Required so that charge is never lost/shared  
Clock Generator previously discussed

 


ECE1371


7-8
 
## Basic Sampling Switch

- **MOSFET used as sample-and-hold**  
When CLK is HIGH,  $V_{OUT}$  follows  $V_{IN}$  through the low-pass filter created by  $R_{ON}$  and C  
 $R_{ON}$  varies depending on  $V_{IN}$ ,  $V_{OUT}$ , and  $V_{DD}$



When CLK is LOW,  $V_{OUT}$  holds the value on C

 


ECE1371

7-9
 
## On-Resistance Variation

- With an NMOS sampling switch, as  $V_{IN}$  approaches  $V_{DD} - V_{TH}$ ,  $R_{ON}$  increases dramatically  
In smaller technologies, as  $V_{DD}$  decreases the swing on  $V_{IN}$  is severely limited

$$R_{ON} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{DD} - V_{IN} - V_{TH})}$$



Sampling switch must be sized for worst case  $R_{ON}$  so that the bandwidth is still sufficient

ECE1371


7-10

## On-Resistance Variation

- PMOS switches suffer from the same problem as  $V_{IN}$  approaches  $V_T$
- Complementary switch can allow rail-to-rail input swings

Ignoring variation of  $V_{TH}$  with  $V_{IN}$ ,  $R_{ON,eq}$  is constant with  $V_{IN}$  if

$$\mu_n C_{ox} \frac{W}{L} = \mu_p C_{ox} \frac{W}{L}$$

 

ECE1371

7-11

## Settling Accuracy

- Two situations to consider
  - 1) Discrete-time signal  
When analyzing a signal within the switched-capacitor circuit (for example, at the output of the first OTA)
  - 2) Continuous-time signal  
When analyzing a signal that is sampled at the input

ECE1371

7-12

## Settling Accuracy – DT

- Discrete-Time Signal

Settling Error =  $e^{-T/4RC}$

For N-bit accuracy in T/4 seconds

$$R_{ON}C < \frac{T}{4N \ln 2}$$


This is the maximum  $R_{ON}$  (for a given C)

- Example:

Assume 1 GHz to 4 GHz variation of  $\frac{1}{2\pi R_{ON}C}$

Input sinusoidal signal at 50 MHz

For  $f_s=100\text{MHz}$ ,  $N=22$  bits with discrete-time signal (typically you are limited by the OTA)

 

ECE1371

7-13

## Settling Accuracy – CT

- Continuous-Time Signal

$R_{ON}C$  acts as a low-pass filter and introduces amplitude and phase change

Variations in the input signal size cause variations in  $R_{ON}$ , causing distortion in the sampled signal

Both the amplitude and phase vary – which one causes distortion?

ECE1371


7-14

## Amplitude Error

- Less significant error

Due to variation in magnitude of low-pass filter

At 50 MHz (with same  $R_{ON}C$  variation as DT case), maximum possible error is 0.1%

 

ECE1371


7-15

## Distortion in sampled CT input

- Input ~50 MHz, sampled at 100MHz

Distortion at 57dB, or ~9 bits

This is larger than the maximum possible error due to amplitude variation

 

ECE1371


7-16

## Phase Error

- More significant error

Due to variation in phase of low-pass filter

At 50 MHz (with same  $R_{ON}C$  variation as DT case), maximum possible error is a few percent - error is less than that

 

ECE1371

7-17

## Charge Injection

- When a transistor turns off, the channel charge  $Q_{CH}$  goes into the circuit

Doesn't exactly divide in half - depends on impedance seen at each terminal and the clock transition time

$$Q_{CH} = WLC_{ox}(V_{DD} - V_{IN} - V_{TH})$$

- Charge into  $V_{IN}$  has no impact on output node

Doesn't create error in the circuit

- Charge into C causes error  $\Delta V$  in  $V_{OUT}$

$$\Delta V = \frac{Q_{CH}}{2C} = \frac{WLC_{ox}(V_{DD} - V_{IN} - V_{TH})}{2C}$$

ECE1371

7-18

## Charge Injection

- In previous analysis, charge injection introduces a gain and offset error  
This is still linear and could be tolerated or corrected

$$V_{OUT} = V_{IN} - \Delta V$$

$$= V_{IN} \left( 1 + \frac{WLC_{ox}}{2C} \right) - \frac{WLC_{ox}(V_{DD} - V_{TH})}{2C}$$

- But...  
 $V_{TH}$  is actually a function of  $\sim \sqrt{V_{IN}}$   
Introduces non-linear term that cannot be corrected in the circuit

ECE1371

7-19

## Charge Injection vs. Speed

- Charge injection  
Proportional to transistor size (WL)
- Speed  
 $R_{ON}$  inversely proportional to aspect ratio (W/L)
- Figure of Merit  
Product of speed (1/ $\tau$ ) and charge injection (1/ $\Delta V$ )

$$(\tau \Delta V)^{-1} = \left( \frac{C}{\mu_n C_{ox} (W/L) (V_{DD} - V_{IN} - V_{TH})} \right)^{-1} \left( \frac{WLC_{ox}(V_{DD} - V_{IN} - V_{TH})}{C} \right)^{-1}$$


$$= \frac{\mu_n}{L^2}$$

ECE1371

7-20

## Clock Feedthrough

- Overlap capacitance allows clock to couple from the gate to drain/source terminals  
Change in voltage  $\Delta V$  independent of the input signal  
Error is an offset voltage which is cancelled with differential operation

 

ECE1371

7-21

## Charge Error Cancellation


- Differential operation  
Cancels offset errors, depending on the matching between differential circuits  
Applies to signal dependent portion of charge injection error, and clock feedthrough error
- Complementary Switches  
Error cancelled for 1 input level  
 $W_n L_n C_{ox} (V_{CLK} - V_{IN} - V_{THN}) = W_p L_p C_{ox} (V_{IN} - |V_{THP}|)$   
Clock feedthrough cancelled depending on similarity of overlap capacitance for PMOS and NMOS switches

ECE1371

7-22

## Charge Error Cancellation

- Dummy Switch  
Use second transistor to remove charge injection by main transistor  
Inverted clock operates on dummy switch  
Charge from M1:  $q_{M1} = W_1 L_1 C_{ox} (V_{CK} - V_{IN} - V_{TH1}) / 2$   
Charge from M2:  $q_{M2} = W_2 L_2 C_{ox} (V_{CK} - V_{IN} - V_{TH2})$   
If charge splits equally in M1 (not quite true), then with M2 half the size of M1,  $q_{M1} = q_{M2}$

 


ECE1371

7-23
 
## Sample and Hold Amplifier

- Input dependent charge from  $S_1$  onto C  
When  $S_1$  turns off, charge  $q$  adds to C  
 $V_{OUT}$  is then equal to  $V_{IN} + q/C$  where  $q$  has a non-linear dependence on  $V_{IN}$




We can improve on this by making  $V_{OUT}$  independent of sampling switch charge...

ECE1371

7-24

## S/H Amplifier

- Two phases
  - Phase 1:  $S_1$  and  $S_2$  closed,  $V_{IN}$  sampled on C
  - Phase 2:  $S_3$  closed, C is tied to  $V_{OUT}$
- Phase 1
  - Charge on C is  $CV_{IN}$
  - $S_2$  opens, injecting signal indep. charge at node X
  - Then  $S_1$  opens, injecting signal dependent charge q onto  $C + C_p$

 


ECE1371

7-25
 
## S/H Amplifier

- Phase 2
  - Node X is a virtual ground and charge on  $C_p$  is zero
  - Charge on C is still  $CV_{IN}$
  - $S_3$  injects charge on X that must be discharged due to virtual ground node – it does not disturb charge on C
  - $\therefore V_{OUT} = V_{IN}$



$S_1 / S_3$  are non-overlapping,  $S_2$  slightly ahead of  $S_1$

ECE1371


7-26

## Gain of the S/H

- Finite OTA gain reduces gain of sampler
  - On Phase 1, C charges to  $V_{IN}$
  - On Phase 2, node X goes from 0 to  $V_X = -V_{OUT}/A$
  - Charge comes from C, changing  $q_C$  to  $CV_{IN} + C_p V_X$
  - $V_{OUT} - (CV_{IN} + C_p V_X)/C = V_X$

$$V_{OUT} = \frac{V_{IN}}{1 + \frac{1}{A} \left( \frac{C_p}{C} + 1 \right)}$$

$$\approx V_{IN} \left[ 1 - \frac{1}{A} \left( \frac{C_p}{C} + 1 \right) \right]$$

 


ECE1371

7-27

## Speed of the S/H

- In sampling mode (Phase 1)
  - At node X,  $R_X \sim 1/G_m$ ,  $\tau_1 \sim (R_{on1} + 1/G_m)C$
- In amplification mode (Phase 2)
  - Replace charge on C by voltage source  $V_{IN}$  (like switching in voltage source at start of Phase 2)
  - After analysis,  $\tau_2 = (C_L C_p + C_p C + CC_L)/G_m C$
  - Reduces to  $\tau_2 \sim C_L/G_m$  if  $C_p$  is small

 


ECE1371

7-28

## Basic Amplifier

- Sampling phase when  $S_1$  and  $S_2$  closed
  - Input signal sampled onto  $C_1$
- Amplifying phase when  $S_3$  closed
  - Charge on  $C_1$  transferred to  $C_2$  so that the final output is  $V_{OUT} = \frac{C_1}{C_2} V_{IN}$

 


ECE1371

7-29

## Basic Amplifier

- $S_2$  must open before  $S_1$  for the charge injection to be signal independent
  - Charge from  $S_2$  opening is deposited on  $C_1$ , but is not signal dependent
  - Charge from  $S_1$  opening causes glitch in  $V_{OUT}$
  - When  $S_3$  closes,  $V_{OUT}$  goes to final value, regardless of what happened between  $S_2$  opening and  $S_3$  closing

 


ECE1371

7-30

## Precision Gain-2

- **Sampling phase** when  $S_1, S_2, S_3$  closed  
Input signal sampled onto  $C_1$  and  $C_2$
- **Amplifying phase** when  $S_4, S_5$  closed  
Charge on  $C_1$  is transferred to  $C_2$ , doubling the charge on  $C_2$   
Final output is  $2V_{IN}$  since  $C_1 = C_2$

 

ECE1371

7-31

## Precision Gain-2

- **How is it more precise?**  
The feedback factor in both gain circuits is

$$\frac{C_2}{C_2 + C_1 + C_p}$$

In the precision Gain-2 circuit,  $C_1 = C_2$ , while the basic amplifier has  $C_1 = 2C_2$ , resulting in a smaller feedback factor and a slower circuit


The gain error is inversely proportional to the feedback factor, so the precision circuit is more accurate for a given amplifier gain A

$$\frac{V_{OUT}}{V_{IN}} \approx 2 \left( 1 - \frac{C_2 + C_1 + C_p}{AC_2} \right)$$

ECE1371

7-32

## Resistor Equivalence of SC

 

- **Average current through switched-capacitor**

$$\phi_1 : Q_1 = CV_1 \quad \phi_2 : Q_2 = CV_2$$

$$I_{AVG} = \frac{Q_1 - Q_2}{T} = \frac{C(V_1 - V_2)}{T}$$

- **Equivalent current through a resistor ( $f_{IN} \ll f_S$ )**


$$I_{EQ} = \frac{V_1 - V_2}{R_{EQ}}$$

$$R_{EQ} = \frac{T}{C} = \frac{1}{Cf_S}$$

ECE1371

7-33

## Switched-Capacitor Integrator

 


- **Two non-overlapping clock phases control  $s_1, s_2$**   
Phase 1: Sampling phase – input is sampled onto capacitor  $C_1$   
Phase 2: Integrating phase – additional charge is added to previous charge on  $C_2$

ECE1371

7-34

## Switched-Capacitor Integrator

 

- **Final charge on L.S. of  $C_2$  is  $+V_0[n+1]C_2$**

$$+V_0[n+1]C_2 = +V_0[n]C_2 - V_1[n]C_1$$


$$zV_0(z)C_2 = V_0(z)C_2 - V_1(z)C_1$$

$$\frac{V_0(z)}{V_1(z)} = -\frac{C_1}{C_2} \frac{1}{z-1}$$

ECE1371

7-35

## Parasitic Sensitive

 


- Parasitic capacitances  $C_{p1}, C_{p3}$  and  $C_{p4}$  have no impact on transfer function
- $C_{p2}$  in parallel with  $C_1$ , changes transfer function

$$\frac{V_0(z)}{V_1(z)} = -\frac{(C_1 + C_{p2})}{C_2} \frac{1}{z-1}$$

ECE1371

7-36

## Parasitic Insensitive

 

- Transfer function is non-inverting, delaying

$$\frac{V_O}{V_I}(z) = \frac{C_1}{C_2} \frac{1}{z-1}$$

ECE1371

7-37


## Parasitic Insensitive

- Parasitics have no impact on transfer function  
Better linearity since non-linear capacitors are unimportant
- Top plate on virtual ground node  
Minimizes parasitics, improves amplifier speed and resolution, reduces noise coupled to node
- Two extra switches needed  
More power to drive the switches for the same on-resistance

ECE1371

7-38

## Delay-Free Integrator

 

- Same structure, still parasitic insensitive
- Transfer function is inverting, delay-free

$$\frac{V_O}{V_I}(z) = -\frac{C_1}{C_2} \frac{z}{z-1}$$

ECE1371

7-39

## Bootstrapping

- At low supply voltages, signal swing is limited  
Maximum distortion determines the tolerable variation in  $R_{ON}$ , and this limits the signal swing
- Want to increase  $V_{GS}$  on the sampling switch  
Can do this by increasing the supply voltage for the sampling switch, but this requires slower thick oxide devices  
Alternatively, add a constant voltage to the input signal and use that as the gate voltage – keep  $V_{GS}$  constant, reducing the variation in  $R_{ON}$


ECE1371

7-40

## Bootstrapped Circuit

- Basic operation  
 $\phi_2$ : C is charged to  $V_{DD}$  and gate of sampling switch is discharged to  $V_{SS}$  (turned off)  
 $\phi_1$ :  $V_{IN}$  is added to voltage across C, sampling switch turns on, gate voltage of the sampling switch is  $V_{IN} + V_{DD}$

Ideally, there is always  $V_{GS} = V_{DD}$  for the sampling switch

 

ECE1371

7-41

## Bootstrapped Circuit

- C must be sized so that charge sharing between gate capacitance of switch is not significant

$$V_G = V_{IN} + \frac{C}{C + C_G} V_{DD}$$

- Rise time controlled by size of  $S_4$ , fall time controlled by size of  $S_5$

- Extra transistors required to limit gate-source voltages to  $V_{DD}$  and prevent overstress  
See Dessouky, JSSC Mar.2001

ECE1371


7-42

# Switched-Capacitor CMFB

- Two parts to the circuit
  - First, sense the common mode of the output
  - Second, compare the common mode to the expected common mode, and adjust the bias accordingly
- Sensing
  - Could use 2 resistors – they are either too small and reduce the gain, or they can get prohibitively large
  - Could use 2 capacitors – they don't reduce the gain, but the voltage across them is undefined
  - The voltage across them can be refreshed every clock cycle
 
# Switched-Capacitor CMFB


- One alternative...
  - Phase 1: precharge capacitors to ideal value
  - Phase 2: sense the difference and adjust the bias accordingly



But... there may be large changes in the tail current bias

 
# Switched-Capacitor CMFB

- Solution: Part of the tail current source can be controlled by a constant bias voltage
  - Will this work?


 
# Switched-Capacitor CMFB

- Alternatively, use 2 capacitors so that only a fraction of the charge is shared to adjust the bias voltage
  - Typically,  $C_2$  is 4-10 times  $C_1$



# NLCOTD: Schmitt Trigger

# What You Learned Today

- Errors introduced with simple sampling switch
  - RON variation, charge injection
- Main SC Circuits – S/H, Gain and Integrators
  - Parasitic Insensitive
  - Signal-independent charge injection
- Bootstrapped Circuit
- Switched Capacitor CMFB