

**ECE1371 Advanced Analog Circuits
Lecture 9**

AMPLIFIER DESIGN

Richard Schreier

`richard.schreier@analog.com`

Trevor Caldwell

`trevor.caldwell@utoronto.ca`


Course Goals

- **Deepen Understanding of CMOS analog circuit design through a top-down study of a modern analog system**
The lectures will focus on Delta-Sigma ADCs, but you may do your project on another analog system.
- **Develop circuit insight through brief peeks at some nifty little circuits**
The circuit world is filled with many little gems that every competent designer ought to recognize.

Date	Lecture		Ref	Homework	
2008-01-07	RS	1	Introduction: MOD1 & MOD2	S&T 2-3, A	Matlab MOD2
2008-01-14	RS	2	Example Design: Part 1	S&T 9.1, J&M 10	Switch-level sim
2008-01-21	RS	3	Example Design: Part 2	J&M 14, S&T B	Q-level sim
2008-01-28	TC	4	Pipeline and SAR ADCs	J&M 11,13	Pipeline DNL
2008-02-04	ISSCC – No Lecture				
2008-02-11	RS	5	Advanced $\Delta\Sigma$	S&T 4, 6.6, 9.4, B	CTMOD2; Proj.
2008-02-18	Reading Week – No Lecture				
2008-02-25	RS	6	Comparator and Flash ADC	J&M 7	
2008-03-03	TC	7	SC Circuits	Raz 12, J&M 10	
2008-03-10	TC	8	Amplifier Design		
2008-03-17	TC	9	Amplifier Design		
2008-03-24	TC	10	Noise in SC Circuits	S&T C	
2008-03-31	RS	11	Switching Regulator		
2008-04-07	Project Presentations				
2008-04-14	TC	12	Matching & MM-Shaping		Project Report

NLCOTD: Ring Oscillators

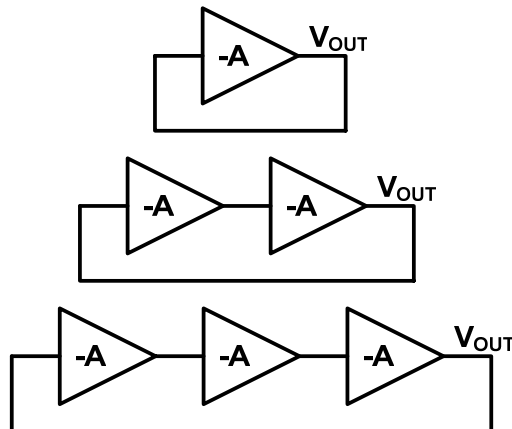- Which of these circuits will oscillate?



Highlights

(i.e. What you will learn today)

1. How to design a folded-cascode OTA
2. Learn important trade-offs for OTA design
Including simulated examples
3. Gain-boosting design example for OTA

ECE1371

9-5

Design Specifications

- **Amplifier for 12-bit, 100MHz Pipeline ADC**
1.5bit/stage => Closed-loop gain of 2
- **Target Bandwidth: 100MHz**
T=10ns
Assume ~1.5ns rise/fall/non-overlap time
Try to settle within < 3.5ns
Settling Error < -80dB
If it is a critically damped system where $\omega_{p2} = 4\beta\omega_{unity}$
 $\beta\omega_{unity} = 500\text{MHz}$ to settle in 2ns
If it is single-pole settling
 $\beta\omega_{unity} = 500\text{MHz}$ to settle in 3ns

ECE1371

9-6

Design Specifications

- **Target Gain $A\beta$: 75 dB**
Input-referred error must be better than 12-bit
With all the other sources of error, put it at 13-bit
(kT/C noise is ~ 12.3 -bit)
- **Swing: ± 800 mV differential**
Assume noise has been calculated based on this swing requirement
Input signal ± 800 mV differential
Output signal will also be ± 800 mV differential
Each side of the OTA should swing from CM ± 400 mV (output CM will be around 900mV)

ECE1371

9-7

Design Specifications

- **Capacitor Sizing**
Based on noise requirements
 $C_1 = 2$ pF
 $C_2 = 1$ pF
 $C_L = 1$ pF
(assume 2nd stage is half the size of 1st stage – this means that input referred noise contribution is 3dB below the 1st stage)
- **Power**
Pipeline Target FOM: 160dB
 $74\text{dB} + 10\log_{10}(100\text{MHz}/P) = 160\text{dB}$
 $P = 250\text{mW}$

ECE1371

9-8

Amplifier Topology


- From Lecture 8...

Topology	Gain	Output Swing	Speed	Power Dissipation	Noise
Telescopic	Medium	Medium	Highest	Low	Low
Folded-Cascode	Medium	Medium	High	Medium	Medium
Two-Stage	High	Highest	Low	Medium	Low
Gain-Boosted	High	Medium	Medium	High	Medium

ECE1371

9-9

Folded-Cascode OTA

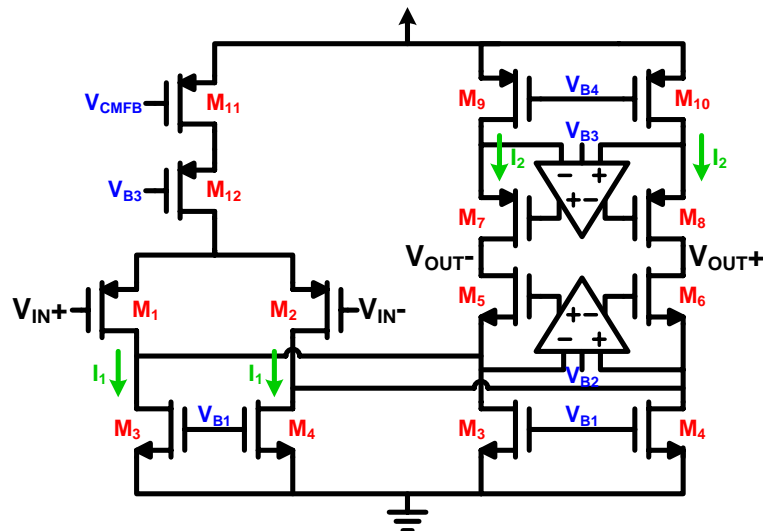


ECE1371

9-10

Biasing

- Use two wide-swing cascode current mirrors for V_{B3} , V_{B4} and V_{B1} , V_{B2}
 M_{B1} is n times smaller so that V_{EFF} is \sqrt{n} times bigger
- What if M_{B2} and M_{B3} are only a single finger?
 M_{B1} cannot be 5-6 times smaller

 

ECE1371

9-11

Amplifier Topology

- Why Folded-Cascode instead of Telescopic?
 - ✓ Better swing – with Telescopic, it is difficult to get the desired swing (assuming $V_{EFF} \sim 200\text{mV}$ + margins, and only 1.8V supply)
 - ✓ Low (or high) Input CM (saves power since switches are smaller)
 - ✗ Slower (lower non-dominant pole) and less power efficient

ECE1371

9-12

Amplifier Topology

- Why PMOS input pair? (we will see more of this)
 - ✓ Input CM: with PMOS input pair, input CM is lower, NMOS switches are used to pass the signal
 - ✓ Non-dominant pole: larger since folding node uses NMOS devices which have smaller capacitance for a given V_{EFF}
 - ✓ Flicker noise: smaller in PMOS devices (not too important in high-speed design)
 - ✗ Larger β in NMOS: For the same transconductance, the input capacitance from NMOS input devices will be smaller

ECE1371

9-13

Amplifier Topology

- How should currents I_1 and I_2 be ratioed?

Amplifier transconductance g_m is determined by the transconductance of M_1 and M_2 => high current I_1

Output impedance r_{OUT} is determined by the output impedance of M_3 - M_{10} => low current I_2

I_1 should not be too much larger than I_2 due to amplifier slewing (more on this...)

ECE1371

9-14

Amplifier Topology

- How should currents I_1 and I_2 be ratioed?

But... increased transconductance increases C_{IN} and decreases β

Recall (assuming no load capacitance C_L):


$$\beta\omega_{unity} = \frac{\beta g_m}{C_{L,eff}} = \frac{g_m}{C_1 + C_{IN}}$$

So... once C_{IN} approaches C_1 , $\beta\omega_{unity}$ does not increase linearly with g_m

Slewing

- Extra care must be taken if OTA slews

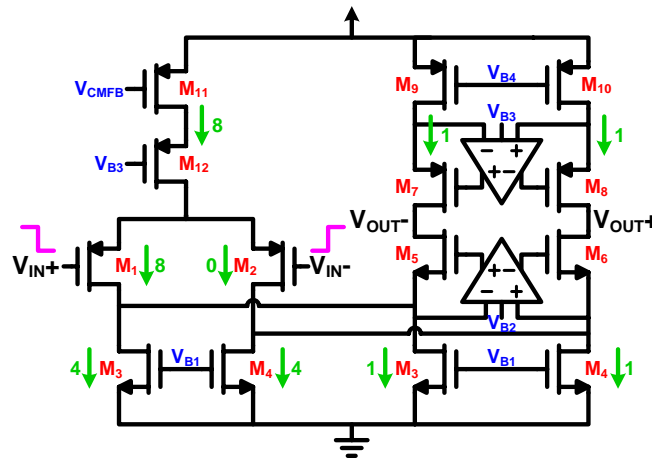Example: $I_1=4I_2$, Where does the excess current go?




Slewing


- M_4 absorbs current from capacitance at V_{OUT+} , M_1, M_{11}, M_{12} go into triode until the current is equal to $I_{D,M3}$
Capacitance at V_{OUT-} draws current from M_9
- Therefore, size the currents I_1 and I_2 the same
 $M_{1,2}$ can still be sized to increase transconductance
Slewing is no longer a major problem (can be more power efficient)
- More likely to happen when output changes are large (e.g. no signal, just noise in the output)

Aside: OTA Output Signal

- Input Feed-forward $\Delta\Sigma$

 

- Pipeline ADC Stage

 

Current Source

- **Why Cascode instead of Large L?**
Both can give a high output impedance...
 - ✓ Smaller capacitance to ground – increased impedance at high frequency, maintaining a higher CMRR (which is proportional to the tail current source impedance)
 - ✗ Larger voltage across transistors (doesn't matter in this case since there is lots of room for the input CM)
 - ✗ More complicated biasing (doesn't matter in this case since V_{B3} is already generated)

Transistor Lengths

- **Generally minimum channel length is not used**
Use ~1.5x minimum L for analog design
Moderately improves output impedance without sacrificing too much speed
Better matching between transistors
Reduce impact of short channel effects (threshold variation, mobility degradation, velocity saturation, DIBL, hot carrier effects)
- **If bandwidth is imperative, use minimum L**

Choosing V_{EFF}

- **Input Pair (M_1, M_2)**
 - Larger V_{EFF} means faster transistors, smaller transistors (increasing β)
 - Smaller V_{EFF} causes more slewing since it can easily be switched with large transients, but has lower noise and larger g_m
- **Current Source Transistors (M_3, M_4)**
 - Responsible for non-dominant pole
 - Larger V_{EFF} reduces noise and parasitic capacitances, improves non-dominant pole

Power

- **The power consumed by the 1st-stage OTA will be a significant fraction of the total power**
 - It will be a good indication of the FOM you'll be targeting for your design
- **Pipeline ADC**
 - With S/H, other stages, and other overhead (clocks, buffers, biasing, comparators, etc.) first stage will probably consume 25-30% of the total power
- **$\Delta\Sigma$ ADC**
 - Since other stages are smaller, but other overhead still exists (possibly a higher resolution quantizer), first stage will probably consume 40-60% of the total power

Quick Design / 1st Iteration


- 1:1 ratio between 1st and 2nd current branch
- Input transistor size: 9u/0.18um fingers
- Size every other transistor with a $V_{EFF} \sim 180mV$
 - PMOS: 55uA for 9um/0.24um fingers
 - NMOS: 55uA for 2um/0.24um fingers
- Use 140 fingers (more on this...)

ECE1371

9-23

AC Testbench

- V_{OUT}/V_{IN} gives loop gain $A\beta$
 - C_1, C_2 and input capacitance of 2nd OTA gives proper feedback network

 


ECE1371

9-24

AC Simulation

$\beta\omega_{\text{unity}}$: 561 MHz, PM: 84.9 deg., DC Gain: 31.4 dB

 

ECE1371

9-25

AC Simulation

- **Observations...**

- Gain is low**

- This can be corrected when gain-boosting is added, which should give about 40dB or more using folded-cascode gain-boosters

- Phase Margin is high**

- This can be traded with bandwidth – the unity gain is not as high as it could be (β could be increased)

- The 2nd pole will reduce somewhat when gain-boosting is added (increased capacitance on the critical node), so it is worth having extra PM at this stage of the design

ECE1371

9-26

Optimizing Bandwidth


- **Why choose 140 fingers?**
Once the V_{EFF} 's have been determined, there is nothing else to design except the size of the amplifier
- **Increasing the number of fingers reduces β**
An optimal point is eventually reached beyond which no further bandwidth improvements are achieved
- **A parametric sweep can be performed to find this optimal point**
Keep in mind: more fingers = more power

ECE1371

9-27

Optimizing Bandwidth

- **Optimal point ~ 140 fingers**
4 branches x 140 fingers x 55uA = 30.8mA

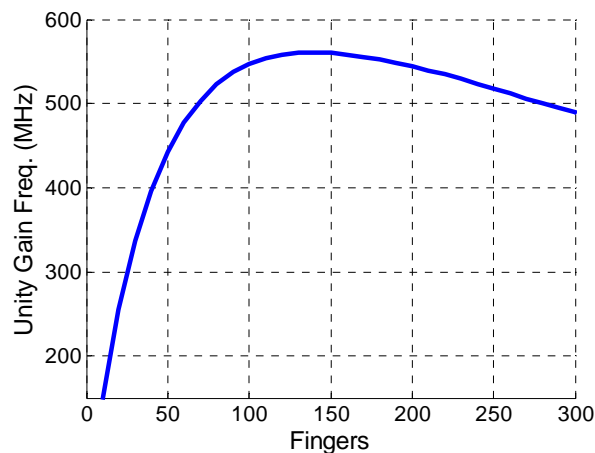


ECE1371

9-28

What about NMOS input?

- We can try the same simulations with an NMOS input – what should happen?
Larger bandwidth ($\beta\omega_{\text{unity}}$ larger), less phase margin ($\beta\omega_{\text{unity}}$ larger, ω_{p2} smaller)

 

ECE1371

9-29

What about NMOS input?


- Unity-gain is only 400MHz with an 80 degree PM
Although it is 70% less power!
- Make it more stable with larger PMOS V_{EFF}
Change PMOS fingers to 2um/0.24um
PMOS V_{EFF} becomes ~300mV
- Result
50 fingers, UG = 551MHz, PM = 79.8, DC Gain = 34.9dB
Swing reduced by 120mV, SNR reduced by 1.5dB,
Capacitor (and amplifier) increased by ~35%
Still about 50% less than the original power

ECE1371

9-30

Transient Testbench

- **Make sure settling behaviour is as expected**
Configured in amplification phase
Use differential step at input for full-scale output

 


ECE1371

9-31

Transient Testbench

- **Settles to within 0.01% of final value in 2.1ns**
Similar to predicted settling of 2-pole system
Zero adds some time (measured as $\sim 0.05\text{ns}$)

 

ECE1371

9-32

Gain-Boosting

- **Need to increase the DC gain without losing too much bandwidth or stability**
Gain-Boosting theoretically decouples improved gain from frequency response
- **Single-Ended or Differential**
Single-ended has lower-frequency mirror pole, slows down gain-booster (more difficult to optimize pole-zero doublet)
Differential gain-boosting does not increase common-mode gain of overall amplifier significantly
Differential requires CMFB

ECE1371

9-33

Gain-Booster Design

- **Type of Amplifier**
Input CM is very close to rail (either VDD or VSS)
Output CM is approximately mid-rail
Want ~40dB gain with moderate to high speed (single-stage with cascoding)

=> Choose differential Folded-Cascode (Telescopic cannot handle the input/output CM, single-ended not fast enough)
PMOS input for NMOS (V_{B2}) biases
NMOS input for PMOS (V_{B3}) biases

ECE1371

9-34

Gain-Booster Design


- **Gain**
Need another 43-44dB for the 75dB total
- **Frequency response**
 $\beta\omega_{\text{unity}} \sim 560\text{MHz}$, $\omega_{p2} \sim 4\text{GHz}$
Gain-booster unity-gain should be $\sim 1\text{GHz}$
- **V_{EFF}**
Can use higher V_{EFF} 's since swing is not as important
- **Input Pair**
Size of PMOS input pair in the V_{B2} gain-booster impacts the non-dominant pole and should be kept small

ECE1371

9-35

Gain-Boosted Loop

- **Source Follower introduces a gain of ~ 0.75**
(assuming deep N-well is not used – body effect is present)
This reduces the bandwidth by the same amount
Gain-Boosted amplifier A needs a unity-gain frequency of approximately 1.33 GHz
- **Also, add a compensation capacitor of $\sim 100\text{fF}$ so that parasitics do not dominate the capacitance at that node**

 


ECE1371

9-36

V_{B2} Gain-Booster AC Simulation

ω_{unity} : 901 MHz, PM: 64.2 deg., DC Gain: 46.8 dB

 


ECE1371

9-37

V_{B3} Gain-Booster AC Simulation

ω_{unity} : 703 MHz, PM: 55.7 deg., DC Gain: 46.4 dB

 

ECE1371

9-38

Size of Gain-Boosters

- V_{B2} gain booster is similar to main amplifier
Size of amplifier is 6
Compensation capacitor is 100fF
4 branches x 6 fingers x 55uA = 1.32mA
- V_{B3} gain booster has NMOS inputs
Size of amplifier is 20
Compensation capacitor is 200fF
4 branches x 20 fingers x 55uA = 4.4mA
Much larger since load capacitance on PMOS transistors is ~4x larger

ECE1371

9-39

Pole-Zero Doublet

- Recall settling behaviour

$$1 - e^{-\beta\omega_{\text{unity}}t} + \frac{\omega_z - \omega_p}{\beta\omega_{\text{unity}}} e^{-\omega_z t}$$

- Advantage of PMOS main amplifier
Distance between $\beta\omega_{\text{unity}}$ and ω_{p2} is larger
More room to have $\beta\omega_{\text{unity}} < \omega_{u,\text{GB}} < \omega_{p2}$
The farther $\omega_{u,\text{GB}}$ is from $\beta\omega_{\text{unity}}$, the closer together the pole and zero are in the doublet
=> Smaller impact of pole-zero doublet


ECE1371

9-40

Main Amplifier with Gain-Booster

$\beta\omega_{\text{unity}}$: 545 MHz, PM: 74.1 deg., DC Gain: 79.5 dB

Where is the pole-zero doublet?

 


ECE1371

9-41

Transient Response

- Settles to within 0.01% of final value in 2.54ns
Very small 8mV overshoot (0.5%)
About 25% slower with gain-booster

 

ECE1371

9-42

CMFB Loop Stability


- Two different CMFB loops to look at
 - Continuous-time CMFB for gain-boosters
 - Discrete-time CMFB for main amplifier
- Analyze loop gain through CMFB network
 - Break the loop somewhere (tail current)
 - Load the amplifier as it was when the loop was broken
 - Analyze the gain from the tail current to the tail current control voltage
 - Make sure all voltages are at their correct DC values

ECE1371

9-43

CMFB in Gain-Boosters

- Continuous-time CMFB should be sufficient
 - Swing is not as important since voltages should not change very much

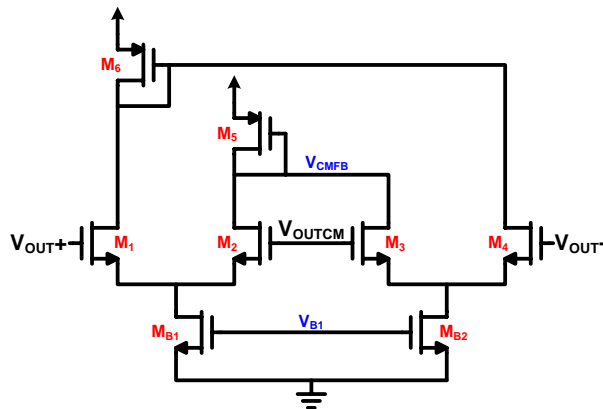


ECE1371

9-44

CMFB in Main Amplifier

- As presented in SC lecture
 - Allows larger swing than continuous-time CMFB
 - Large capacitors overload the output more than is necessary, while small capacitors cause CM offset voltages from charge injection
 - Typically use minimum size switches/transmission gates depending on the voltage level passed

 

ECE1371

9-45

Summary of Results

- Full-scale (+/- 800mV differentially) settling time
 - DC Gain: 79dB
 - Phase Margin: 74 deg.
 - 0.01% (80dB): 2.54ns with 0.5% overshoot
- Power
 - $(30.8\text{mA} + 1.3\text{mA} + 4.4\text{mA}) \times 1.8\text{V} = 66\text{mW}$
 - ~25% of total power => total power ~ 250mW
- Common Modes
 - Design based on using 400mV input CM and 900mV output CM
 - 400mV should allow all switches to be relatively small (except the ones attached to the output)

ECE1371

9-46

NLCOTD: Ring Oscillators

ECE1371

9-47

What You Learned Today

1. Design of a folded-cascode OTA
2. Important trade-offs in OTA design
3. Gain-boosting design example for OTA

ECE1371

9-48