

# **Lecture 7**

## **Amplifier Design 1**

**Trevor Caldwell**  
**[trevor.caldwell@awaveip.com](mailto:trevor.caldwell@awaveip.com)**

# Lecture Plan

Date	Lecture (Wednesday 2-4pm)		Reference	Homework
2020-01-07	1	MOD1 & MOD2	PST 2, 3, A	1: Matlab MOD1&2
2020-01-14	2	MODN + $\Delta\Sigma$ Toolbox	PST 4, B	2: $\Delta\Sigma$ Toolbox
2020-01-21	3	SC Circuits	R 12, CCJM 14	
2020-01-28	4	Comparator & Flash ADC	CCJM 10	3: Comparator
2020-02-04	5	Example Design 1	PST 7, CCJM 14	
2020-02-11	6	Example Design 2	CCJM 18	4: SC MOD2
2020-02-18	Reading Week / ISSCC			
2020-02-25	7	Amplifier Design 1		Project
2020-03-03	8	Amplifier Design 2		
2020-03-10	9	Noise in SC Circuits		
2020-03-17	10	Nyquist-Rate ADCs	CCJM 15, 17	
2020-03-24	11	Mismatch & MM-Shaping	PST 6	
2020-03-31	12	Continuous-Time $\Delta\Sigma$	PST 8	
2020-04-07	Exam			
2020-04-21	Project Presentation (Project Report Due at start of class)			


# Circuit of the Day: Cascode Current Mirror

- How do we bias cascode transistors to optimize signal swing?
- Standard cascode current mirror wastes too much swing

$$V_X = V_{EFF} + V_T$$

$$V_Y = 2V_{EFF} + 2V_T$$

 Minimum  $V_Z$  is  $2V_{EFF} + V_T$ ,  
which is  $V_T$  larger than  
necessary



# What you will learn...

- **Choice of  $V_{\text{EFF}}$**   
Several trade-offs with Noise, Bandwidth, Power,...
- **Amplifier Topology**
- **Amplifier Settling**  
Dominant Pole, Zero and Non-Dominant Pole
- **Gain-Boosting**  
Stability, Pole-Zero Doublet
- **Delaying vs. Non-Delaying stages**

# Choice of Effective Voltage

- **Effective Voltage**  $V_{\text{EFF}} = V_{\text{GS}} - V_{\text{T}}$

$$V_{\text{EFF}} = \frac{2I_{\text{D}}}{g_{\text{m}}} = \sqrt{\frac{2I_{\text{D}}}{\mu_{\text{n}} C_{\text{ox}} \frac{W}{L}}}$$

Assumes square-law model

In weak-inversion, this relationship will not hold

- **What are the trade-offs when choosing an appropriate effective voltage?**

Noise

Power

Bandwidth

Matching

Linearity

Swing

# Thermal Noise and $V_{EFF}$

- **Noise Current and Noise Voltage**

$$\overline{I_n^2} = 4kT\gamma g_m \qquad \overline{V_n^2} = \frac{4kT\gamma}{g_m}$$

- **Ex. Common Source with transistor load**


CS transistor has input referred noise voltage proportional to  $V_{EFF}$

$$\overline{V_n^2} = V_{EFF,1} \frac{4kT\gamma}{2I_D}$$

Current source has input referred noise voltage inversely proportional to  $V_{EFF}$

$$\overline{V_n^2} = \frac{4kT\gamma}{2I_D} \frac{V_{EFF,1}^2}{V_{EFF,2}}$$

# Thermal Noise and $V_{EFF}$

 

- **Total Noise**

$$\overline{V_n^2} = \frac{4kT\gamma}{2I_D} V_{EFF,1} \left( 1 + \frac{V_{EFF,1}}{V_{EFF,2}} \right)$$

Use small  $V_{EFF}$  for input transistor, large  $V_{EFF}$  for load (current source) transistor

# Bandwidth and $V_{EFF}$

- Bandwidth dependent on transistor unity gain frequency  $f_T$

$$f_T = \frac{g_m}{2\pi(C_{GS} + C_{GD})}$$

If  $C_{GS}$  dominates capacitance

$$f_T \approx \frac{1.5\mu_n}{2\pi L^2} V_{EFF}$$

Small  $L$ , large  $\mu$  maximizes  $f_T$

For a given current, decreasing  $V_{EFF}$  increases  $W$ , increases  $C_{GS}$ , and slows down the transistor

- $f_T$  increases with  $V_{EFF}$




# Linearity and $V_{EFF}$

- Look at distortion through a CS amplifier

Compare amplitude of fundamental and second-order distortion term

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{EFF} + V_A \cos(\omega t))^2$$
$$= I + \underbrace{\mu_n C_{ox} \frac{W}{L} V_{EFF} V_A}_{V_F} \cos(\omega t) + \underbrace{\frac{1}{4} \mu_n C_{ox} \frac{W}{L} V_A^2}_{V_{HD2}} (1 + \cos(2\omega t))$$
 
$$\Rightarrow \frac{V_{HD2}}{V_F} = \frac{V_A}{4V_{EFF}}$$



- Linearity increases with  $V_{EFF}$

# Power and $V_{EFF}$

- **Efficiency of a transistor is  $g_m/I_D$**


Transconductance for a given current – high efficiency results in lower power

Bipolar devices have  $g_m = I_C/V_t$ , while (square-law) MOS devices have  $g_m = 2I_D/V_{EFF}$

- **$V_{EFF}$  is inversely proportional to  $g_m/I_D$**


Increasing  $V_{EFF}$  reduces efficiency of the transistor

 Biassing in weak inversion increases efficiency


 
# Matching and $V_{EFF}$

- With low  $V_{EFF}$ , transistor is in weak inversion  
What happens with mismatch in  $V_t$ ?
- Use a current-mirror as an example with mismatched threshold voltages



# Matching and $V_{EFF}$

- In strong inversion with  $V_t$  mismatch there is a quadratic relationship

$$\frac{I_{OUT}}{I_{IN}} = \frac{(V_{GS} - V_{t,2})^2}{(V_{GS} - V_{t,1})^2}$$

1mV error in  $V_t$  is ~1% error in  $I_{OUT}$  (for  $V_{EFF} \sim 200\text{mV}$ )

- In weak inversion with  $V_t$  mismatch there is an exponential relationship

$$\frac{I_{OUT}}{I_{IN}} = \frac{e^{\frac{V_{GS} - V_{t,1}}{nV_T}}}{e^{\frac{V_{GS} - V_{t,2}}{nV_T}}} = e^{\frac{V_{t,2} - V_{t,1}}{nV_T}}$$

1mV error in  $V_t$  is ~4% error in  $I_{OUT}$

# Swing and $V_{EFF}$

- **Minimum  $V_{DS}$  of a transistor to keep it in saturation is  $V_{EFF}$**

Usually  $V_{DS}$  is  $V_{EFF} + 50\text{mV}$  or more to keep  $r_o$  high (keep the transistor in the saturation region)

With limited supply voltages, the larger the  $V_{EFF}$ , the larger the  $V_{DS}$  across the transistor, less room for signal swing

- **With large  $V_{EFF}$ ...**


Can't cascode – reduced OTA gain

Stage gain is smaller – input referred noise is larger (effectively the SNR at the stage output is less)
 
# Speed-Efficiency Product

- What is the optimal  $V_{\text{EFF}}$  using a figure of merit defined as the product of  $f_T$  and  $g_m/I_D$

Optimal point at  $V_{\text{EFF}} = 130\text{mV}$  in  $0.18\mu\text{m}$



# Summary of Trade-Offs

- **Benefits of larger  $V_{EFF}$** 
  - Larger bandwidth
  - Higher linearity
  - Better device matching
  - Lower noise for current-source transistors
- **Benefits of smaller  $V_{EFF}$** 
  - Better efficiency – lower power
  - Larger signal swings
  - Better noise performance for input transistors

**Good starting point:  $V_{EFF} \sim V_{DD}/10$**

# Amplifier Design - Topology


Topology	Gain	Output Swing	Speed	Power Dissipation	Noise
Telescopic	Medium	Medium	Highest	Low	Low
Folded-Cascode	Medium	Medium	High	Medium	Medium
Two-Stage	High	Highest	Low	Medium	Low
Gain-Boosted	High	Medium	Medium	High	Medium

From Razavi Ch.9



# Amplifier Errors

- Two errors: Dynamic and Static

 


- Static Errors

Limit the final settling accuracy of the amplifier  
 Capacitor Mismatch ( $C_1/C_2$  error)

Finite OTA gain

$$\frac{V_o}{V_i}(z) = \frac{C_1}{C_2} \left( \frac{1}{z - \frac{1 + (C_2 + C_1)/C_2 A}{1 + 1/A}} \right)$$

# Amplifier Errors

 

- **Dynamic Errors: Occurs in the integration phase when a 'step' is applied to the OTA**
  - Slewing**
  - Finite bandwidth**
  - Feedforward path**
  - Non-dominant poles**

# Static Amplifier Errors

- **First look at frequency independent response**

Static error term  $1/A\beta$

$$\frac{V_o}{V_i} = -\frac{C_1}{C_2} \frac{1}{1 + 1/A\beta} \approx -\frac{C_1}{C_2} \left( 1 - \frac{1}{A\beta} \right)$$

$$\beta = \frac{C_2}{C_1 + C_2 + C_{IN}}$$


- **Example: 0.1% error at output (Gain = 4)**

$$C_1 = 4\text{pF}, C_2 = 1\text{pF}, C_{IN} = 1\text{pF}$$

$$\frac{V_o}{V_i} \approx -4 \left( 1 - \frac{6}{A} \right)$$

**$A > 6000$  for 0.1% error**

# Dynamic Amplifier Errors

 

- What is the transfer function of this circuit?

By inspection...

Gain is  $-C_1/C_2$

Zero when  $V_X s C_2 = V_X G_m$

Pole at  $\beta G_m / C_{L,eff}$  where  $C_{L,eff} = C_2(1-\beta) + C_L$

$$\frac{V_o}{V_i} = -\frac{C_1}{C_2} \frac{1 - \frac{sC_2}{G_m}}{1 + \frac{sC_{L,eff}}{\beta G_m}}$$

# Single-Pole Settling Error

- Step response of 1st-order (unity-gain) system

Unit step  $\frac{1}{s}$  through system  $\frac{1}{1 + s/\beta\omega_{unity}}$

Inverse Laplace transform of  $\frac{1}{s(1 + s/\beta\omega_{unity})}$

Step response is  $1 - e^{-\beta\omega_{unity}t}$

Error is  $e^{-\beta\omega_{unity}t}$

Settles to N-bit accuracy in  $t > \frac{N \ln 2}{\beta\omega_{unity}}$

# Pole and Zero Settling Error

- Step response, 1st-order with feedforward zero

Unit step  $\frac{1}{s}$  through system  $\frac{1 + s/\omega_z}{1 + s/\beta\omega_{unity}}$

Inverse Laplace transform of  $\frac{1 + s/\omega_z}{s(1 + s/\beta\omega_{unity})}$

Step response is  $1 - e^{-\beta\omega_{unity}t} + \frac{\beta\omega_{unity}}{\omega_z} e^{-\beta\omega_{unity}t}$

Error is  $e^{-\beta\omega_{unity}t} - \frac{\beta\omega_{unity}}{\omega_z} e^{-\beta\omega_{unity}t}$

Settles to N-bit accuracy in  $t > \frac{N \ln 2}{\beta\omega_{unity}} + \frac{\ln(1 - \beta\omega_{unity}/\omega_z)}{\beta\omega_{unity}}$

# Effect of Zero on Settling

- Zero slows down settling time

Additional settling term

$$-\frac{\beta\omega_{unity}}{\omega_z} e^{-\beta\omega_{unity}t}$$

Coefficient a function of feedback factor  $\beta$

$$-\frac{\beta\omega_{unity}}{\omega_z} = \frac{\beta G_m / C_{L,eff}}{G_m / C_2} = \frac{\beta C_2}{(1-\beta)C_2 + C_L}$$

- To reduce impact of feedforward zero...


Smaller  $\beta$  (one of the few advantages of reducing  $\beta$ )

Larger  $C_L$

# Effect of Zero on Settling

- Example of settling behaviour

$$\beta = 1/2, C_L = C_2/2$$

 



# Two-Pole Settling Error

- Dominant and non-dominant pole, 2<sup>nd</sup>-order sys.

(assumes  $\omega_{p2} \gg \omega_{p1} = \omega_{unity}/A$ )

Unit step  $\frac{1}{s}$  through system  $\frac{1}{\omega_{p2} \cdot \beta\omega_{unity} s^2 + \beta\omega_{unity} s + 1}$

Step response is dependent on relative values of  $\beta\omega_{unity}$  and  $\omega_{p2}$

3 Cases:


Overdamped,  $\omega_{p2} > 4\beta\omega_{unity}$

Critically damped,  $\omega_{p2} = 4\beta\omega_{unity}$

Underdamped,  $\omega_{p2} < 4\beta\omega_{unity}$
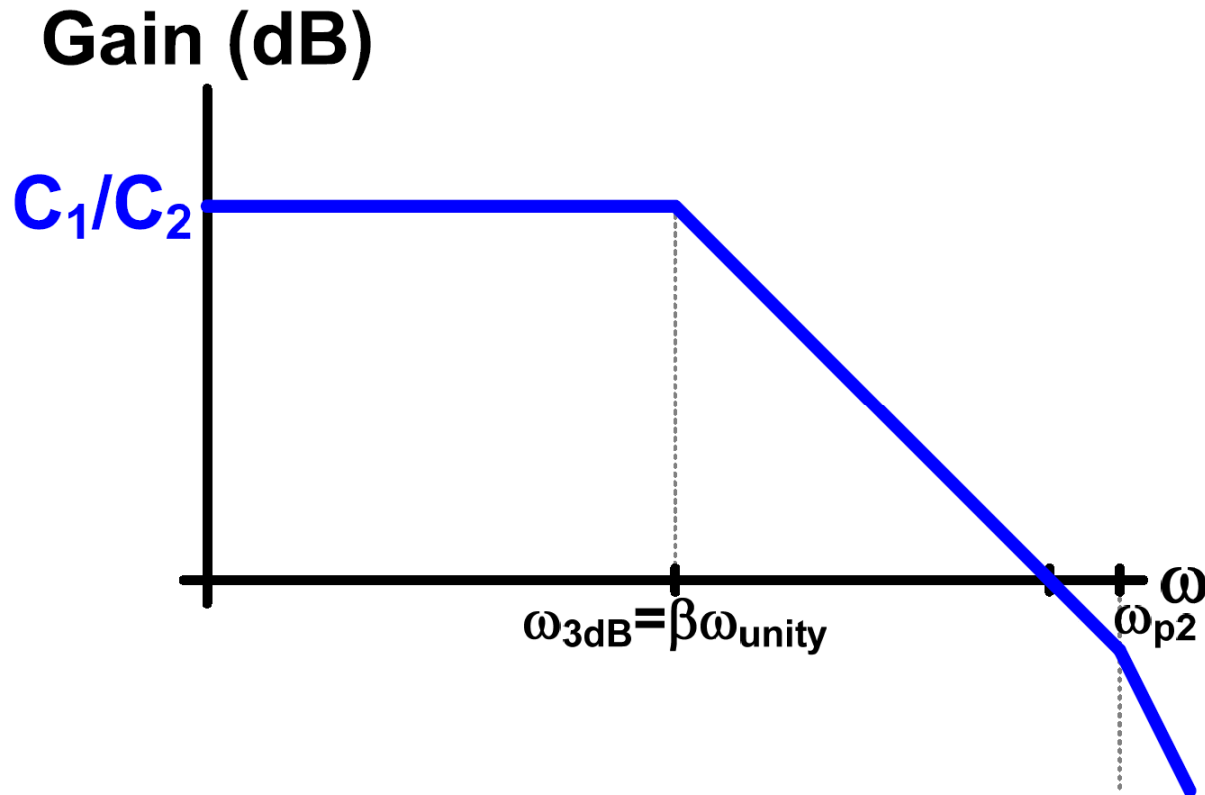
# Two-Pole Settling Error

- Closed loop response of the amplifier (ignoring zero, including 2<sup>nd</sup> pole)



# Two-Pole Settling Error

- **Overdamped,  $\omega_{p2} > 4\beta\omega_{unity}$**

2<sup>nd</sup> pole much larger than unity-gain frequency

Similar to 1<sup>st</sup>-order settling as 2<sup>nd</sup> pole approaches infinity

Step response is  $1 - \frac{B}{B-A} e^{-At} - \frac{A}{A-B} e^{-Bt}$

$$A, B = \frac{\omega_{p2}}{2} \pm \frac{\sqrt{\omega_{p2}^2 - 4\omega_{p2}\beta\omega_{unity}}}{2} \approx \omega_{p2}, \beta\omega_{unity}$$

- **Critically damped,  $\omega_{p2} = 4\beta\omega_{unity}$**

No overshoot

Step response is  $1 - e^{-2\beta\omega_{unity}t} - 2\beta\omega_{unity}te^{-2\beta\omega_{unity}t}$

# Two-Pole Settling Error

- Underdamped,  $\omega_{p2} < 4\beta\omega_{unity}$

Minimum settling time depending on desired SNR  
Increasing overshoot as  $\omega_{p2}$  decreases

Step response is


$$1 - e^{-\frac{\omega_{p2}}{2}t} \cos\left(t\sqrt{\beta\omega_{unity}\omega_{p2} - \frac{\omega_{p2}^2}{4}}\right) - \frac{e^{-\frac{\omega_{p2}}{2}t} \sin\left(t\sqrt{\beta\omega_{unity}\omega_{p2} - \frac{\omega_{p2}^2}{4}}\right)}{\sqrt{\frac{4\beta\omega_{unity}}{\omega_{p2}} - 1}}$$

# Two-Pole Settling

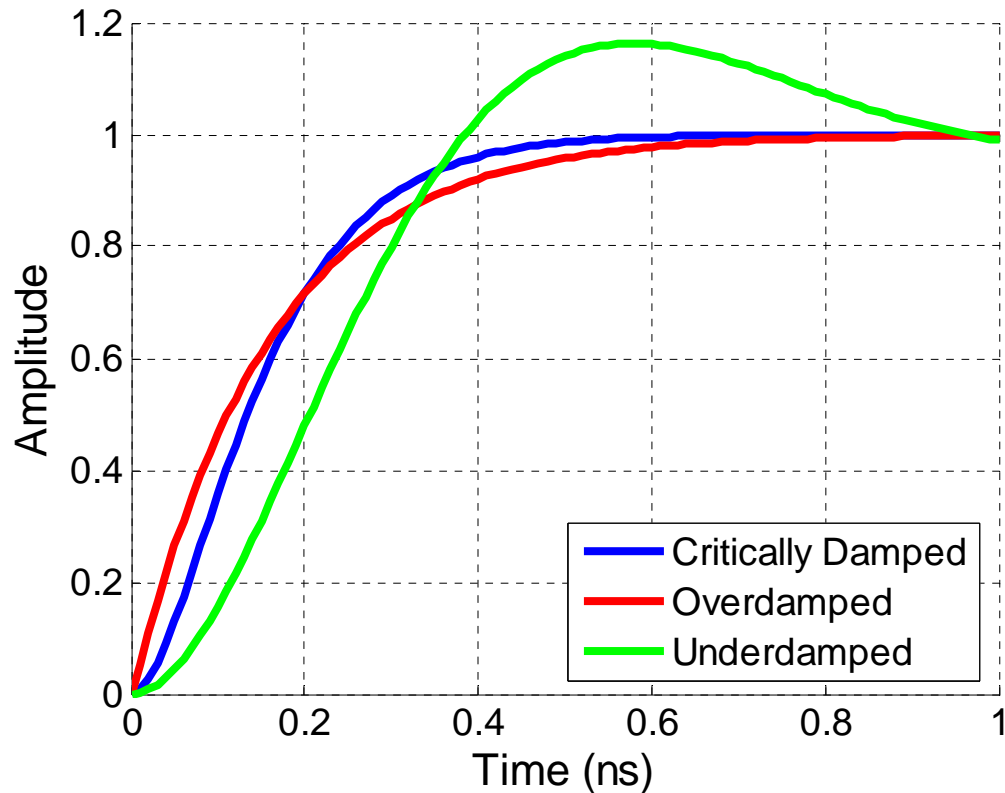- **Example:**


$$\beta\omega_{unity}/2\pi = 1\text{GHz}$$

$$\omega_{p2}/2\pi = 1\text{GHz}, 4\text{GHz}, 100\text{GHz}$$



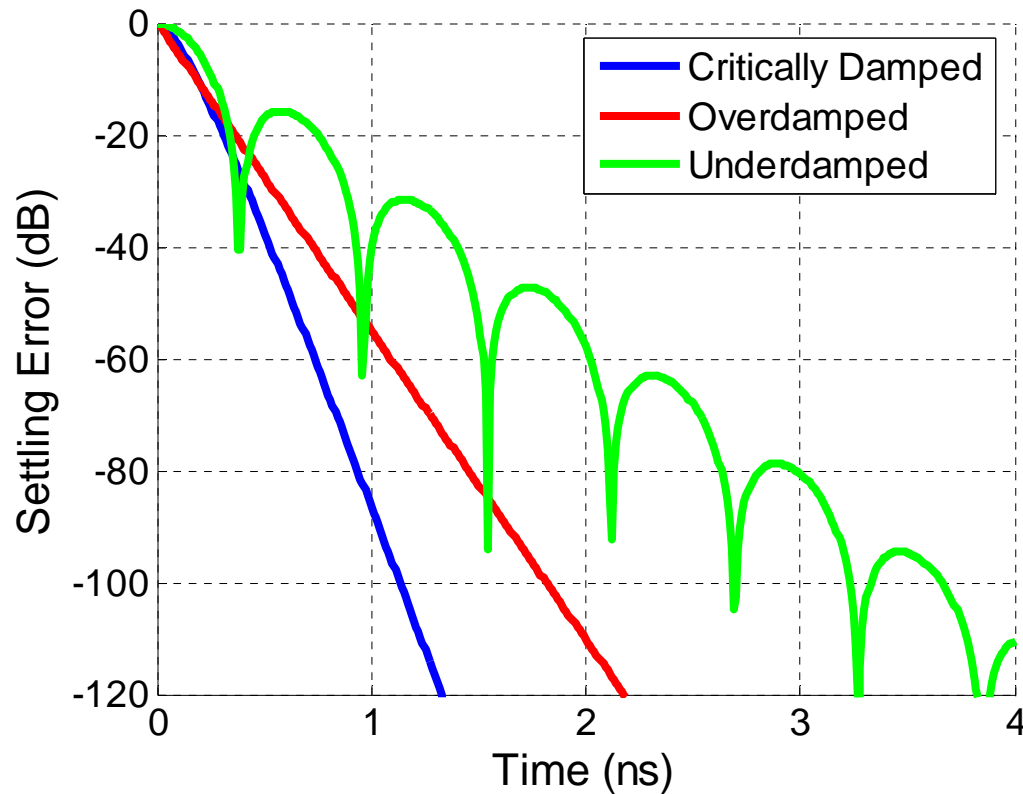
# Two-Pole Settling

- **Critically damped system settles faster than single-pole system**


 
# Two-Pole Settling

- Underdamped system gives slightly better settling time depending on the desired SNR



# Two-Pole Settling

- For a two-pole system, phase margin can be used equivalently

$$PM = 90 - \frac{180}{\pi} \tan^{-1} \left( \frac{\omega_{p2}}{\beta \omega_{unity}} \right)$$

Critically damped: PM = 76 degrees

Underdamped: PM < 76 degrees

(45 degrees if  $\omega_{p2} = \beta \omega_{unity}$ )

Overdamped: PM = 76 to 90 degrees



# Gain-Boosting

- Increase output impedance of cascoded transistor

Impedance boosted by gain of amplifier A


$$V_{OUT}/V_{IN} = -g_m R_{OUT}$$

$$R_{OUT} \sim A g_m r_o^2$$

- Trade-offs

Does not require extra headroom

 Amplifier requires some power, but does not have to be very fast




# Gain-Boosting

- Need to analyze gain-boosting loop to ensure that it is stable

Cascade of amplifier A and source follower from node Y to node X

 - Load capacitance at node Y  
May need extra capacitance  $C_C$  to stabilize loop




# Gain-Boosting

$A_{\text{ORIG}}$ : Original amplifier response without gain-boosting

$A_{\text{ADD}}$ : Frequency response of feedback amplifier A

 $A_{\text{TOT}}$ : Gain-boosted amplifier frequency response




# Gain-Boosting

- **Stability of gain-booster amplifier**

For 1<sup>st</sup>-order roll-off, the unity-gain frequency of the additional amplifier must be greater than the 3dB frequency of the original stage

$$\omega_{3dB} < \omega_{UG,A}$$

 (if  $\omega_{3dB} > \omega_{UG,A}$  there will be a discontinuity in the 1<sup>st</sup> order roll-off between  $\omega_{UG,A}$  and  $\omega_{3dB}$ )



# Gain-Boosting

- **2<sup>nd</sup> pole of feedback loop is equivalent to 2<sup>nd</sup> pole of main amplifier**


Set unity-gain frequency of additional amplifier lower than 2<sup>nd</sup> pole of main amplifier

$$\omega_{UG,A} < \omega_{2nd}$$

- **Only 45 degree phase margin if  $\omega_{UG,A} = \omega_{2nd}$**

$\omega_{UG,A} \sim \omega_{2nd}/3$  for a phase margin of  $\sim 71$  degrees

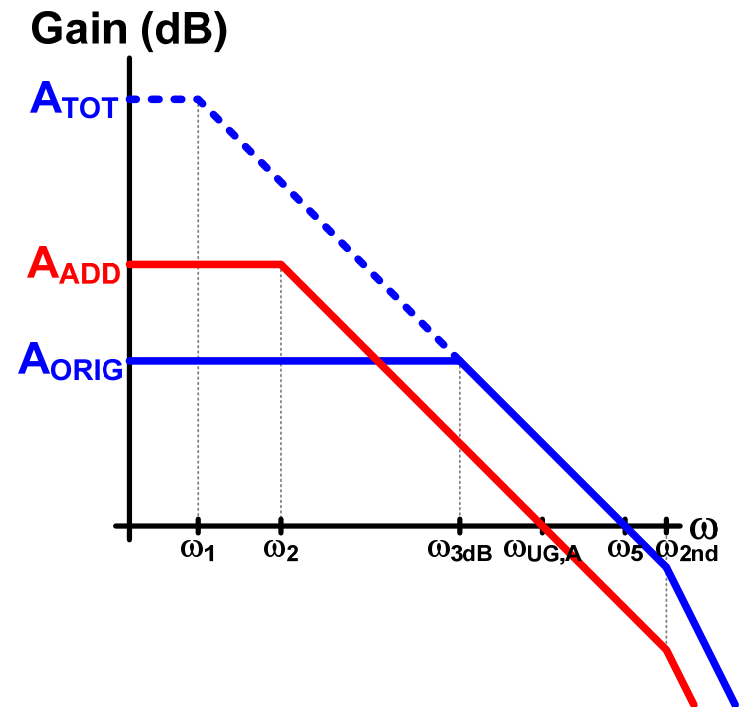$\omega_{UG,A} \sim \omega_{2nd}/4$  for a phase margin of 76 degrees



# Gain-Boosting

- **Pole-zero doublet occurs at  $\omega_{UG,A}$**   
Must ensure that this time constant does not dominate the settling behaviour
- **Set  $\beta\omega_5$  (3dB frequency of closed loop amplifier response) below  $\omega_{UG,A}$**   
Ensures that time constant is dominated by 3dB frequency and not the pole-zero doublet  
$$\beta\omega_5 < \omega_{UG,A}$$

**Final Constraint:  $\beta\omega_5 < \omega_{UG,A} < \omega_{2nd}$**


# Pole-Zero Doublet

$Z_{CL}$ : Load Capacitance

$Z_{OUT}$ : gain-boosted output impedance  $\sim (1+A)g_m r_o^2$

$Z_{ORIG}$ : cascoded output impedance  $\sim g_m r_o^2$

$Z_{TOT}$ : Total Output Impedance

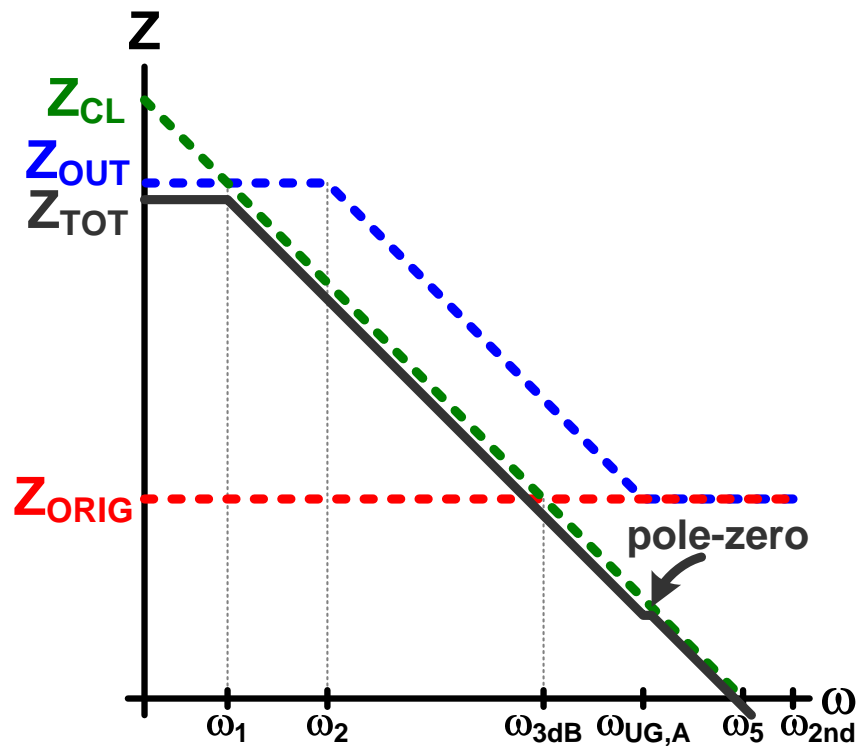

# Pole-Zero Doublet

- **Why is this a problem?**

**Doublet introduces a slower settling component in the step response**

**Step response (where  $\omega_z$  and  $\omega_p$  are the doublet pole and zero locations,  $\sim\omega_{UG,A}$ ):**

$$1 - e^{-\beta\omega_{unity}t} + \frac{\omega_z - \omega_p}{\beta\omega_{unity}} e^{-\omega_z t}$$

**A higher-frequency doublet will always have an impact but will die away quickly**

**A lower-frequency doublet will not have as large an impact, but it will persist much longer**




# Delaying vs. Non-Delaying Stage

- Depending on the architecture and stage sizing, this can be a power concern

Large  $C_L$  reduces the power efficiency of an amplifier

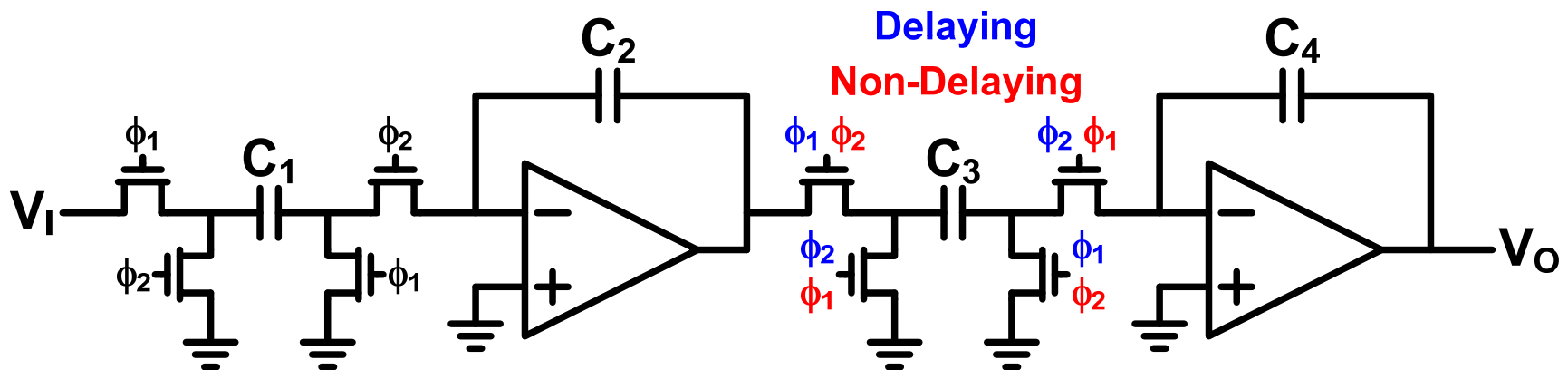Larger amplifier results in a smaller feedback factor and reduced bandwidth



# Delaying Stage

- **Delaying**

Following stage does not load the output

Very little  $C_L$  on output of the amplifier

- **Example:**

1<sup>st</sup> stage 4x larger than 2<sup>nd</sup> stage

( $C_3 = 0$  for delaying,  $C_3 = C_1/4$  for non-delaying)

Each stage has gain of 2 ( $C_1/C_2 = 2$ ,  $C_3/C_4 = 2$ )

$$C_{L,eff} = \frac{C_2(C_1 + C_{IN})}{C_1 + C_2 + C_{IN}} + C_3 = \beta(C_1 + C_{IN}) + C_3$$

$$(\beta\omega_{unity})_{delay} = \frac{\beta g_m}{C_{L,eff}} = \frac{g_m}{C_1 + C_{IN}} \quad P_{delay} \propto g_m$$

# Non-Delaying Stage

- **Non-Delaying**

Following stage loads the output

Applicable in pipeline ADCs, sometimes  $\Delta\Sigma$  (usually following stages much smaller, depending on OSR)

Opamp is wasted during the non-amplifying stage (could power it down to save power)

- **Example (continued):**

$$(\beta\omega_{unity})_{non-delay} = \frac{\beta g_m}{C_{L,eff}} = \frac{g_m}{1.75C_1 + 1.5C_{IN}}$$

Increase  $g_m$  by 1.75  $\rightarrow$   $C_{IN}$  increases by 1.75 (approximately the same bandwidth with 1.75x power)

$$P_{non-delay} \propto 1.75g_m \text{ for } (\beta\omega_{unity})_{non-delay} \approx (\beta\omega_{unity})_{delay}$$

# Amplifier Stability

- **Both phases are important**
  - Different loading on sampling and amplification phase
- **Feedback factor is larger in sampling phase than amplification phase**
  - Amplifier could potentially go unstable if it was originally sized for optimal phase margin in the amplification mode
- **Non-Delaying stages are more susceptible to instability in sampling phase since a much smaller load capacitance is present**

# Amplifier Stability

- **Example:**

$$C_1 = 2\text{pF}, C_2 = 1\text{pF}, C_{IN} = 1\text{pF}$$


$$C_L = 0.5\text{pF (load of subsequent stage)}$$

## Delaying Stage


**Amplification:**  $\beta\omega_{\text{unity}} = g_m/3\text{pF}$

**Sampling:**  $\beta = 1/2$ ,  $C_{L,\text{eff}} = 1\text{pF}$ ,  $\beta\omega_{\text{unity}} = g_m/2\text{pF}$

 **Phase Margin:**  $73 \rightarrow 65$  (assume same  $\omega_{p2}$ )



**Amplification**

 

**Sampling**


# Amplifier Stability

## Non-Delaying Stage


Amplification:  $\beta = 1/4$ ,  $C_{L,\text{eff}} = 1.25\text{pF}$ ,  $\beta\omega_{\text{unity}} = g_m/5\text{pF}$

Sampling:  $\beta = 1/2$ ,  $C_{L,\text{eff}} = 0.5\text{pF}$ ,  $\beta\omega_{\text{unity}} = g_m/1\text{pF}$

 Phase Margin:  $73 \rightarrow 33$  (assume same  $\omega_{p2}$ )



Amplification

 

Sampling

# Circuit of the Day: Cascode Current Mirror

# What You Learned Today

- **Choice of  $V_{EFF}$**   
Trade-offs with various parameters
- **Amplifier Topology**
- **Amplifier Step Response**
- **Gain-Boosting**
- **Choice of Delaying/Non-Delaying Stages**  
Impact on stability of sampling/integrating phases