

# **Lecture 12**

## **Continuous-Time $\Delta\Sigma$ ADCs**

**Trevor Caldwell**  
**[trevor.caldwell@awaveip.com](mailto:trevor.caldwell@awaveip.com)**

# Lecture Plan


Date	Lecture (Wednesday 2-4pm)		Reference	Homework
2020-01-07	1	MOD1 & MOD2	PST 2, 3, A	1: Matlab MOD1&2
2020-01-14	2	MODN + $\Delta\Sigma$ Toolbox	PST 4, B	2: $\Delta\Sigma$ Toolbox
2020-01-21	3	SC Circuits	R 12, CCJM 14	
2020-01-28	4	Comparator & Flash ADC	CCJM 10	3: Comparator
2020-02-04	5	Example Design 1	PST 7, CCJM 14	
2020-02-11	6	Example Design 2	CCJM 18	4: SC MOD2
2020-02-18	Reading Week / ISSCC			
2020-02-25	7	Amplifier Design 1		Project
2020-03-03	8	Amplifier Design 2		
2020-03-10	9	Noise in SC Circuits		
2020-03-17	10	Nyquist-Rate ADCs	CCJM 15, 17	
2020-03-24	11	Mismatch & MM-Shaping	PST 6	
2020-03-31	12	Continuous-Time $\Delta\Sigma$	PST 8	
2020-04-07	Exam			
2020-04-21	Project Presentation (Project Report Due at start of class)			

# What you will learn...

- **What is a Continuous-Time  $\Delta\Sigma$  modulator**
- **Continuous-time circuits for  $\Delta\Sigma$  ADCs**  
Loop filter, amplifiers, DACs, Direct Feedback
- **Benefits of Continuous-Time circuits**  
... And a couple disadvantages
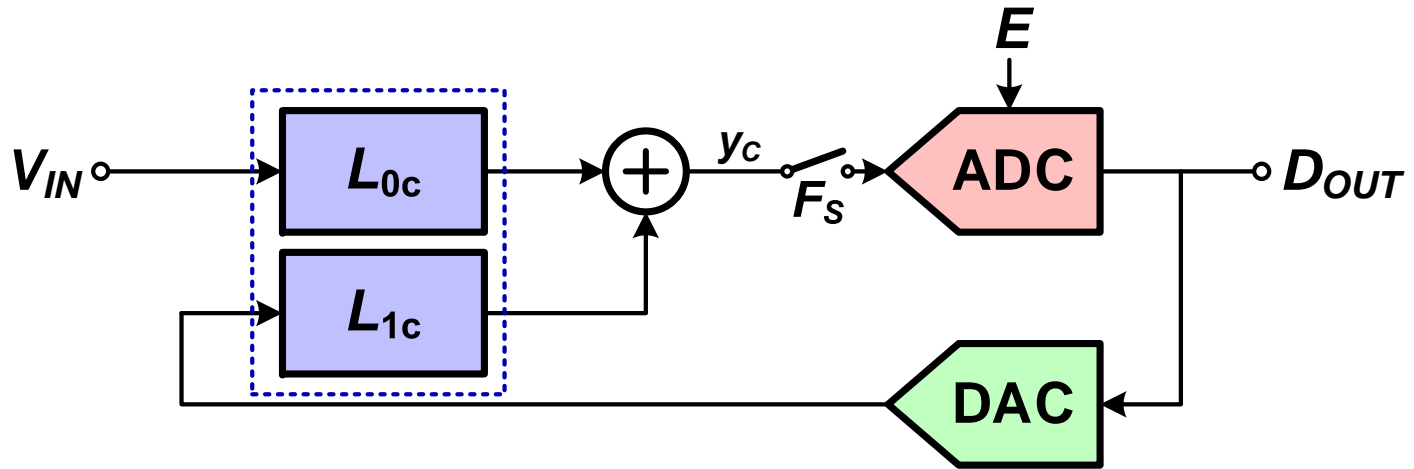
# What is a Continuous-Time $\Delta\Sigma$ ?

- General continuous-time  $\Delta\Sigma$  ADC



Filters  $L_{0c}$ ,  $L_{1c}$  are continuous-time

Output is identical to discrete-time  $\Delta\Sigma$  ADC as long as



$$y[n] = y_c(t)|_{t=nT_s}$$

Satisfied if impulse responses are equal at  $nT_s$

$$Z^{-1}\{L_1(z)\} = \mathcal{L}^{-1}\{L_{1c}(s)\}|_{t=nT_s} \leftarrow L_{1c}(s) \text{ includes DAC}(s) \text{ and ADC}(s)$$

 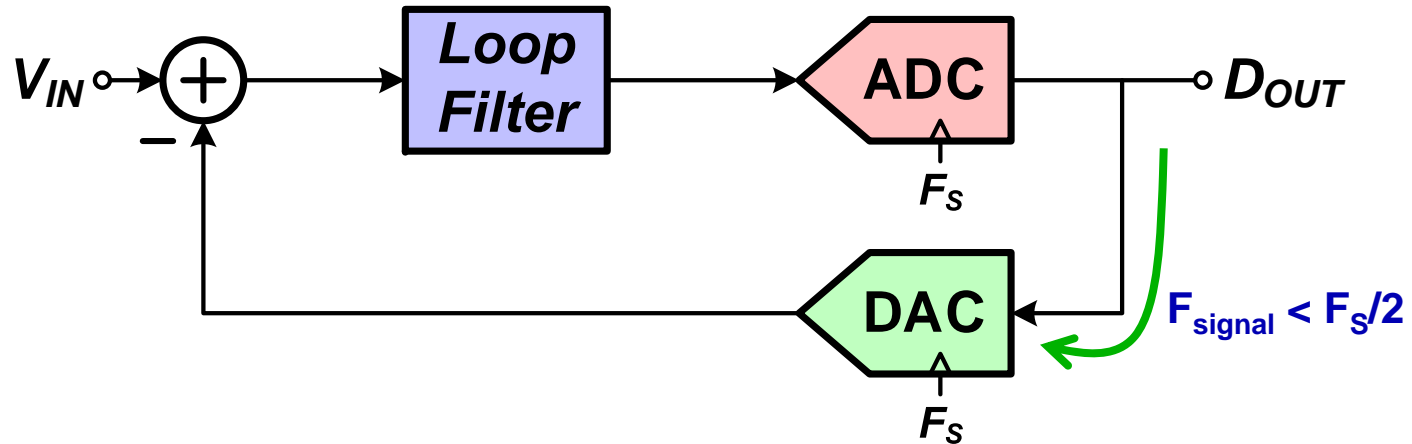
# What is a Continuous-Time $\Delta\Sigma$ ?

- Design  $L_{1c}$  (Loop Filter) like any negative feedback system



# What is a Continuous-Time $\Delta\Sigma$ ?

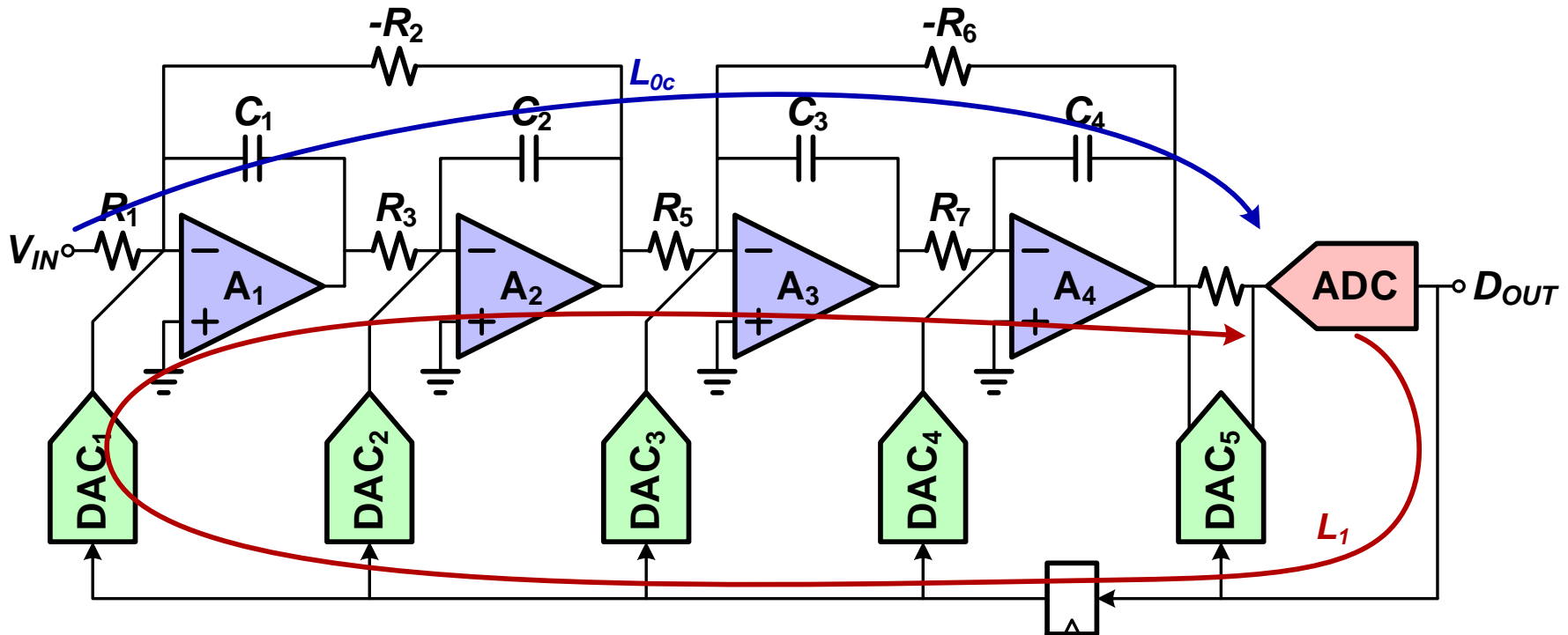- Example: 4<sup>th</sup>-order Continuous-Time FB  $\Delta\Sigma$  ADC



$$L_1(e^{j2\pi f}) = \sum_{n=-\infty}^{\infty} L_{1c}(j2\pi(f + nf_s))$$


Includes DAC(s)  
and ADC(s)

$$NTF(z) = \frac{1}{1 - L_1(z)}$$

$$STF(s) = L_{0c}(s) \cdot NTF(e^s)$$

# What is a Continuous-Time $\Delta\Sigma$ ?

 - Example: 4<sup>th</sup>-order Continuous-Time FB  $\Delta\Sigma$  ADC



# Circuit differences for CT $\Delta\Sigma$ ADC

- **Loop Filter**

  - Resistor (or  $G_M$ ) and capacitor passives instead of only capacitors

  - No switches (no aliasing at loop filter front-end)

  - Amplifiers can be designed more efficiently: feed-forward amplifiers

- **DACs**

  - Typically current-mode instead of switched-capacitor

  - Choice of Return-to-Zero or Non-Return-to-Zero pulses

- **Direct Feedback DAC**


  - Additional DAC path to compensate for excess loop delay in CT loop filter


 
# Loop Filters in CT $\Delta\Sigma$ ADCs


- **Gm-C Integrator**

- ☺ Higher speed
- ☹  $G_M$  variation causes  $G_M/C$  coefficient variation
- ☹ Reduced linearity



- **RC Integrator**

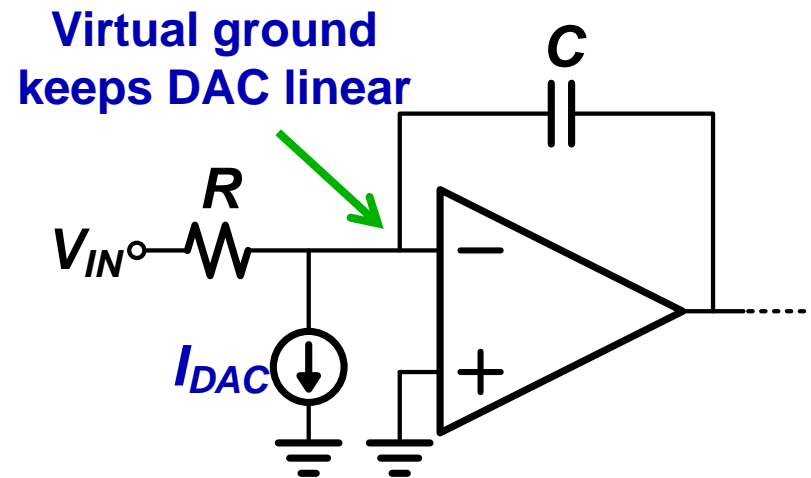- ☺ R and C variation can be easily tuned
- ☺ Feedback improves linearity of amplifier, DAC
- ☹ Lower speed





# Loop Filters in CT $\Delta\Sigma$ ADCs

- Resonators

RC integrators: easily programmable

 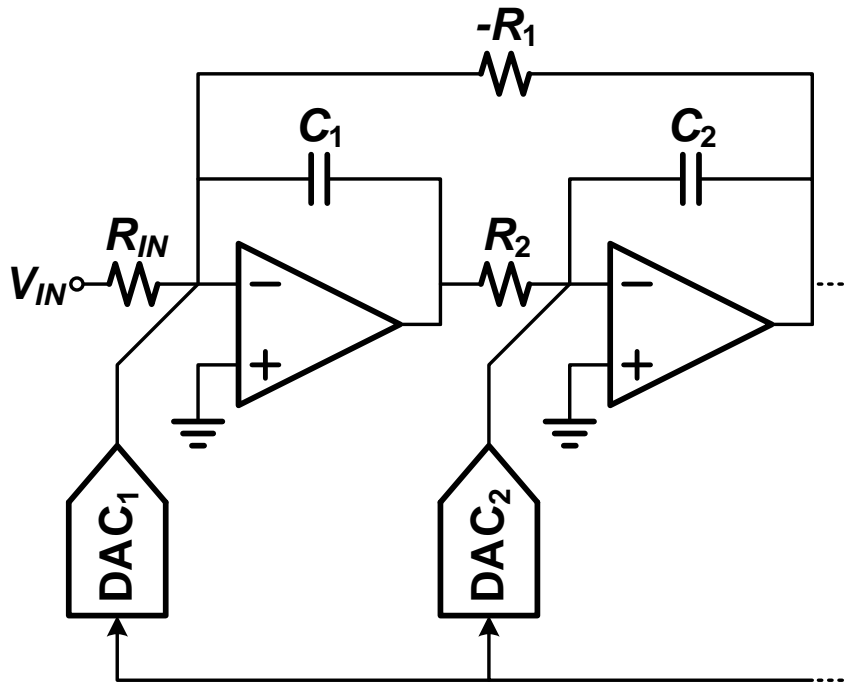LC tank: lower noise, higher Q, fewer degrees of freedom, no virtual ground node



# Loop Filters in CT $\Delta\Sigma$ ADCs

- **DT amplifier design (from Amp Design lecture)**

Amplifier designed with 1<sup>st</sup>-order settling response, main concern is settling behavior (eg, no pole-zero doublets)

If amplifier settles to sufficient accuracy in  $\sim T/2$  seconds, NTF will be as expected

- **CT amplifier design**

Amplifier can be conditionally stable, 1<sup>st</sup>-order settling not required

Amplifier gain within signal band must be sufficiently high for NTF noise suppression in-band



Can use *feed-forward amplifiers*

# Feed-forward Amplifiers

- **Efficient for continuous-time circuits**

Lower unity-gain required for a given bandwidth

 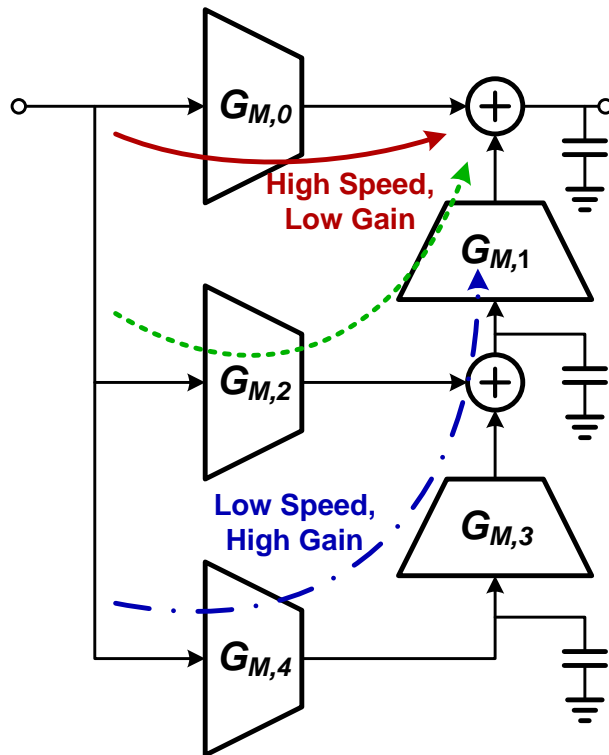
Conditionally stable: phase  $< -180^\circ$  at  $f < f_{\text{unity}}$   
phase  $> -180^\circ$  at  $f_{\text{unity}}$


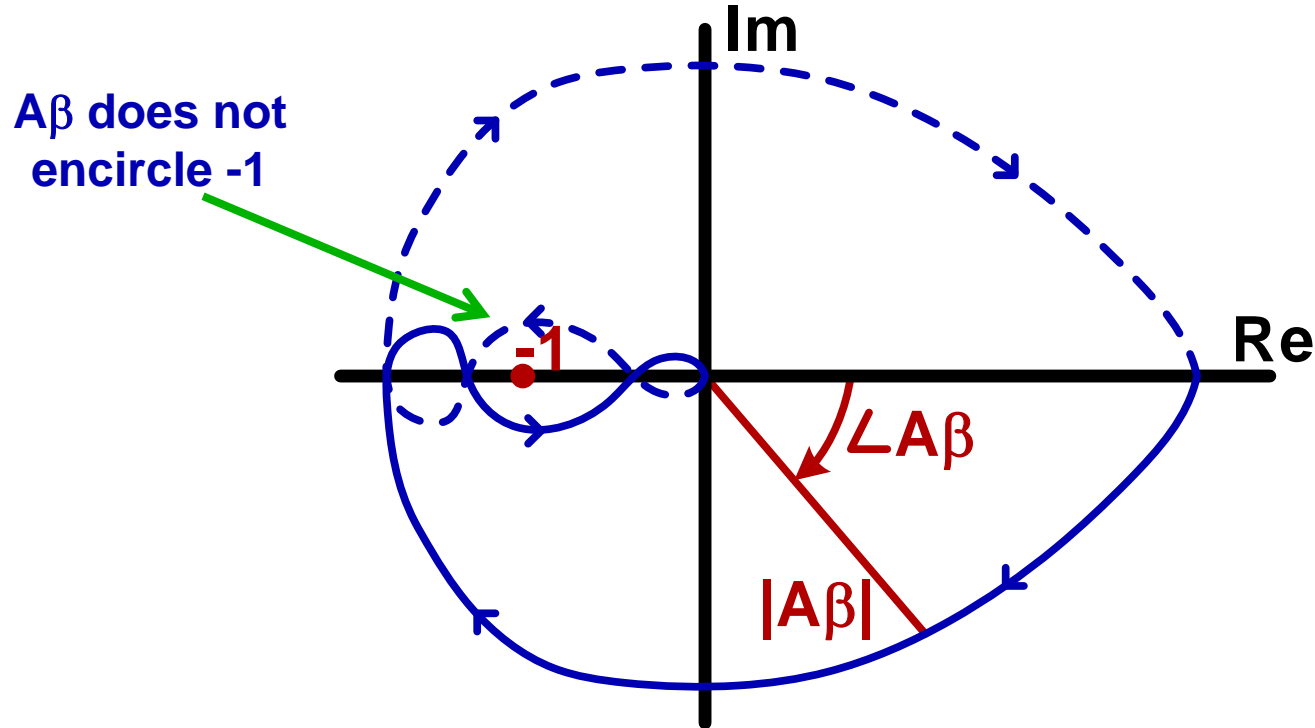
# Feed-forward Amplifiers

- Nyquist stability criterion

If the loopgain transfer function  $A\beta$  has no RHP poles, then it is closed-loop stable iff the Nyquist diagram has no encirclements of the -1 point



# Feed-forward Amplifiers

- **Efficient for continuous-time circuits**

  - Cascaded gains rather than cascoded gains

  - Appropriate for new technologies with smaller  $g_m r_{out}$

  - High-speed (low OSR) CT modulators almost exclusively use them


- **Not appropriate for discrete-time circuits**

  - Slow pole-zero settling

  - High-frequency noise aliases back in band
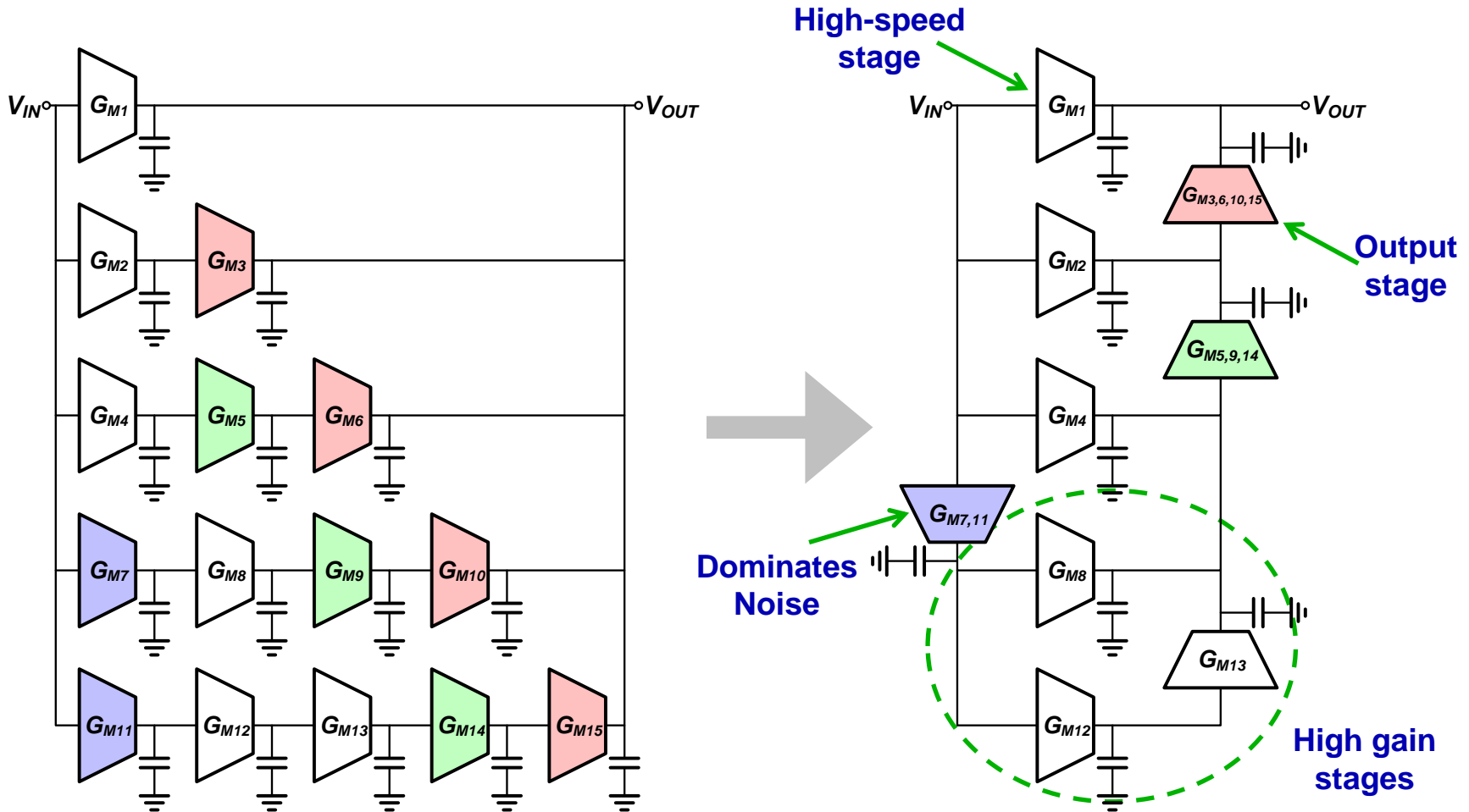
# Feed-forward Amplifiers

- Fewest  $G_M$  stages:  $2N-1$  for  $N^{\text{th}}$ -order amplifier




# Feed-forward Amplifiers

- Individual  $G_M$  stages

First-order complementary stages for high  $G_M$  efficiency

Combination of differential + pseudo-differential pairs


Capacitive coupling used when necessary

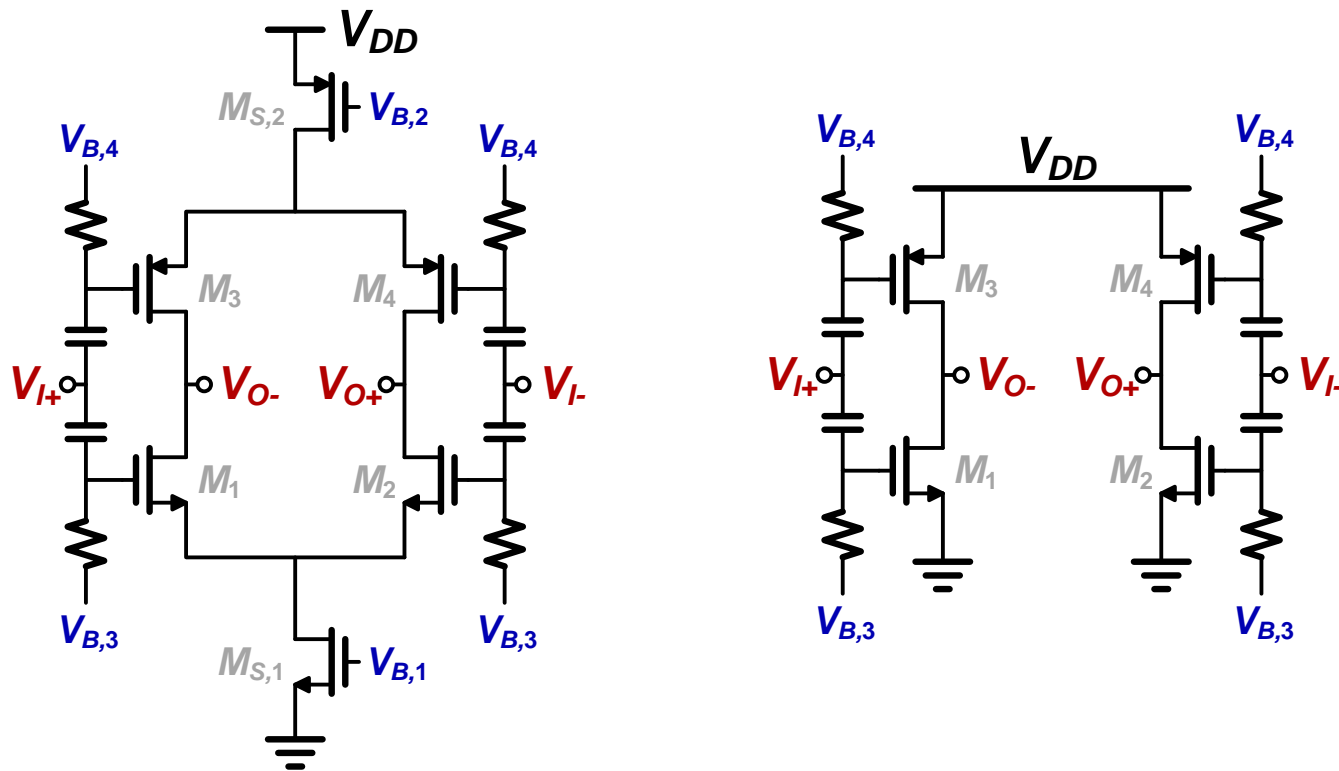



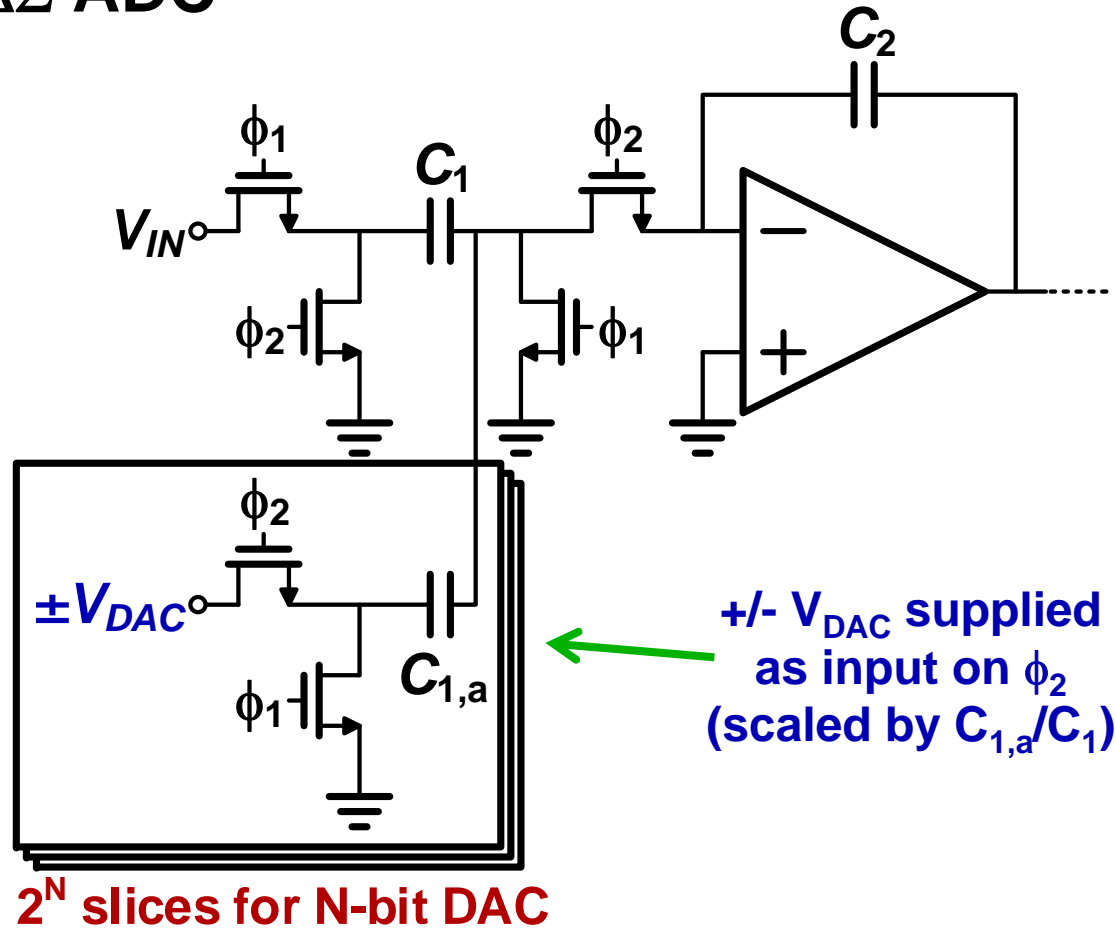
# DACs in DT $\Delta\Sigma$ ADCs

- Typical switched-capacitor DAC for a Discrete-Time  $\Delta\Sigma$  ADC


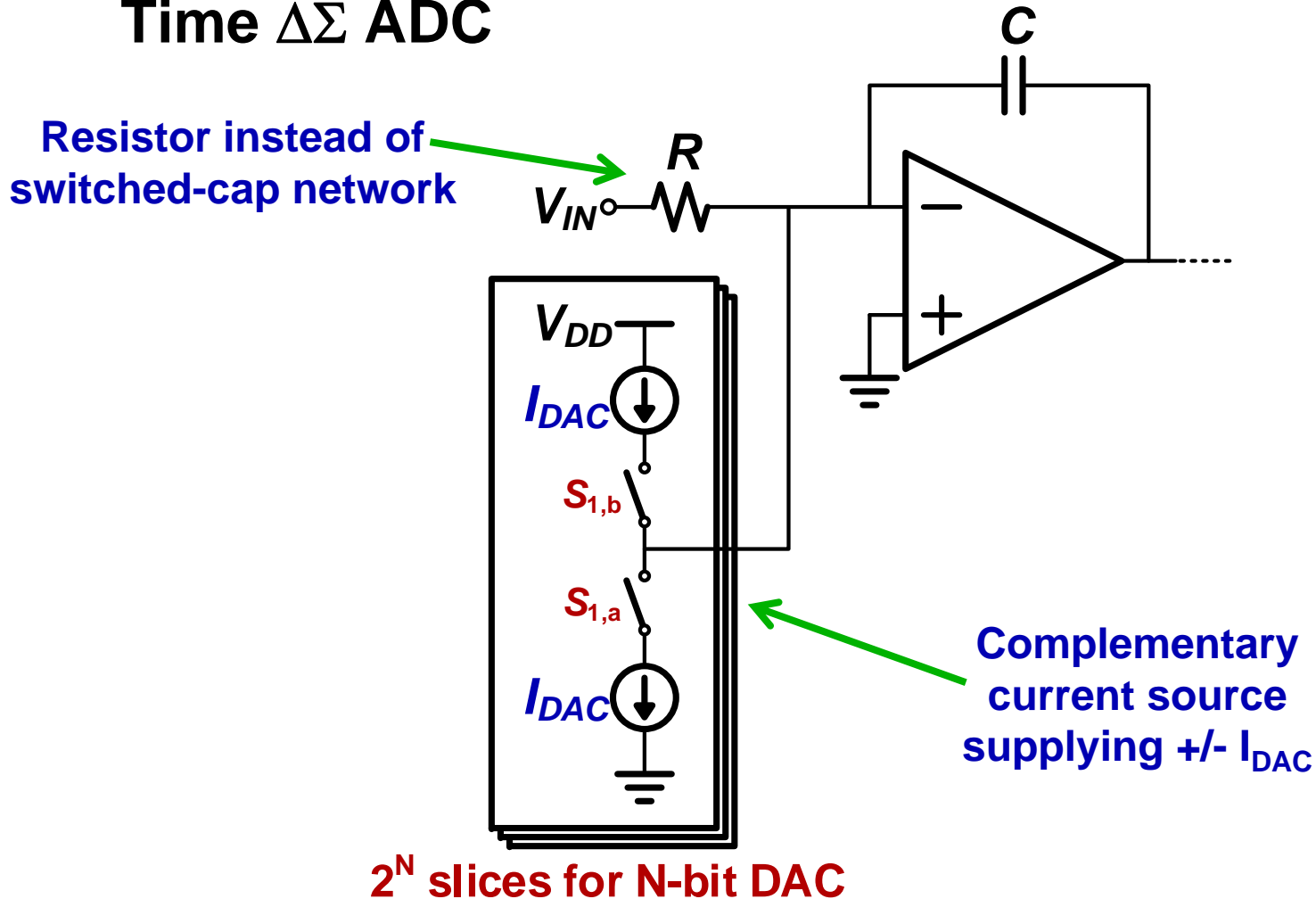
# DACs in CT $\Delta\Sigma$ ADCs

- Typical current-mode DAC for a Continuous-Time  $\Delta\Sigma$  ADC





# DACs in CT $\Delta\Sigma$ ADCs

- **Benefits of complementary DAC**

All current used as signal current

Smaller  $g_m$ , smaller (3dB) noise current

$$\overline{i_n^2} = 4kT\gamma g_m$$

- **Benefits of NMOS (or PMOS) DAC**

Only NMOS (or PMOS) current sources are sized for matching, lower total area

$$\left. \frac{\sigma_I}{I} \right|_{VT} = \sigma_{VT} \frac{2}{V_{GS} - V_T} = \frac{A_{VT}}{\sqrt{WL}} \frac{2}{(V_{GS} - V_T)}$$

Fewer transistor in stack, more headroom for  $V_{EFF}$  in current sources (slightly lower noise)

# DACs in CT $\Delta\Sigma$ ADCs


- **Return-to-Zero vs Non-Return-to-Zero**

**RZ:** DAC pulse only lasts a fraction of the period  $T$

Improved linearity, reduced jitter tolerance

**NRZ:** DAC pulse lasts entire period  $T$

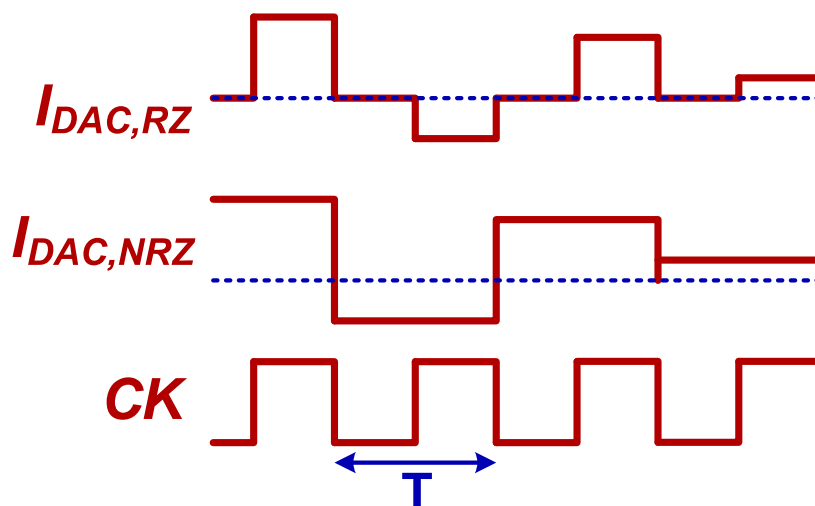Nonlinear due to mismatch in rise/fall time (even order), improved jitter tolerance




# Flash/DAC Path in CT $\Delta\Sigma$ ADCs

- Effect of Quantizer/DAC Delay

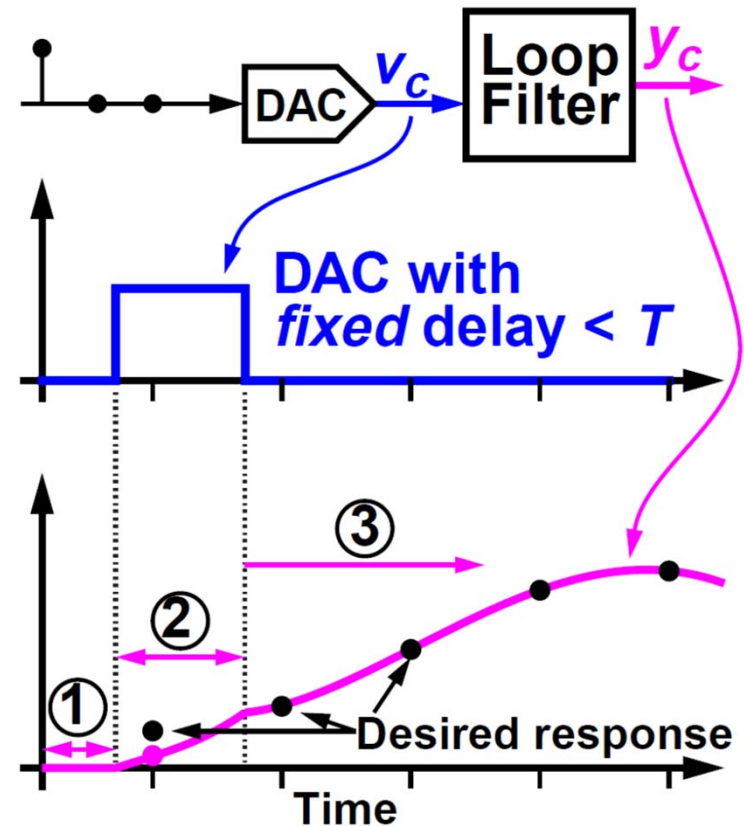
- 1) Loop outputs zero until DAC pulse begins
- 2) Loop responds as if input were a step
- 3) Loop follows trajectory of an  $n^{\text{th}}$ -order linear system with zero input but non-zero initial conditions

→ Coefficients are adjusted so samples of pulse response match the desired impulse response except at the first point; The NTF will be wrong.


 
# Flash/DAC Path in CT $\Delta\Sigma$ ADCs

- To compensate for the Feedback Delay and fix the first sample, add a direct feedback DAC



Direct Feedback DAC corrects the first sample

- With enough DACs, one for each errant sample, any finite number of points can be repaired  
In principle, the delay of the main feedback path can be anything, but the system becomes sensitive to coefficient errors






# Flash/DAC Path in CT $\Delta\Sigma$ ADCs

- Flash/DAC path can limit speed of a CT  $\Delta\Sigma$  ADC

Use flash reference shuffling

 Removes shuffling delay from critical flash/DAC path and adds it to the flash ADC block



# CT vs DT $\Delta\Sigma$ Modulators

- **Advantages of continuous-time circuits**

- Ease of Integration

- Anti-aliasing

- Noise filtering

- Amplifier current requirements (lower power)

- Improved metastability

- Bandpass  $\Delta\Sigma$  ADC

- **Disadvantages of continuous-time circuits**

- Accurate TF regardless of  $F_{CK}$

- RC tuning


- Jitter

# Advantages of CT $\Delta\Sigma$ Modulators


- Integration with other circuits

Easily interface with other CT circuitry

 No power-hungry high-resolution input buffer required



Continuous-Time

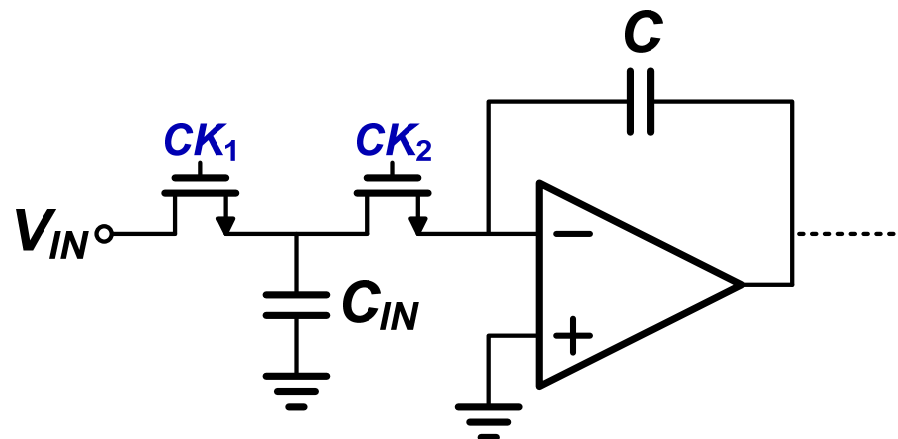


Discrete-Time
 
# Advantages of CT $\Delta\Sigma$ Modulators

- Inherent Anti-Aliasing

CT STF attenuates signals at multiples of  $F_s$






# Advantages of CT $\Delta\Sigma$ Modulators

- **Feed-forward and feedback STF comparison**

Out-of-band peaking in FF STF, less immune to blockers

Reduced anti-aliasing in FF STF

 


# Advantages of CT $\Delta\Sigma$ Modulators

- **Noise Aliasing**

In CT  $\Delta\Sigma$ , sampling/aliasing occurs at the flash A/D input, some noise gets filtered before aliasing

 In DT  $\Delta\Sigma$ , noise aliases at all stages in modulator and never gets filtered





# Advantages of CT $\Delta\Sigma$ Modulators

- **Maximum Amplifier Current**

**Continuous-time: Consistently low output current**

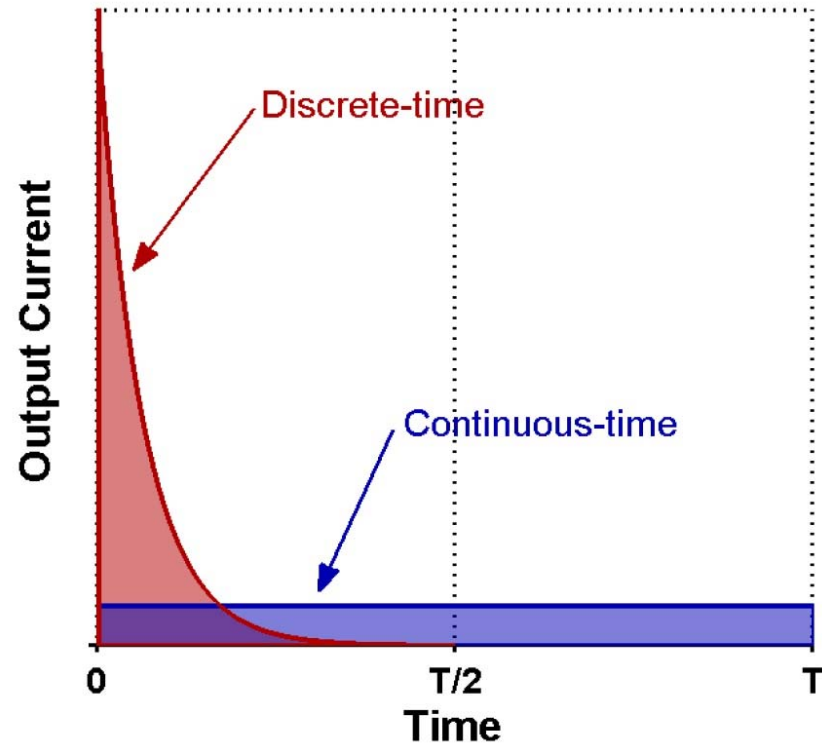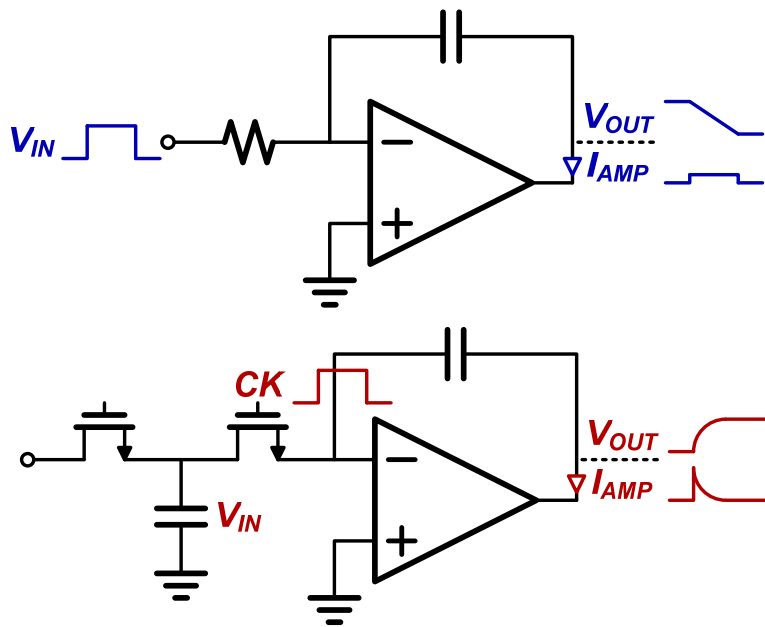**Discrete-time: Same total charge, 16x peak current (assuming  $5\tau$  settling in  $T/2$ )**






# Advantages of CT $\Delta\Sigma$ Modulators

- **Bandpass  $\Delta\Sigma$  ADCs**

Same general structure as low pass CT  $\Delta\Sigma$  ADC

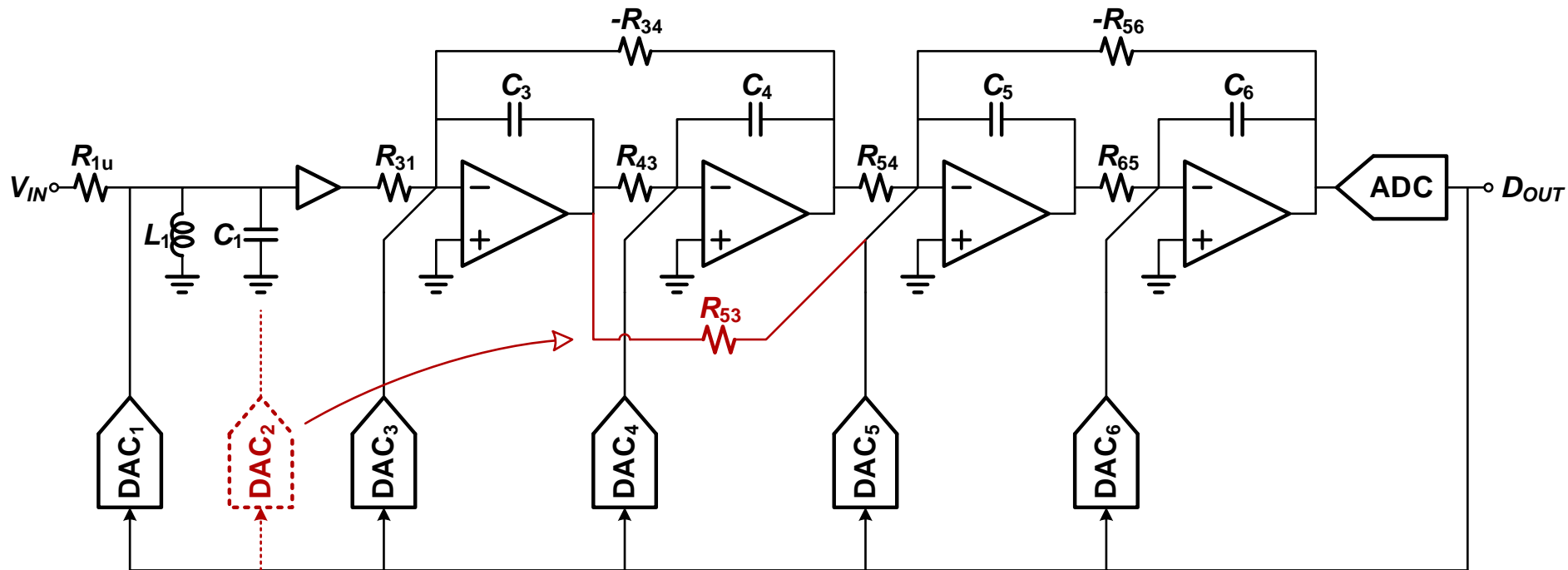Use LC or Active-RC resonators to move NTF zeros to frequencies other than DC





# Advantages of CT $\Delta\Sigma$ Modulators

- **Bandpass  $\Delta\Sigma$  ADCs**

NTF becomes a bandpass transfer function

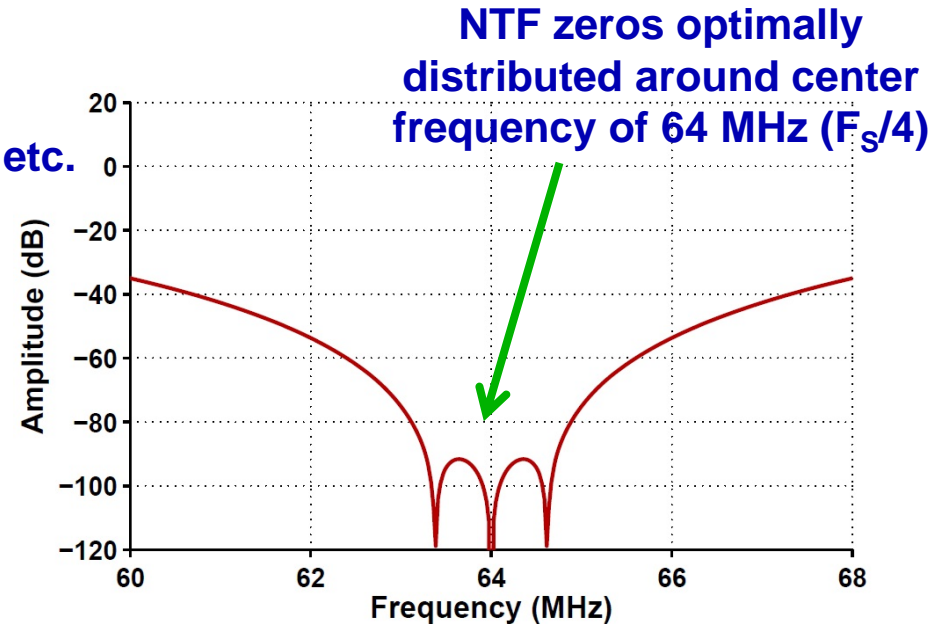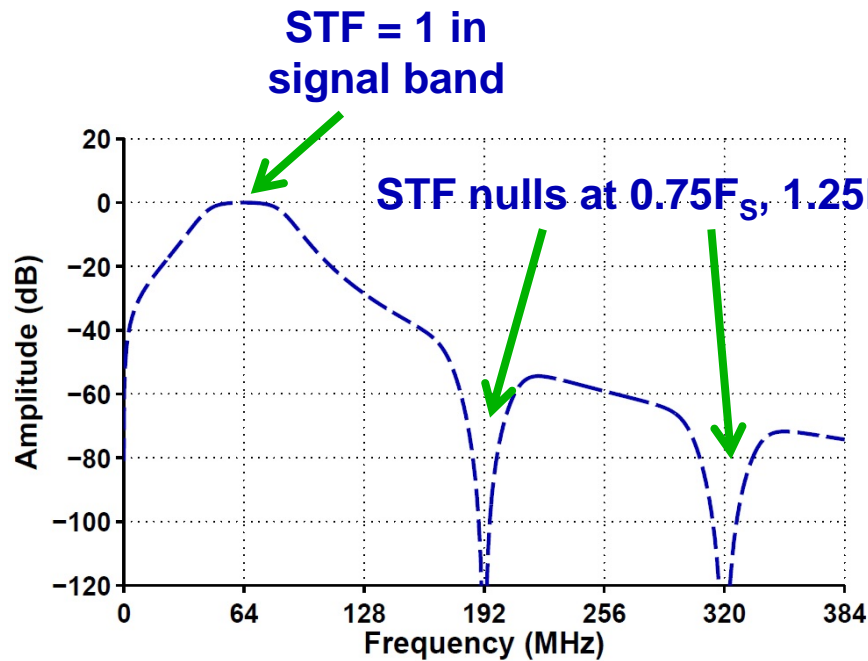Anti-aliasing preserved; STF has nulls at multiples of center frequency




# CT ADCs are faster than DT ADCs

- **DT switches are difficult in smaller technologies**
  - DT needs bootstrapping
  - No switch settling required in CT  $\Delta\Sigma$  ADCs
- **CT amplifiers have higher bandwidths**
  - Feed-forward amplifiers require lower unity-gain freqs, less peak current
- **CT  $\Delta\Sigma$  operations have a full period T**
  - DT ADCs perform sample/integrate operations in T/2
- **CT  $\Delta\Sigma$  has lower metastability error**
  - Metastability error can limit maximum frequency of ADC
  - In CT, full period T is available in feedback (with direct feedback path)
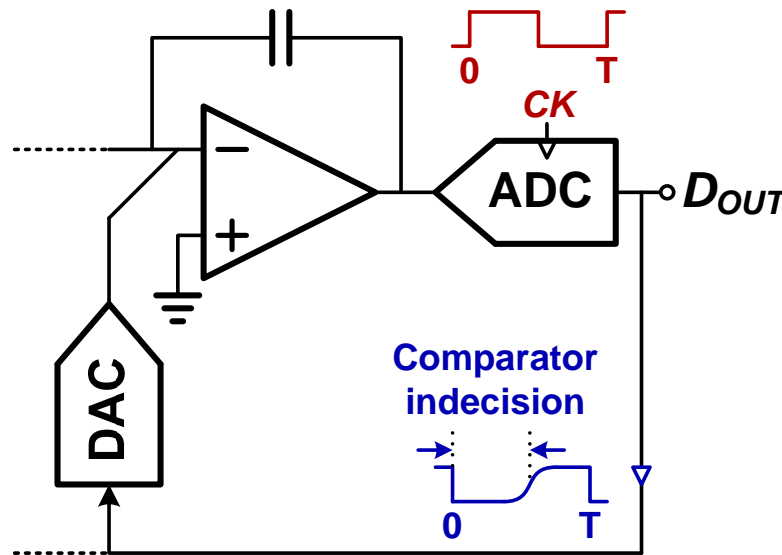
# Metastability



- Indecision in comparator causes late DAC pulse  
DAC signal is different from digital output  $D_{OUT}$   
Introduces error at input of  $\Delta\Sigma$  modulator  
Typically causes larger errors in DT  $\Delta\Sigma$  over CT  $\Delta\Sigma$


 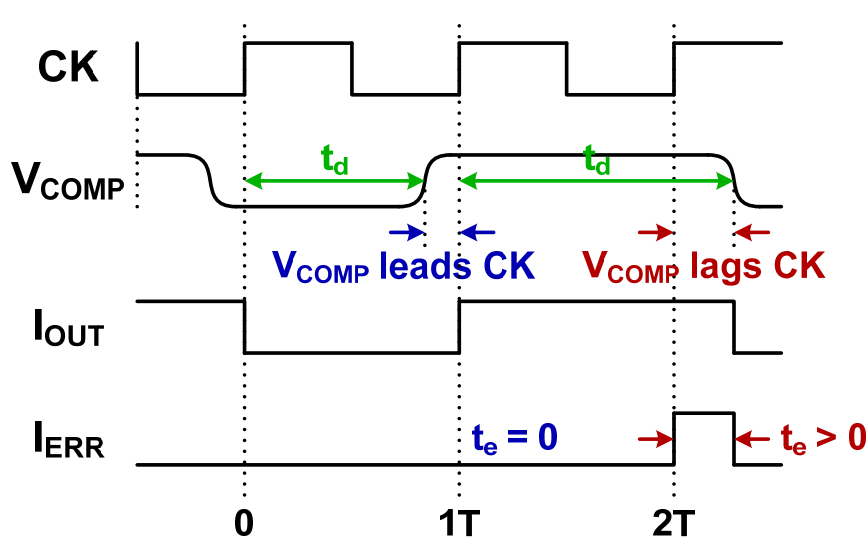
# Metastability in CT $\Delta\Sigma$

- Continuous-Time Front-End

Error occurs when comparator metastability causes DAC pulse to arrive late



# Metastability in CT $\Delta\Sigma$


- Comparator delay  $t_d$  depends on  $V_{IN}$

$\tau_{\text{regen}}$ : latch regeneration time constant

$V_0$ : voltage below which metastability introduces error

$T_{\text{meta}}$ : delay above which metastability introduces error

 $t_0$ : delay for an input of 1V (large signal delay)



# Metastability in CT $\Delta\Sigma$

- **Signal to Metastability Noise Ratio (SMNR)**

M-element flash has only one comparator near threshold with a metastability error

Oversampling advantage reduces metastability noise by OSR

$$SMNR = OSR \frac{M^2/2}{\sigma_{e_{meta}}^2}$$
$$\sigma_{e_{meta}}^2 = 2 \left( \frac{2\tau_{regen}}{T} \right)^2 \cdot \frac{e^{-(T_{meta}-t_0)/\tau_{regen}}}{V_{LSB}}$$



Ex: OSR = 8, M = 16,  $V_{LSB} = 25\text{mV}$ ,  $\tau_{regen} = 10\text{ps}$ ,  $t_0 = 100\text{ps}$

**For SMNR > 80dB,  $1/T < 2.7\text{GHz}$**
 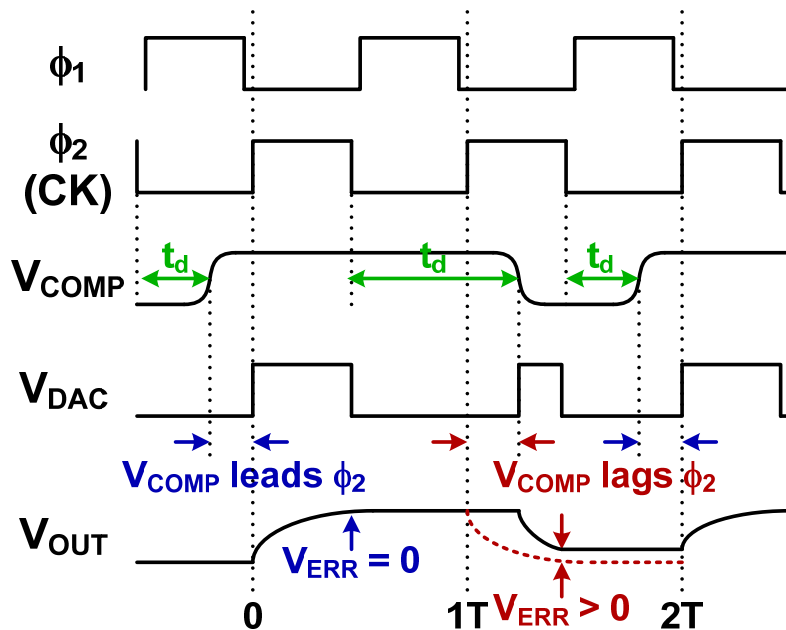
# Metastability in DT $\Delta\Sigma$

- Discrete-Time Front-End

Error occurs when comparator metastability gives amplifier less time to settle





# Recent High-Speed CT and DT ADCs

Continuous-Time	Architecture	Bandwidth	SNR/DR	Power	$F_s$	CMOS
Dong et al. ISSCC16	1-2 MASH (LP)	465 MHz	69 dB	930 mW	8 GHz	28 nm
Wu et al. ISSCC16	4 <sup>th</sup> -order FF (LP)	160 MHz	72 dB	40 mW	2.9 GHz	16 nm
Shibata et al. JSSC12	6 <sup>th</sup> -order FB (BP/LP)	150 MHz	74 dB	750 mW	4 GHz	65 nm
Bolatkale et al. JSSC11	3 <sup>rd</sup> -order FF (LP)	125 MHz	70 dB	260 mW	4 GHz	45 nm
Caldwell et al. CICC13	4 <sup>th</sup> -order FB (LP)	100 MHz	60 dB	95 mW	1.5 GHz	65 nm
Ho et al. VLSI14	4 <sup>th</sup> -order FF (LP)	80 MHz	73 dB	23 mW	2.2 GHz	20 nm
Srinivasan et al. ISSCC12	3 <sup>rd</sup> -order FF (LP)	60 MHz	62 dB	20 mW	6 GHz	45 nm
Dong et al. ISSCC14	0-3 MASH (LP)	53 MHz	83 dB	235 mW	3.2 GHz	28 nm
Yoon et al. ISSCC15	3-1 MASH (LP)	50 MHz	85 dB	78 mW	1.8 GHz	28 nm

Discrete-Time	Architecture	Bandwidth	SNR/DR	Power	$F_s$	CMOS
Ali et al. ISSCC14	Pipeline	500 MHz	69 dB	1200 mW	1 GHz	65 nm
Chen et al. VLSI11	TI Pipeline (x2)	1500 MHz	61 dB	500 mW	3 GHz	40 nm
Wu et al. ISSCC16	TI Pipeline (x4)	500 MHz	56 dB	300 mW	4 GHz	16 nm



# Disadvantages of CT $\Delta\Sigma$ Modulators

- RC Tuning

CT  $\Delta\Sigma$  transfer functions depend on RC time constants

Tuning required to match RC with sampling frequency

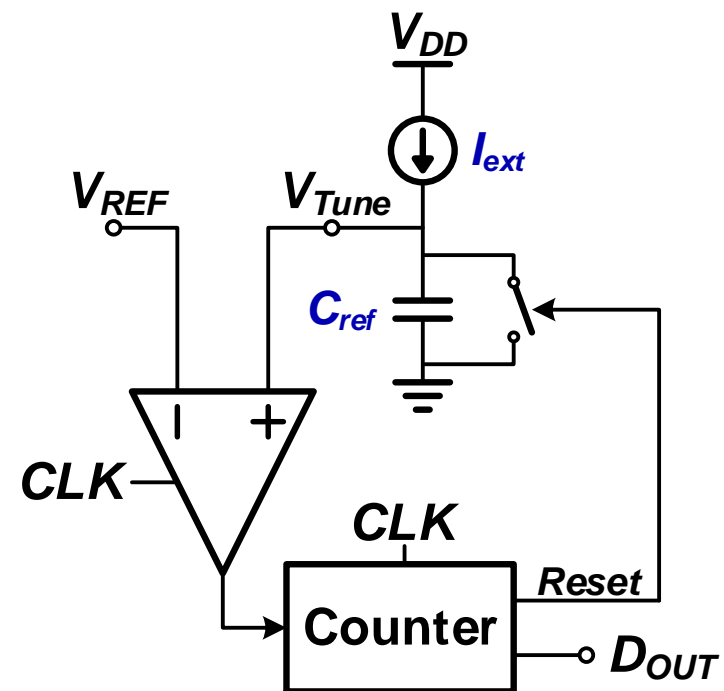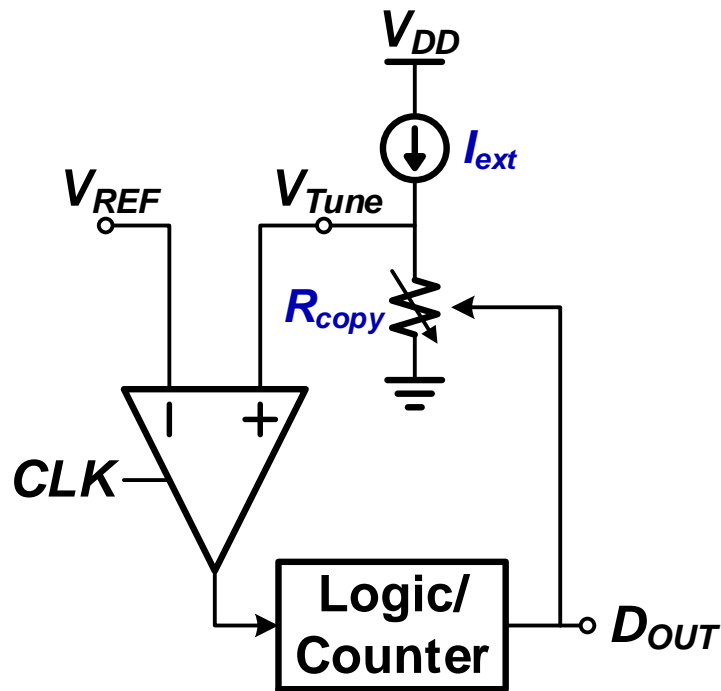
On-chip tuning is simple with modern technologies


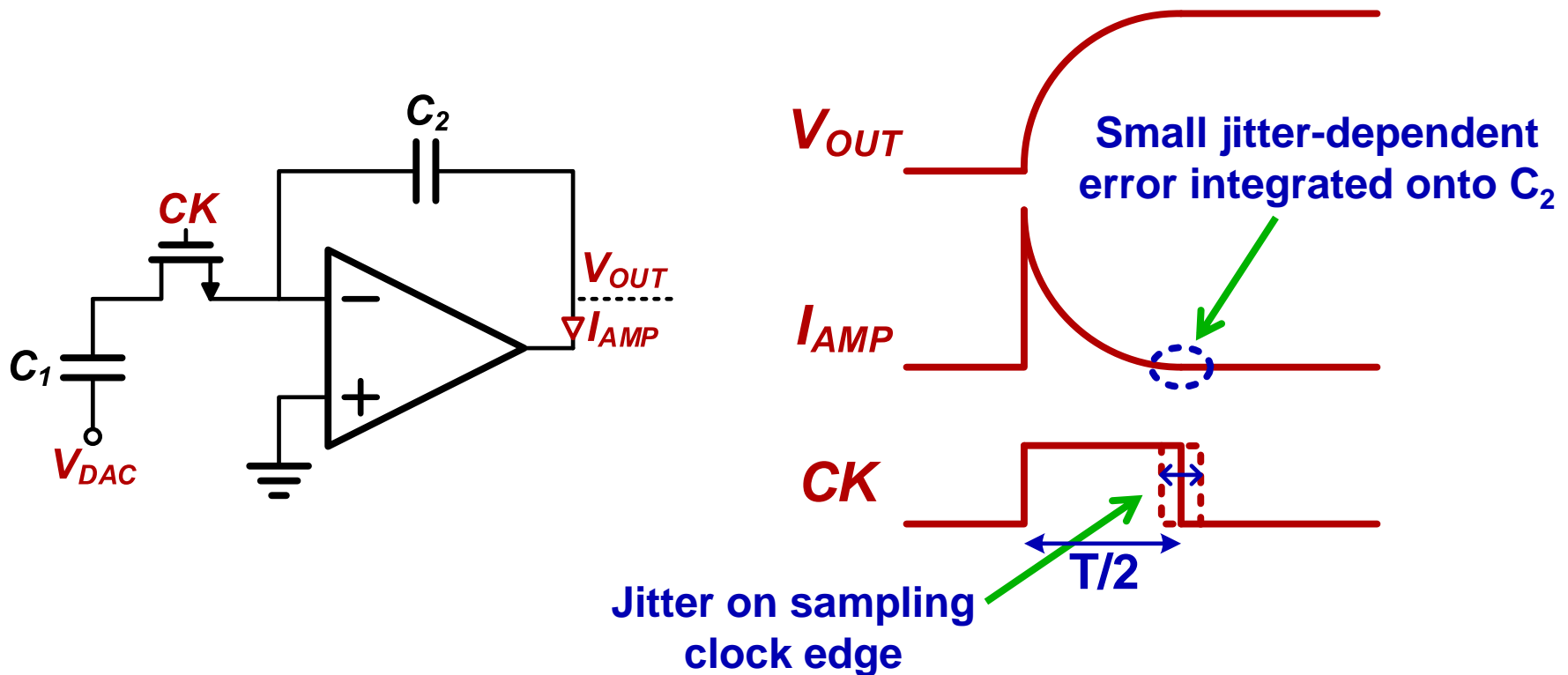
# Disadvantages of CT $\Delta\Sigma$ Modulators

- **Jitter in DT feedback DAC**

DAC signal is mostly supplied at start of clocking period  
Error from jitter is small relative to total DAC signal





# Disadvantages of CT $\Delta\Sigma$ Modulators

- **Jitter in CT feedback DAC**


DAC signal is uniform throughout clocking period

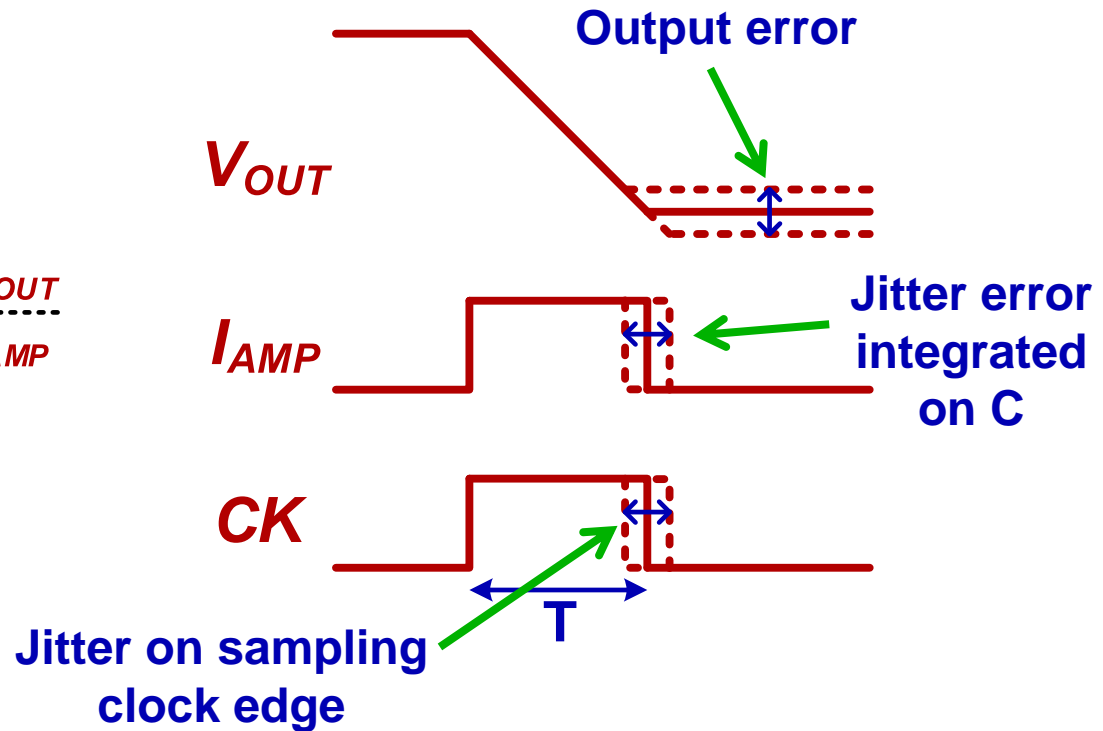 Error from jitter is larger relative to total DAC signal



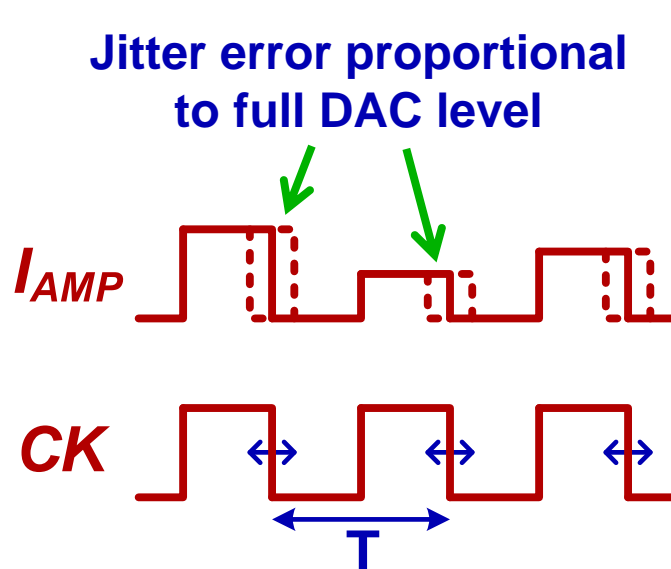
# Disadvantages of CT $\Delta\Sigma$ Modulators

- **Return-to-Zero (RZ) vs Non-Return-to-Zero (NRZ)**  
NRZ has less jitter than RZ DAC pulses  
Similarly, multi-bit DACs have less jitter than single-bit



Return-to-Zero

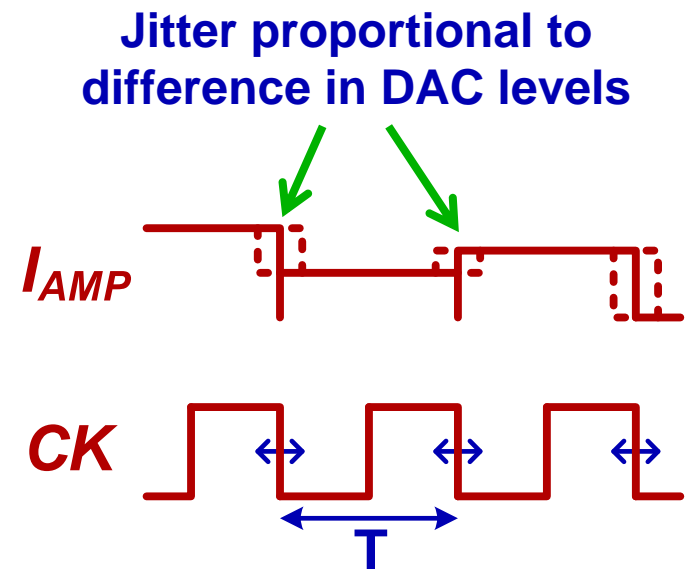

Non-Return-to-Zero

# What You Learned Today

- **Continuous-Time  $\Delta\Sigma$  modulator**
- **Compare DT and CT  $\Delta\Sigma$  ADCs**  
Differences in loop filter, amplifiers, DACs, DFB
- **Advantages and disadvantages of CT circuits**  
CT  $\Delta\Sigma$  ADCs are faster than DT