

Lecture 6

Example Design 2


Trevor Caldwell
trevor.caldwell@awaveip.com

Lecture Plan

Date	Lecture (Wednesday 2-4pm)		Reference	Homework
2020-01-07	1	MOD1 & MOD2	PST 2, 3, A	1: Matlab MOD1&2
2020-01-14	2	MODN + $\Delta\Sigma$ Toolbox	PST 4, B	2: $\Delta\Sigma$ Toolbox
2020-01-21	3	SC Circuits	R 12, CCJM 14	
2020-01-28	4	Comparator & Flash ADC	CCJM 10	3: Comparator
2020-02-04	5	Example Design 1	PST 7, CCJM 14	
2020-02-11	6	Example Design 2	CCJM 18	4: SC MOD2
2020-02-18	Reading Week / ISSCC			
2020-02-25	7	Amplifier Design 1		Project
2020-03-03	8	Amplifier Design 2		
2020-03-10	9	Noise in SC Circuits		
2020-03-17	10	Nyquist-Rate ADCs	CCJM 15, 17	
2020-03-24	11	Mismatch & MM-Shaping	PST 6	
2020-03-31	12	Continuous-Time $\Delta\Sigma$	PST 8	
2020-04-07	Exam			
2020-04-21	Project Presentation (Project Report Due at start of class)			

Circuit of the Day: Non-Overlap Clock Gen

 - Our switched-capacitor circuits require two non-overlapping clocks. How do we generate them?




What you will learn...


- **Transistor-level implementation of MOD2**
Op-amp, SC CMFB, comparator, clock generator
- **MOD2 variants**
- **Variable quantizer gain**

Review: MOD2


- Standard Block Diagram

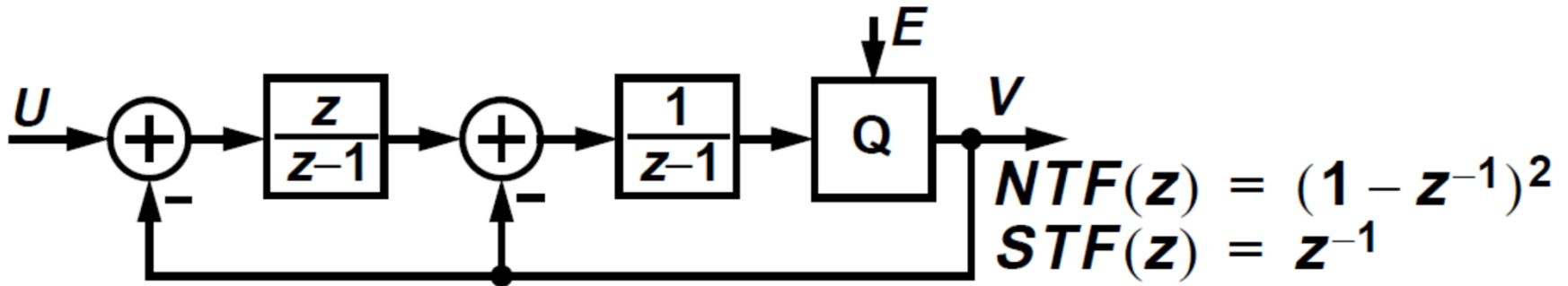

- Scaled Block Diagram

 

Review: Schematic

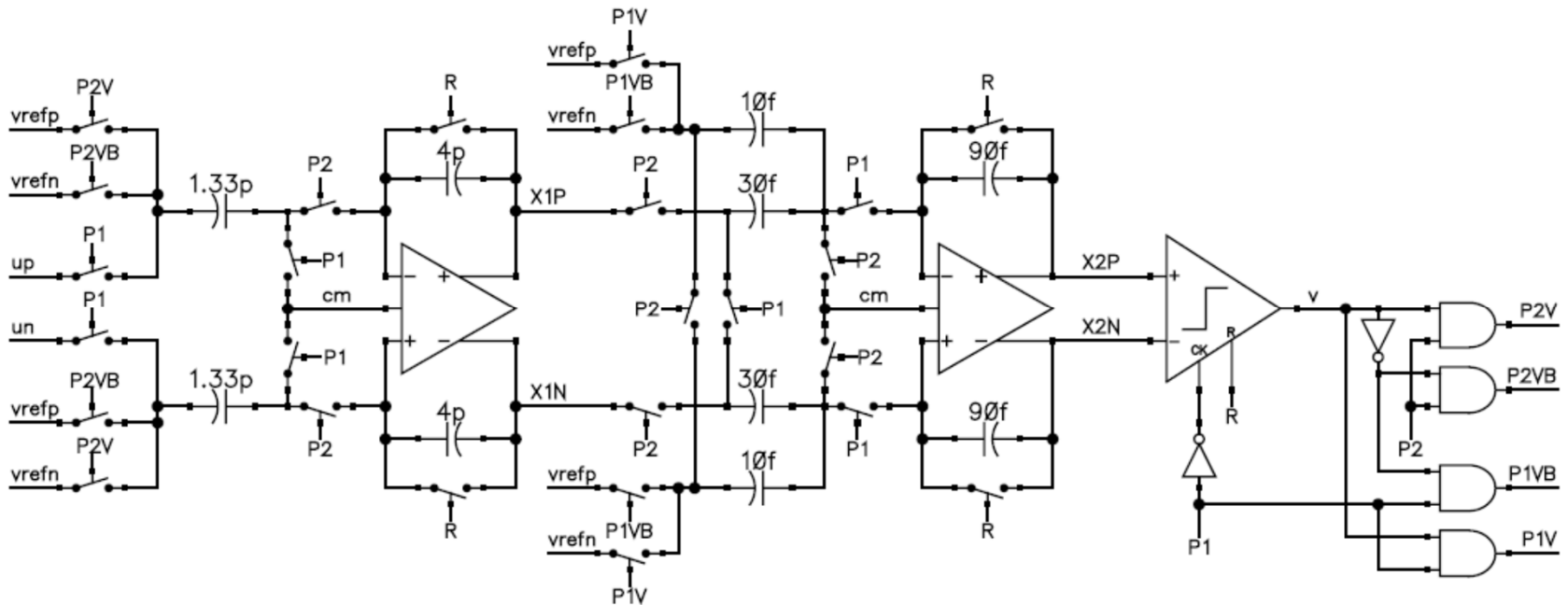


- **1st-stage capacitor sizes set for SNR = 100 dB @ OSR = 500 and -3 dBFS input**

$V_{ref} = +/- 1V$ and the full-scale input range is $+/- 1V$

- **2nd-stage capacitor sizes set by minimum allowable capacitance**

Review: Simulated Spectrum

 

Review: Implementation Summary

- ✓1) **Choose a viable SC topology and manually verify timing**
- ✓2) **Do dynamic-range scaling**
You now have a set of capacitor ratios
Verify operation: loop filter, timing, swing, spectrum
- ✓3) **Determine absolute capacitor sizes**
Verify noise
- 4) **Determine op-amp specs and construct a transistor-level schematic**
Verify everything
- 5) **Layout, fab, debug, document ...**


Effect of Finite Op Amp Gain

- Linear Theory

Suppose the amplifier has finite DC gain A

Define $\mu = 1/A$

 To determine the effect on the integrator pole, look at the SC integrator with zero input



Effect of Finite Op Amp Gain


- A fraction of q_2 leaks away each clock cycle

$$q_2(n+1) = (1 - \varepsilon)q_2(n) \text{ where } \varepsilon = \mu C_1/C_2$$

- The integrator is lossy with a pole at $z = 1 - \varepsilon$

$$\frac{V_{out}(z)}{V_{in}(z)} = \frac{C_1/C_2}{z - (1 - \varepsilon)}$$

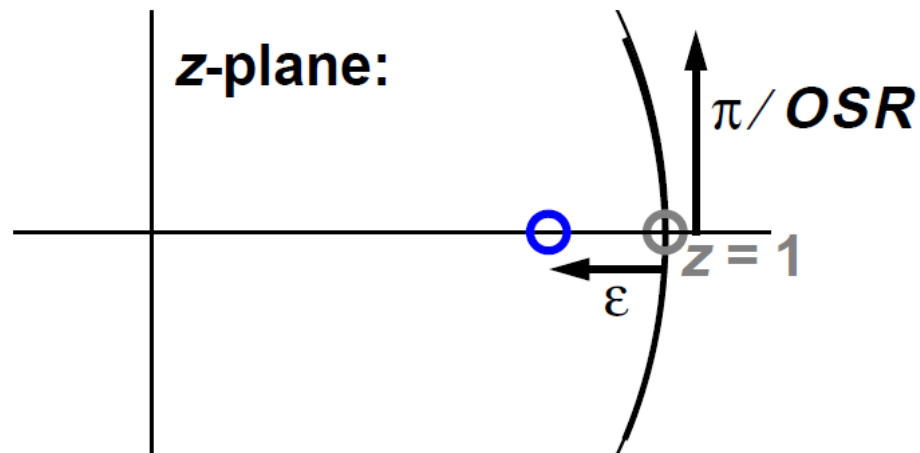- Error ε becomes significant once it approaches $\varepsilon \approx \pi/OSR$



Op Amp Gain Requirement

- According to linear theory, finite op amp gain should not degrade the noise significantly as long as

$$A > (C_1/C_2)(OSR/\pi)$$

- For our implementation of MOD2, where $C_1/C_2 = 1/3$ and $OSR = 500$, this leads to


$$A > 50 = 34\text{dB}$$

- As OSR decreases, gain requirement goes down
This does not account for non-linearities that decrease with higher DC gain

Op Amp Transconductance

- **Settling Time**

Model the op amp as a simple g_m

 

- **This is a single time constant circuit with**

$$\tau = C_{eff} / (\beta g_m)$$

Settling Requirements

- If g_m is linear, incomplete settling has the same effect as a coefficient error and thus g_m can be very low
- In practice, the g_m is not linear and we need to ensure nearly complete settling
- As a worst case scenario, let's require transients to settle to 1 part in 10^5

This should be more than enough for -100dBc distortion

Settling Requirements

- If linear settling is allocated 1/4 of a clock period

$$e^{-\frac{T/4}{\tau}} = 10^{-5} \rightarrow \tau = \frac{T}{4 \ln 10^5} = 20 \text{ns}$$

$$g_m = \frac{C_{eff}}{\beta \tau} = \frac{C_{eff}}{\beta} 4 f_s \ln 10^5$$


- For INT1 of our MOD2

$$C_{eff} = \left(\frac{4\text{p} \cdot 1.33\text{p}}{4\text{p} + 1.33\text{p}} + 30\text{f} \right) = 1.0\text{pF}$$

- For $\beta = 3/4$, $f_s = 1\text{MHz} \rightarrow g_m = 61\mu\text{A/V}$

Slewing

 
- The maximum charge transferred through C1 is



- If we require the slew current to be enough to transfer q_{max} in 1/4 of a clock period, then

$$I_{slew} = \frac{q_{max}}{T/4} \approx 5 \mu\text{A}$$

Op-Amp Design

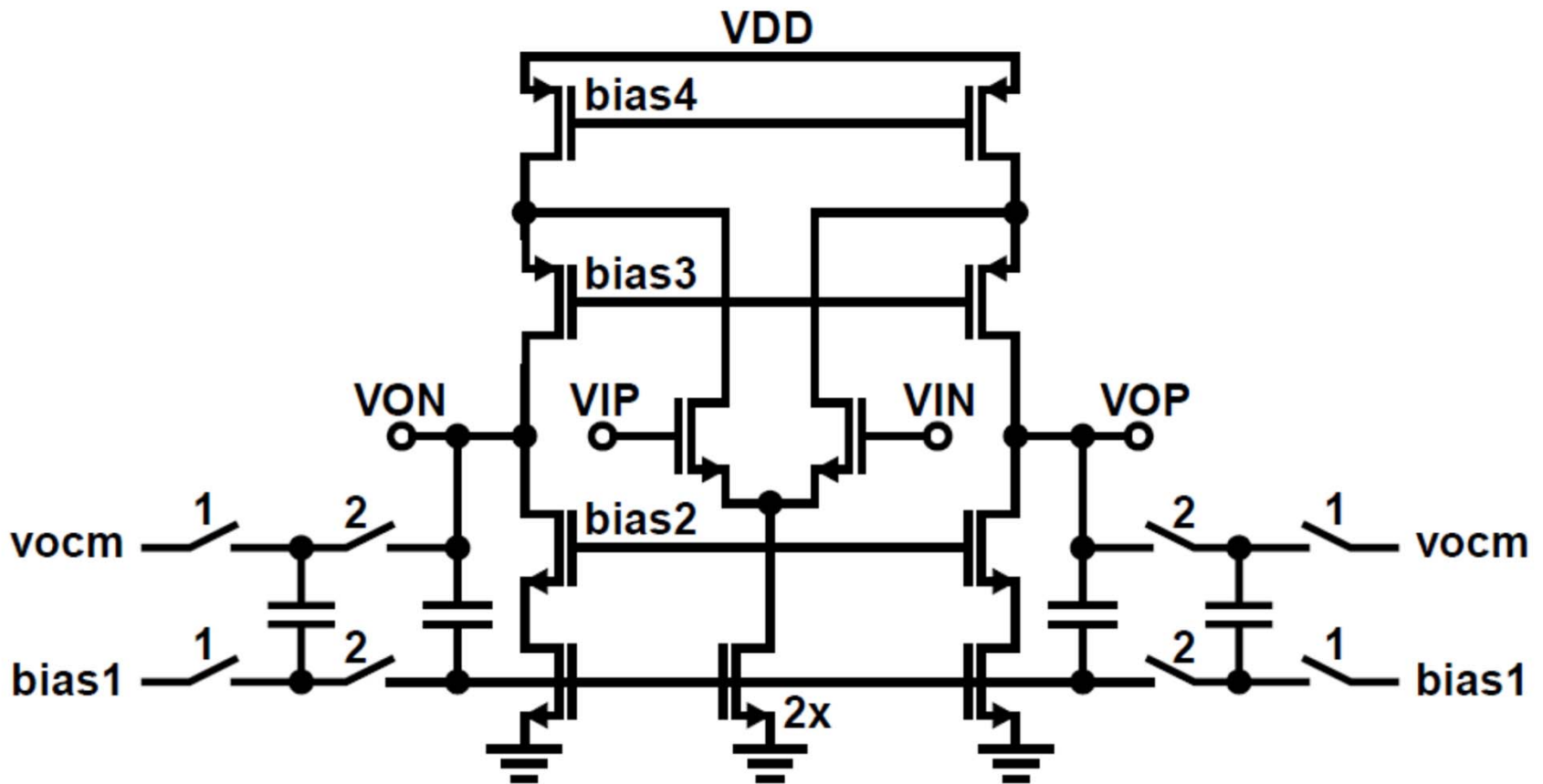


- **Folded-cascode op-amp with switched-capacitor common-mode feedback**

Op-Amp Design: Bias Current

Bias Currents


Slew Currents

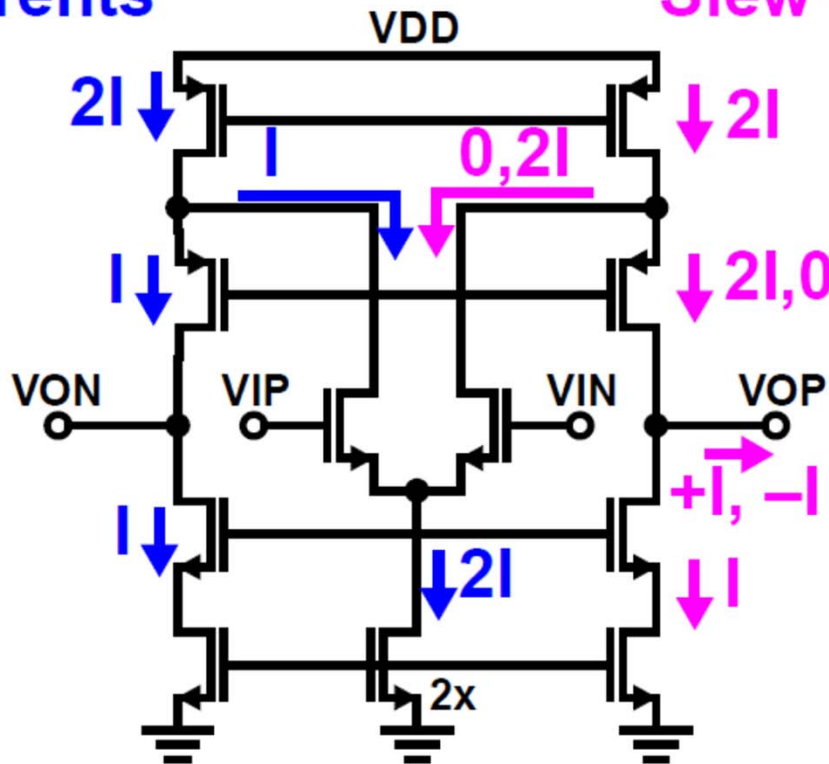

Not good practice to let currents go to 0. Need to increase the current in output leg.


- Slew constraint dictates $I > 5\mu\text{A}$

Op-Amp Design: g_m

 



- **Square-law MOSFET model: $g_m = 2I_D/\Delta V$**
- **$I_D = 5\mu\text{A}$, $g_m \geq 60\mu\text{A}/\text{V} \rightarrow \Delta V \leq 167\text{mV}$**
Usually $\Delta V \approx 100 - 200\text{mV}$, so we should be able to get high enough g_m

Ideal Common-Mode Feedback

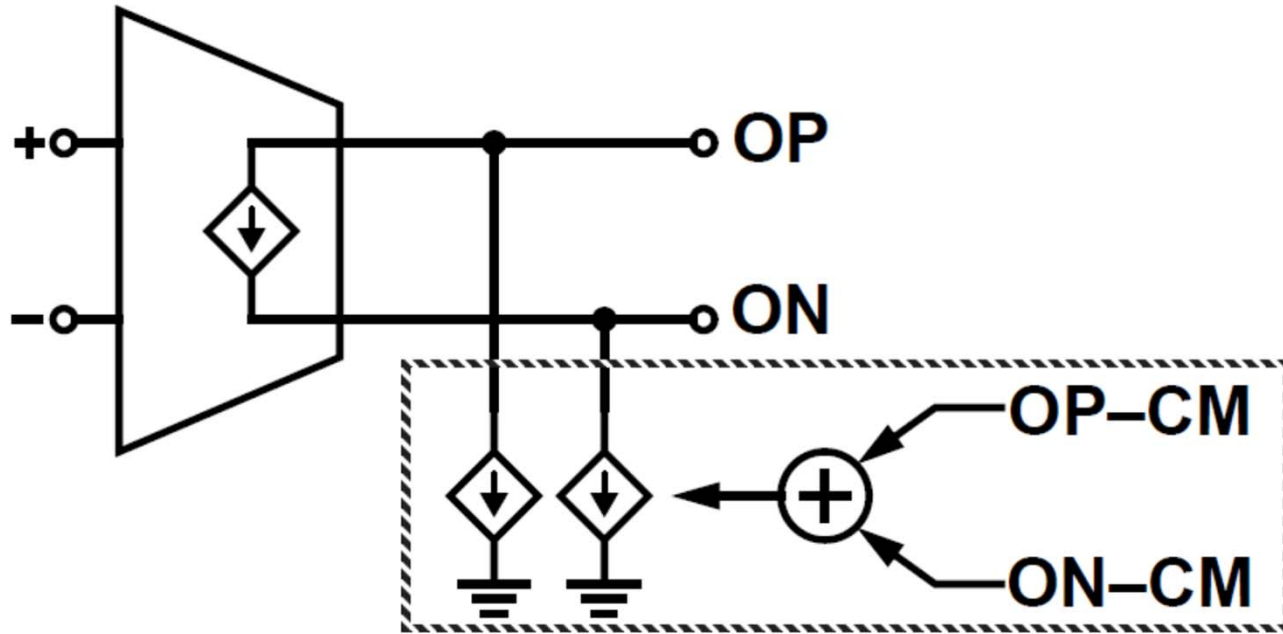

- Can use this circuit to speed up the simulation


Latched Comparator

  

- **Falling phase 1 initiates regenerative action**
S and R connected to a Set/Reset latch

Switch Resistance

- Sampling Phase

 


- If R_{sw} is constant, it has only a filtering (linear) effect which is benign
- The on-resistance of MOS switches varies with V_{gs} (and hence V_{in})
→ Must make MOS switches large enough

Switch Resistance


- Integration Phase

Differential
Half-Circuit:

 


- R_{sw} increases the settling time by a factor of $1 + 2g_m R_{sw}$
- Set $R_{sw} \leq \frac{1}{20g_m}$ to make the increase in τ small
- So in our MOD2, we want $R_{sw} \leq 0.7k\Omega$


Simulated Waveforms

 


Expanded Waveforms

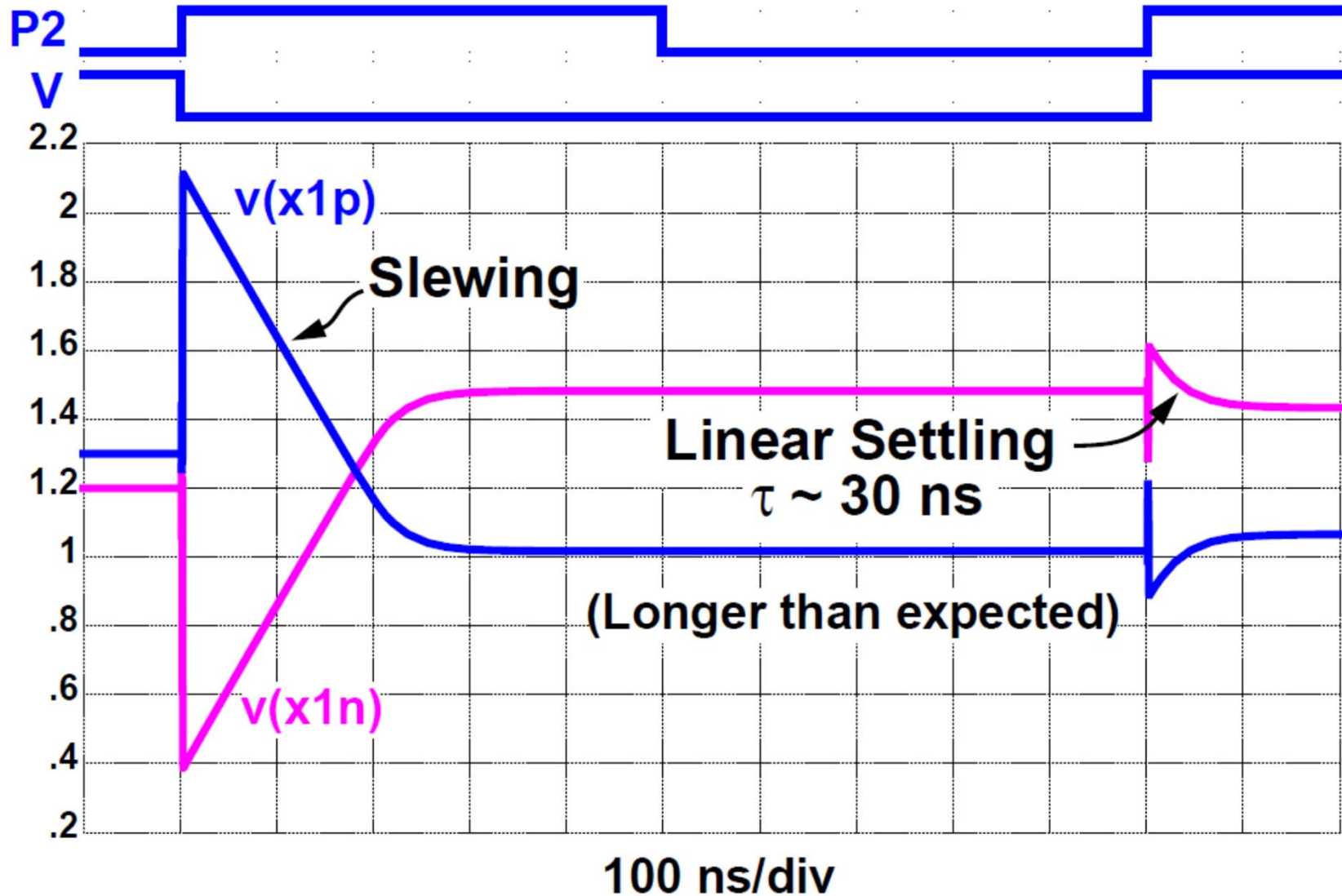

Simulated Spectrum

 


Topological Variant: Feed-Forward

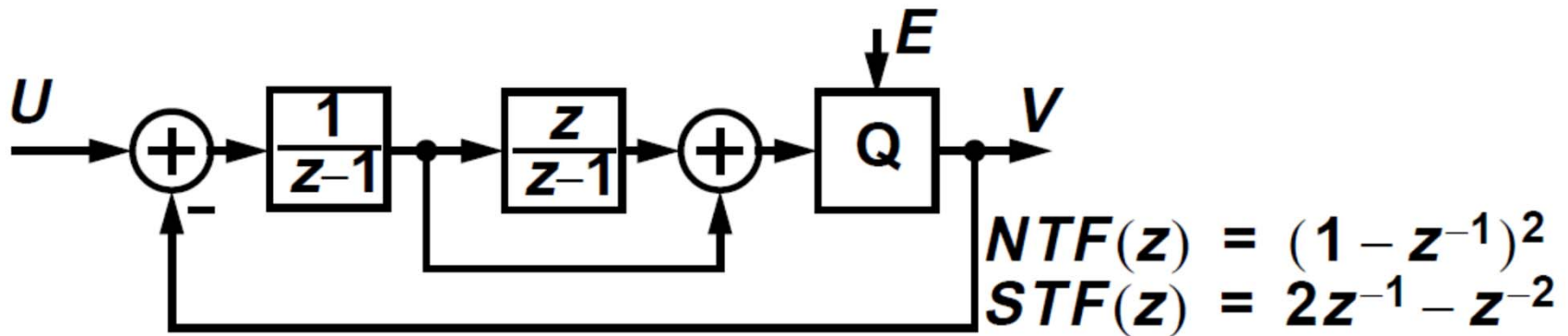


- **Output of first integrator has no DC component**
Dynamic range requirements of this integrator are relaxed
- **Although $|STF| \approx 1$ near $\omega = 0$, $|STF| = 3$ for $\omega = \pi$**
Instability is more likely

Topological Variant: Input Feed-Forward

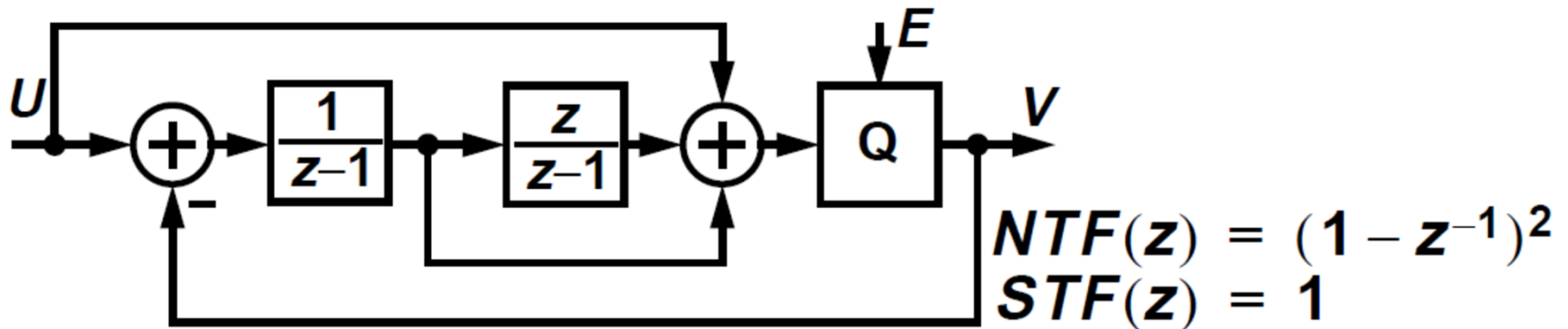

- **No DC component in either integrator's output**
Reduced dynamic range requirements in both integrators, especially for multi-bit modulators
- **Perfectly flat STF**
No increased risk of instability
- **Timing is tricky**

Topological Variant: Error Feedback

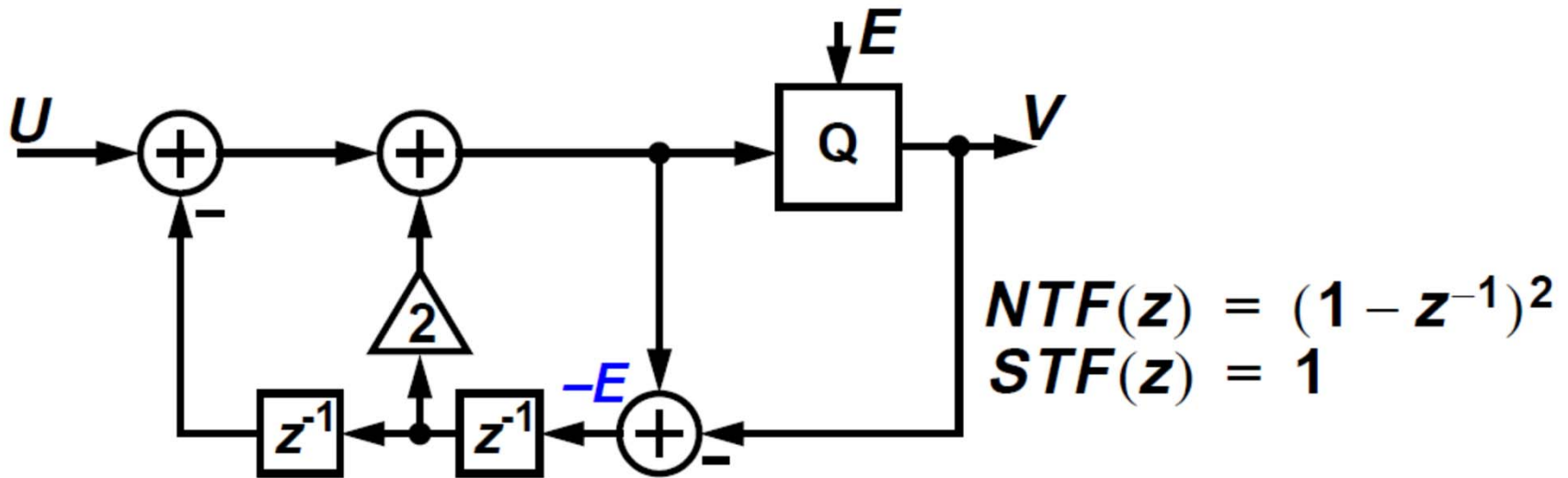


- Simple
- Very sensitive to gain errors
 - Only suitable for digital implementations


Is MOD2 the only 2nd-order modulator?

- **Except for filtering provided by the STF, any modulator with the same NTF as MOD2 has the same input-output behaviour as MOD2**
 - SQNR curve is the same
 - Tonality of the quantization noise is unchanged
- **Internal states, sensitivity, thermal noise, etc can differ from realization to realization**
- **A 2nd-order modulator is truly different only if it possesses a different 2nd-order NTF**


A Better 2nd-Order NTF

 

NTF Comparison

 


SNR vs Amp Comparison

 



MOD2 Internal Waveforms

- Input at 75% of Full-Scale

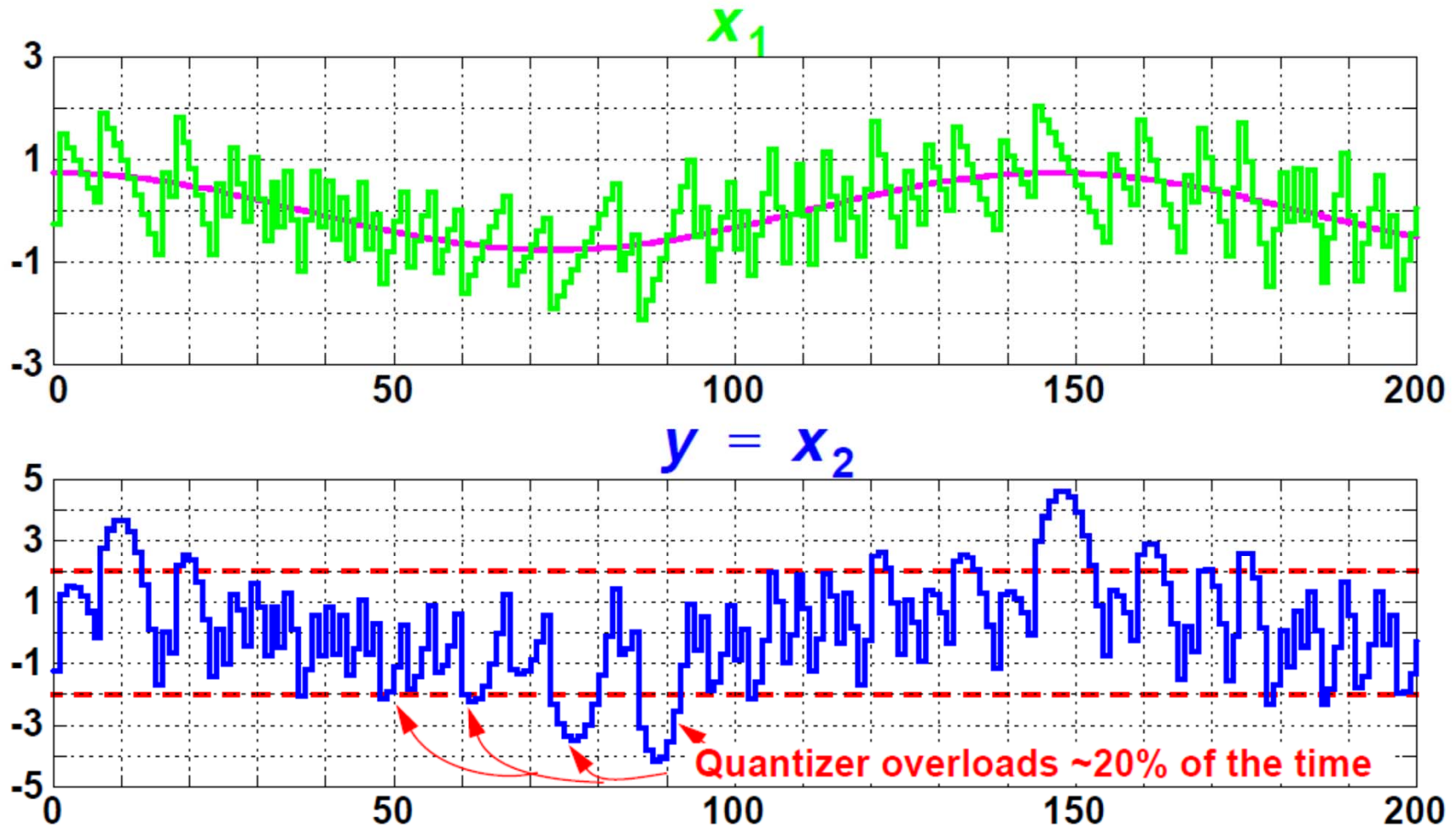


MOD2b Internal Waveforms

- Input at 75% of Full-Scale

  

Gain of a Binary Quantizer

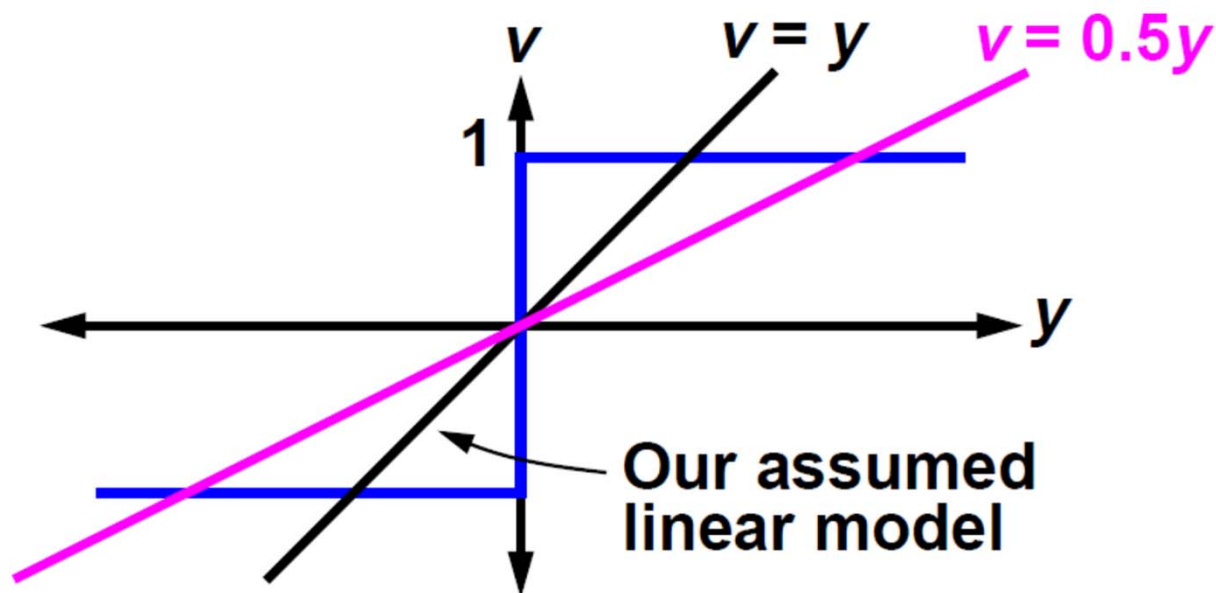

- The effective gain of a binary quantizer is not known a priori
- The gain (k) depends on the statistics of the quantizer's input
 - Halving the signal doubles the gain


Gain of the Quantizer in MOD2

- The effective gain of a binary quantizer can be computed from the simulation data using the following equation [PST Eq 2.14]


$$k = \frac{E[|y|]}{E[y^2]}$$

- $k \neq 1$ alters the NTF
 
$$NTF_k(z) = \frac{NTF_1(z)}{k + (1 - k)NTF_1(z)}$$



Revised PSD Prediction

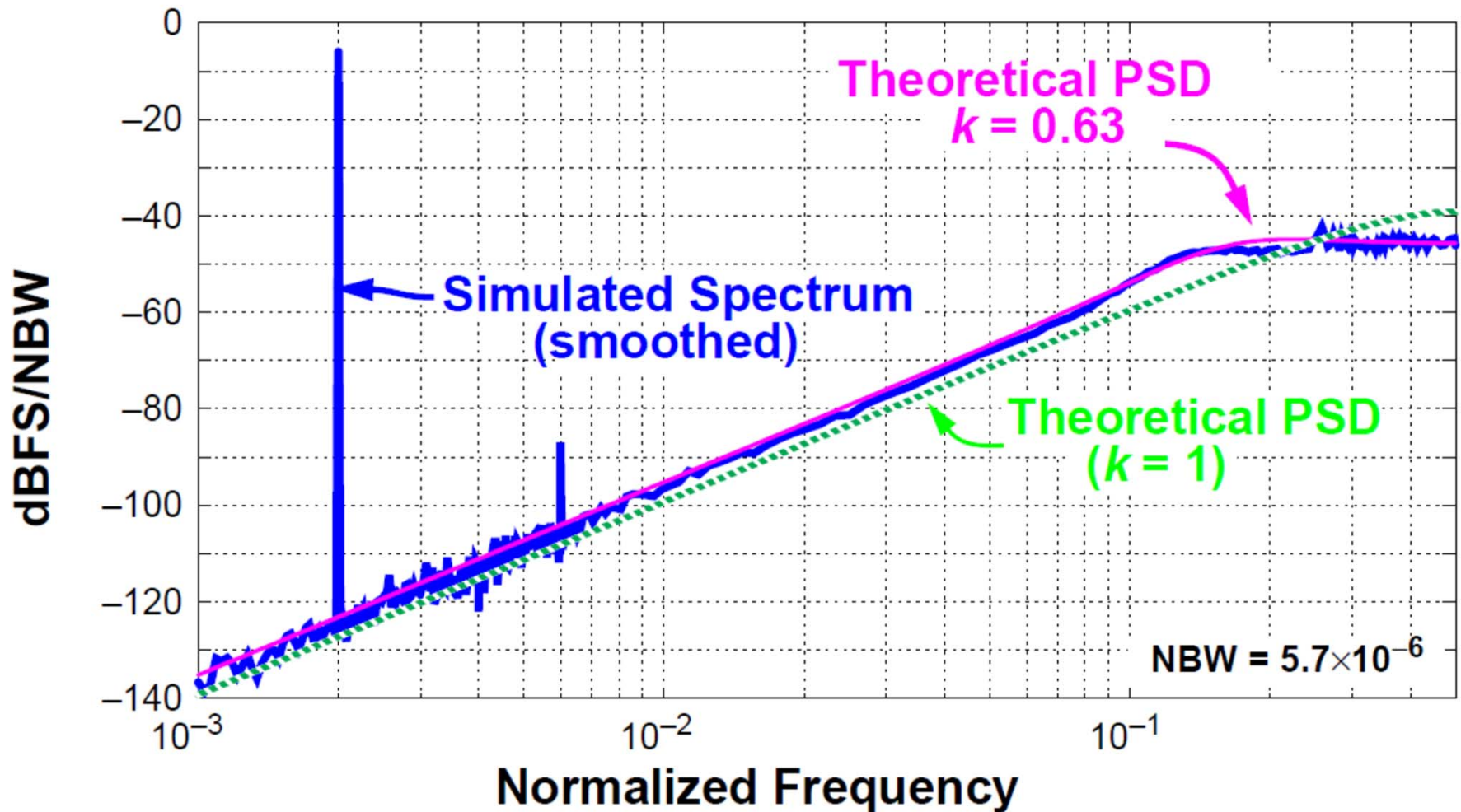

- Much more similar to theoretical PSD


Variable Quantizer Gain

- When the input is small (below -12 dBFS) the effective gain of MOD2's quantizer is $k = 0.75$
- MOD2's 'small-signal NTF' is thus



$$NTF(z) = \frac{(z - 1)^2}{z^2 - 0.5z + 0.25}$$

- This NTF has 2.5 dB less quantization noise suppression than the $(1 - z^{-1})^2$ NTF derived from the assumption that $k = 1$
- As the input signal increases, k decreases and the suppression of quantization noise degrades
SQNR increases less quickly than the signal power. Eventually the SQNR saturates and then decreases as the signal power reaches full-scale.

 Circuit of the Day: Non-Overlap Clock Gen




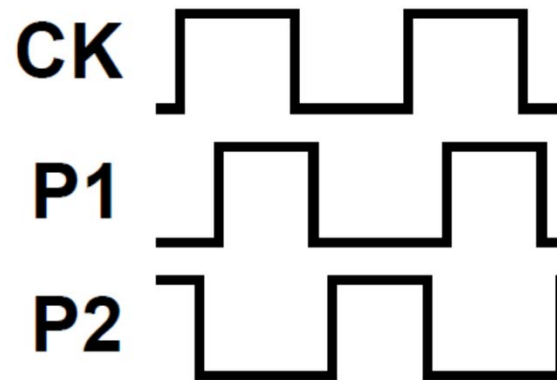 Circuit of the Day: Non-Overlap Clock Gen




- Non-overlap time set by NOR's t_{PLH}

Clocking Details, Early/Late Phases

 

- Charge injected via M1 is (non-linearly) signal-dependent while charge injection from M2 is signal-independent
- Open M2 (early) then open M1 (late) so that charge injected from C_{gs1} cannot enter C1

Clocking Details, Bottom-plate sampling

 


- Parasitic capacitance on the right terminal of C1 degrades the op-amp feedback factor β
- C_p for the top plate is smaller, so use the top plate for the right terminal and the bottom plate for the left

Complementary Clock Alignment


- We need complementary clocks if transmission gates are used for the switches

Q. How do we align them?

 
A. Carefully size the inverters relative to their capacitive loads, or use a transmission gate to mimic an inverter delay:



 **Need to match delay
of 3 INVs to 2 INVs**



Professional Clock Generator

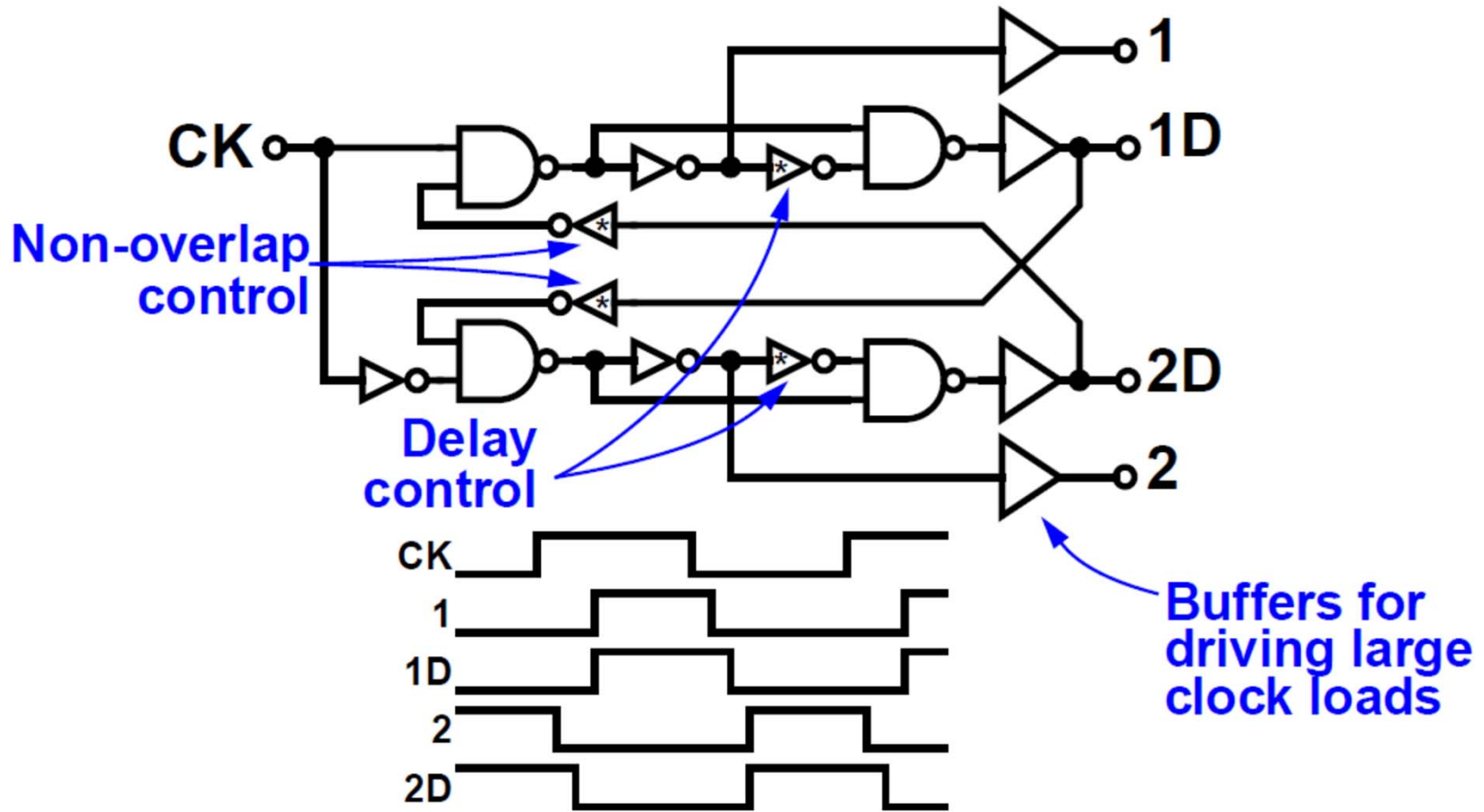

- To maximize the time available for settling, make the early and late phases start at the same time

Homework #4 (Due Feb 25*)

- **Construct a differential switched-capacitor implementation of MOD2 using ideal elements (switches, capacitors, amplifiers, comparator) and verify it.**
- **Scale the circuit such that the full-scale differential input range is $[-1,+1]$ V and the op amp swing is $0.5 V_{p,diff}$ at -6 dBFS. You may assume that -0.5 V and $+0.5$ V references are available and that the input is available in differential form.**
- **Choose capacitor values such that the SNR with a -6 dBFS input will be 90 dB when $OSR = 128$. You may assume that the only source of noise is kT/C noise.**

Homework #4 Deliverables

- 1. Block diagram after dynamic-range scaling**
- 2. Schematic with all cap values and clock phases clearly labelled**
- 3. Open-loop impulse response plot (short transient sim)**
- 4. Time-domain plots of input signal and integrator outputs for a -6 dBFS input (transient sim)**
- 5. Spectrum of output data for a -6 dBFS input, with SNDR calculated**
- 6. kT/C noise calculation (justify your choice of C)**

What You Learned Today

- **Transistor-level implementation of MOD2**
Op-amp, SC CMFB, comparator, clock generator
- **MOD2 variants**
- **Variable quantizer gain**