

# **Lecture 9**

## **Noise in Switched-Capacitor Circuits**

**Trevor Caldwell**  
**[trevor.caldwell@awaveip.com](mailto:trevor.caldwell@awaveip.com)**

# Lecture Plan

Date	Lecture (Wednesday 2-4pm)		Reference	Homework
2020-01-07	1	MOD1 & MOD2	PST 2, 3, A	1: Matlab MOD1&2
2020-01-14	2	MODN + $\Delta\Sigma$ Toolbox	PST 4, B	2: $\Delta\Sigma$ Toolbox
2020-01-21	3	SC Circuits	R 12, CCJM 14	
2020-01-28	4	Comparator & Flash ADC	CCJM 10	3: Comparator
2020-02-04	5	Example Design 1	PST 7, CCJM 14	
2020-02-11	6	Example Design 2	CCJM 18	4: SC MOD2
2020-02-18	Reading Week / ISSCC			
2020-02-25	7	Amplifier Design 1		Project
2020-03-03	8	Amplifier Design 2		
2020-03-10	9	Noise in SC Circuits		
2020-03-17	10	Nyquist-Rate ADCs	CCJM 15, 17	
2020-03-24	11	Mismatch & MM-Shaping	PST 6	
2020-03-31	12	Continuous-Time $\Delta\Sigma$	PST 8	
2020-04-07	Exam			
2020-04-21	Project Presentation (Project Report Due at start of class)			

# Circuit of the Day: Constant- $G_M$ Biasing

- How do we bias transistors so that the transconductance does not depend on:
  - Temperature
  - Process
  - Supply Voltage
- Make it dependent on a bias resistor  $R_B$

$$g_m \propto \frac{1}{R_B}$$

# What you will learn...

- **How to analyze noise in switched-capacitor circuits**
- **Significance of switch noise vs. OTA noise**
  - Power efficient solution**
  - Impact of OTA architecture**
- **Design example for  $\Delta\Sigma$  modulator**

# Review


- Previous analysis of  $kT/C$  noise (ignoring OTA/opamp noise)

Phase 1:  $kT/C_1$  noise (on each side)

Phase 2:  $kT/C_1$  added to previous noise (on each side)

Total Noise (input referred):  $2kT/C_1$

Differentially:  $4kT/C_1$

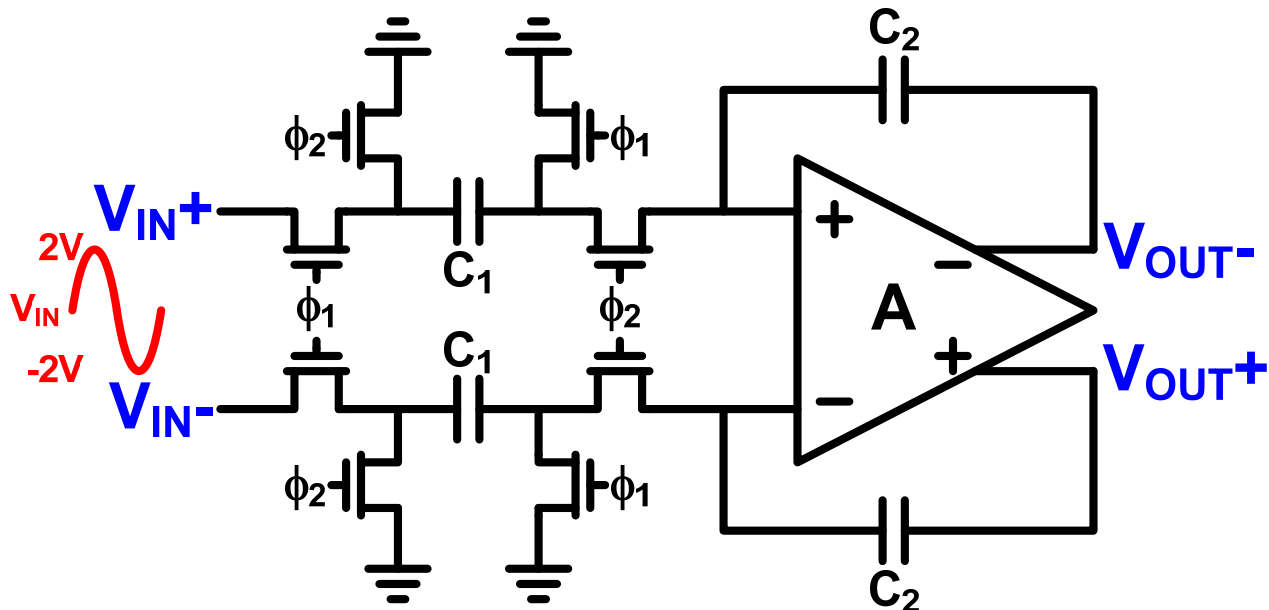

# Review

- **SNR (differential)**

Total noise power:  $4kT/C_1$

Signal power:  $(2V)^2/2$

SNR:  $V^2C_1/2kT$

- **SNR (single-ended)**

Total noise power:  $2kT/C_1$  (sampling capacitor  $C_1$ )

Signal power:  $V^2/2$  (signal from  $-V$  to  $V$ )


SNR:  $V^2C_1/4kT$

# Noise in an Integrator

- Two noise sources  $V_{C_1}$  and  $V_{OUT}$

$V_{C_1}$ : Represents input-referred sampled noise on input switching transistors + OTA

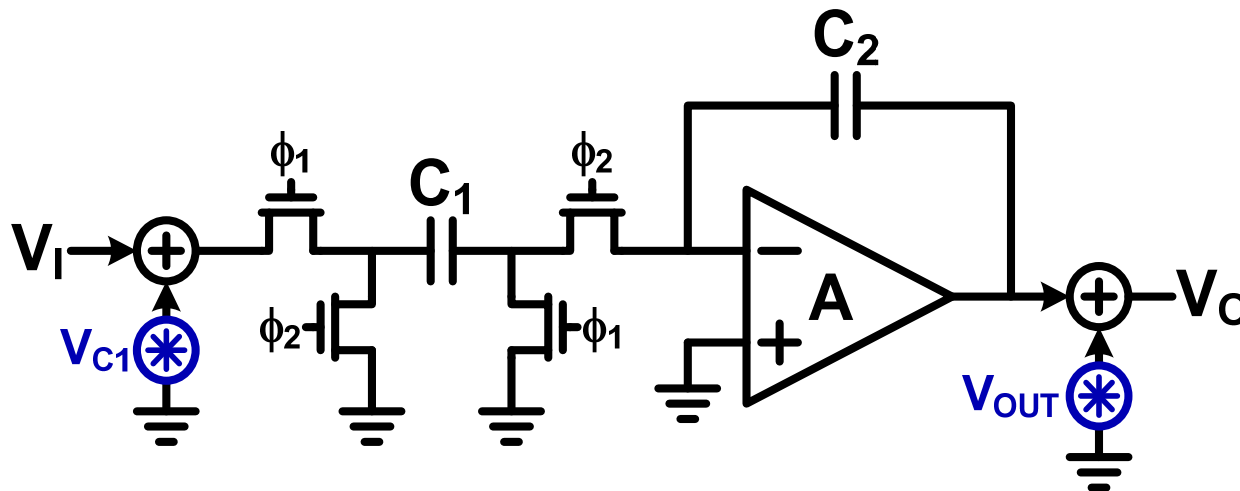$V_{OUT}$ : Represents output-referred (non-sampled) noise from OTA




# Thermal Noise in OTAs

- **Single-Ended Example**

Noise current from each transistor is  $\overline{I_n^2} = 4kT\gamma g_m$

Assume  $\gamma = 2/3$

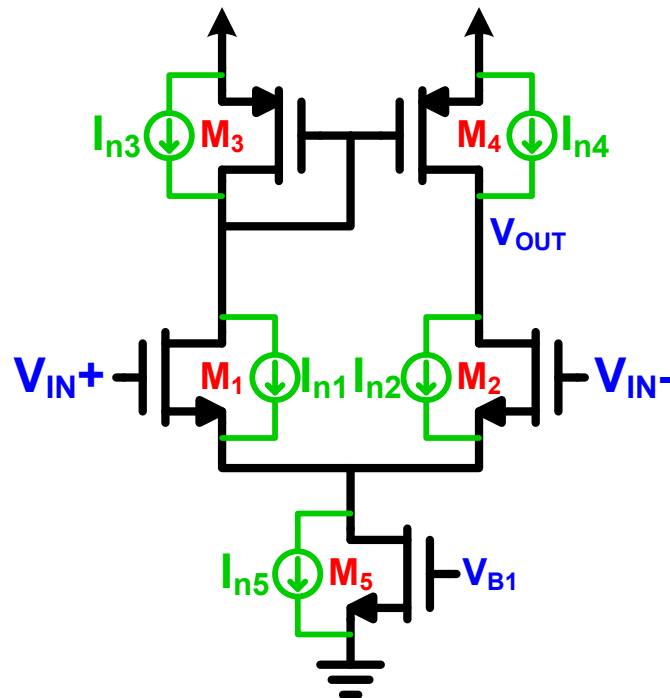



# Thermal Noise in OTAs

- **Single-Ended Example**

Thermal noise in single-ended OTA

Assuming paths match, tail current source  $M_5$  does not contribute noise to output

PSD of noise voltage in  $M_1$  (and  $M_2$ ):  $\frac{8}{3} \frac{kT}{g_{m1}}$

PSD of noise voltage in  $M_3$  (and  $M_4$ ):  $\frac{8}{3} \frac{kT g_{m3}}{g_{m1}^2}$


Total input referred noise from  $M_1 - M_4$

$$S_{n,eq} = \frac{16}{3} \frac{kT}{g_{m1}} \left( 1 + \frac{g_{m3}}{g_{m1}} \right) = \frac{16}{3} \frac{kT}{g_{m1}} n_M$$

Noise multiplier  $n_M$  depends on architecture
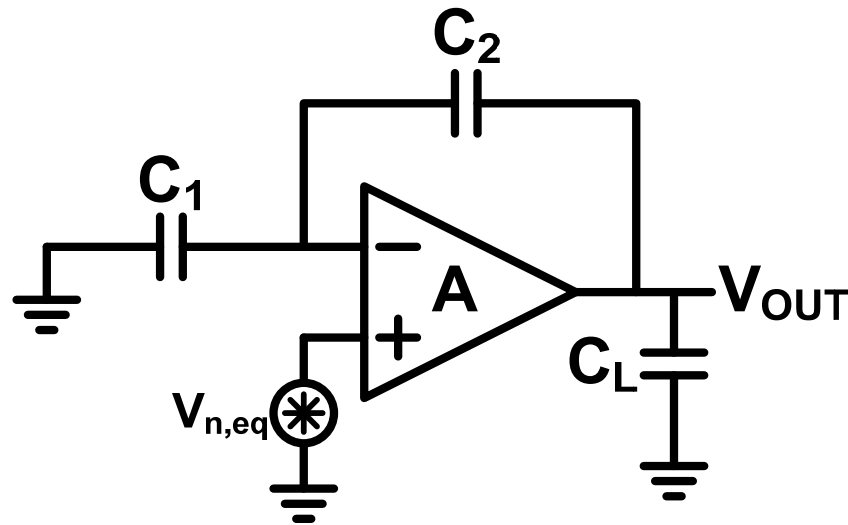
# OTA with capacitive feedback

- **Analyze output noise in single-stage OTA**  
Use capacitive feedback in the amplification / integration phase of a switched-capacitor circuit



# OTA with capacitive feedback

- Transfer function of closed loop OTA

$$H(s) = \frac{V_{OUT}}{V_{n,eq}} = \frac{G}{1 + s/\omega_o}$$

where the DC Gain and 1st-pole frequency are

$$G \approx \frac{1}{\beta} = 1 + C_1 / C_2 \quad \omega_o = \frac{\beta g_{m1}}{C_o}$$

Load capacitance  $C_o$  depends on the type of OTA – for a single-stage, it is  $C_L + C_1 C_2 / (C_1 + C_2)$ , while for a two-stage, it is the compensation capacitor  $C_C$

# OTA with capacitive feedback

- Integrate total noise at output


$$\begin{aligned}\overline{V_{OUT}^2} &= \int_0^{\infty} S_{n,eq}(f) |H(j2\pi f)|^2 df \\ &= \frac{16}{3} \frac{kT}{g_{m1}} n_M \frac{\omega_o}{4} G^2 \\ &= \frac{4kT}{3\beta C_o} n_M\end{aligned}$$

Minimum output noise for  $\beta=1$  is  $\frac{4kT}{3C_o} n_M$

Not a function of  $g_{m1}$  since bandwidth is proportional to  $g_{m1}$  while PSD is inversely proportional to  $g_{m1}$

# OTA with capacitive feedback

- Graphically...

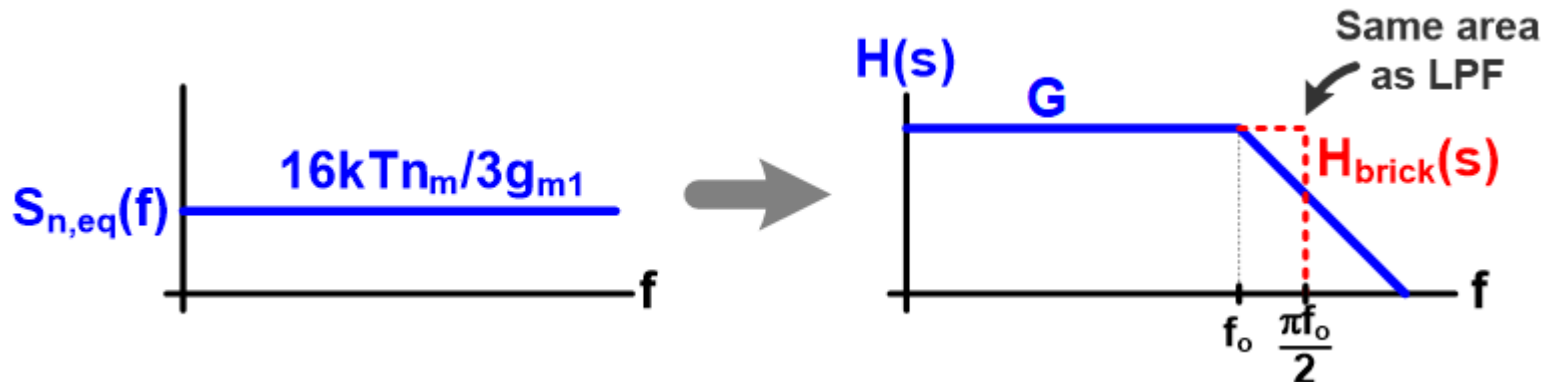

Noise is effectively filtered by equivalent brick wall response with cut-off frequency  $\pi f_o/2$  (or  $\omega_o/4$  or  $1/4\tau$ )

Total noise at  $V_{OUT}$  is the integral of the noise within the brick wall filter (area is simply  $\pi f_o/2 \times G^2$ )


# Sampled Thermal Noise

- What happens to noise once it gets sampled?


Total noise power is the same

Noise is aliased – folded back from higher frequencies to lower frequencies

PSD of the noise increases significantly

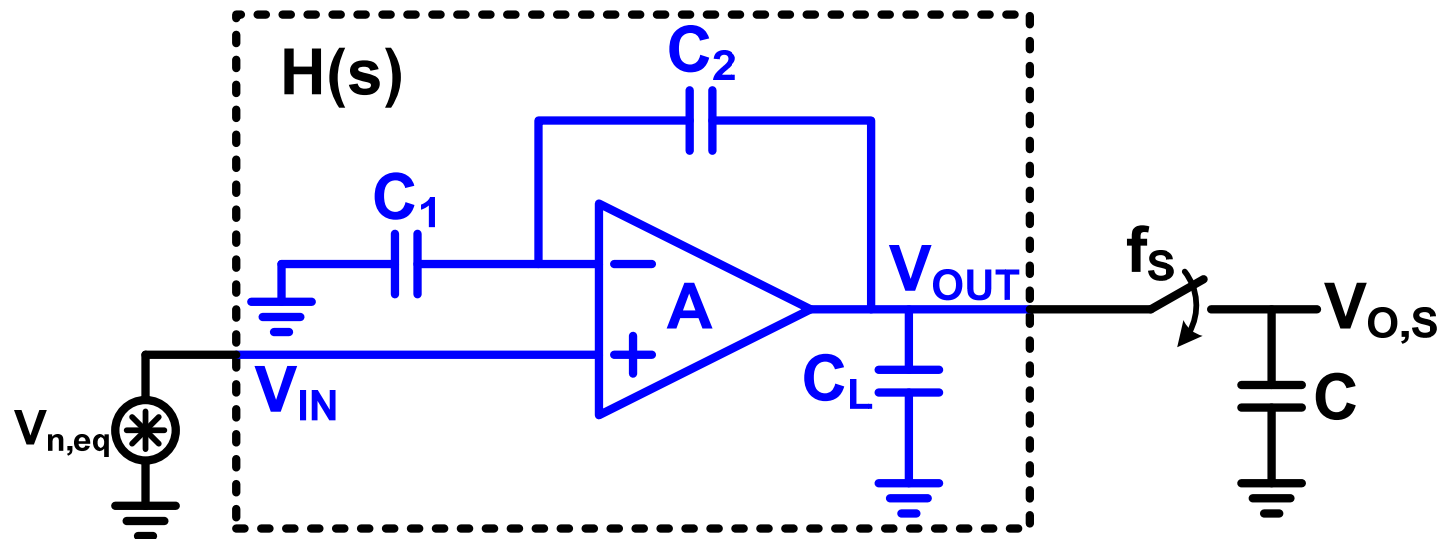

# Sampled Thermal Noise

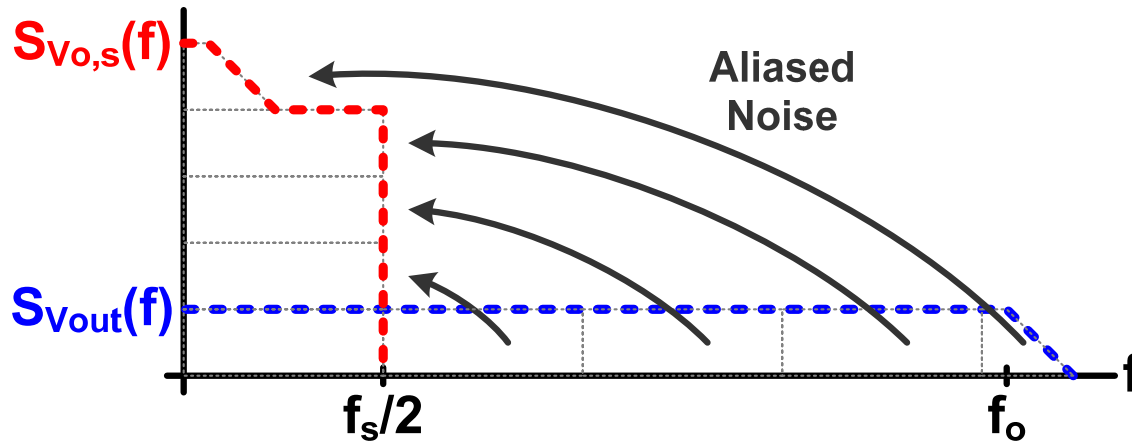

- Same total area, but PSD is larger from 0 to  $f_s/2$

$$S_{V_{o,s}}(f) = \frac{\overline{V_{OUT}^2}}{f_s/2} = \frac{G^2 S_{n,eq}}{4\tau f_s/2} = \frac{4kT}{3\beta C_o} n_M \frac{1}{f_s/2}$$

Low frequency PSD  $G^2 S_{n,eq}$  is increased by  $\frac{\pi f_o/2}{f_s/2} = \frac{\pi f_o}{f_s}$

# Sampled Thermal Noise

- $1/f_0$  is the settling time of the system, while  $1/2f_s$  is the settling period for a two-phase clock

$$e^{-\frac{1/2f_s}{\tau}} < 2^{-(N+1)}$$

$$\frac{\pi f_0}{f_s} > (N + 1) \ln 2$$

PSD is increased by at least  $(N + 1) \ln 2$

If  $N = 10$  bits, PSD is increased by 7.6, or 8.8dB


- This is an inherent disadvantage of sampled-data systems (compared to continuous-time)

But noise is reduced by oversampling ratio after digital filtering


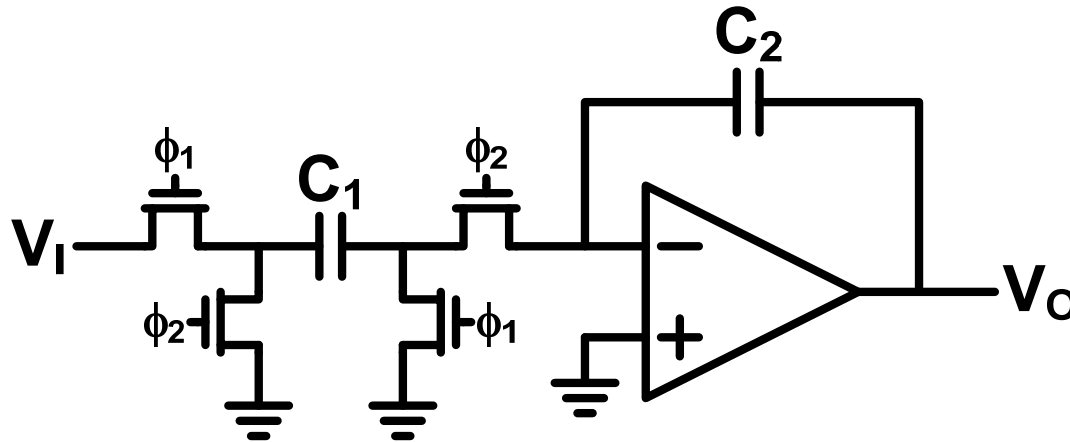
# Noise in a SC Integrator


- Using the parasitic-insensitive SC integrator



- Two phases to consider
  - 1) Sampling Phase
    - Includes noise from both  $\phi_1$  switches
  - 2) Integrating Phase
    - Includes noise from both  $\phi_2$  switches and OTA

# Noise in a SC Integrator

- Phase 1: Sampling

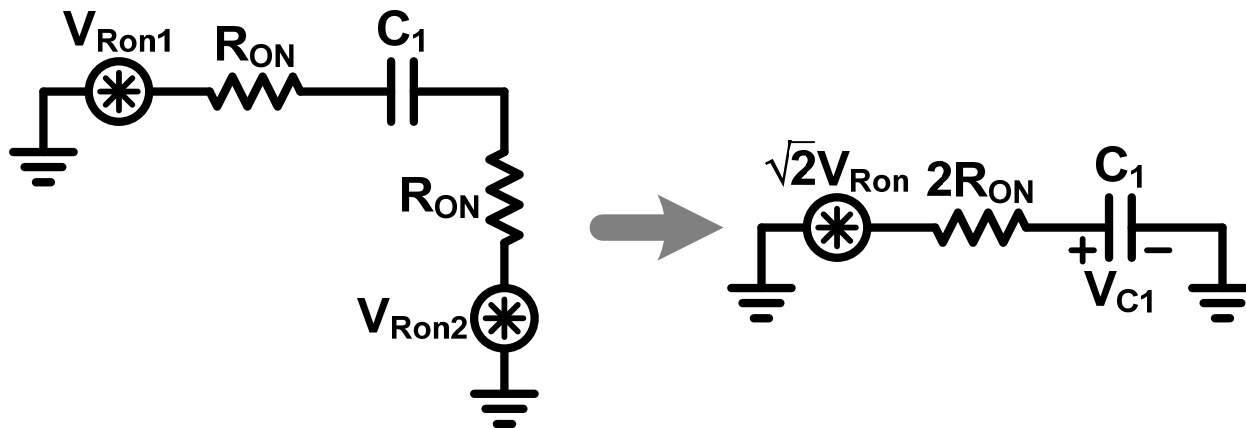

Noise PSD from two switches:  $S_{Ron}(f) = 8kTR_{ON}$

Time constant of R-C filter:  $\tau = 2R_{ON}C_1$

Noise voltage across  $C_1$

$$\overline{V_{C1,sw1}^2} = \int_0^{\infty} S_{Ron}(f) \left| \frac{1}{1 + s\tau} \right|^2 df$$

# Noise in a SC Integrator

- **Phase 1: Sampling**

Integrated across entire spectrum, total noise power in  $C_1$  is


$$\overline{V_{C_1,sw1}^2} = \frac{8kTR_{ON}}{4\tau} = \frac{kT}{C_1}$$

Independent of  $R_{ON}$  (PSD is proportional to  $R_{ON}$ , bandwidth is inversely proportional to  $R_{ON}$ )

After sampling, charge is trapped in  $C_1$

# Noise in a SC Integrator

- Phase 2: Integrating

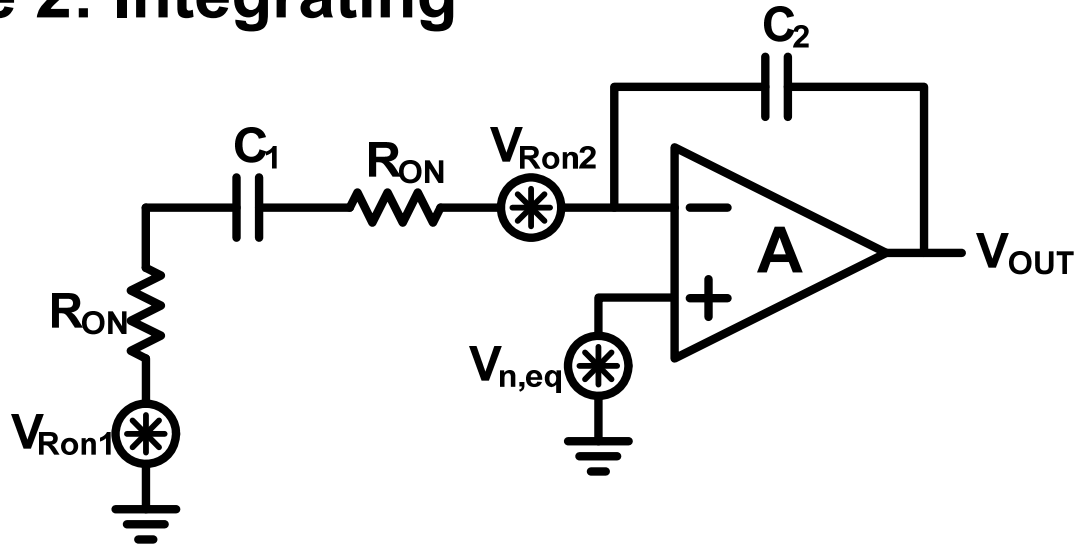

- Two noise sources: switches and OTA


Noise PSD from two switches:  $S_{Ron}(f) = 8kTR_{ON}$

Noise PSD from OTA:  $S_{vn,eq}(f) = \frac{16}{3} \frac{kT}{g_{m1}} n_M$

Noise power across  $C_1$  charges to  $2\overline{V_{Ron}^2} + \overline{V_{n,eq}^2}$

# Noise in a SC Integrator

- What is the time-constant?

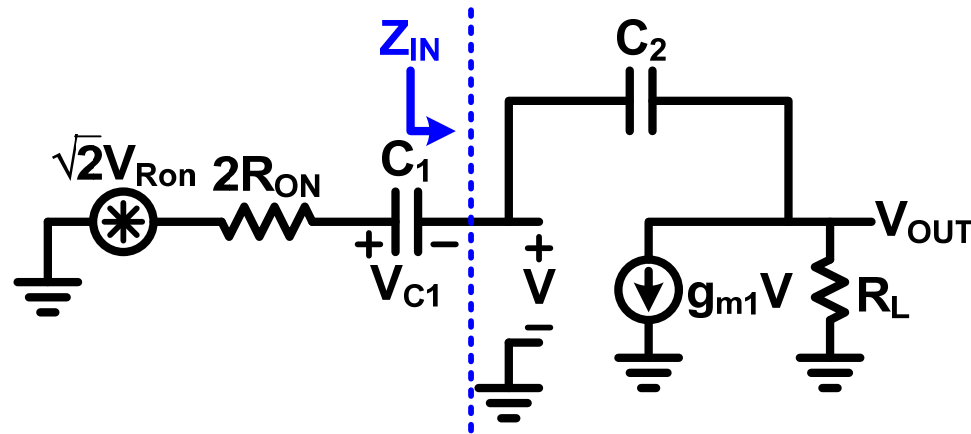

Analysis shows that 
$$Z_{IN} = \frac{1/sC_2 + R_L}{1 + g_{m1}R_L}$$

For large  $R_L$ , assume that 
$$Z_{IN} \approx \frac{1}{g_{m1}}$$

Resulting time constant 
$$\tau = (2R_{ON} + 1/g_{m1})C_1$$

# Noise in a SC Integrator

- Total noise power with both switches and OTA on integrating phase

$$\overline{V_{C1,op}^2} = \frac{S_{vn,eq}(f)}{4\tau}$$

$$= \frac{16kT}{3g_{m1}} \frac{n_M}{4(2R_{ON} + 1/g_{m1})C_1}$$

$$= \frac{4kT}{C_1} \frac{n_M}{(1+x)}$$

$$\overline{V_{C1,sw2}^2} = \frac{S_{Ron}(f)}{4\tau}$$

$$= \frac{8kTR_{ON}}{4(2R_{ON} + 1/g_{m1})C_1}$$

$$= \frac{kT}{C_1} \frac{x}{(1+x)}$$

Introduced extra parameter  $x = 2R_{ON}g_{m1}$

# Noise in a SC Integrator

- Total noise power on C1 from both phases

$$\begin{aligned}\overline{V_{C1,diff}^2} &= \overline{V_{C1,op}^2} + \overline{V_{C1,sw1}^2} + \overline{V_{C1,sw2}^2} \\ &= \frac{4kT}{3C_1} \frac{n_M}{(1+x)} + \frac{kT}{C_1} \frac{x}{(1+x)} + \frac{kT}{C_1} \\ &= \frac{kT}{C_1} \left( \frac{4n_M/3 + 1 + 2x}{1+x} \right)\end{aligned}$$


Lowest possible noise achieved if  $x \rightarrow \infty$

In this case,  $\overline{V_{C1}^2} = \frac{2kT}{C_1}$

What was assumed to be the total noise was actually the least possible noise!
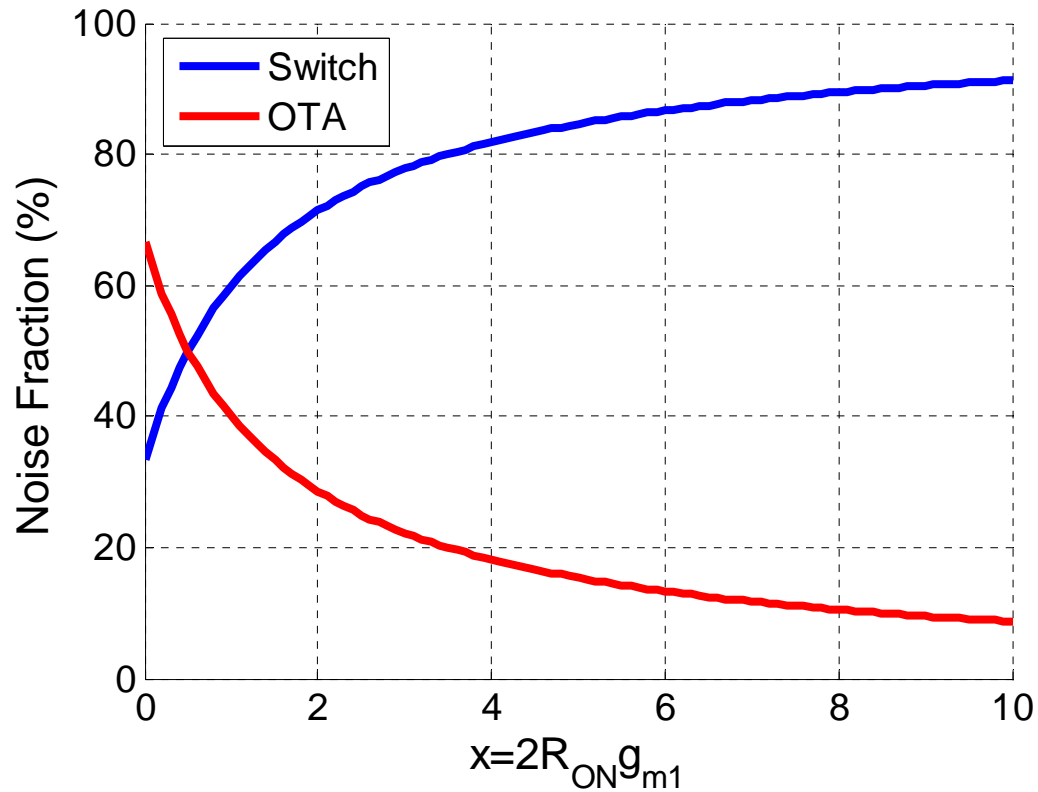
# Noise Contributions

- Percentage noise contribution from switches and OTA (assume  $n_M=1.5$ )





# Noise Contributions

- When  $R_{ON} \gg 1/g_{m1}$  ( $x \gg 1$ )...

Switch dominates both bandwidth and noise

Total noise power is minimized

- When  $R_{ON} \ll 1/g_{m1}$  ( $x \ll 1$ )...

OTA dominates both bandwidth and noise

Power-efficient solution

Minimize  $g_{m1}$  (and power) for a given settling time and noise

$$g_{m1} = \frac{kT}{\tau V_{C1}^2} \left( \frac{4}{3} n_M + 1 + 2x \right)$$

Minimized for  $x=0$

# Amplifier Noise

- How much larger can the noise get?

Depends on  $n_M$ ... (table excludes cascode noise)


Architecture	Relative $V_{EFF}$ 's	$n_M$	Maximum Noise ( $x=0$ )	+dB
Telescopic/ Diff.Pair	$V_{EFF,1} = V_{EFF,n}/2$	1.5	$3 \cdot kT/C_1$	1.76
Telescopic/ Diff.Pair	$V_{EFF,1} = V_{EFF,n}$	2	$3.67 \cdot kT/C_1$	2.63
Folded Cascode	$V_{EFF,1} = V_{EFF,n}/2$	2.5	$4.33 \cdot kT/C_1$	3.36
Folded Cascode	$V_{EFF,1} = V_{EFF,n}$	4	$6.33 \cdot kT/C_1$	5.01

# Separate Input Capacitors

- Using separate input caps increases noise

Each additional input capacitor adds to the total noise

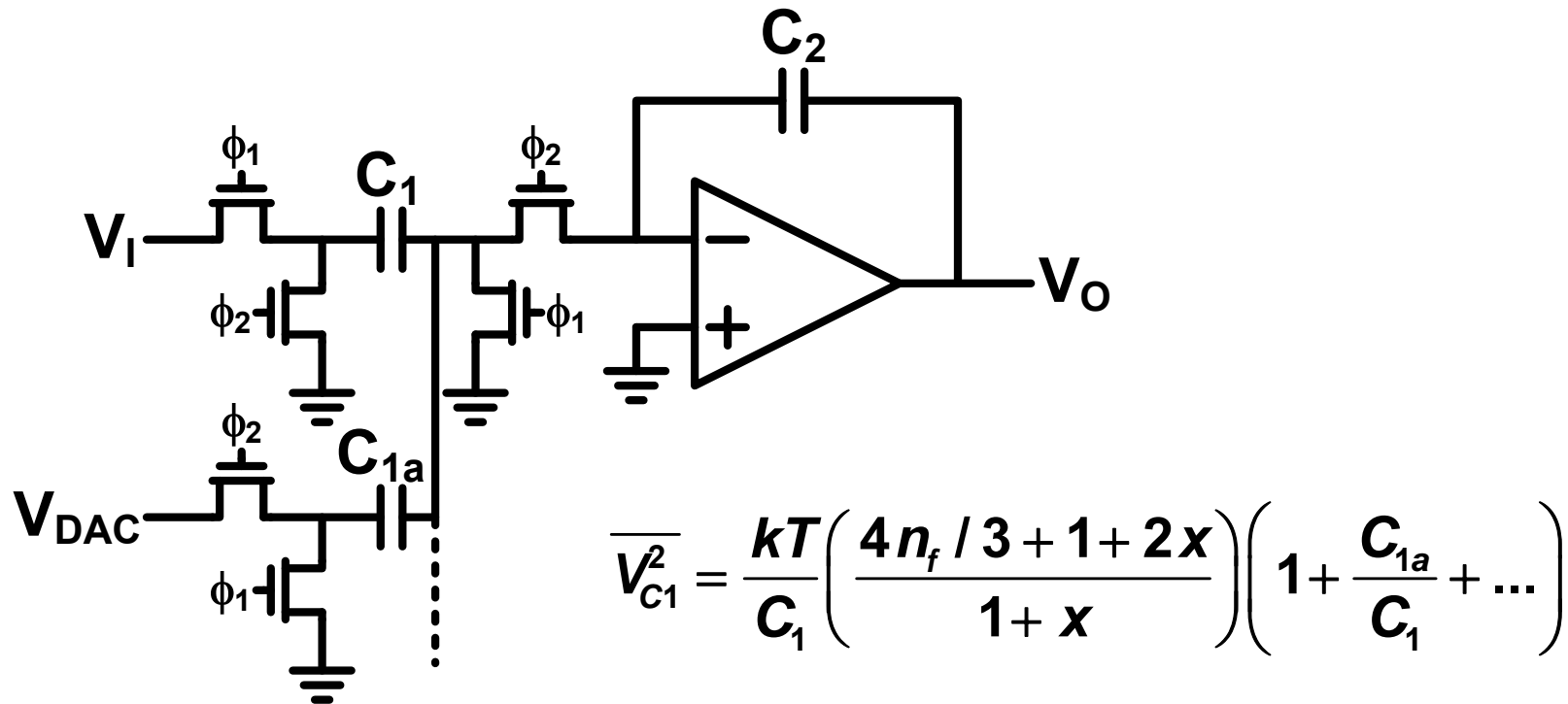Separate caps help reduce signal dependent disturbances in the DAC reference voltages



# Differential vs. Single-Ended

- **Single-Ended Noise**

$$\overline{V_{C1,se}^2} = \frac{kT}{C_1} \left( \frac{4n_M/3 + 1 + 2x}{1 + x} \right)$$

- **Differential Noise**

$$\begin{aligned} \overline{V_{C1,diff}^2} &= \overline{V_{C1,op}^2} + \overline{V_{C1,sw1}^2} + \overline{V_{C1,sw2}^2} \\ &= \frac{4kT}{3C_1} \frac{n_M}{(1+x)} + \frac{2kT}{C_1} \frac{x}{(1+x)} + \frac{2kT}{C_1} \\ &= \frac{kT}{C_1} \left( \frac{4n_M/3 + 2 + 4x}{1+x} \right) \end{aligned}$$

- **Relative Noise (for  $n_f=1.5$ ,  $x=0$ )**

$$\frac{\overline{V_{C1,diff}^2}}{\overline{V_{C1,se}^2}} = \frac{4n_M/3 + 2 + 4x}{4n_M/3 + 1 + 2x} = \frac{4}{3}$$

# Differential vs. Single-Ended

- All previous calculations assumed single-ended operation

For same settling time,  $g_{m1,2}$  is the same, resulting in the same total power **[0dB]**

Differential input signal is twice as large **[gain 6dB]**

Differential operation has twice as many caps and therefore twice as much capacitor noise (assume same size per side –  $C_1$  and  $C_2$ ) **[lose ~1.2dB for  $n_M=1.5$ ,  $x=0...$  less for larger  $n_M$ ]**


- Net Improvement: ~4.8dB

# Noise in an Integrator

- What is the total output-referred noise in an integrator?

Assume an integrator transfer function
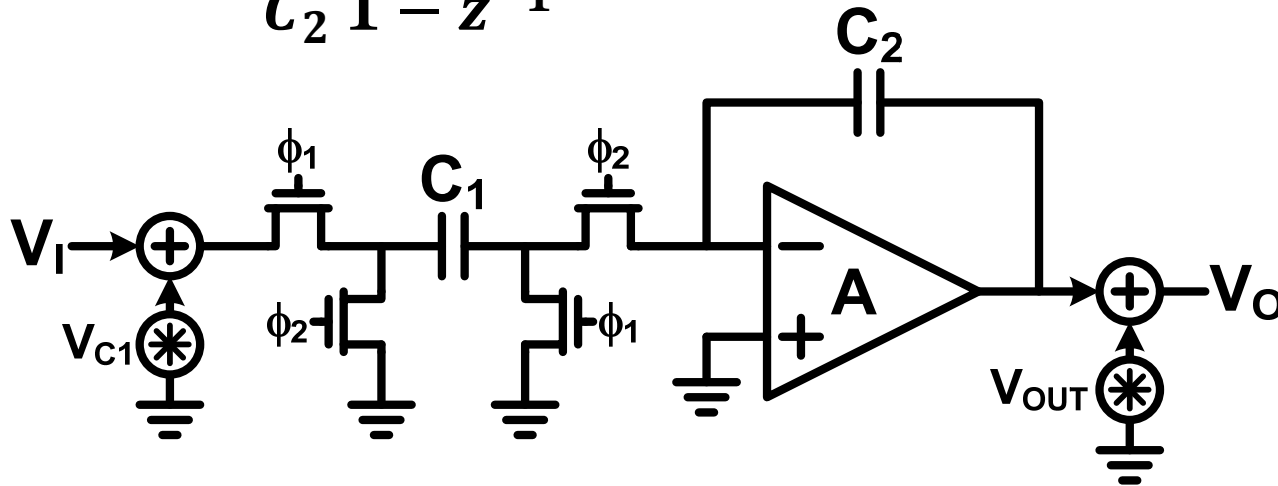
$$H(z) = \frac{C_1}{C_2} \frac{z^{-1}}{1 + (1 + C_1/C_2)/A - \left(1 + \frac{1}{A}\right) z^{-1}}$$
$$\approx \frac{C_1}{C_2} \frac{z^{-1}}{1 - z^{-1}}$$



# Noise in an Integrator

- Total output-referred noise PSD

$$S_{INT}(f) = S_{C1}(f)|H(z)|^2 + S_{OUT}(f)$$

where  $\overline{V_{OUT}^2} = \frac{4kT}{3\beta C_0} n_M$

and  $\overline{V_{C1}^2} = \frac{kT}{C_1} \left( \frac{4n_M/3 + 1 + 2x}{1 + x} \right)$

Since all noise sources are sampled, white PSDs

$$S_x = \frac{\overline{V_x^2}}{f_s/2}$$

To find output-referred noise for a given OSR in a  $\Delta\Sigma$  modulator:

$$\overline{V_{INT}^2} = \int_0^{f_s/(2 \cdot OSR)} S_{INT}(f) df$$

# Noise in a $\Delta\Sigma$ Modulator

- **How do we find the total input-referred noise in a  $\Delta\Sigma$  modulator?**
  - 1) **Find all thermal noise sources**
  - 2) **Find PSDs of the thermal noise sources**
  - 3) **Find transfer functions from each noise source to the output**
  - 4) **Using the transfer functions, integrate all PSDs from DC to the signal band edge  $f_s/2 \cdot \text{OSR}$**
  - 5) **Sum the noise powers to determine the total output thermal noise**
  - 6) **Input noise = output noise (assuming STF is  $\sim 1$  in the signal band)**



# Noise in a $\Delta\Sigma$ Modulator

- Example

$f_s = 100\text{MHz}$ ,  $T = 10\text{ns}$ ,  $\text{OSR} = 32$


$\text{SNR} = 80\text{dB}$  (13-bit resolution)

Input Signal Power =  $0.25\text{V}^2$  (-6dB from  $1\text{V}^2$ )

Noise Budget: 75% thermal noise


Total input referred thermal noise:
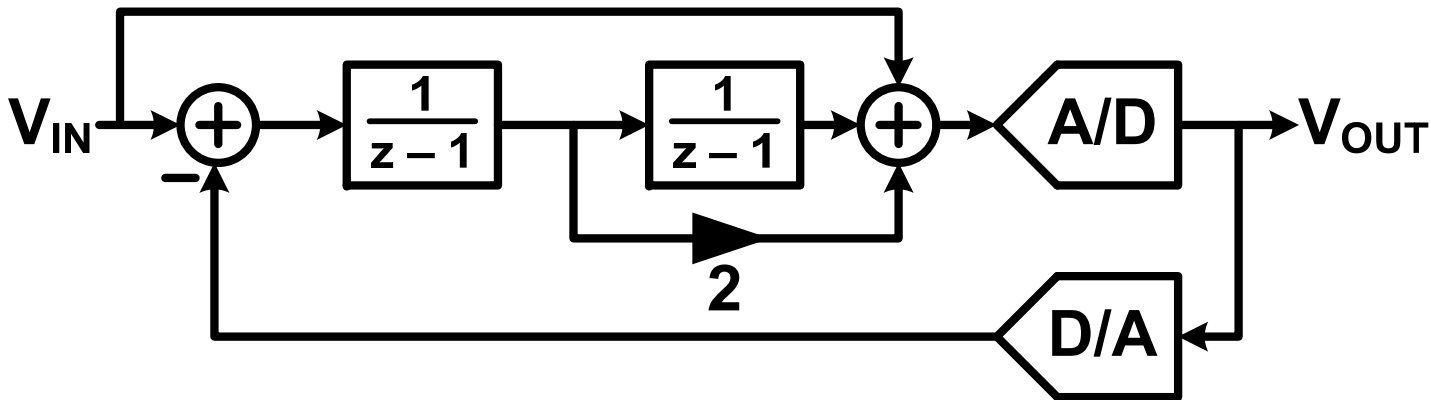
$$\overline{V_{TH}^2} = 0.75 \cdot 10^{(-6 - \text{SNR})/10} \cdot 1\text{V}^2 = (43.4\mu\text{V})^2$$



# Noise in a $\Delta\Sigma$ Modulator

## 1) Find all thermal noise sources

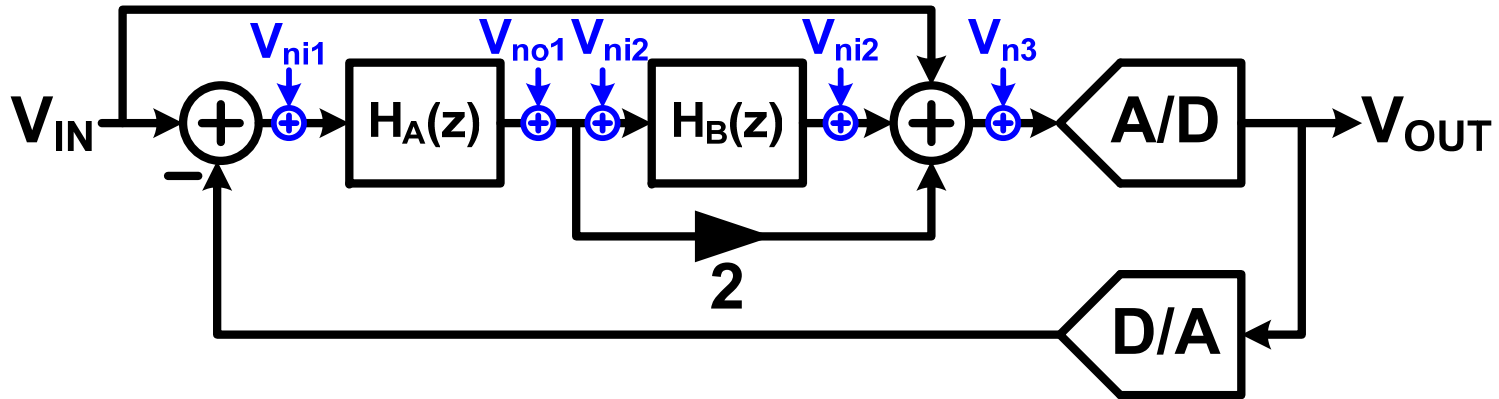

$$\overline{V_{ni1}^2} = \frac{kT}{C_{1A}} \left( \frac{4n_{M,A}/3 + 1 + 2x_A}{1 + x_A} \right)$$

$$\overline{V_{ni2}^2} = \frac{kT}{C_{1B}} \left( \frac{4n_{M,B}/3 + 1 + 2x_B}{1 + x_B} \right)$$

$$\overline{V_{no1}^2} = \frac{4kT}{3\beta_A C_{OA}} n_{M,A}$$

$$\overline{V_{no2}^2} = \frac{4kT}{3\beta_B C_{OB}} n_{M,B}$$

$$\overline{V_{n3}^2} = \frac{2kT}{C_{f1}} \left( 1 + \frac{C_{f2}}{C_{f1}} + \frac{C_{f3}}{C_{f1}} \right) = \frac{2kT}{C_{f1}} (1 + 2 + 1)$$

# Noise in a $\Delta\Sigma$ Modulator

## 2) Find PSDs of the thermal noise sources

For each of the mean square voltage sources,

$$S_x = \frac{\overline{V_x^2}}{f_s / 2}$$

## 3) Find transfer functions from each noise source to the output

Assume ideal integrators

$$H_A(z) = H_B(z) = \frac{z^{-1}}{1 - z^{-1}}$$

$$STF(z) = 1$$

$$NTF(z) = (1 - z^{-1})^2 = \frac{1}{1 + 2H(z) + H(z)^2}$$

# Noise in a $\Delta\Sigma$ Modulator

- 3) Find transfer functions from each noise source to the output

From input of  $H_A(z)$  to output...

$$\begin{aligned} NTF_{i1}(z) &= (2H(z) + H(z)^2) NTF(z) \\ &= \frac{2H(z) + H(z)^2}{1 + 2H(z) + H(z)^2} = 2z^{-1} - z^{-2} \end{aligned}$$

From output of  $H_A(z)$  to output...

$$\begin{aligned} NTF_{o1}(z) &= (2 + H(z)) NTF(z) \\ &= \frac{2 + H(z)}{1 + 2H(z) + H(z)^2} = (1 - z^{-1})(2 - z^{-1}) \end{aligned}$$

# Noise in a $\Delta\Sigma$ Modulator

## 3) Find transfer functions from each noise source to the output

From input of  $H_B(z)$  to output...

$$\begin{aligned} NTF_{i_2}(z) &= H(z)NTF(z) \\ &= \frac{H(z)}{1 + 2H(z) + H(z)^2} = z^{-1}(1 - z^{-1}) \end{aligned}$$


From output of  $H_B(z)$  to output (equal to transfer function at input of summer to output)...

$$NTF_{o_2}(z) = NTF(z) = (1 - z^{-1})^2$$

# Noise in a $\Delta\Sigma$ Modulator

## 3) Find transfer functions from each noise source to the output

Most significant is  $\text{NTF}_{i1}$

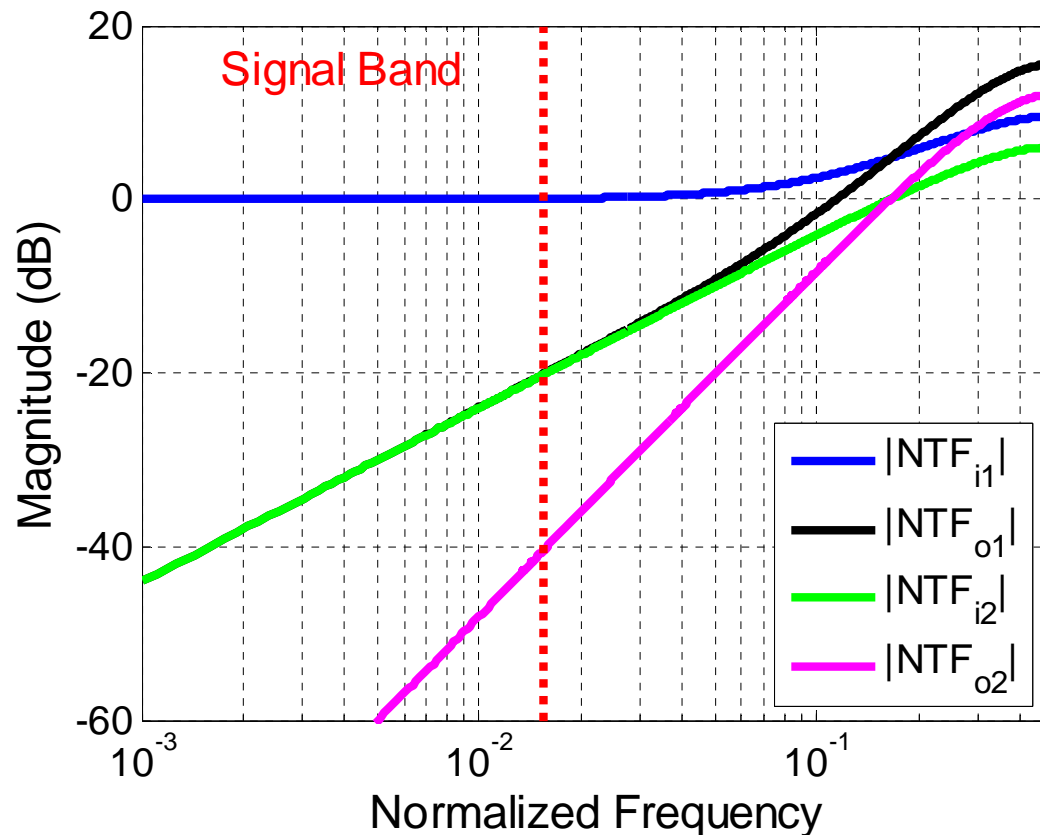

# Noise in a $\Delta\Sigma$ Modulator

- 4) Using the transfer functions, integrate all PSDs from DC to the signal band edge  $f_s/2 \cdot \text{OSR}$

Use MATLAB/Maple to solve the integrals...

$$\begin{aligned}\overline{V_{i1}^2} &= \frac{\overline{V_{ni1}^2}}{f_s/2} \int_0^{f_s/(2 \cdot \text{OSR})} |NTF_{i1}(f)|^2 df \\ &= \frac{\overline{V_{ni1}^2}}{f_s/2} \left[ \frac{5f_s}{2 \cdot \text{OSR}} - \frac{2f_s}{\pi} \sin\left(\frac{\pi}{\text{OSR}}\right) \right]\end{aligned}$$

$$\begin{aligned}\overline{V_{o1}^2} &= \frac{\overline{V_{no1}^2}}{f_s/2} \int_0^{f_s/(2 \cdot \text{OSR})} |NTF_{o1}(f)|^2 df \\ &= \frac{\overline{V_{no1}^2}}{f_s/2} \left[ \frac{7f_s}{\text{OSR}} + \frac{2f_s}{\pi} \sin\left(\frac{\pi}{\text{OSR}}\right) \cos\left(\frac{\pi}{\text{OSR}}\right) - \frac{9f_s}{\pi} \sin\left(\frac{\pi}{\text{OSR}}\right) \right]\end{aligned}$$

# Noise in a $\Delta\Sigma$ Modulator

- 4) Using the transfer functions, integrate all PSDs from DC to the signal band edge  $f_s/2 \cdot \text{OSR}$

$$\overline{V_{i2}^2} = \frac{\overline{V_{ni2}^2}}{f_s/2} \left[ \frac{f_s}{\text{OSR}} - \frac{f_s}{\pi} \sin\left(\frac{\pi}{\text{OSR}}\right) \right]$$

$$\overline{V_{o2}^2} = \frac{\overline{V_{no2}^2} + \overline{V_{n3}^2}}{f_s/2} \left[ \frac{3f_s}{\text{OSR}} + \frac{f_s}{\pi} \sin\left(\frac{\pi}{\text{OSR}}\right) \cos\left(\frac{\pi}{\text{OSR}}\right) - \frac{4f_s}{\pi} \sin\left(\frac{\pi}{\text{OSR}}\right) \right]$$

(Some simplifications can be made for large OSR)



# Noise in a $\Delta\Sigma$ Modulator

- 5) Sum the noise powers to determine the total output thermal noise

Assume  $x_A = x_B = 0.1$  and  $n_{M,A} = n_{M,B} = 1.5$

$$\overline{V_{TH}^2} \approx \frac{2.9kT}{C_{1A}} \frac{1}{OSR} + \frac{2kT}{\beta_A C_{OA}} \frac{\pi^2}{3OSR^3} + \frac{2.9kT}{C_{1B}} \frac{\pi^2}{3OSR^3} + \frac{2kT}{\beta_B C_{OB}} \frac{\pi^4}{5OSR^5} + \frac{8kT}{C_{f1}} \frac{\pi^4}{5OSR^5}$$

With an OSR of 32, first term is most significant (assume  $\beta_A = \beta_B = 1/3$ )

$$\overline{V_{TH}^2} \approx 9.1 \times 10^{-2} \frac{kT}{C_{1A}} + 6.0 \times 10^{-4} \frac{kT}{C_{OA}} + 2.9 \times 10^{-4} \frac{kT}{C_{1B}} + \dots$$

# Noise in a $\Delta\Sigma$ Modulator

- 6) Input noise = output noise (assuming STF is  $\sim 1$  in the signal band)

$$\overline{V_{TH}^2} \approx 9.1 \times 10^{-2} \frac{kT}{C_{1A}} = (43.4 \mu V)^2$$

$$\rightarrow C_{1A} = 200 \text{fF}$$

Assuming other capacitors are smaller than  $C_{1A}$ , then subsequent terms are insignificant and the approximation is valid

If lower oversampling ratios are used, other terms may become more significant in the calculation

# Noise in a Pipeline ADC

- **Similar procedure to  $\Delta\Sigma$  modulator, except transfer functions are much easier to compute**
- **Differences...**
  - Input refer all noise sources**
  - Gain from each stage to the input is a scalar**
  - Noise from later stages will be more significant since typical stage gains are as low as 2**
  - Sample-and-Hold adds extra noise which is input referred with a gain of 1**
  - Entire noise power is added since the signal band is from 0 to  $f_s/2$  (OSR=1)**


# Noise in a Pipeline ADC

- Example

If each stage has a gain  $G_1, G_2, \dots, G_N$

$$\overline{N_i^2} = \overline{V_{ni1}^2} + \frac{\overline{V_{no1}^2} + \overline{V_{ni2}^2}}{G_1^2} + \frac{\overline{V_{no2}^2} + \overline{V_{ni3}^2}}{G_1^2 G_2^2} + \dots + \frac{\overline{V_{noN}^2}}{G_1^2 G_2^2 \dots G_N^2}$$

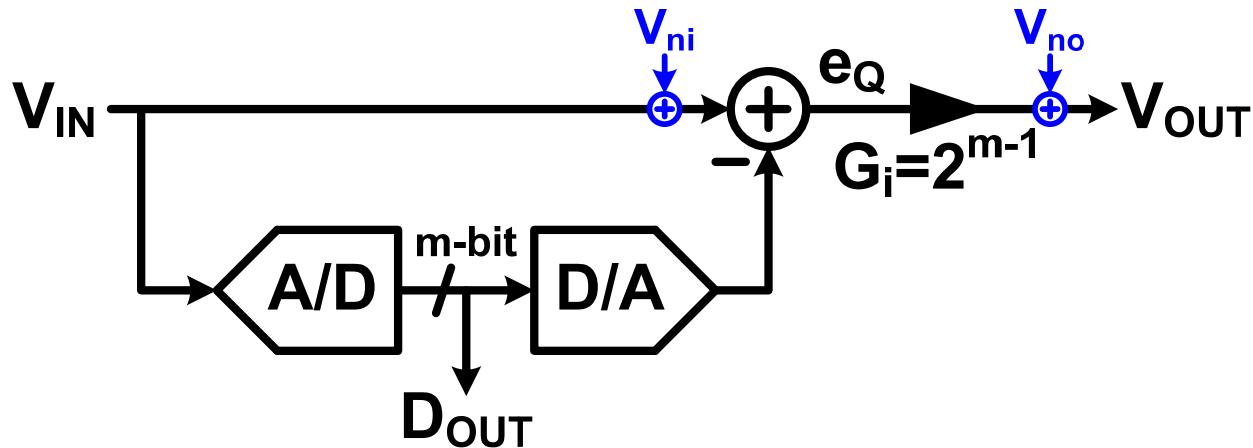S/H stage noise will add directly to  $V_{ni1}$



# Circuit of the Day: Constant- $G_M$ Biasing

# Further Reading

- **Appendix C of *Understanding Delta-Sigma Data Converters*, Schreier and Temes (1<sup>st</sup> edition)**
- **Schreier et al., *Design-Oriented Estimation of Thermal Noise in Switched-Capacitor Circuits*, TCAS-I, Nov. 2005**